

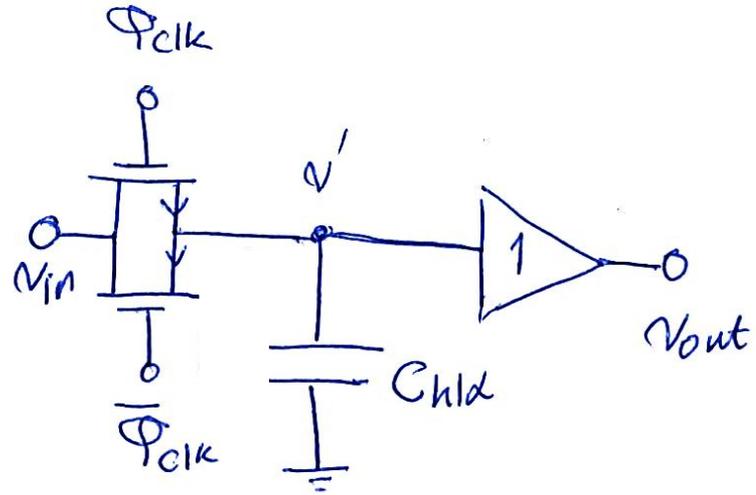




Exercise 1

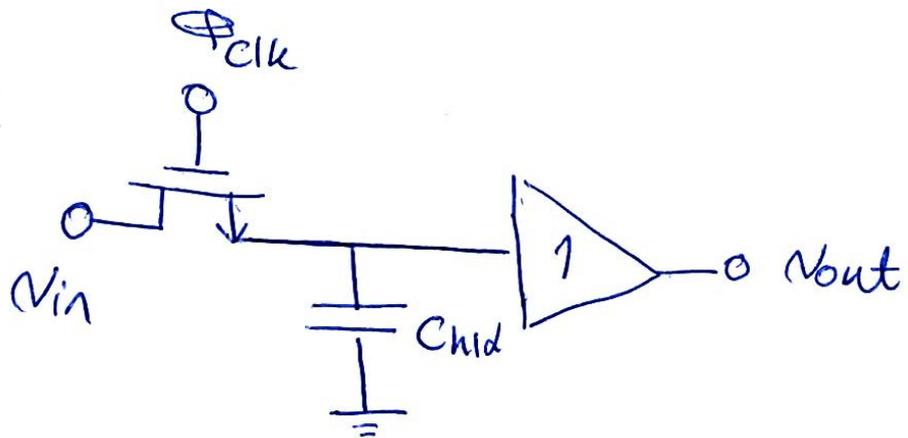



Exercise 1

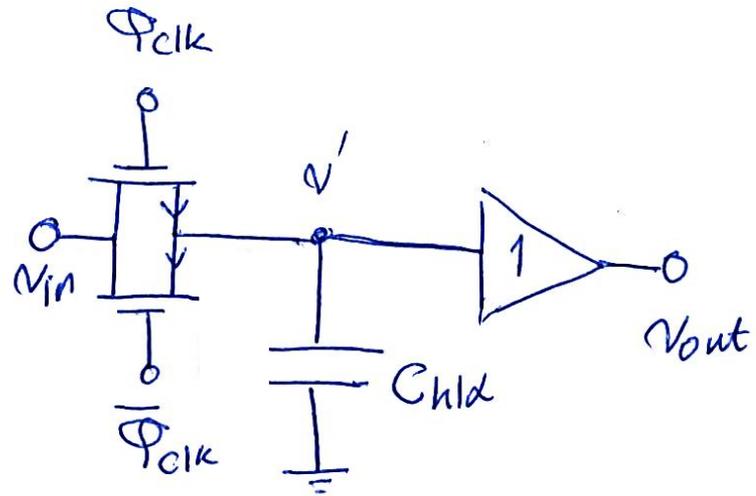

Exercise 1

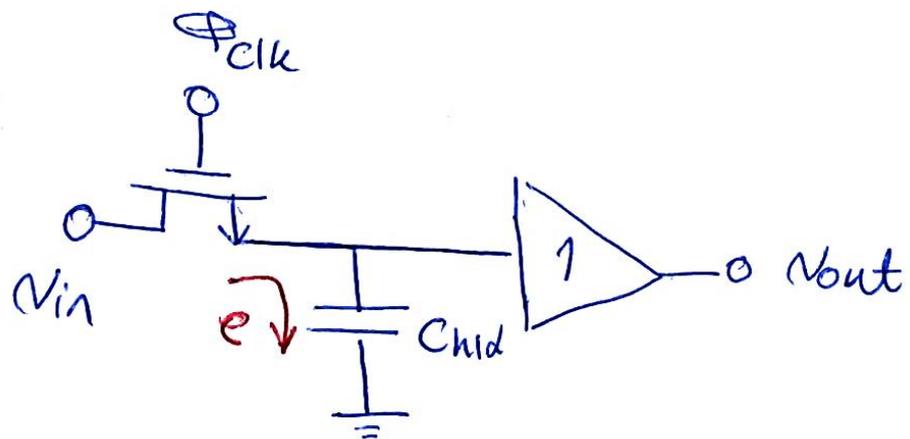
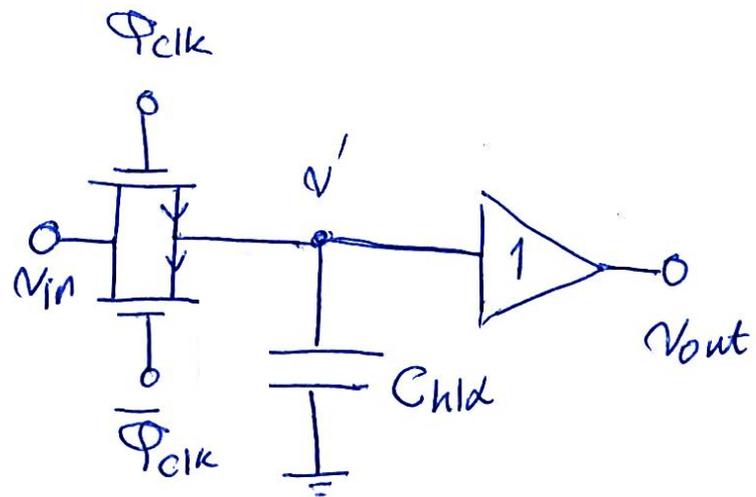


Exercise 1

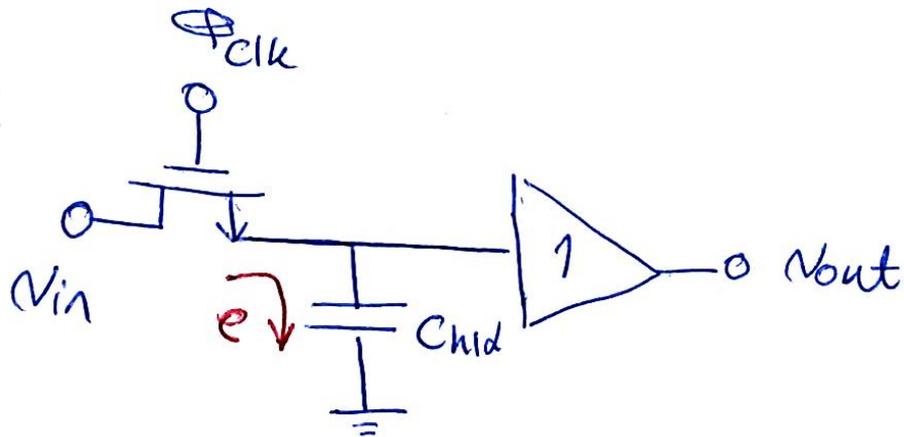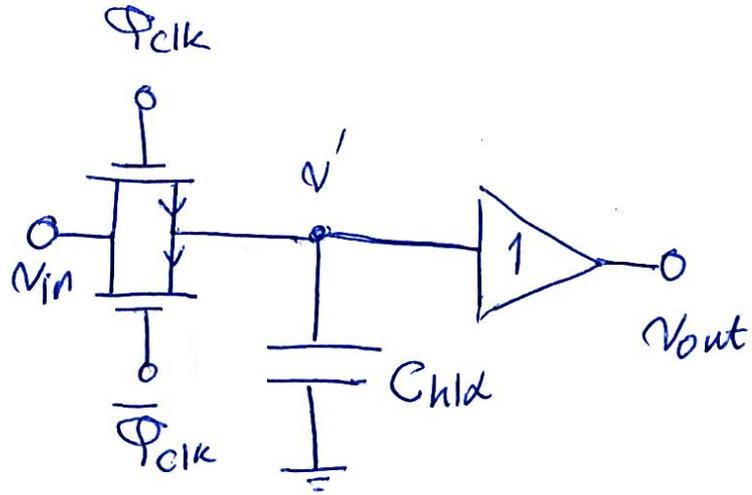


Problem:
Charge injection

Exercise 1

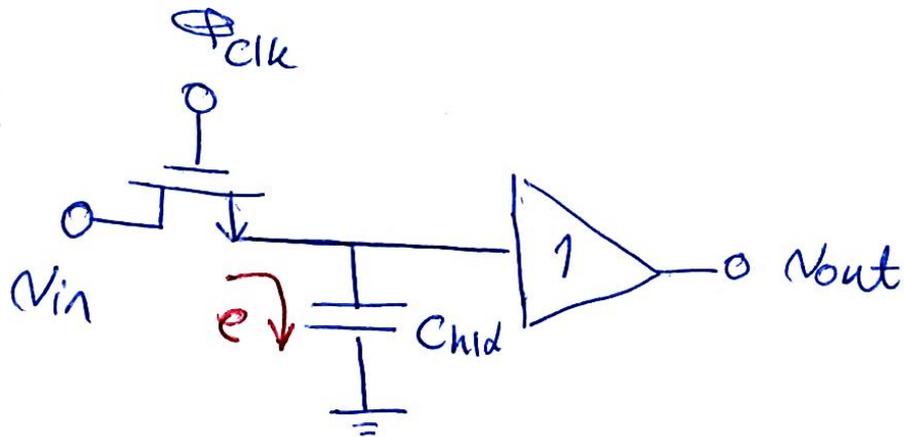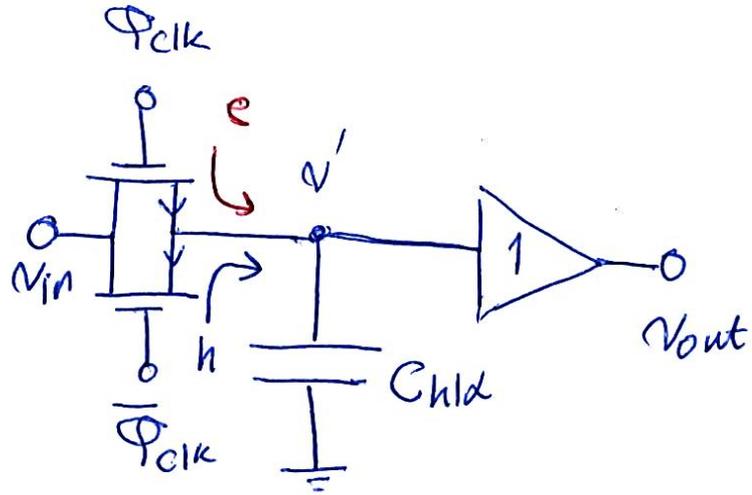


Problem:
Charge injection

Exercise 1

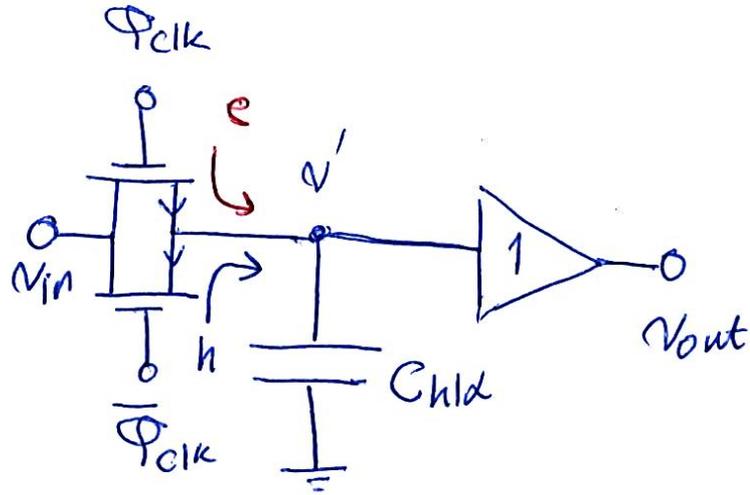

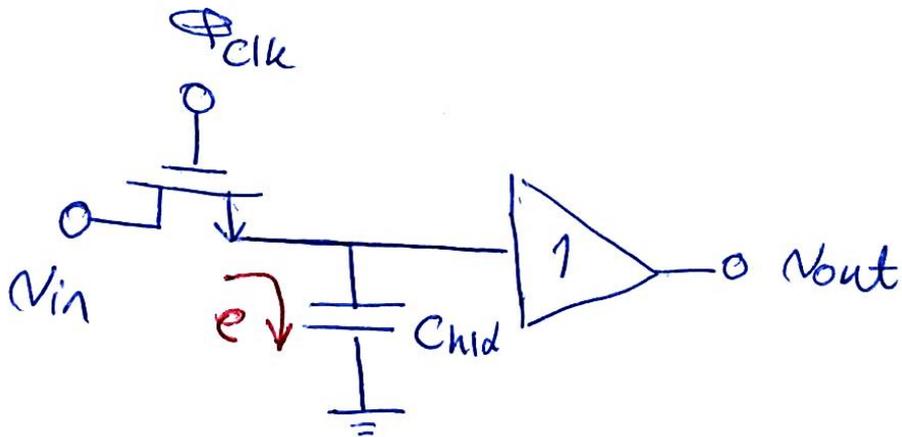Solution:
Charge injection \downarrow
accuracy \uparrow



Problem:
Charge injection

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0$$

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0 \Rightarrow V_G - V_S - V_{th0} = 0$$

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0 \Rightarrow V_G - V_S - V_{th0} = 0$$

The transistor is initially "on".

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0 \Rightarrow V_G - V_S - V_{th0} = 0$$

The transistor is initially "on": $V_{DS} \approx 0$

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0 \Rightarrow V_G - V_S - V_{th0} = 0$$

The transistor is initially "on": $V_{DS} \approx 0 \Rightarrow V_S \approx V_D$

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0 \Rightarrow V_G - V_S - V_{th0} = 0$$

The transistor is initially "on": $V_{DS} \simeq 0 \Rightarrow V_S \simeq V_D$

$$V_G - V_S - V_{th0} \simeq V_G - V_D - V_{th0} = 0$$

Exercise 1

* Assuming v_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0 \Rightarrow V_G - V_S - V_{th0} = 0$$

The transistor is initially "on": $V_{DS} \simeq 0 \Rightarrow V_S \simeq V_D$

$$V_G - V_S - V_{th0} \simeq V_G - V_D - V_{th0} = 0$$

$$V_G = V_D + V_{th0}$$

Exercise 1

* Assuming V_{in} is constant during 1.5 ns of transition.

The n-channel transistor turns off when:

$$V_{GS} - V_{th0} = 0 \Rightarrow V_G - V_S - V_{th0} = 0$$

The transistor is initially "on": $V_{DS} \approx 0 \Rightarrow V_S \approx V_D$

$$V_G - V_S - V_{th0} \approx V_G - V_D - V_{th0} = 0$$

$$V_G = V_D + V_{th0} \quad \text{which means}$$

$$\Phi_{clk} = V_{in} + 0.8 \text{ V}$$

Exercise 1

The p-channel transistor turns off:

$$V_G = \bar{V}_D + V_{t_{p0}} \quad \text{which means}$$

$$\bar{\Phi}_{clk} = V_{in} - 0.9 \text{ V}$$

Exercise 1

The p-channel transistor turns off:

$$V_G = V_D + V_{tp0} \quad \text{which means}$$

$$\overline{\Phi}_{clk} = V_{in} - 0.9 \text{ V} \Rightarrow \Phi_{clk} = 0.9 - V_{in}$$

Exercise 1

The p-channel transistor turns off:

$$V_G = \bar{V}_D + V_{t_{p0}} \quad \text{which means}$$

$$\bar{\Phi}_{\text{clk}} = V_{\text{in}} - 0.9 \text{ V} \Rightarrow \Phi_{\text{clk}} = 0.9 - V_{\text{in}}$$

The difference between the Φ voltages for the two cases is:

$$\Delta\Phi = 0.1 - 2V_{\text{in}} \quad ; \quad -1 \leq V_{\text{in}} \leq 1$$

Exercise 1

The p-channel transistor turns off:

$$V_G = V_D + V_{t_{p0}} \quad \text{which means}$$

$$\bar{\Phi}_{\text{clk}} = V_{\text{in}} - 0.9 \text{ V} \Rightarrow \Phi_{\text{clk}} = 0.9 - V_{\text{in}}$$

The difference between the Φ voltages for the two cases is:

$$\Delta\Phi = 0.1 - 2V_{\text{in}} \quad ; \quad -1 \leq V_{\text{in}} \leq 1$$

$$|\Delta\Phi|_{\text{max}} = ?$$

Exercise 1

The p-channel transistor turns off:

$$V_G = V_D + V_{t_{po}} \quad \text{which means}$$

$$\bar{\Phi}_{clk} = V_{in} - 0.9 \text{ V} \Rightarrow \Phi_{clk} = 0.9 - V_{in}$$

The difference between the Φ voltages for the two cases is:

$$\Delta\Phi = 0.1 - 2V_{in} \quad ; \quad -1 \leq V_{in} \leq 1$$

$$|\Delta\Phi|_{\max} = ?$$

$|\Delta\Phi|$ is maximized at $V_{in} = -1$ for which, $|\Delta\Phi|_{\max} = 2.1 \text{ V}$

Exercise 1


$$\Delta t_{\max} = ?$$

We can find the answer using the proportion method.

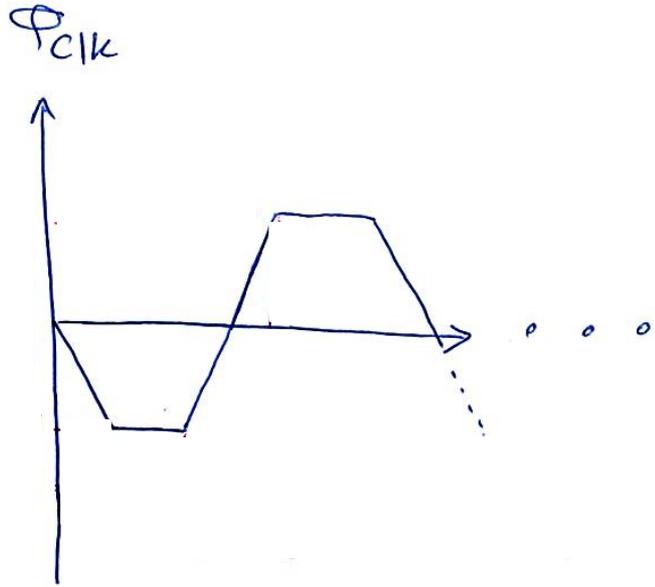Exercise 1

$$\Delta t_{\max} = ?$$

We can find the answer using the proportion method.




Volt

time

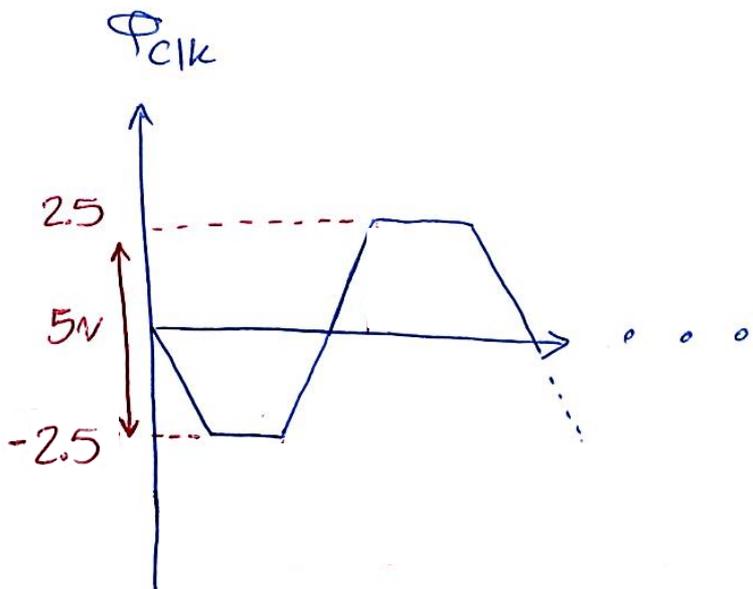Exercise 1

$$\Delta t_{\max} = ?$$

We can find the answer using the proportion method.




$$\frac{\text{Volt}}{5}$$

$$\frac{\text{time}}$$

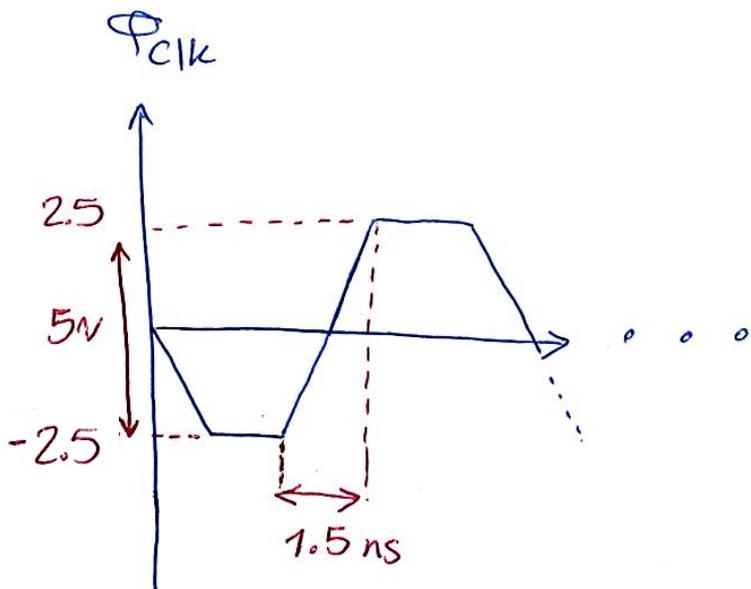Exercise 1

$$\Delta t_{\max} = ?$$

We can find the answer using the proportion method.




$$\frac{\text{Volt}}{5}$$

$$\frac{\text{time}}{1.5 \text{ ns}}$$

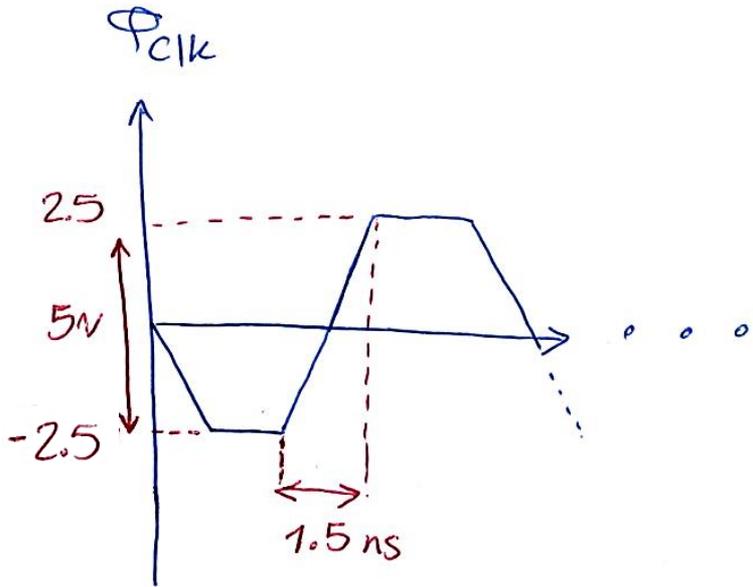Exercise 1

$$\Delta t_{\max} = ?$$

We can find the answer using the proportion method.




<u>Volt</u>
5
2.1

<u>time</u>
1.5 ns
Δt_{\max}

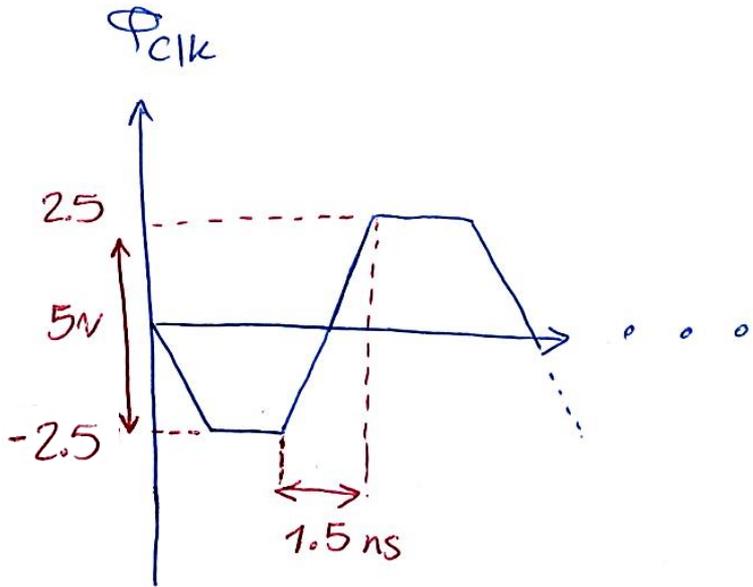Exercise 1

$$\Delta t_{\max} = ?$$


We can find the answer using the proportion method.




<u>Volt</u>	<u>time</u>
5	1.5 ns
2.1	Δt_{\max}

$$\Delta t_{\max} = \frac{2.1}{5} \times 1.5 \text{ ns} = \underline{\underline{0.63 \text{ ns}}}$$

Exercise 2

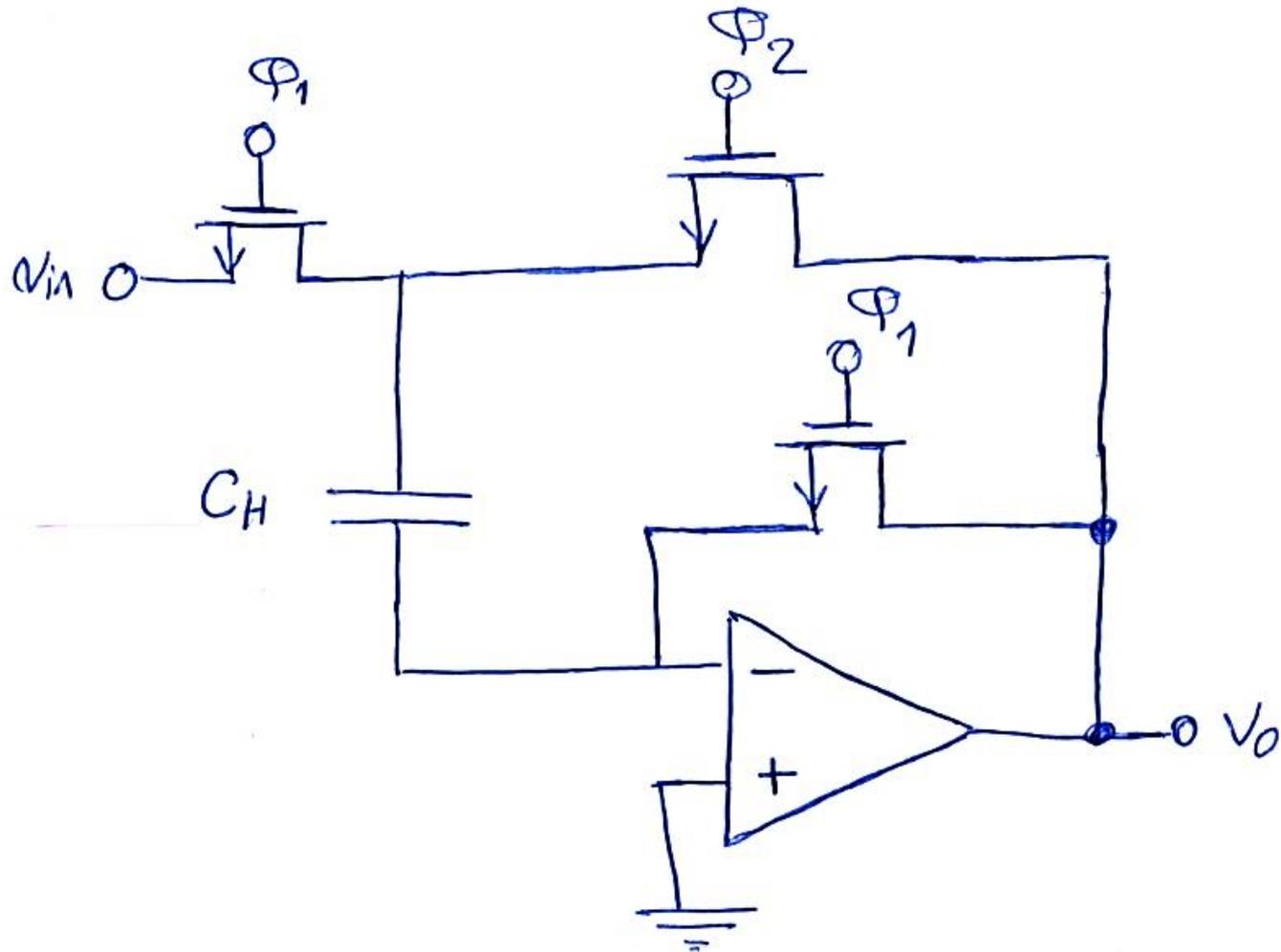


Exercise 2

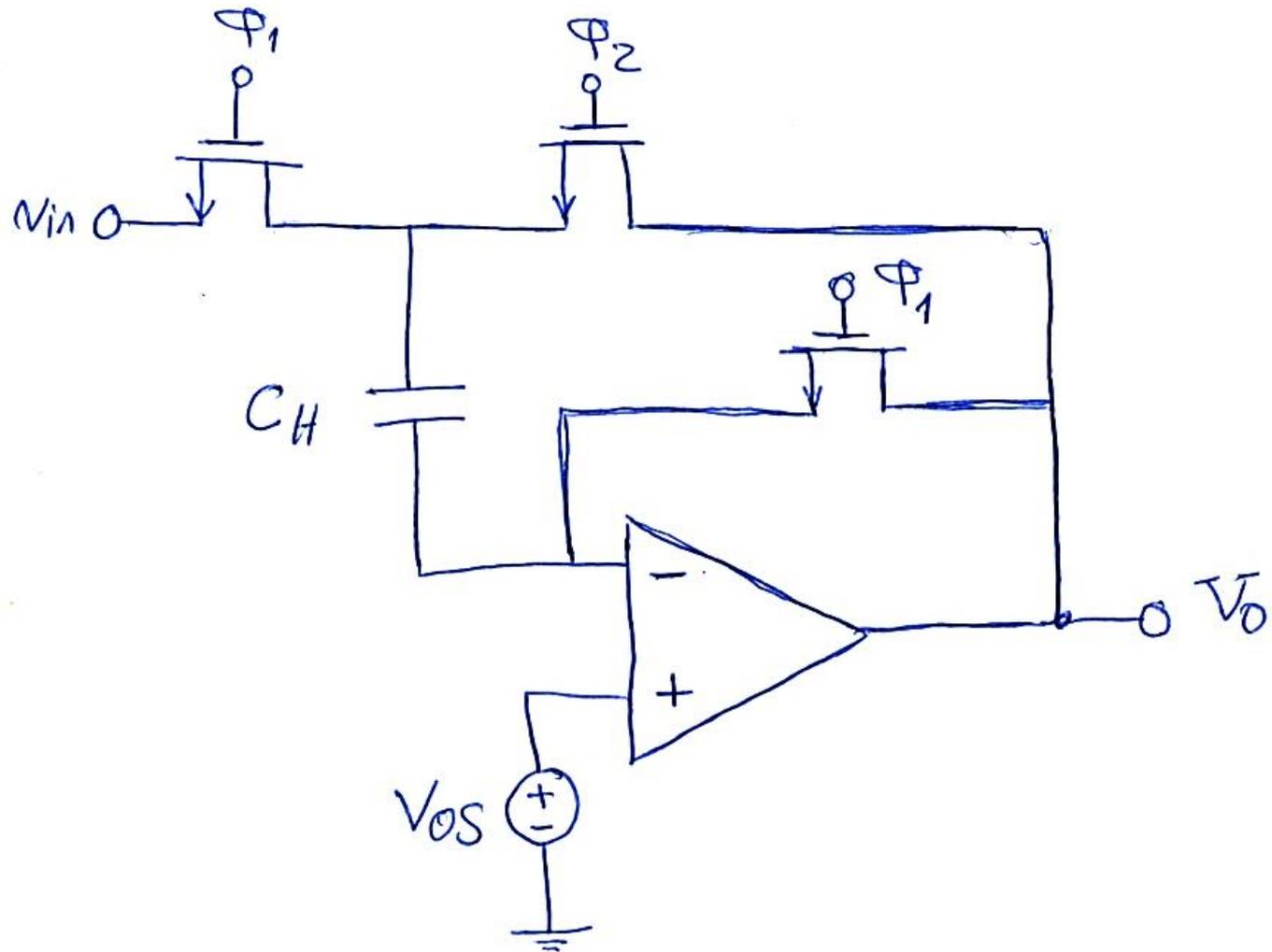


Exercise 2

When Φ_1 is ON:

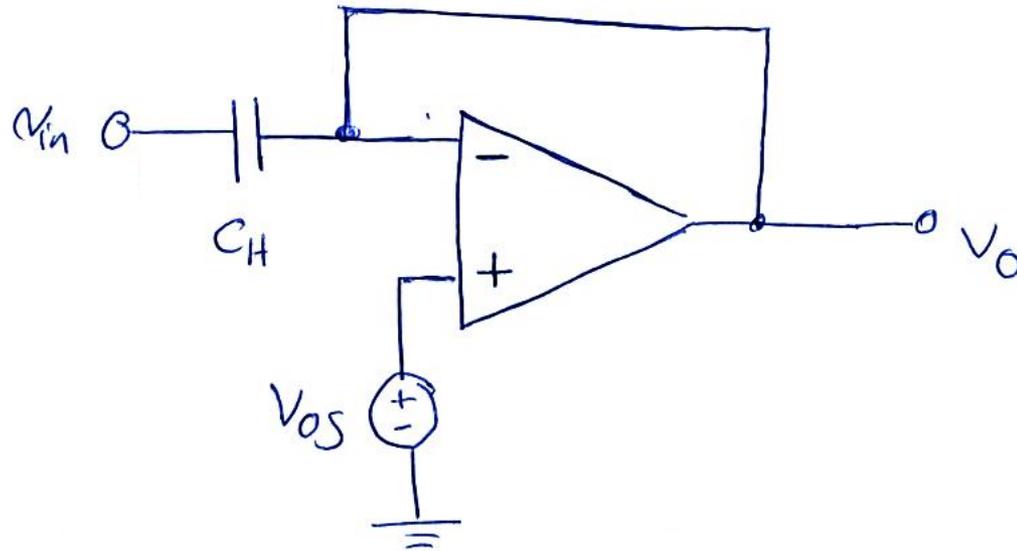

Exercise 2

When Φ_1 is ON:

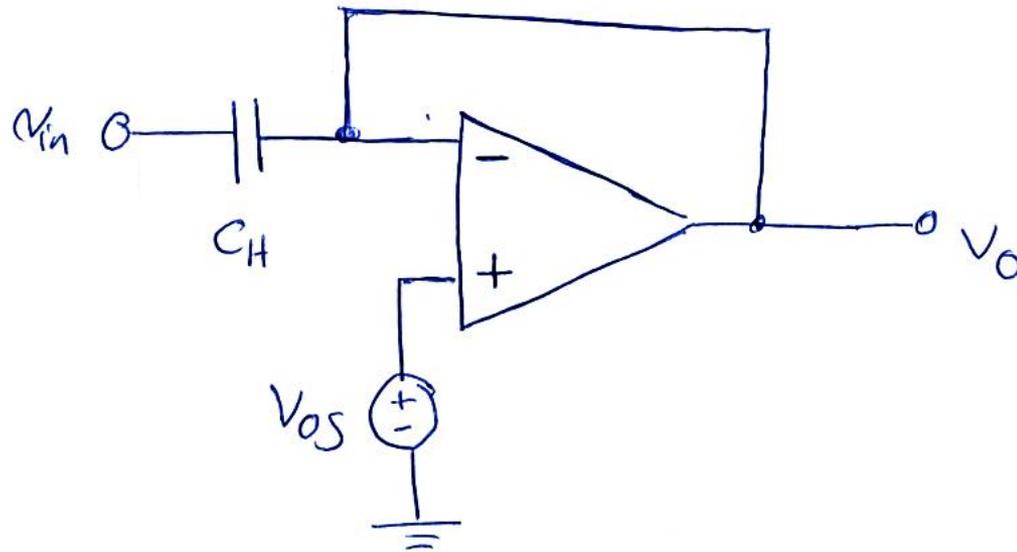


For any op-Amp:

$$A(V_+ - V_-) = V_{out}$$

Exercise 2

When Φ_1 is ON:

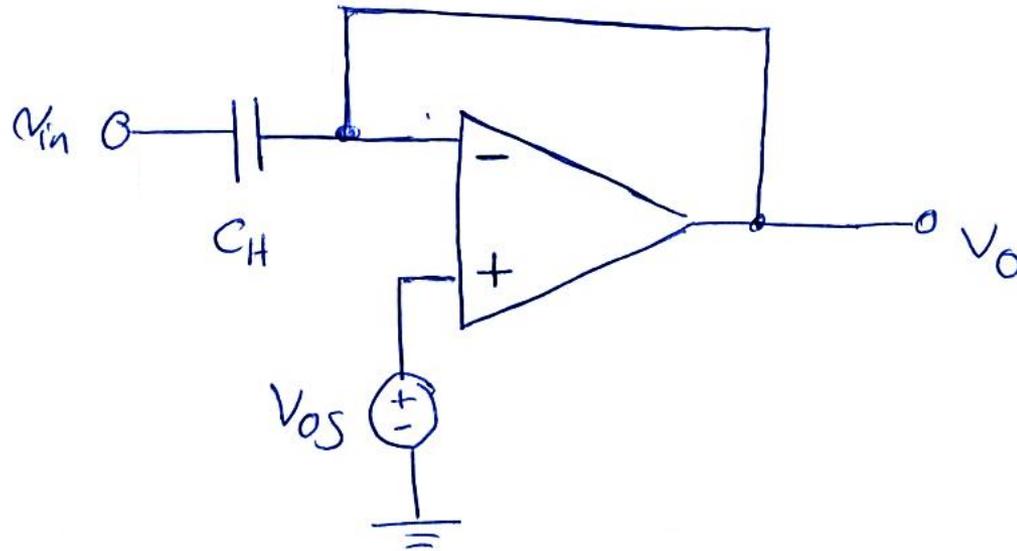


For any op-Amp:

$$A(V_+ - V_-) = V_{out} \Rightarrow A(V_{OS} - V_O) = V_O$$

$$V_{OS} - V_O = \frac{V_O}{A} \Rightarrow V_O \left(1 + \frac{1}{A}\right) = V_{OS}$$

Exercise 2

When Φ_1 is ON:

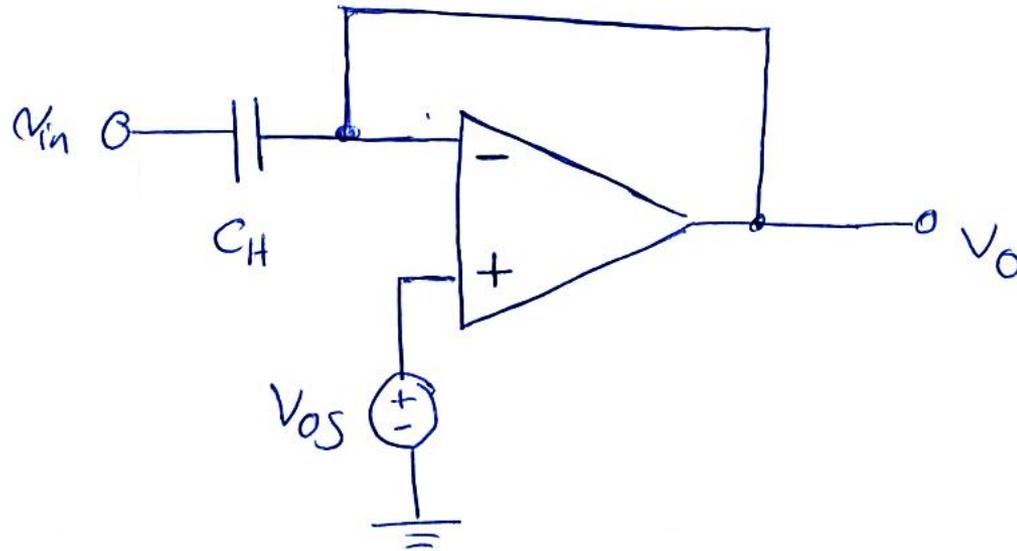


For any op-Amp:

$$A(V_+ - V_-) = V_{out} \Rightarrow A(V_{OS} - V_O) = V_O$$

$$V_{OS} - V_O = \frac{V_O}{A} \Rightarrow V_O \left(1 + \frac{1}{A}\right) = V_{OS} \Rightarrow V_O = \left(\frac{A}{A+1}\right) V_{OS}$$

Exercise 2


When ϕ_1 is ON:

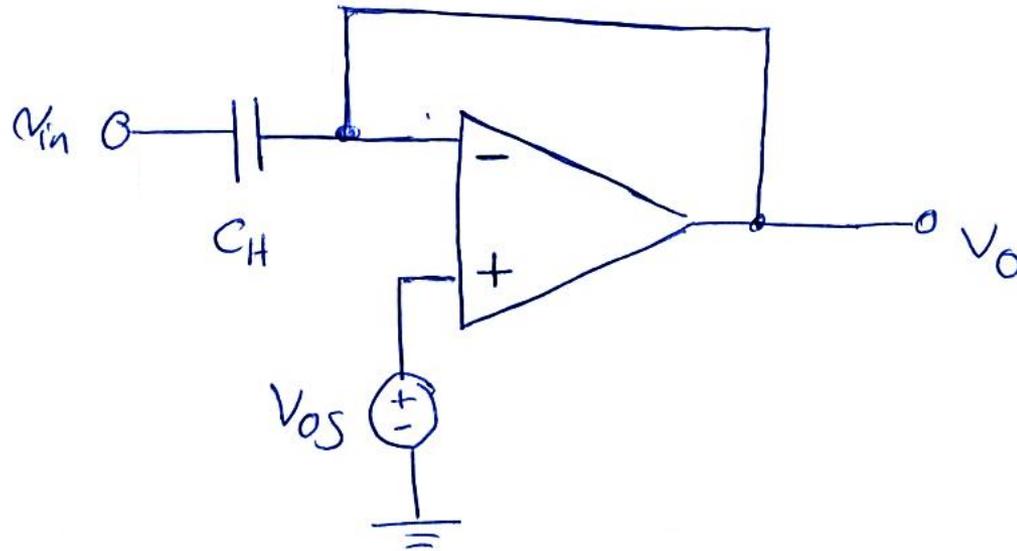

So, during sample mode, voltage across C_H is " $V_{in} - \frac{A}{A+1} V_{OS}$ ".

Exercise 2

When Φ_1 is ON:

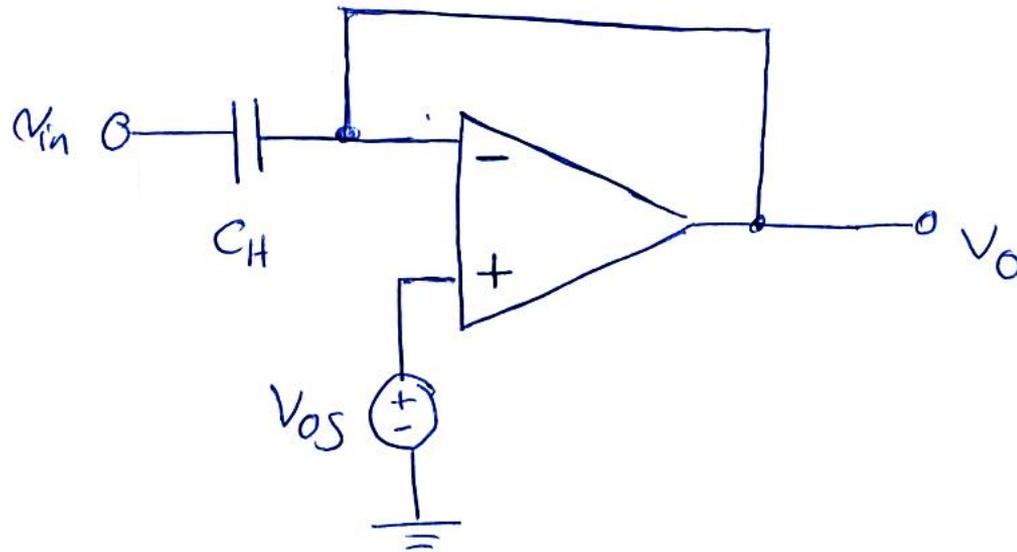


So, during sample mode, voltage across C_H is $V_{in} - \frac{A}{A+1} V_{OS}$.

?

Exercise 2

When Φ_1 is ON:

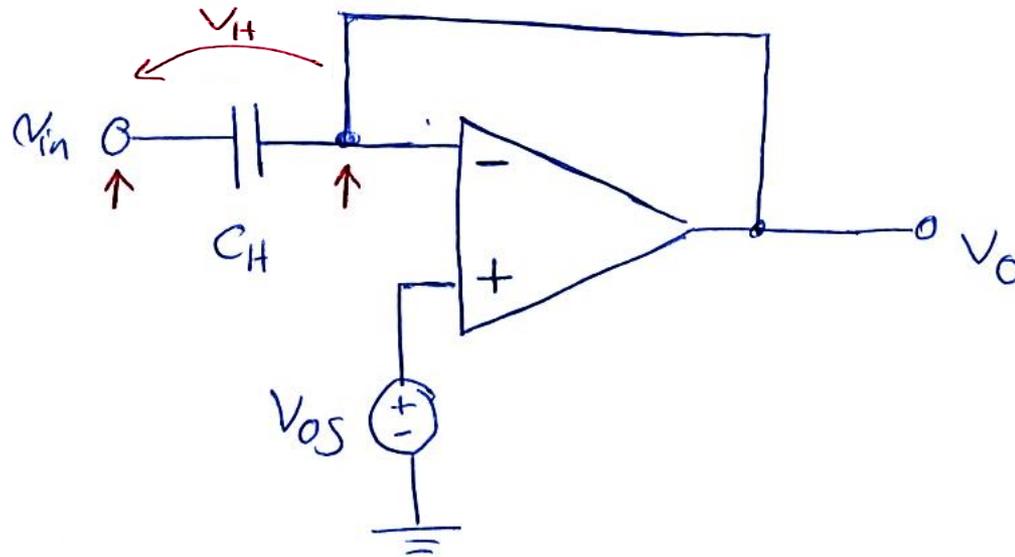


So, during sample mode, voltage across C_H is " $V_{in} - \frac{A}{A+1} V_{OS}$ "
?

$$V_H = V_{in} - V_O = V_{in} - \frac{A}{A+1} V_{OS}$$


Exercise 2

When Φ_2 is ON:

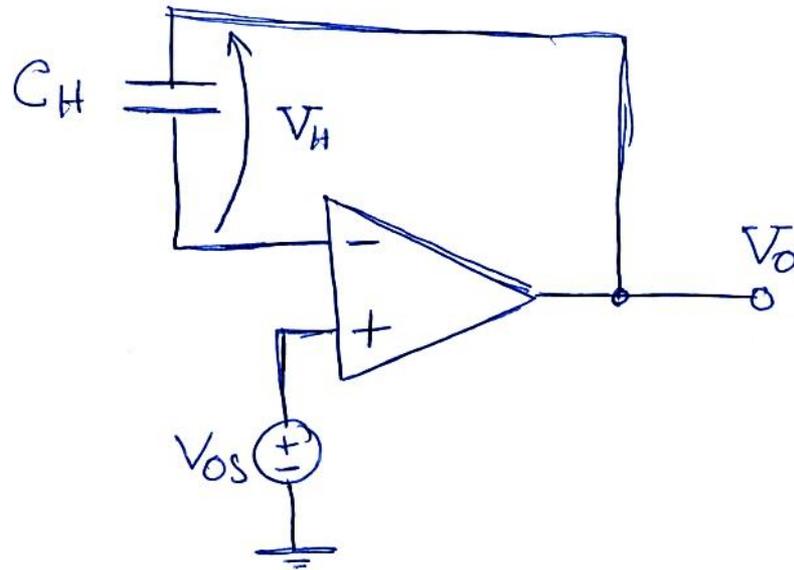

Exercise 2

When Φ_2 is ON:

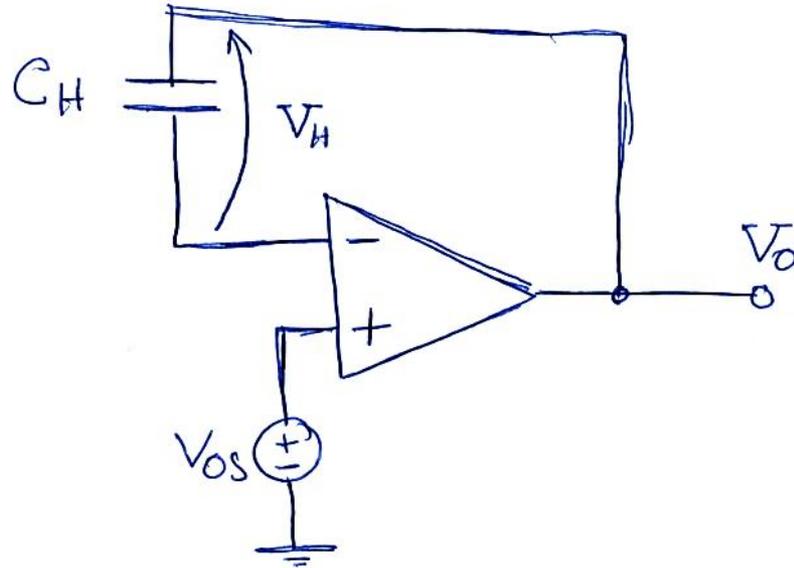


For all op-Amp:

$$A (V_+ - V_-) = V_{out}$$

Exercise 2

When Φ_2 is ON:

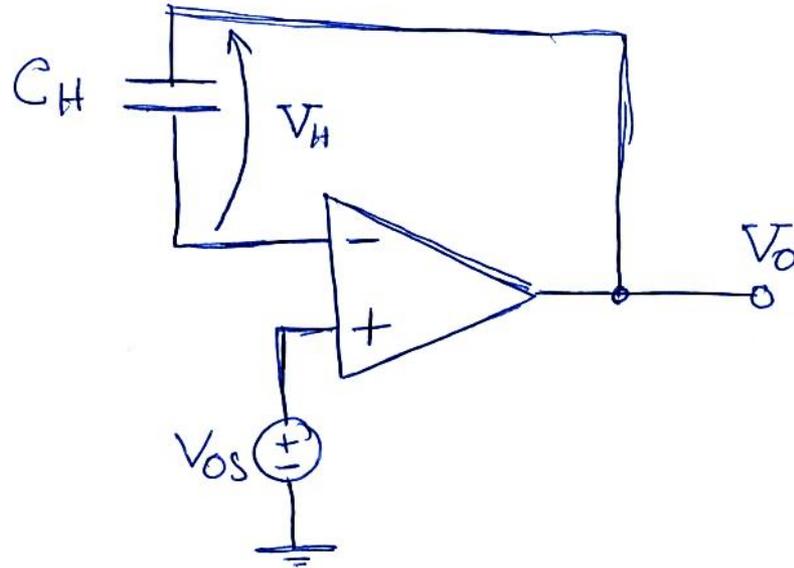


For all op-Amp:

$$A (V_+ - V_-) = V_{out}$$

$$V_+ = V_{OS}$$

Exercise 2

When Φ_2 is ON:

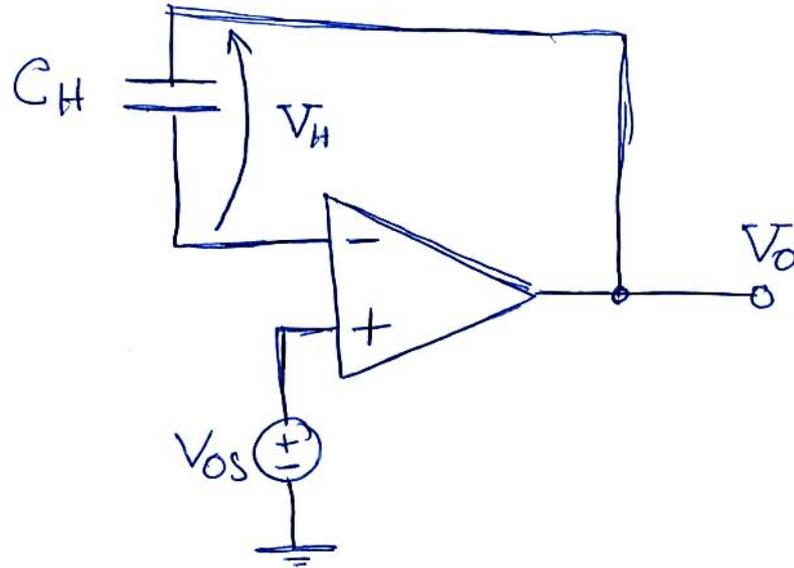

For all op-Amp:


$$A (V_+ - V_-) = V_{out}$$

$$V_+ = V_{OS}$$

$$V_- = V_O - V_H$$

Exercise 2

When Φ_2 is ON:

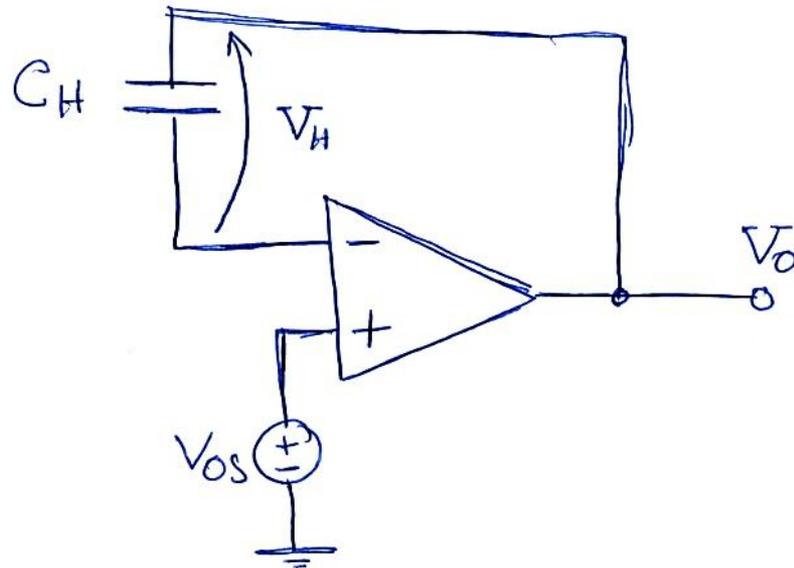

For all op-Amp:


$$A (V_+ - V_-) = V_{out}$$

$$V_+ = V_{OS}$$

$$V_- = V_O - V_H = V_O - \left(V_{in} - \frac{A}{A+1} V_{OS} \right)$$

Exercise 2

When Φ_2 is ON:

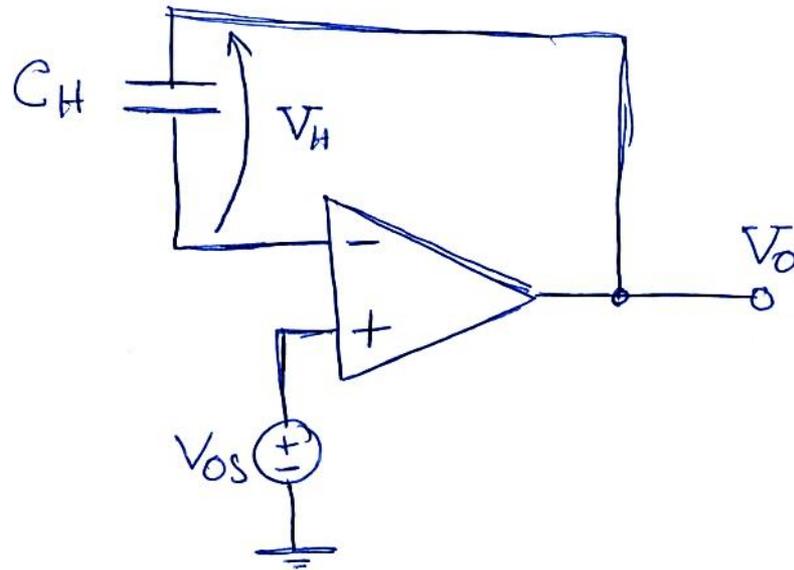


So, I can write,

$$A(V_{OS} - (V_O - (V_{in} - \frac{A}{A+1} V_{OS}))) = V_O \Rightarrow$$

Exercise 2

When Φ_2 is ON:

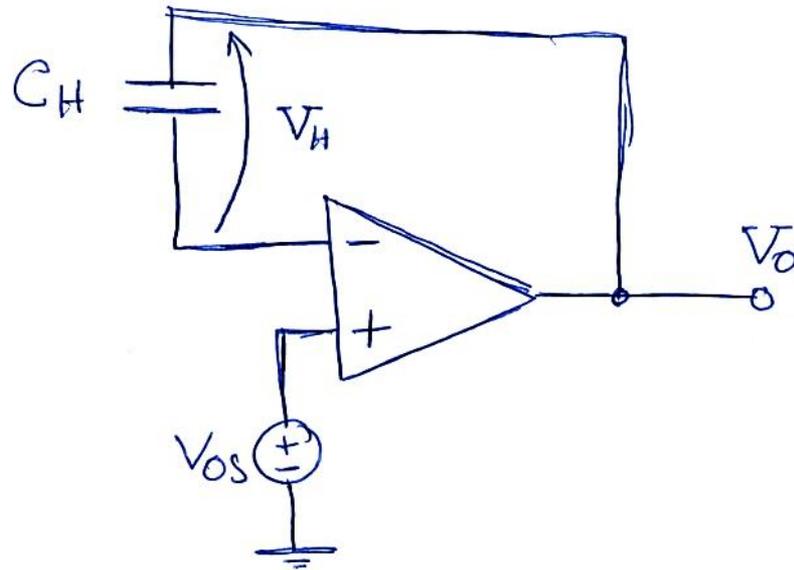


So, I can write,

$$A(V_{OS} - (V_O - (V_{in} - \frac{A}{A+1} V_{OS}))) = V_O \Rightarrow$$

$$V_O = V_{in} - \frac{A}{A+1} V_{OS} - \frac{V_O}{A} + V_{OS}$$

Exercise 2

When Φ_2 is ON:

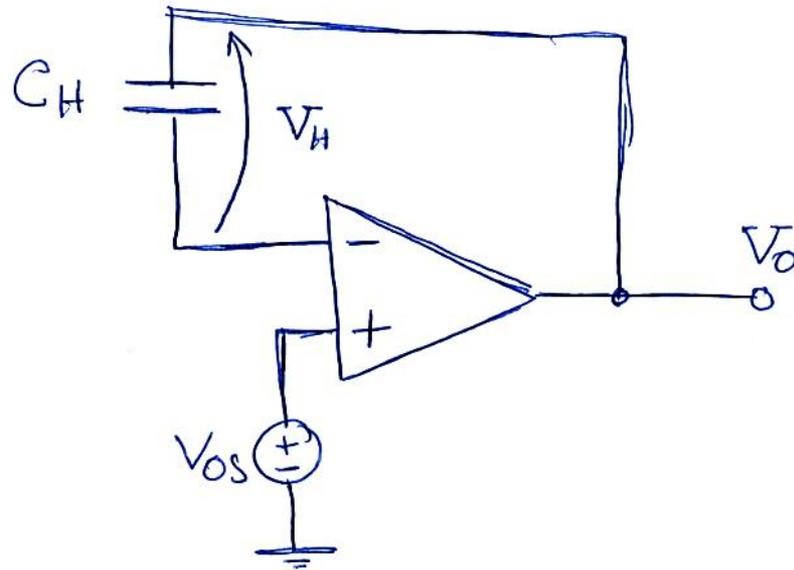

So, I can write,


$$A(V_{OS} - (V_O - (V_{in} - \frac{A}{A+1} V_{OS}))) = V_O \Rightarrow$$

$$V_O = V_{in} - \frac{A}{A+1} V_{OS} - \frac{V_O}{A} + V_{OS}$$

$$V_O(1 + \frac{1}{A}) = V_{in} + \frac{1}{A+1} V_{OS}$$

Exercise 2


When Φ_2 is on:

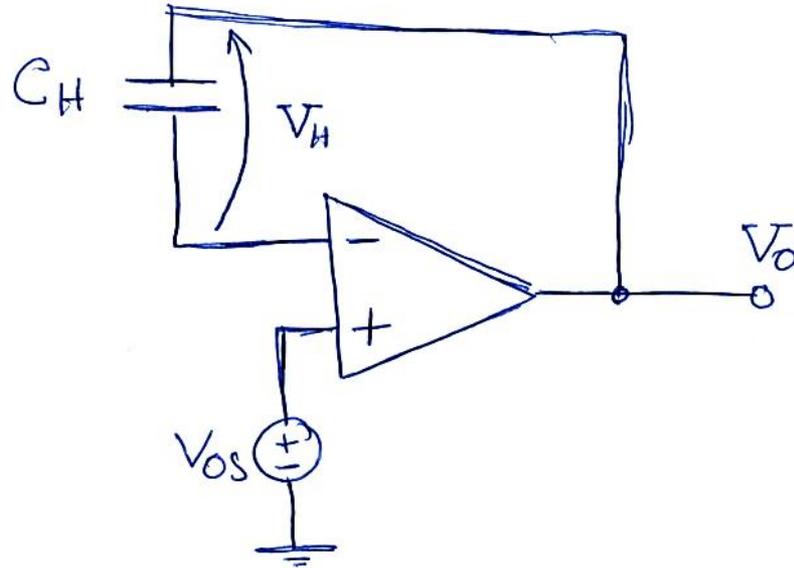

$$V_O = \frac{A}{A+1} V_{in} + \frac{A}{(A+1)^2} V_{OS}$$

Exercise 2

When Φ_2 is on:

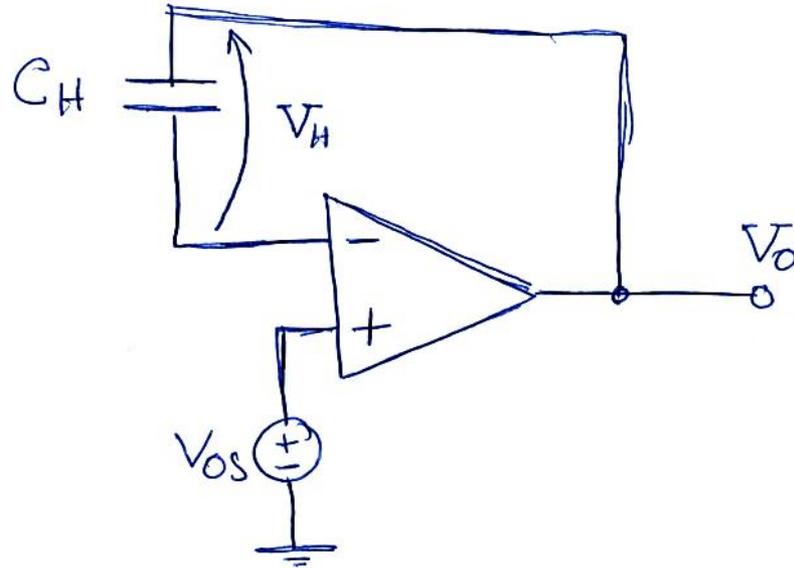

$$V_O = \frac{A}{A+1} V_{in} + \frac{A}{(A+1)^2} V_{OS}$$

if $A \rightarrow \infty \Rightarrow V_O = 1 \times V_{in} + 0 \times V_{OS}$ nice!

Exercise 3,

* Let's denote the "end" of Φ_1 by nT .


* Φ_2 is delayed by T rather Φ_1 .

Exercise 3,

* Let's denote the "end" of Φ_1 by nT .

* Φ_2 is delayed by T rather Φ_1 .

@ $t = nT - T$: Φ_1 is ON

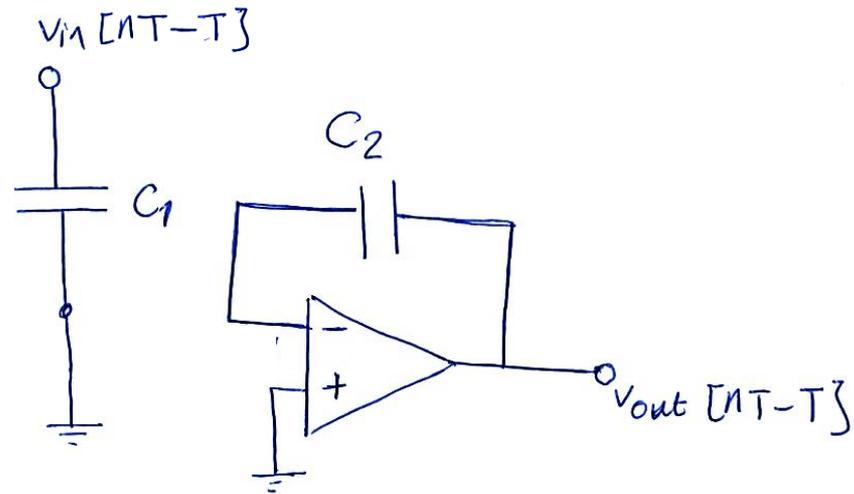


Exercise 3,

* Let's denote the "end" of Φ_1 by nT .

* Φ_2 is delayed by T rather Φ_1 .

@ $t = nT - T$: Φ_1 is ON

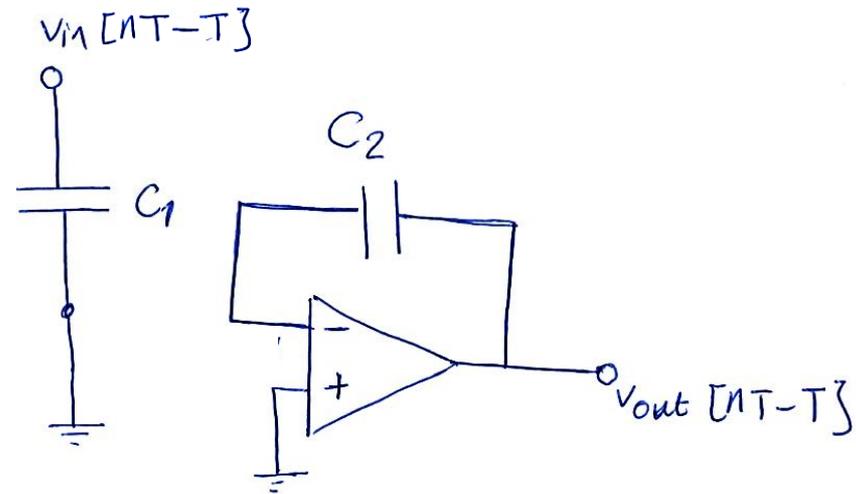


C_1 charged by $V_{in}[nT-T]$

Exercise 3,

* Let's denote the "end" of Φ_1 by nT .

* Φ_2 is delayed by T rather Φ_1 .

@ $t = nT - T$: Φ_1 is ON

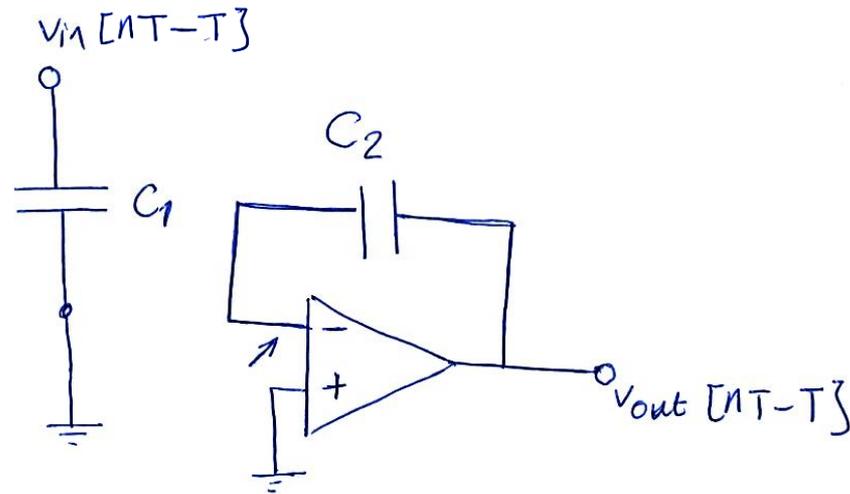


C_1 charged by $V_{in}[nT-T]$

C_2 charged by $V_{out}[nT-T]$

⚠ virtual ground.


Exercise 3,

@ $t = nT$: Φ_2 is ON


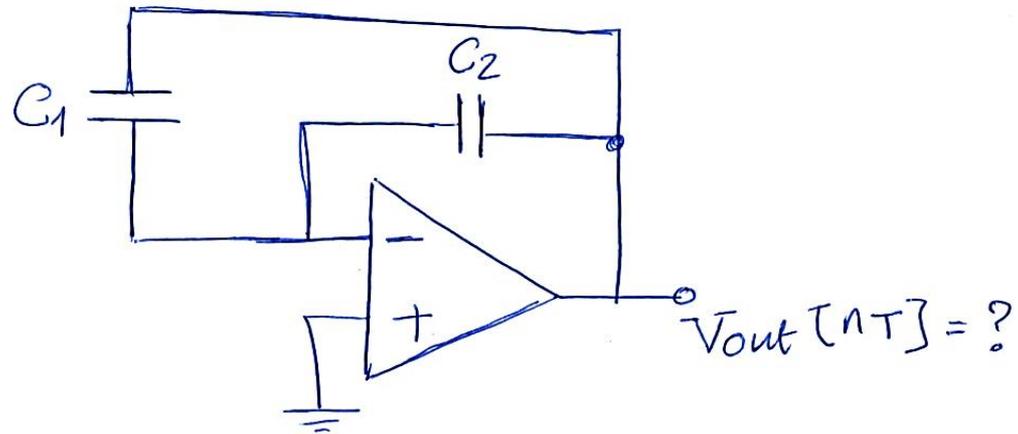


Exercise 3,

@ $t = nT$: Φ_2 is ON

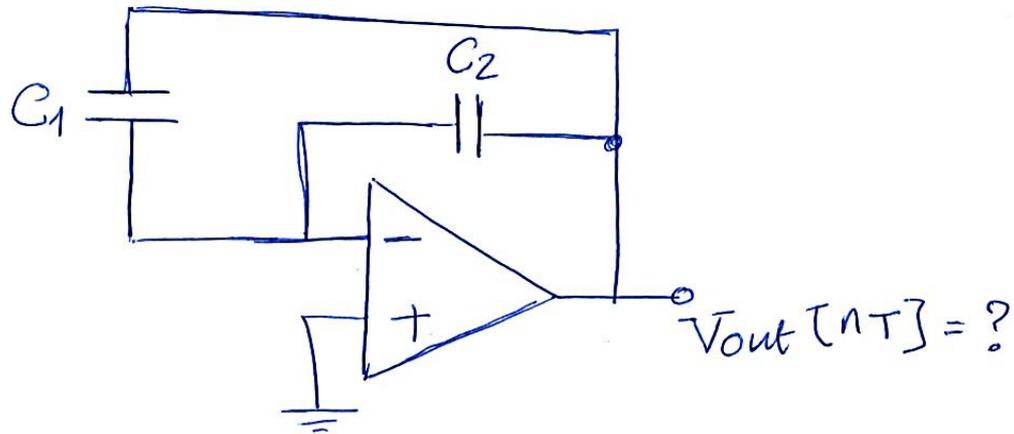


Review:


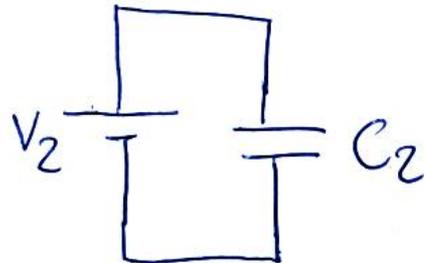
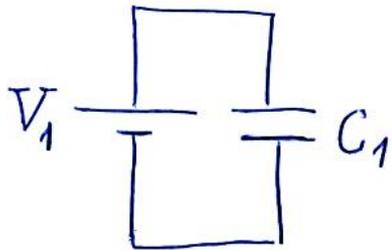


Exercise 3,

@ $t = nT$: Φ_2 is ON

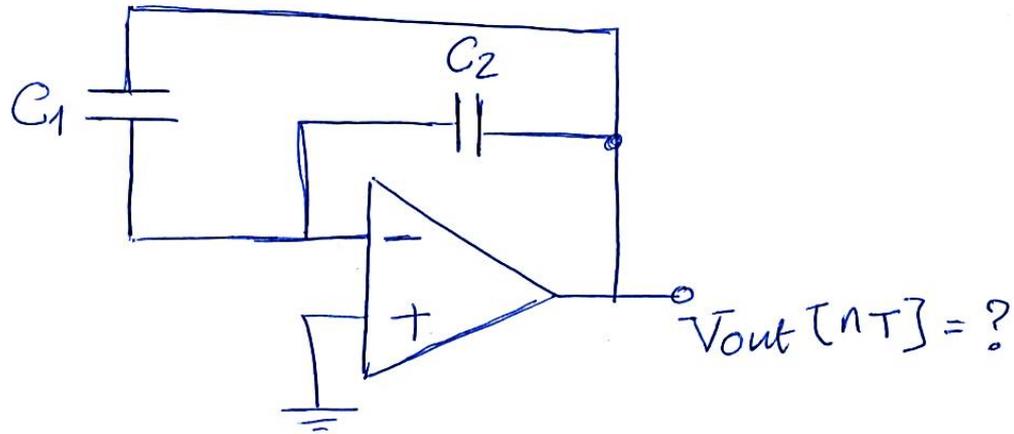

Review:

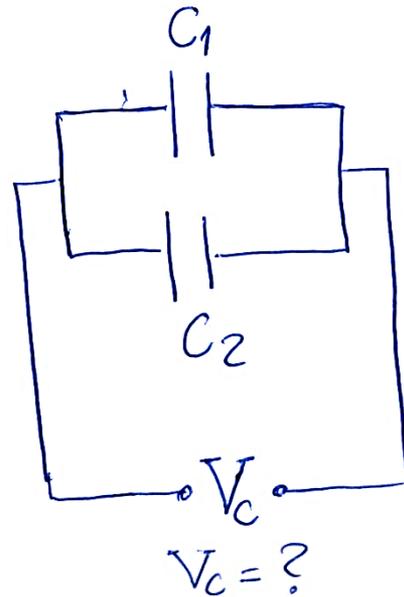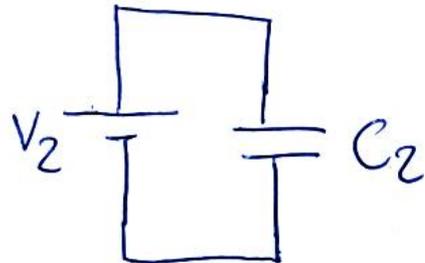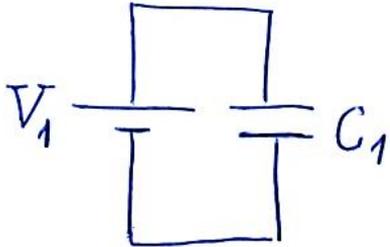

Exercise 3,

Charge Conservation:

$$C_1 V_1 + C_2 V_2 = C_1 V_C + C_2 V_C$$

Exercise 3,

Charge Conservation:

$$C_1 V_1 + C_2 V_2 = C_1 V_C + C_2 V_C \Rightarrow V_C = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$


Exercise 3,

Charge Conservation:

$$C_1 V_1 + C_2 V_2 = C_1 V_C + C_2 V_C \Rightarrow V_C = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

Here is the same:

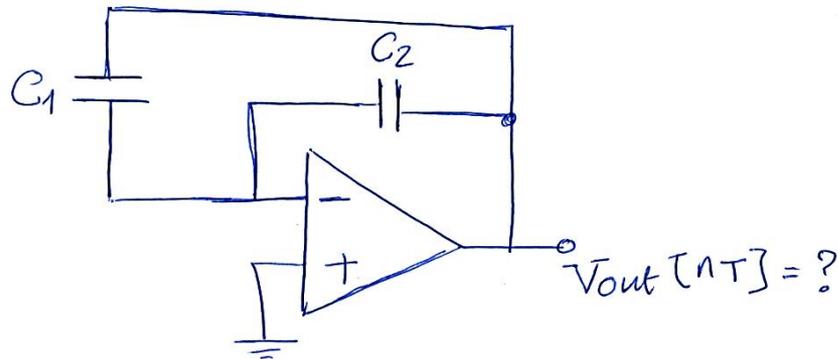C_1 is charged by $V_{in} [nT - T]$, is in parallel with C_2 which is charged by $V_{out} [nT - T]$.




Exercise 3,

Charge Conservation:

$$C_1 V_1 + C_2 V_2 = C_1 V_C + C_2 V_C \Rightarrow V_C = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

Here is the same:

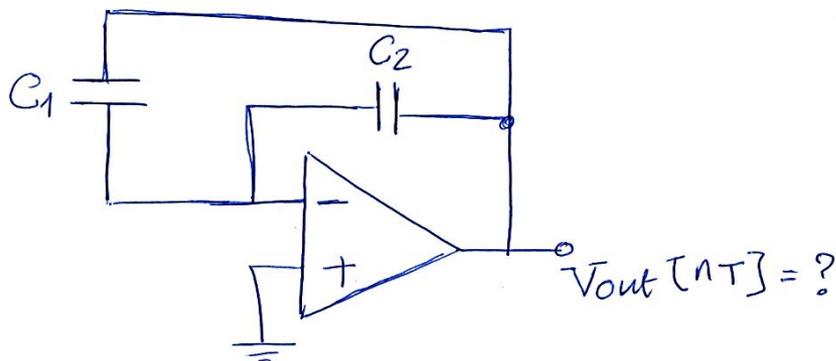C_1 is charged by $V_{in} [NT-T]$, is in parallel with C_2 which is charged by $V_{out} [NT-T]$.



$$V_{out} [NT] = \frac{C_1 V_{in} [NT-T] + C_2 V_{out} [NT-T]}{C_1 + C_2}$$

Exercise 3,

Review:

$$x[n] \xleftrightarrow{zT} X[z]$$

$$x[n-D] \xleftrightarrow{zT} z^{-D} X[z]$$

$$H(z) \xrightarrow{z=e^{j\omega}} H(e^{j\omega})$$

Exercise 3,

We assumed for $\omega T \ll 1$, $z = e^{j\omega T} \approx 1 + j\omega T$
but why? or how?

Exercise 3,

We assumed for $\omega T \ll 1$, $z = e^{j\omega T} \approx 1 + j\omega T$
but why? or how?

Euler Formula:

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Exercise 3,

We assumed for $\omega T \ll 1$, $z = e^{j\omega T} \approx 1 + j\omega T$
but why? or how?

Euler Formula:

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$\text{So, } z = e^{j\omega T} = \cos(\omega T) + j \sin(\omega T)$$

if $\omega T \ll 1$ we can write,

$$z = e^{j\omega T} \approx \cos(0) + j\omega T = 1 + j\omega T$$

Exercise 3,

now, what can I say about Z^{-1} :

$$Z^{-1} = e^{-j\omega T} = \cos(0) - j\omega T = 1 - j\omega T$$

Exercise 3,

now, what can I say about Z^{-1} :

$$Z^{-1} = e^{-j\omega T} = \cos(\omega T) - j\sin(\omega T) \approx 1 - j\omega T$$

so, for the low freq. ($\omega T \ll 1$):

$$\begin{cases} Z = 1 + j\omega T \\ Z^{-1} = 1 - j\omega T \end{cases}$$

Exercise 3,

$$V_{out}[NT] = \frac{C_1 V_{in}[NT-T] + C_2 V_{out}[NT-T]}{C_1 + C_2}$$

if we take ZT from both sides,

Exercise 3,

$$V_{out}[nT] = \frac{C_1 V_{in}[nT-T] + C_2 V_{out}[nT-T]}{C_1 + C_2}$$

if we take zT from both sides,

$$(C_1 + C_2)V_{out}[z] = C_2 z^{-1} V_{out}[z] + C_1 z^{-1} V_{in}[z]$$

$$\Rightarrow \frac{V_{out}[z]}{V_{in}[z]} = \frac{z^{-1}}{1 + \frac{C_2}{C_1}(1 - z^{-1})}$$

Exercise 3,

$$\frac{V_{out}[z]}{V_{in}[z]} = \frac{z^{-1}}{1 + \frac{C_2}{C_1}(1 - z^{-1})}$$

Substituting:

$$z = e^{j\omega T} \approx 1 + j\omega T$$

$$z^{-1} = e^{-j\omega T} \approx 1 - j\omega T$$

Exercise 3,

$$\frac{V_{out}[z]}{V_{in}[z]} = \frac{z^{-1}}{1 + \frac{C_2}{C_1}(1-z^{-1})}$$

Substituting:

$$z = e^{j\omega T} \approx 1 + j\omega T$$

$$z^{-1} = e^{-j\omega T} \approx 1 - j\omega T$$

$$\frac{V_o(e^{j\omega T})}{V_{in}(e^{j\omega T})} = \frac{1 - j\omega T}{1 + j\omega \frac{C_2}{C_1} T}$$

Exercise 3,

What is the f_{3dB} Cutoff Freq. of a LP Filter?

Exercise 3,

What is the f_{3dB} Cutoff Freq. of a LP Filter?

The cut off freq. is defined as the freq. where the amplitude of $H(e^{j\omega})$ is $\frac{1}{\sqrt{2}}$ times the DC amplitude (approximately -3dB, half power).

i.e.

$$|H(e^{j\omega_c})| = \frac{1}{\sqrt{2}} \cdot |H(e^{j0})|$$

Exercise 3,

$$H(e^{j\omega}) = \frac{1 - j\omega T}{1 + j\omega C_2 / C_1 T}$$

Exercise 3,

$$H(e^{j\omega}) = \frac{1 - j\omega T}{1 + j\omega C_2/C_1 T}$$

$$\frac{\sqrt{1 + \omega_c^2 T^2}}{\sqrt{1 + \omega_c^2 T^2 (C_2/C_1)^2}} = \frac{1}{\sqrt{2}} \cdot 1 \Rightarrow 1 + \omega_c^2 T^2 (C_2/C_1)^2 = 2 + \omega_c^2 T^2 \Rightarrow$$

Exercise 3,

$$H(e^{j\omega}) = \frac{1 - j\omega T}{1 + j\omega C_2/C_1 T}$$

$$\frac{\sqrt{1 + \omega_c^2 T^2}}{\sqrt{1 + \omega_c^2 T^2 (C_2/C_1)^2}} = \frac{1}{\sqrt{2}} \cdot 1 \Rightarrow 1 + \omega_c^2 T^2 (C_2/C_1)^2 = 2 + \omega_c^2 T^2 \Rightarrow$$

$$(\omega_c^2 T^2) ((C_2/C_1)^2 - 1) = 1 .$$

Exercise 3,

$$H(e^{j\omega}) = \frac{1 - j\omega T}{1 + j\omega C_2/C_1 T}$$

$$\frac{\sqrt{1 + \omega_c^2 T^2}}{\sqrt{1 + \omega_c^2 T^2 (C_2/C_1)^2}} = \frac{1}{\sqrt{2}} \cdot 1 \Rightarrow 1 + \omega_c^2 T^2 (C_2/C_1)^2 = 2 + \omega_c^2 T^2 \Rightarrow$$

$$(\omega_c^2 T^2) ((C_2/C_1)^2 - 1) = 1. \quad \text{assume } (C_2/C_1)^2 \gg 1 \Rightarrow$$

Exercise 3,

$$H(e^{j\omega}) = \frac{1 - j\omega T}{1 + j\omega C_2/C_1 T}$$

$$\frac{\sqrt{1 + \omega_c^2 T^2}}{\sqrt{1 + \omega_c^2 T^2 (C_2/C_1)^2}} = \frac{1}{\sqrt{2}} \cdot 1 \Rightarrow 1 + \omega_c^2 T^2 (C_2/C_1)^2 = 2 + \omega_c^2 T^2 \Rightarrow$$

$$(\omega_c^2 T^2) ((C_2/C_1)^2 - 1) = 1. \quad \text{assume } (C_2/C_1)^2 \gg 1 \Rightarrow$$

$$\omega_c^2 T^2 (C_2/C_1)^2 = 1 \Rightarrow \omega_c = C_1/C_2 \frac{1}{T} \Rightarrow \omega_c = C_1/C_2 f_{clk} \Rightarrow$$

Exercise 3,

$$H(e^{j\omega}) = \frac{1 - j\omega T}{1 + j\omega C_2/C_1 T}$$

$$\frac{\sqrt{1 + \omega_c^2 T^2}}{\sqrt{1 + \omega_c^2 T^2 (C_2/C_1)^2}} = \frac{1}{\sqrt{2}} \cdot 1 \Rightarrow 1 + \omega_c^2 T^2 (C_2/C_1)^2 = 2 + \omega_c^2 T^2 \Rightarrow$$

$$(\omega_c^2 T^2) ((C_2/C_1)^2 - 1) = 1. \quad \text{assume } (C_2/C_1)^2 \gg 1 \Rightarrow$$

$$\omega_c^2 T^2 (C_2/C_1)^2 = 1 \Rightarrow \omega_c = C_1/C_2 \frac{1}{T} \Rightarrow \omega_c = C_1/C_2 f_{clk} \Rightarrow$$

$$2\pi f_{3dB} = C_1/C_2 f_{clk} \Rightarrow f_{3dB} = \frac{1}{2\pi} C_1/C_2 f_{clk}$$