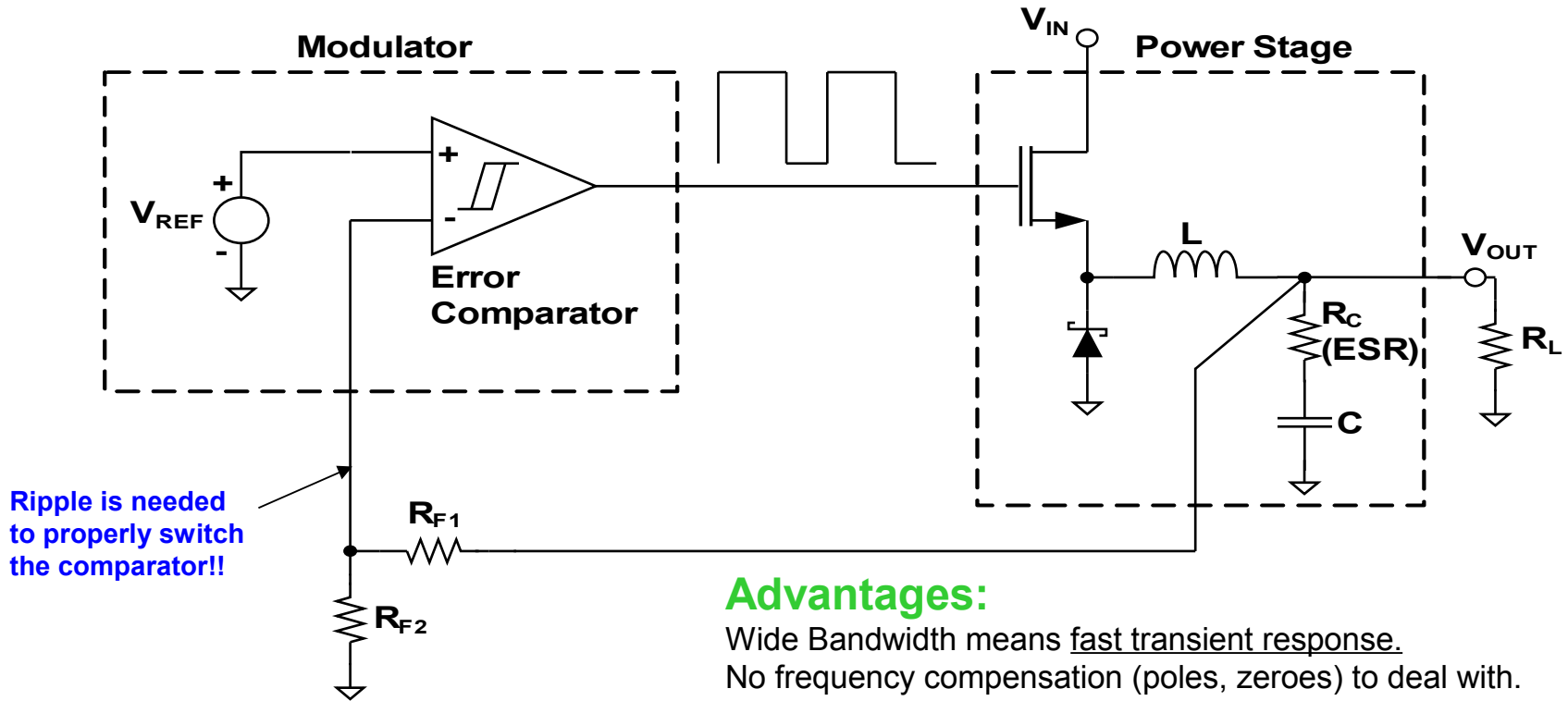


Hysteretic Buck Regulators



Disadvantages:


t_{ON} and t_{OFF} , and therefore the frequency, are functions of:

V_{IN} , V_{OUT} , I_L , L , ESR , ESL , $V_{HYS} \cdot (R_{F1} + R_{F2}) / R_{F2}$, and t_d

→ **Frequency is difficult to control!!**

Constant On-Time (COT) Hysteretic Regulator

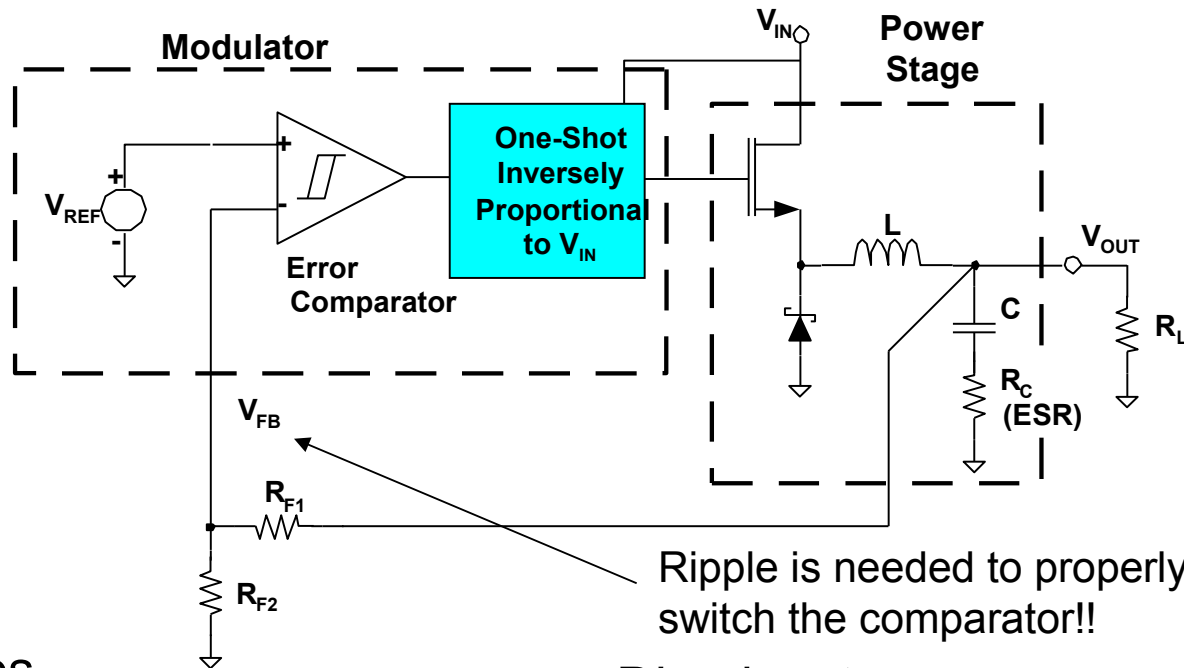ON-time is constant, for a given V_{IN} , as load current varies.



- **Advantages**

1. Constant frequency vs V_{IN}
2. High Efficiency at light load
3. Fast transient response


- **Disadvantages**

1. Requires ripple at feedback comparator
2. Sensitive to output noise, because it translates to feedback ripple

COT regulation with V_{IN} Feedforward

Definition of Duty Cycle:

EQ1

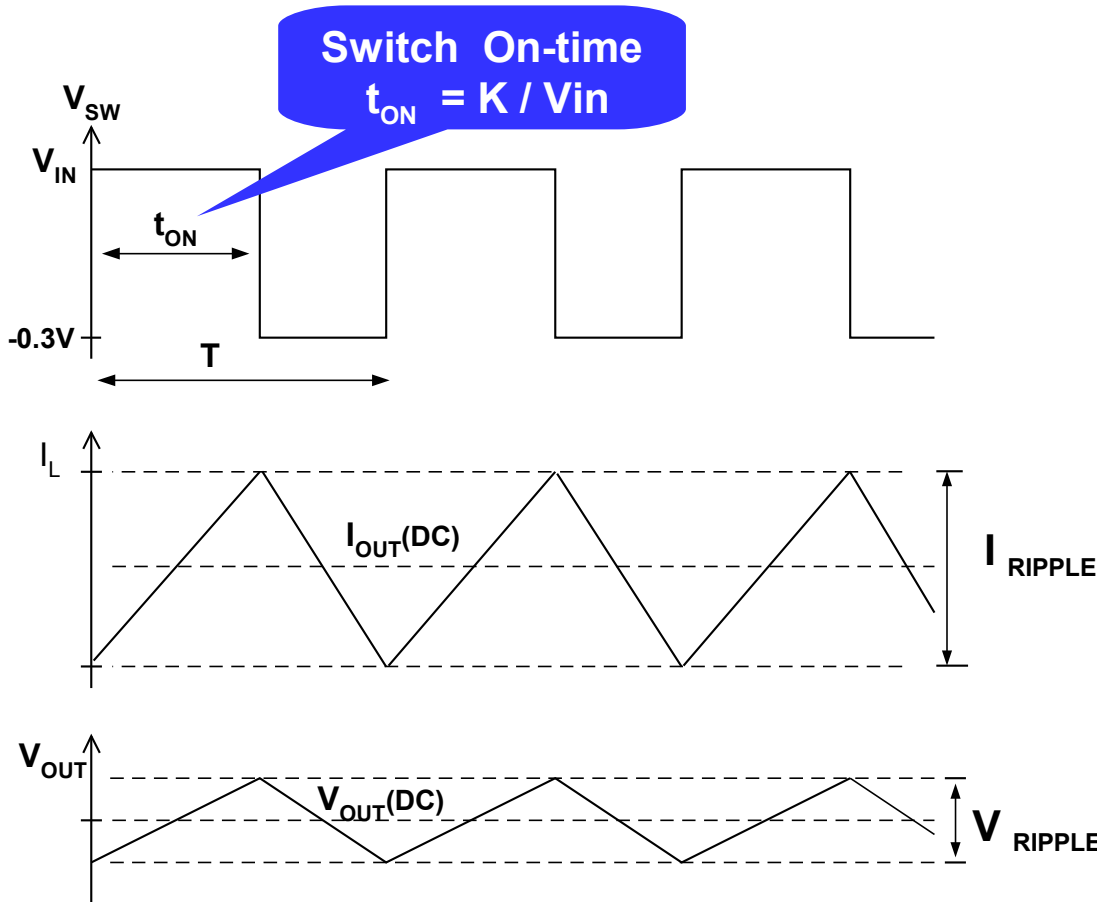

For Buck Regulator:

$$D = \frac{V_{OUT}}{V_{IN}}$$

EQ2

Setting EQ1 = EQ2:

$$t_{ON} \cdot f_{SW} = \frac{V_{OUT}}{V_{IN}}$$

EQ3

For COT with Feed-forward:

$$t_{ON} = \frac{K \cdot R_{ON}}{V_{IN}}$$

K is a constant = 1.3×10^{-10}

EQ4

Insert EQ4 in EQ3:


$$\frac{K \cdot R_{ON}}{V_{IN}} \cdot f_{SW} = \frac{V_{OUT}}{V_{IN}}$$

Solve for f_{SW} :

$$f_{SW} = \frac{V_{OUT}}{K \cdot R_{ON}}$$

Frequency is constant
for constant V_{OUT}

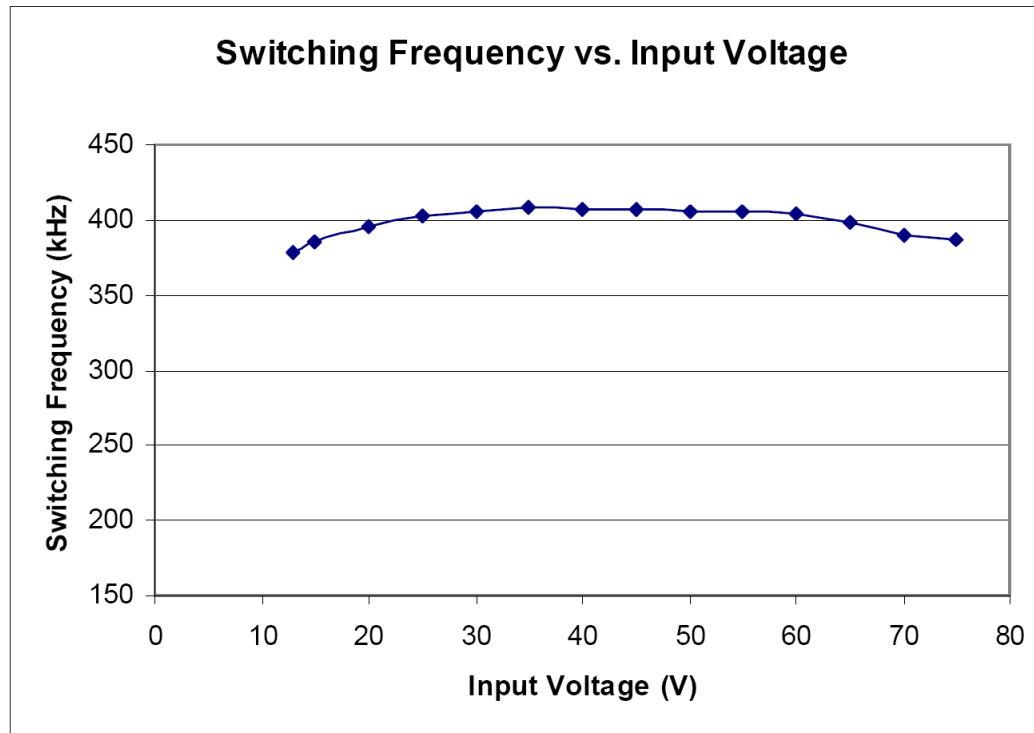
Constant ON-Time Achieves Nearly Constant Frequency



Switching frequency is almost constant; the variations are due to effects of R_{DS-ON} , diode voltage and input impedance of the R_{on} pin

Note: A resistor from V_{IN} to R_{on} sets the ON-time

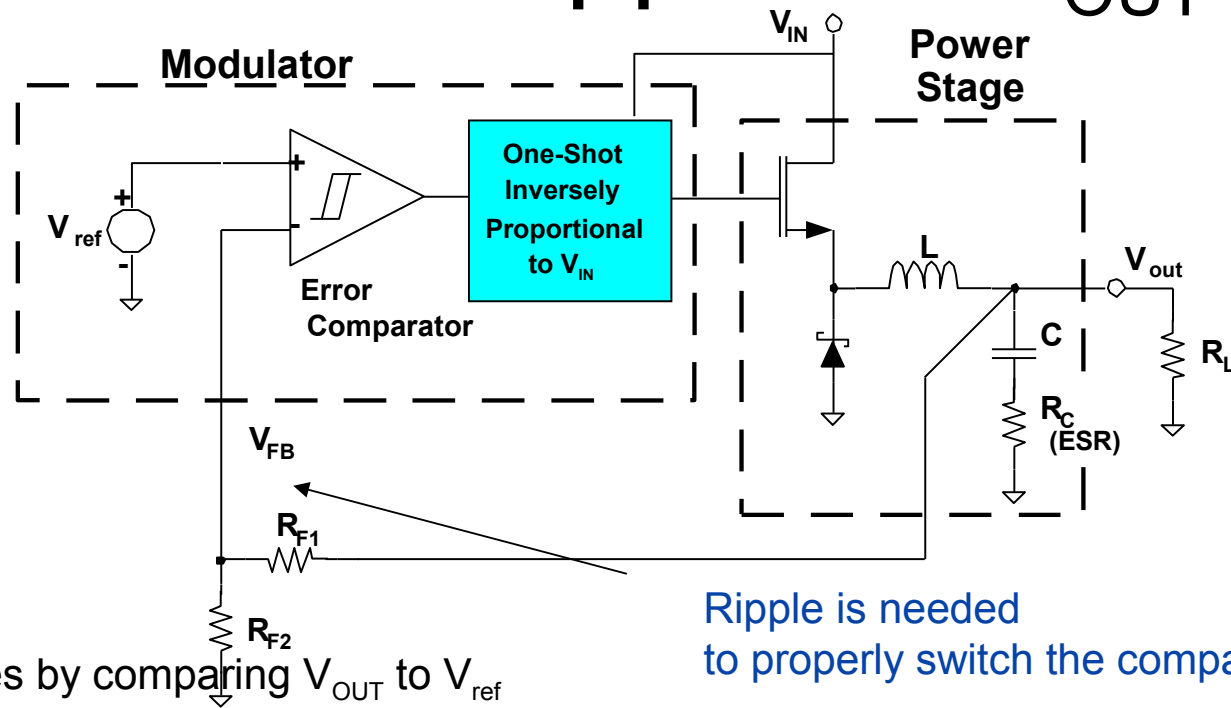COT needs ESR for Sufficient Ripple on V_{OUT}




- COT regulates by comparing V_{OUT} to V_{ref}
- V_{OUT} ripple must be large enough to overcome the comparator hysteresis
- ESR of output capacitor is directly proportional to V_{OUT} ripple
- ESR must be large enough to create sufficient V_{OUT} ripple to properly switch the comparator

New Emulated Ripple Mode (ERM) Constant-On-Time

New patented ERM technology allows COT regulators to:

- Eliminate the need for large output ripple
- Eliminate the need for high ESR output capacitor
- Allows the use of smaller, less expensive ceramic capacitors

How does it work?

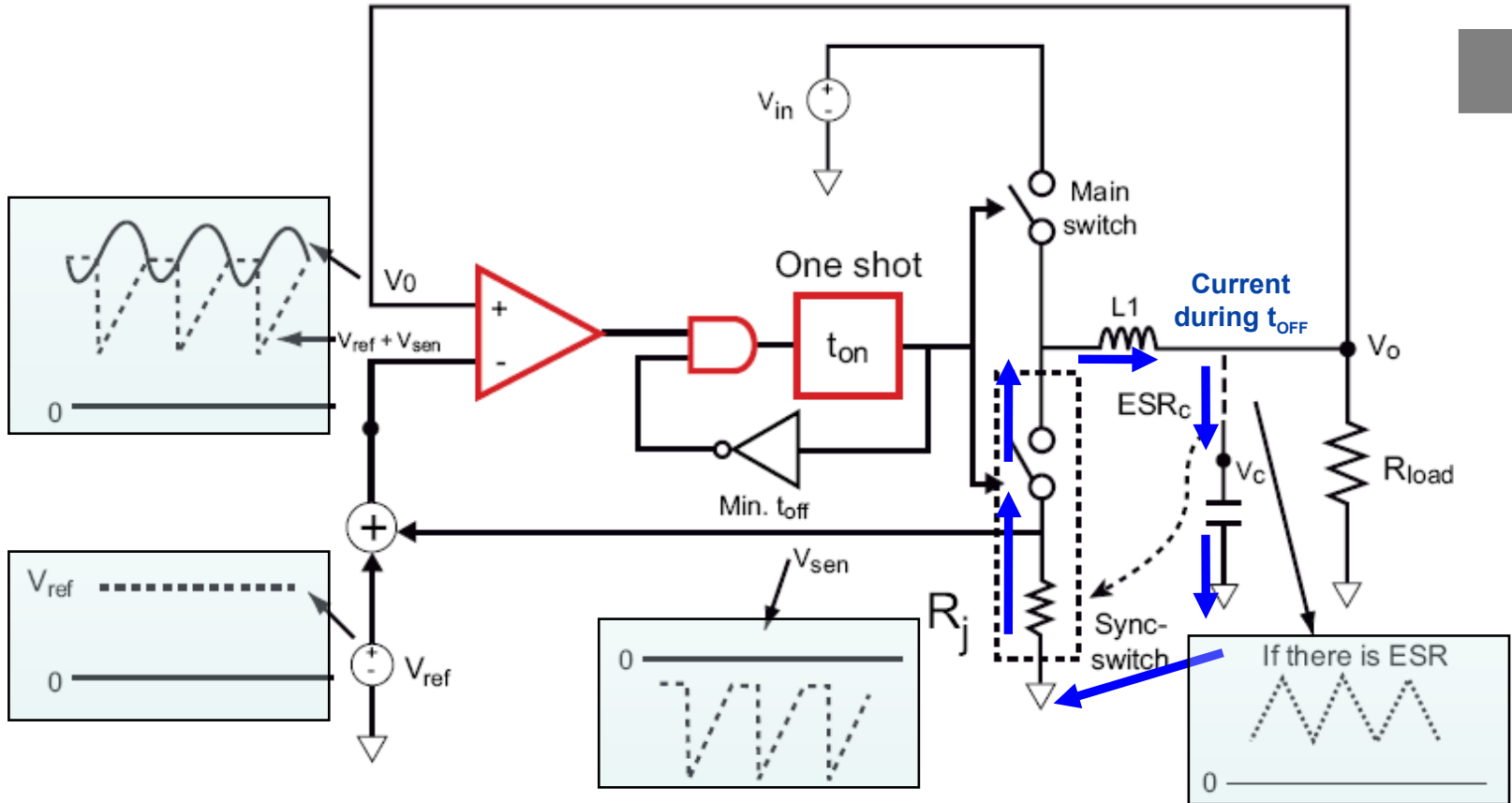

- ESR current can be sensed through R_j (R_{DS_ON} of the Low Side Mosfet)
- The inverted V_{SEN} is the replication of V_{ESR} ripple during t_{OFF}
- This is added to the DC reference voltage V_{ref} before comparing to V_{OUT}
- No ESR is required on the output capacitor

New ERM Constant-On-Time Allows Use of Ceramic Capacitors

Benefits of Ceramic Capacitors:

Clean Output Voltage

- Low Output Ripple
- comparable to voltage-mode and current-mode control schemes

Low profile and small size

- Can reduce required output ESR $\sim 1/3$
- Save PCB area

Not sensitive to Transient Voltage Stress

- Higher reliability

No polarity – ease for production

Summary of Advantages of Constant On Time with ERM

- No loop compensation needed
 - Low external component count
 - Excellent transient response
 - Lower cost
 - Easy to use
 - Reliable
- Operates in fixed frequency mode
 - External discrete component values don't affect frequency
 - Reliable/Robust Operation
 - Makes design easier
- Emulated Ripple Mode (ERM) Circuitry
 - **Allows the use of low ESR output capacitors without additional ESR compensation**
 - Lower output ripple
 - Smaller size (ceramic caps)
 - Lower cost