



# Electromagnetic Energy Conversion

## ELEC0431

Introduction to exercise sessions  
& Exercise session 1: Reminders

11 February 2022

Florent Purnode – Nicolas Davister

Montefiore Institute, Department of Electrical Engineering and Computer Science,  
University of Liège, Belgium

# Contact and organisation

Florent Purnode

- mail: `florent.purnode@uliege.be`
- office: I 158 in Montefiore Institute

Nicolas Davister

- mail: `ndavister@uliege.be`
- office: I 157 in Montefiore Institute


Exercise sessions on Friday mornings from 10.30 to 12.30 am.

Slides/exercise manual will be uploaded on the on the webpage of the course.

# Laboratory sessions

4 sessions:

- Session 1: Transformers
- Session 2: AC synchronous machines
- Session 3: AC asynchronous machines
- Session 4: DC machines

The lab sessions are (so far ) organized face-to-face. The lab manual will be available on the webpage of the course. More information later...

# Reminders

---

Phasors and power in sinusoidal steady state

# Introduction to the RMS value

- Dissipated power with DC current:

$$P = R I^2$$

- Dissipated power with AC current:

$$P(t) = Z i(t)^2 \quad \Rightarrow \quad P_{mean} = R \frac{1}{T} \int_0^T i(t)^2 dt = R \left( \underbrace{\sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}}_{I_{RMS}} \right)^2 = R I_{RMS}^2$$

The **R**oot **M**ean **S**quare value (or **effective** value) is equal to the value of the constant direct current (voltage) that would produce the **same power dissipation** in a resistive load.

# RMS value and harmonic signal

$$F_{RMS} := \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$$

For a harmonic function with frequency  $f$ , pulsation  $\omega = 2\pi f$  and period  $T = \frac{1}{f}$ :

$$f(t) = F_{max} \cos(\omega t)$$

$$\begin{aligned} F_{RMS} &= \sqrt{\frac{1}{T} \int_0^T F_{max}^2 \cos^2(\omega t) dt} = \sqrt{\frac{F_{max}^2}{T} \int_0^T \cos^2(\omega t) dt} \\ &= \sqrt{\frac{F_{max}^2}{T} \frac{T}{2}} = \frac{F_{max}}{\sqrt{2}} \end{aligned}$$

# Important note about notations


## Remark:

The following conventions will be used in the rest of the course for RMS and max/peak values:

$$F_{RMS} \Rightarrow F$$

$$F_{max} \Rightarrow F_m$$

# Introduction to phasors

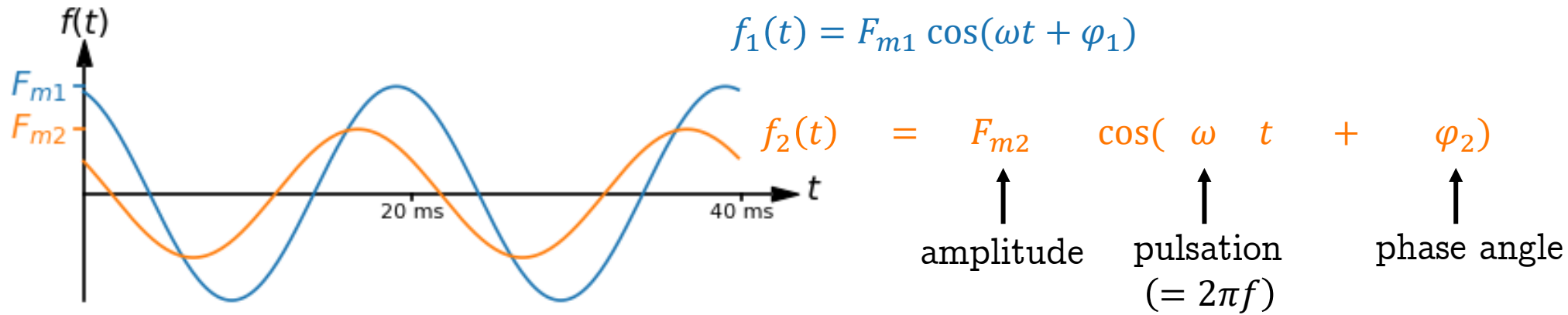

For a given frequency, the values of  $F_m$  and  $\varphi$  completely define the functions. The time evolution is not of interest → higher level representation: the **phasor**.


$$\begin{aligned}
 f(t) &= \sqrt{2} F \cos(\omega t + \varphi) \\
 &= \Re(\sqrt{2} F e^{j(\omega t + \varphi)}) \\
 &= \Re(\underbrace{\sqrt{2} F e^{j\varphi}}_{\bar{F}} e^{j\omega t})
 \end{aligned}$$

$\bar{F}$  is the phasor of  $f(t)$ .

It is a complex number, with its amplitude and its phase angle.





# Phasor diagrams

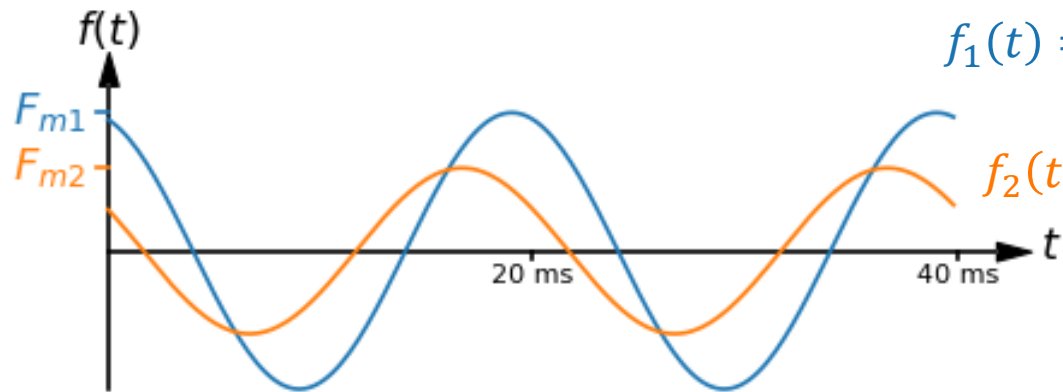

$$f_1(t) = F_{m1} \cos(\omega t + \varphi_1)$$

$$f_2(t) = F_{m2} \cos(\omega t + \varphi_2)$$

Phasor  
diagram

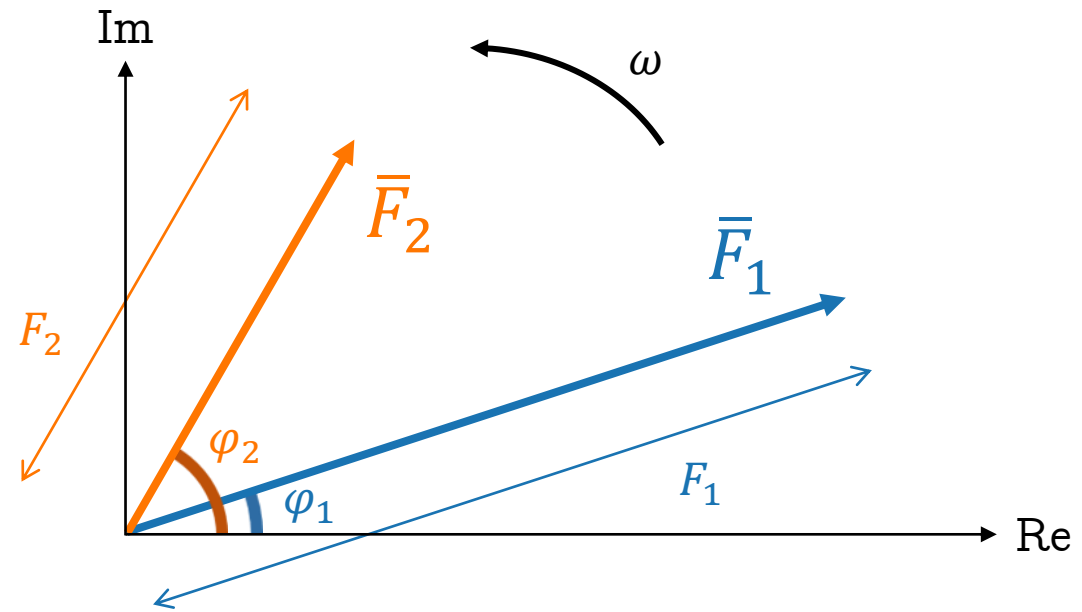 

# Phasor properties

The main assumptions of the phasor approximation are a constant frequency and linearity.

Linearity ensured as Kirchhoff's laws and differential equations are linear.

Time domain

Frequency domain

$f(t)$	$\longleftrightarrow$	$\bar{F}$
$a f(t) + b g(t)$	$\longleftrightarrow$	$a \bar{F} + b \bar{G}$
$\frac{d}{dt}$	$\longleftrightarrow$	$j\omega$
$\int \cdot dt$	$\longleftrightarrow$	$\frac{1}{j\omega}$

# Application of the phasors

The concept of phasor can be applied to electrical quantities such as voltages and currents:

Time domain

---

$$v(t) = \sqrt{2} V \cos(\omega t + \theta)$$

$$i(t) = \sqrt{2} I \cos(\omega t + \psi)$$





Frequency domain

---


$$\bar{V} = V e^{j\theta}$$

$$\bar{I} = I e^{j\psi}$$

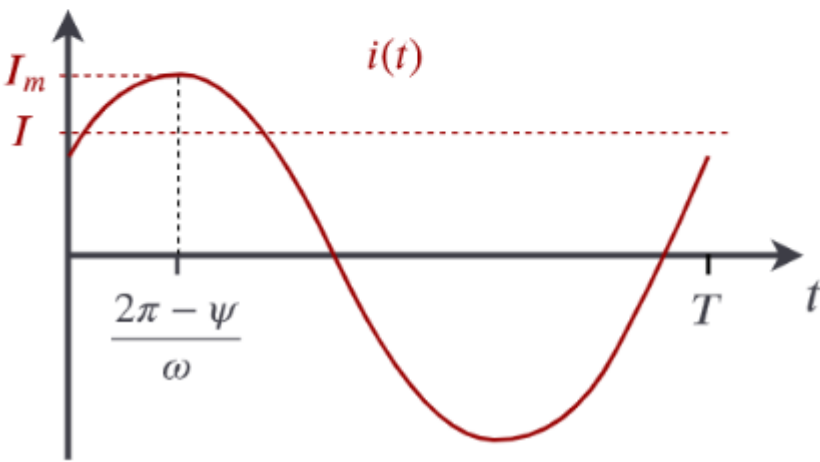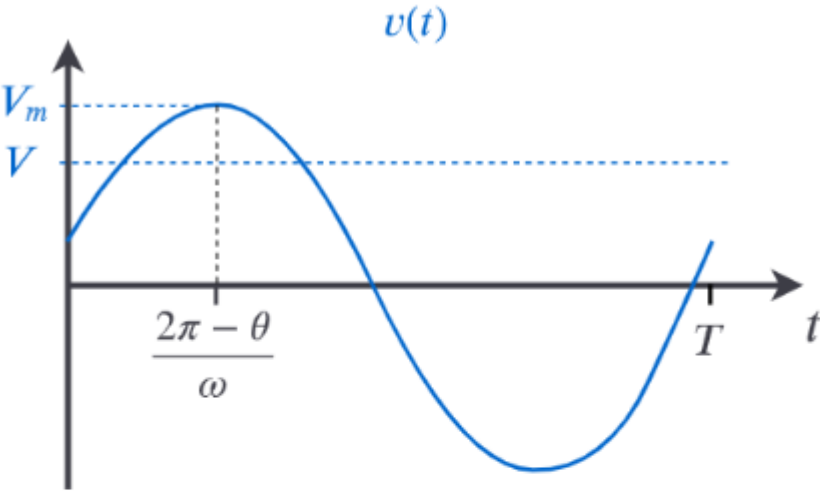
# Alternating voltages and currents – Phasor diagrams



⇔

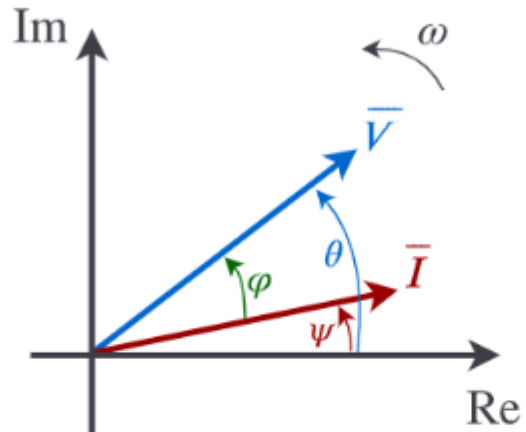

commonly

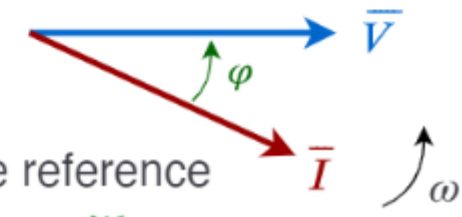

Consider  $\bar{V}$  as the reference with  $\theta = 0$  and  $\varphi = -\psi$

# Product of 2 harmonic functions → instantaneous power




$$p(t) = i(t)v(t)$$



Development on the board

$$p(t) = I V \cos(\theta - \psi) + I V \cos(2\omega t + \psi + \theta)$$
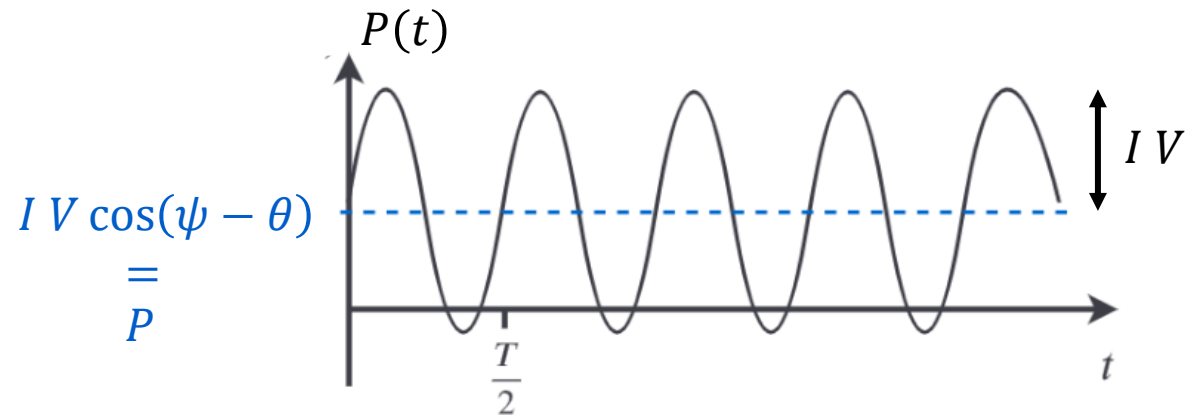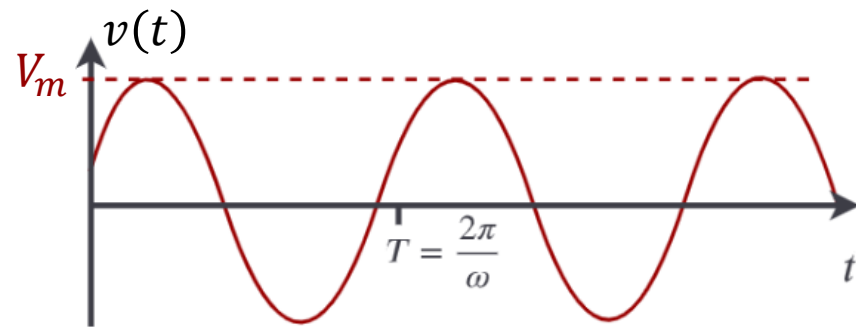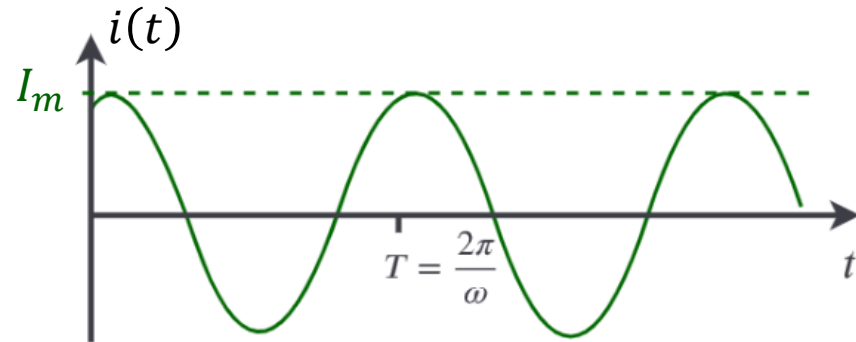
# Product of 2 harmonic functions → instantaneous power



$$p(t) = \underbrace{I V \cos(\theta - \psi)}_{\substack{\text{DC component} \\ = \\ P \\ = \\ \text{Active power}}} + \underbrace{I V \cos(2\omega t + \psi + \theta)}_{\substack{\text{AC component} \\ \text{with double frequency}}}$$

# Power components

$$p(t) = I V \cos(\theta - \psi) + I V \cos(2\omega t + \psi + \theta)$$



Development on the board

$$p(t) = \underbrace{I V \cos(\theta - \psi)} [1 + \cos(2(\omega t + \theta))] + \underbrace{I V \sin(\theta - \psi)} \sin(2(\omega t + \theta))$$


P, the active power

Q, the reactive power

---


Power in the frequency domain  $\rightarrow$  complex power S

$$S = \bar{V} \bar{I}^*$$

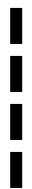

Development on the board
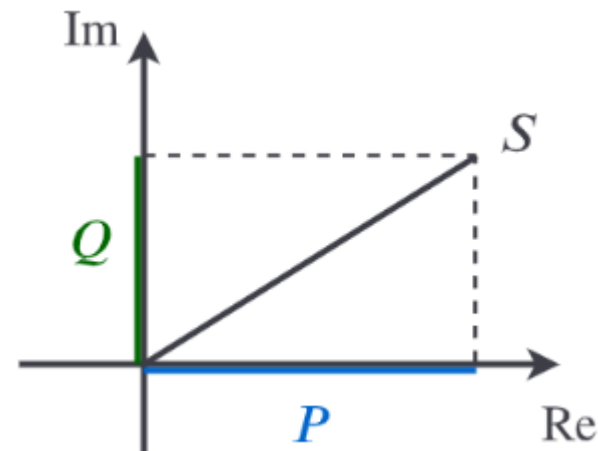
$$S = I V \cos(\theta - \psi) + j I V \sin(\theta - \psi)$$



# Power components

$$S = \bar{V} \bar{I}^*$$

$$= P + j Q$$



Based on that definition, one also defines the apparent power as the norm of the complex power:

$$|S| = \sqrt{P^2 + Q^2} = V I$$




# Power reference of the one-port (“le dipole”)

The signal  $v(t)$  is the voltage across the one-port.

The signal  $i(t)$  is the current through the one-port.

## The “motor” convention

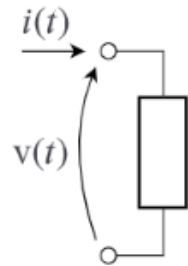


$$i(t) > 0$$

when it enters by the top of the one-port.

$$p(t) = v(t) i(t)$$

is the instantaneous power absorbed by the one-port.

## The “generator” convention

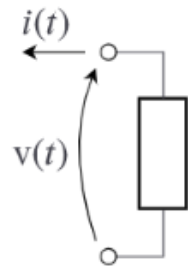

$$i(t) > 0$$



when it leaves by the top of the one-port.

$$p(t) = v(t) i(t)$$

is the instantaneous power produced by the one-port.

# Consumer or producer

"Motor" convention :

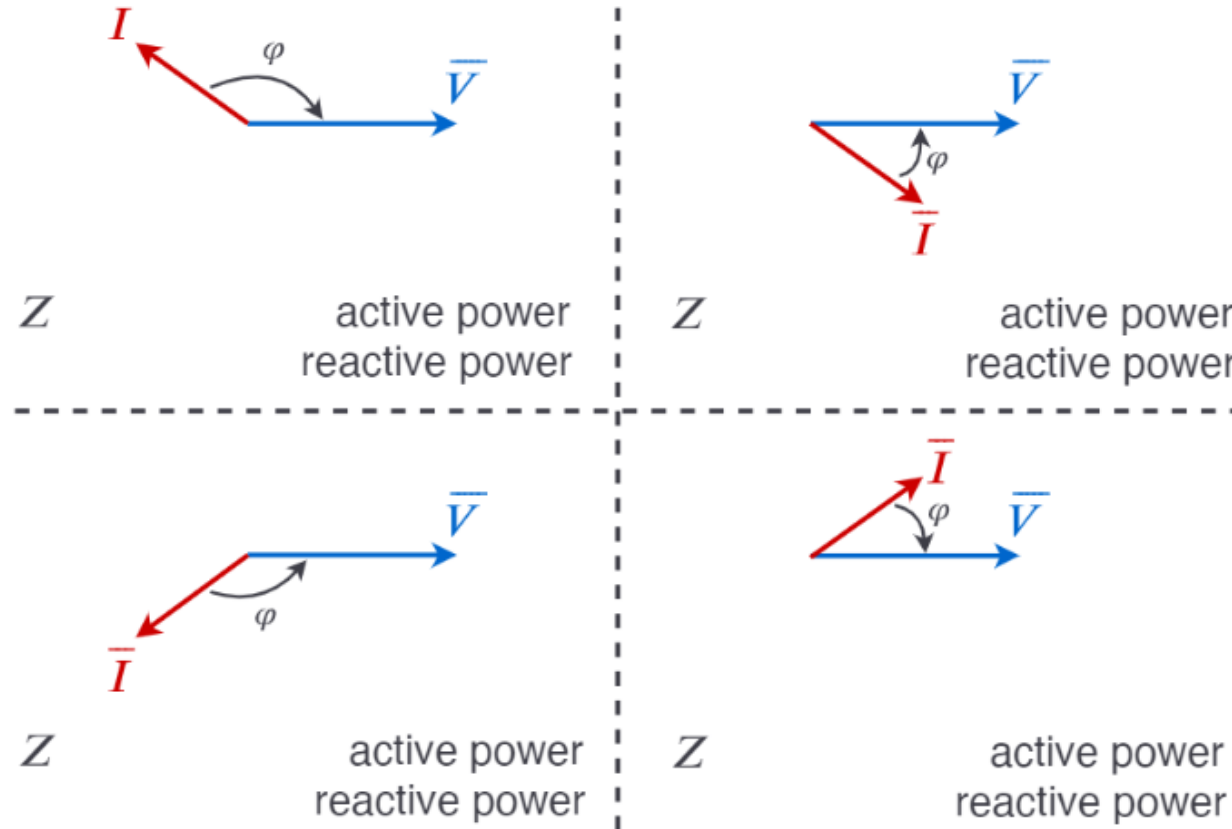
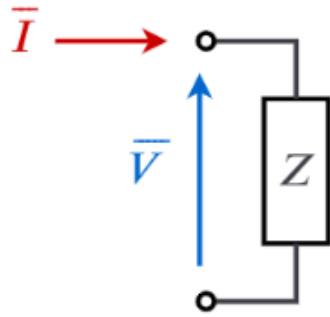


When  $|\varphi| < \frac{\pi}{2}$  : The load ..... active power (  $\cos(\varphi) > 0$  )

When  $\underbrace{\varphi > 0}_{(\bar{I} \text{ is lagging } \bar{V})}$  : The load ..... reactive power (  $\sin(\varphi) > 0$  )

# Consumer or producer (solution)

"Motor" convention :

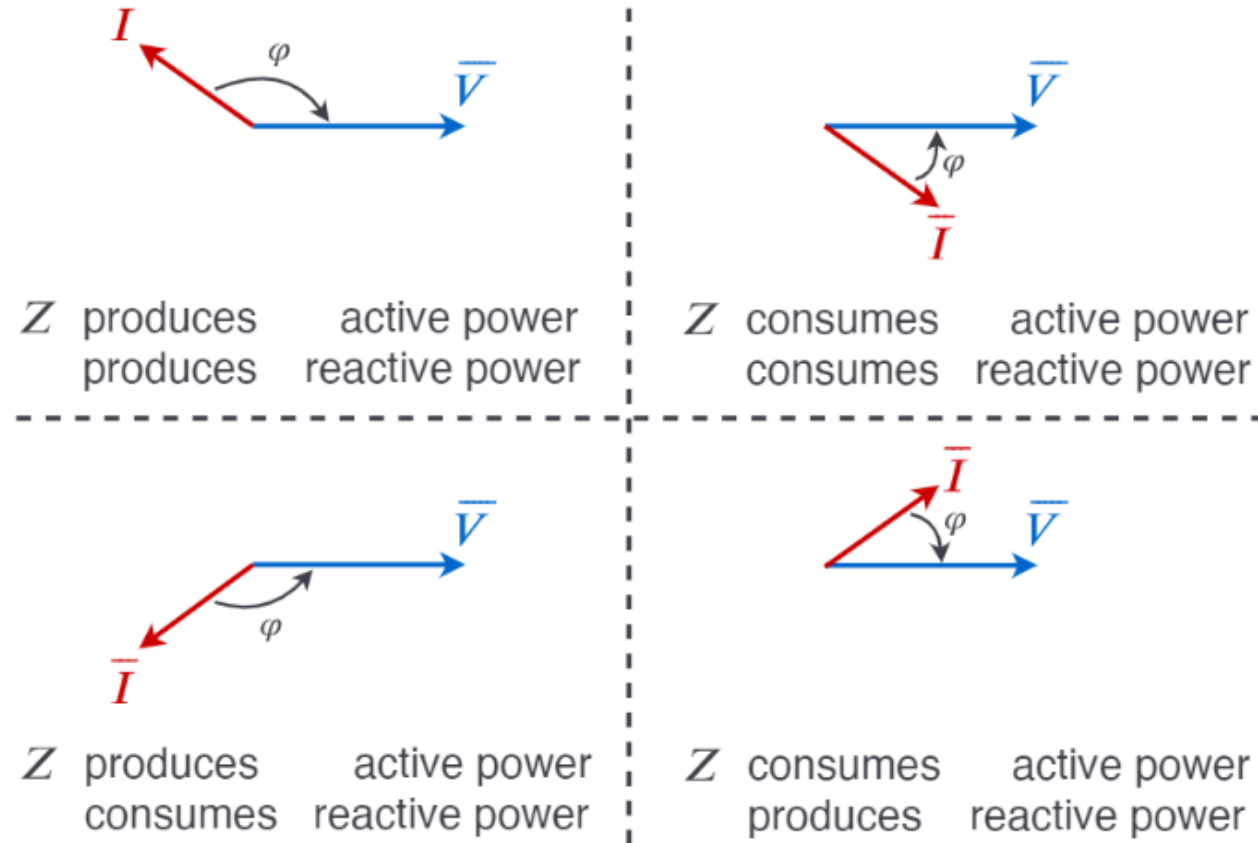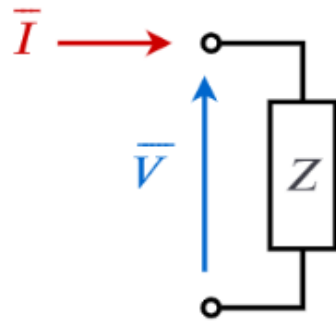

When  $|\varphi| < \frac{\pi}{2}$  : The load consumes active power ( $\cos(\varphi) > 0$ )


When  $\varphi > 0$  : The load consumes reactive power ( $\sin(\varphi) > 0$ )  
 ( $\bar{I}$  is lagging  $\bar{V}$ )

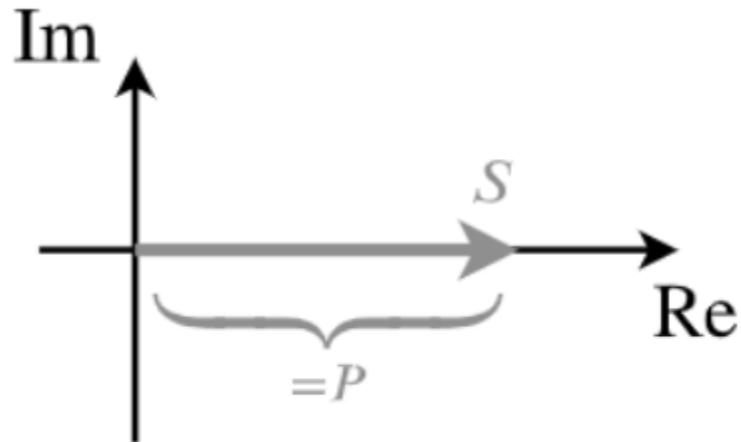
# Complex power and phasors for a resistor

$$\bar{V} = Z \bar{I} \quad \& \quad Z = R$$



$$\Rightarrow S = \bar{V} \bar{I}^* = R \bar{I} \bar{I}^* = R I^2$$





 Only active power
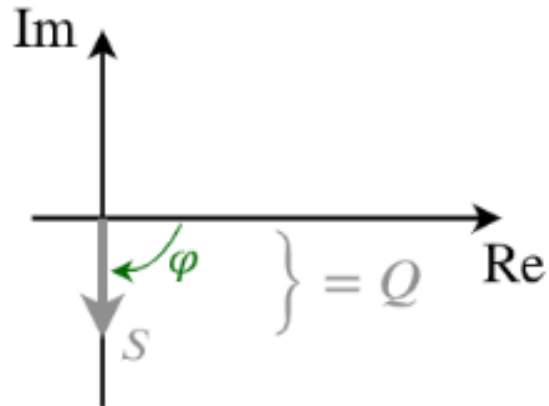
# Complex power and phasors for a capacitor

$$\bar{V} = Z \bar{I} \quad \& \quad Z = \frac{1}{j\omega C}$$

$$\Rightarrow S = \bar{V} \bar{I}^* = \frac{1}{j\omega C} \bar{I} \bar{I}^* = -j \frac{1}{\omega C} I^2$$





 Only reactive power
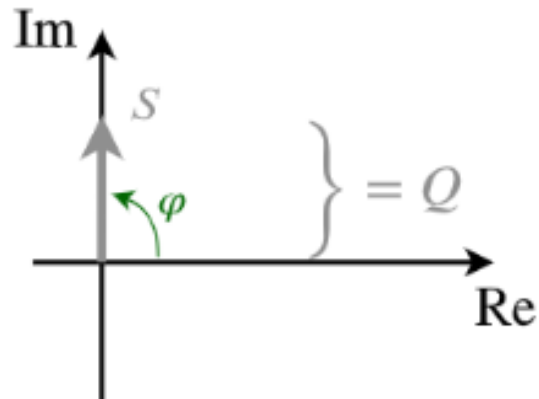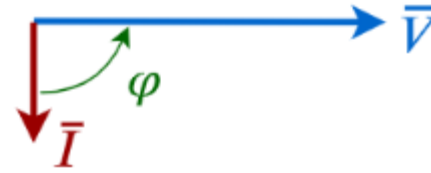
# Complex power and phasors for an inductance

$$\bar{V} = Z \bar{I} \quad \& \quad Z = j\omega L$$

$$\Rightarrow S = \bar{V} \bar{I}^* = j \omega L \bar{I} \bar{I}^* = j \omega L I^2$$



➡ Only reactive power

# Expressions relative to one-ports

$$\bar{V} = Z \bar{I} = (R + j X) \bar{I}$$

---

Z : the impedance     $[\Omega]$

R : the resistance     $[\Omega]$

X : the reactance     $[\Omega]$

---

$$S = Z I^2 \quad [\text{VA}]$$

$$P = R I^2 \quad [\text{W}]$$

$$Q = X I^2 \quad [\text{var}]$$

$$\bar{I} = Y \bar{V} = (G + j B) \bar{V}$$

---

Y : the admittance     $[\text{S}]$

G : the conductance     $[\text{S}]$

B : the susceptance     $[\text{S}]$

---

$$S = Y^* V^2 \quad [\text{VA}]$$

$$P = G V^2 \quad [\text{W}]$$

$$Q = -B V^2 \quad [\text{var}]$$

# Recap complex power basic components

	R	L	C
$\varphi$	0	$\frac{\pi}{2}$	$-\frac{\pi}{2}$
P	$R I^2 = \frac{V^2}{R}$	0	0
Q	0	$X I^2 = \omega L I^2 = \frac{V^2}{\omega L}$	$-B V^2 = -\omega C I^2 = -\frac{I^2}{\omega C}$



# Exercise 1: voltage distribution

The circuit of Figure 1 presents a resistive-inductive load powered with an AC generator of sinusoidal voltage (230 V, 50 Hz). Find the voltages across R and L (magnitude and phase angle) and represent all the voltages on a phasor diagram.

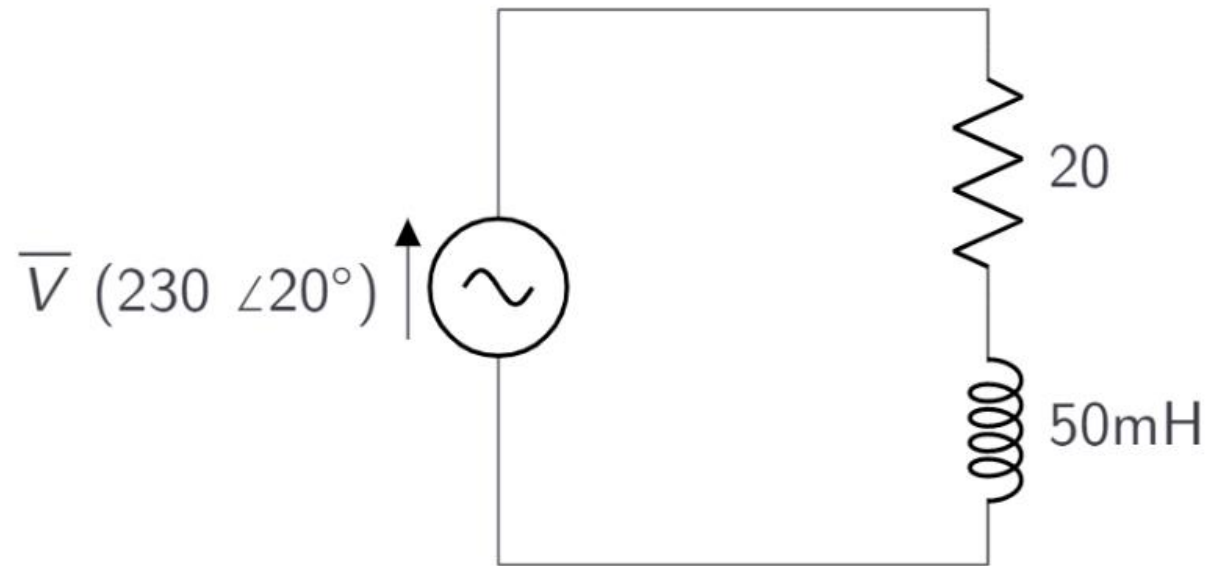


Figure: Resistive-inductive circuit.

# Exercise 2: Reactive power compensation

Your colleague suggests to add a  $50 \mu\text{F}$  capacitor in parallel of the RL load. It is supposed to compensate the reactive power consumed by the inductive load. Is it a good idea ? If so, what would be the exact value of  $C$  needed ?

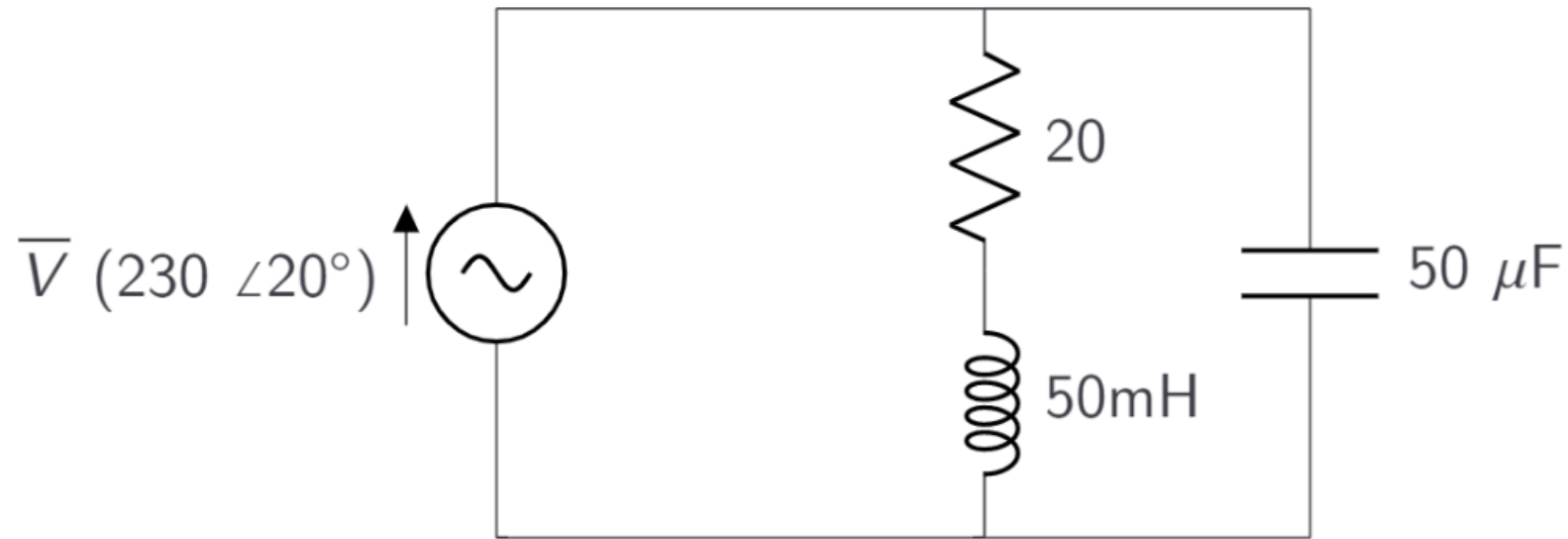

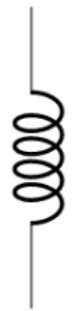
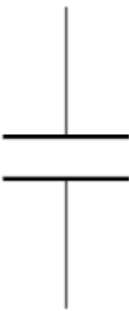
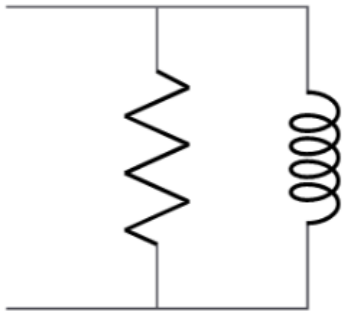
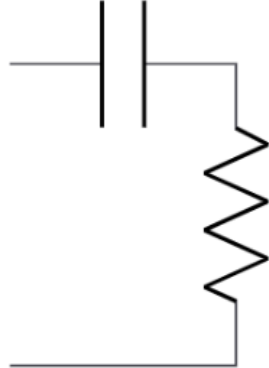


Figure: Inductive circuit with compensation capacitor.

# Exercise 3: one-port small quiz

Fill the cells of the table below with the most appropriate answer among :

=0      <0      >0      =1      <1       $+\infty$        $-\infty$

one-port:					
active power consumed					
reactive power produced					
$\cos \phi$					
$\tan \phi$					