


# ELEC0431 : Exercise session 2

## Reminders of balanced three-phase systems

12 February 2021

Nicolas Davister

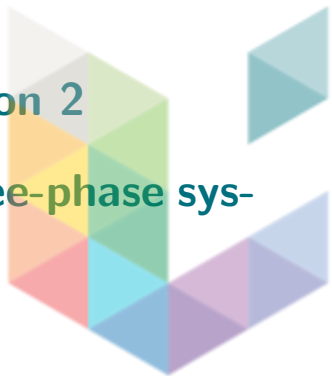Montefiore Institute, Department of Electrical Engineering and Computer Science, University of Liège, Belgium



## Exercise 3 : one-port small quiz

Fill the cells of the table below with the most appropriate answer among :

$=0$

$<0$


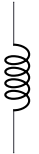
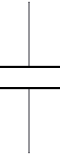
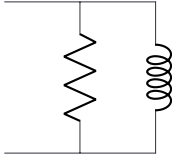
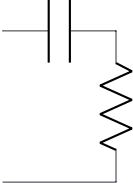
$>0$

$=1$

$<1$

$+\infty$

$-\infty$

one-port:					
active power consumed					
reactive power produced					
$\cos \phi$					
$\tan \phi$					


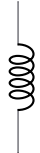
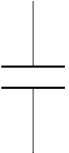
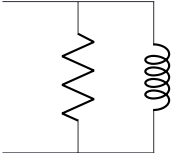
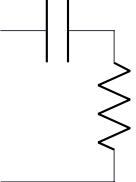
The logo consists of a solid blue square with the word "wooclap" written in white, lowercase, sans-serif font in the center.

**wooclap**

One-port quizz

Wooclap code : JPMAJU

## Exercise 3 : one-port small quiz - solution

one-port:					
active power consumed	$> 0$	$= 0$	$= 0$	$> 0$	$> 0$
reactive power produced	$= 0$	$< 0$	$> 0$	$< 0$	$> 0$
$\cos \phi$	$= 1$	$= 0$	$= 0$	$< 1$	$< 1$
$\tan \phi$	$= 0$	$+\infty$	$-\infty$	$> 0$	$< 0$

## Alternating voltages and currents

Alternating voltages and currents fluctuate over time as sinusoids (or cosinusoids) with a given frequency (AC voltages and currents).



Time domain		Frequency domain
$v(t) = \sqrt{2} V \cos(\omega t + \theta)$	$\iff$	$\bar{V} = V e^{j\theta}$
$i(t) = \sqrt{2} I \cos(\omega t + \psi)$	$\iff$	$\bar{I} = I e^{j\psi}$

For sinusoidal waveforms, the ratio between maximum values and RMS values is

$$\boxed{\begin{aligned} V_m &= \sqrt{2} V \\ I_m &= \sqrt{2} I \end{aligned}}$$

As electrical quantities fluctuate at the same frequency, one can switch from the time domain to the frequency domain (with phasors).
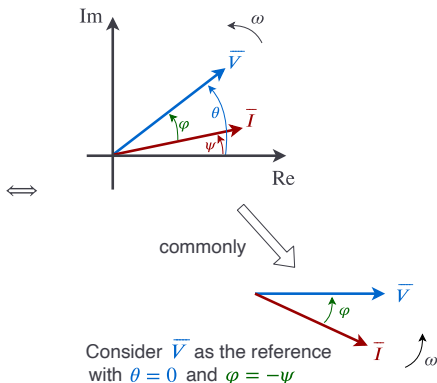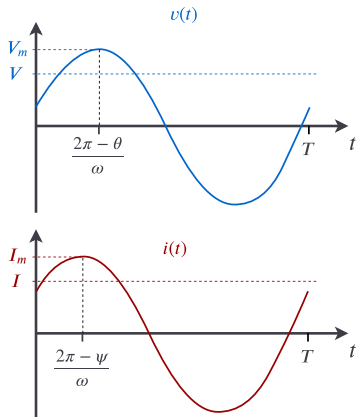
# Alternating voltages and currents - Phasor diagrams



$$\varphi = \theta - \psi$$

(1)

## The complex power and the apparent power

When a component is traveled by a current with a certain voltage across its accesses, some electrical power is consumed (or produced) by this component. Defining the complex power

$$\begin{aligned} S &= \overline{V} \overline{I}^* \\ &= V I e^{j\varphi} \\ &= P + j Q \end{aligned}$$

Remark that only the phase angle difference  $\varphi$  is relevant for the power computation.

The norm of the complex power is called the apparent power :

$$|S| = \sqrt{P^2 + Q^2} = V I \quad (2)$$



**wooclap**

Voltages and frequencies


Wooclap code : NZKDFJ





# Introduction to balanced three-phase systems

## 1 Phase generator

Front view

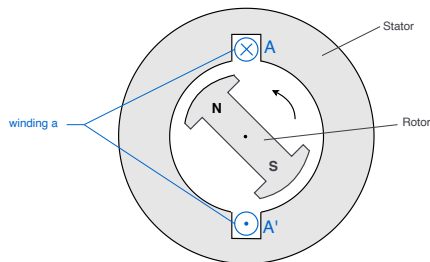

Side view

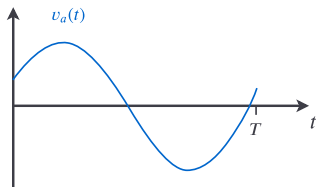
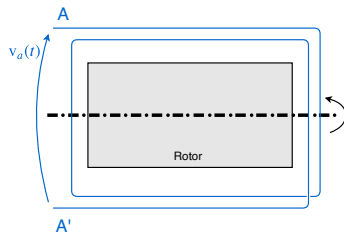


The voltage  $v_a(t)$  is induced in the winding as the magnetic flux created by the rotor varies over time :


$$v_a(t) = -n_a \underbrace{\frac{d\phi(t)}{dt}}_{\text{varying flux}} \quad (3)$$

# Introduction to balanced three-phase systems

## 3 Phase generator

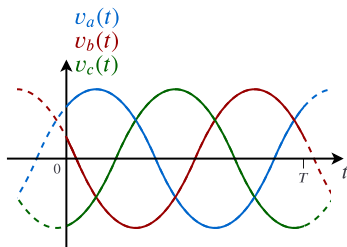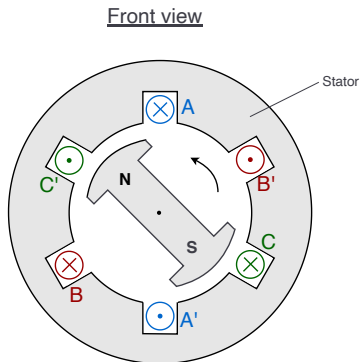


Phasor diagram

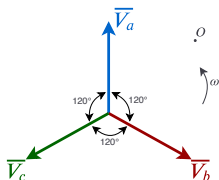

The three-phase generator now possesses 3 windings on its stator.

## 3 Phase circuit

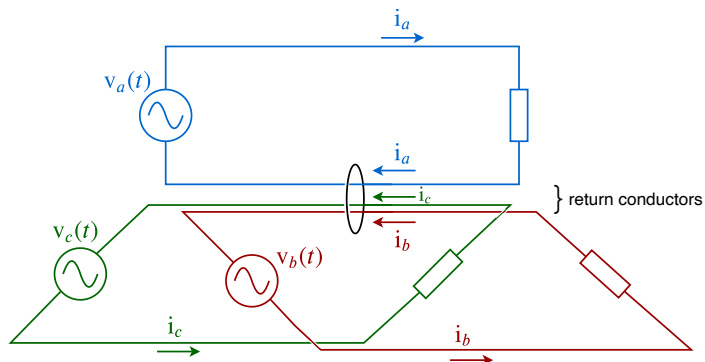

The 3 return conductors can be merged into one return conductor.  
This conductor carries a current


$$i_a + i_b + i_c = 0 \quad (4)$$

and can be removed.

# Introduction to balanced three-phase systems
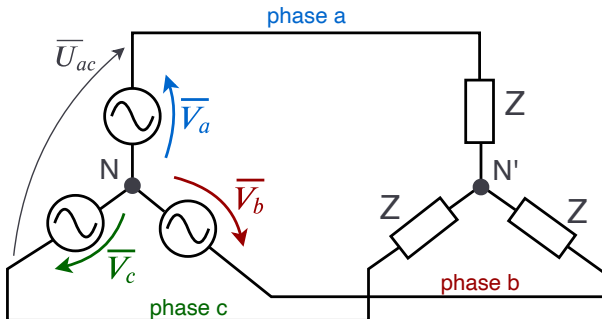
## 3 Phase circuit


The balanced three-phase circuit is the assembly of three identical circuits called phases. The 3 signals are dephased by  $120^\circ$ .


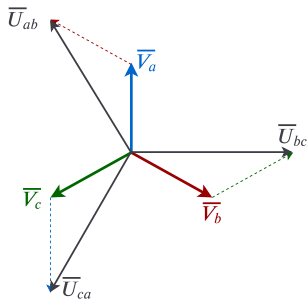
## Line voltages

Line voltages

$$\begin{aligned}\bar{U}_{ab} &= \bar{V}_a - \bar{V}_b \\ \bar{U}_{bc} &= \bar{V}_b - \bar{V}_c \\ \bar{U}_{ca} &= \bar{V}_c - \bar{V}_a\end{aligned}$$




$\bar{V}_a$ ,  $\bar{V}_b$  and  $\bar{V}_c$  are the phase voltages, measured between a phase and the neutral N.

$\bar{U}_{ab}$ ,  $\bar{U}_{bc}$  and  $\bar{U}_{ca}$  are the line voltages (or phase-to-phase voltages), measured between two phases.
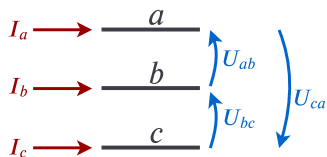
## Introduction to balanced three-phase systems

On a three-phase network without the neutral conductor, one can only measure the line voltages and the line currents.





and the three-phase apparent power will be

$$S = 3 V I \quad (5)$$

$$= \sqrt{3} U I \quad (6)$$

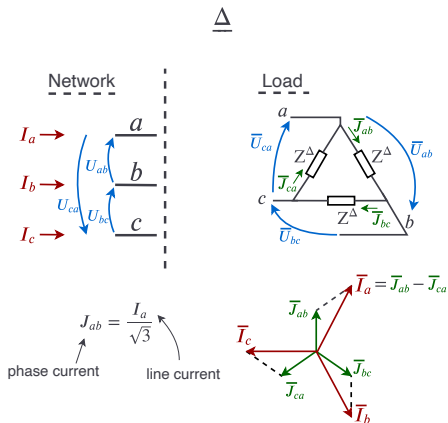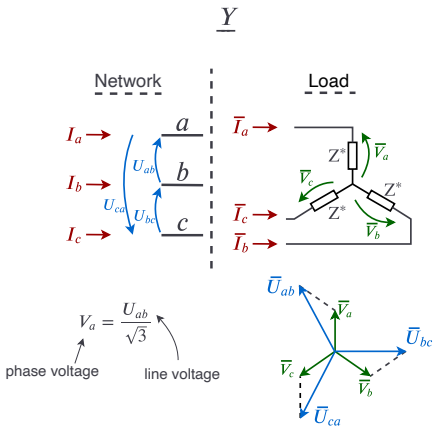
# Three-phase loads under $Y$ and $\Delta$ connections (étoile-triangle)

Three-phase loads can be arranged either in star ( $Y$ ) or in triangle ( $\Delta$ ). The voltages and currents are splitted as following :


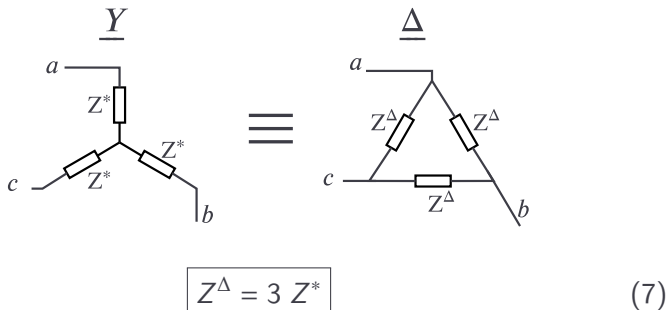
## $Y$ and $\Delta$ equivalents


From the network perspective, the  $Y$  or  $\Delta$  arrangements are equivalent as long as they provide the same line voltages and currents.



Under condition (7), the two loads are equivalents and consume (produce) the same power because  $Z^* = \frac{V}{I}$  and  $Z^\Delta = \frac{U}{J}$ .



# Exercises

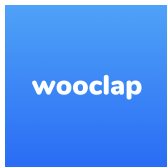

Exercises of session 2

Wooclap code : ZYTYKI

## Exercise 4 : 2-ports characterization

Characterize the 2-ports of Figure 1. In that context, two tests have been performed: a short circuit test and an open circuit test.

- 559 mV and 1.118 A are measured at the access 1 while the access 2 is shorted (short circuit test at 50 Hz).
- 5 V and 4.472 A are measured at the access 1 while the access 2 is left open (open circuit test at 50 Hz).

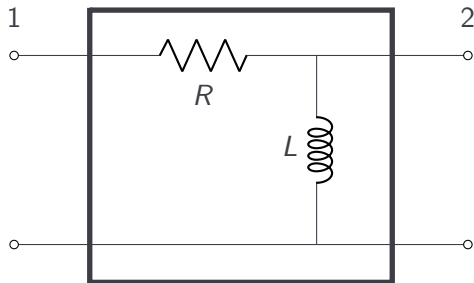


Figure: 2-Ports circuit

## Exercise 4 : 2-ports characterization

Consider that the tests are performed at 50 Hz. The 2-ports could be fully characterized by only one of the two tests if the active power was measured during the tests. The active power can be measured with a wattmeter.

1. Determine the value of  $R$  and  $L$  with the information above.
2. Which test would be necessary ?
3. During that test, an active power of 9.99392 W has been measured. Prove that it gives the correct value of  $R$  and  $L$ .

## Exercise 4 : 2-ports characterization - solution

Short circuit test :

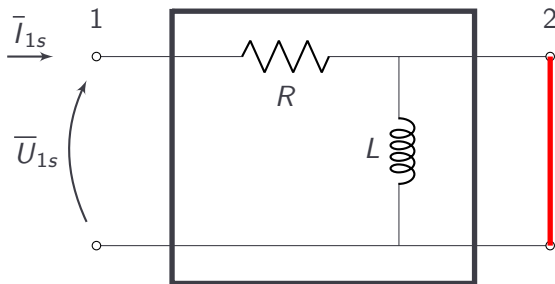


Figure: 2-Ports under short circuit test

$$R = \frac{U_{1s}}{I_{1s}} = \frac{0.559}{1.118} = 0.5 \quad [\Omega] \quad (8)$$

## Exercise 4 : 2-ports characterization - solution

Open circuit test :

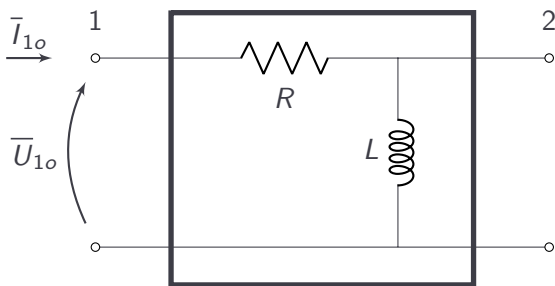


Figure: 2-Ports under open circuit test

$$|Z| = \frac{U_{1o}}{I_{1o}} = \frac{5}{4.472} = 1.118 \quad [\Omega] \quad (9)$$

$$X = \sqrt{|Z|^2 - R^2} = \sqrt{1.118^2 - 0.5^2} = 1 \quad [\Omega] \quad (10)$$

## Exercise 4 : 2-ports characterization - solution

If a wattmeter had been used, only one manipulation would have been required.

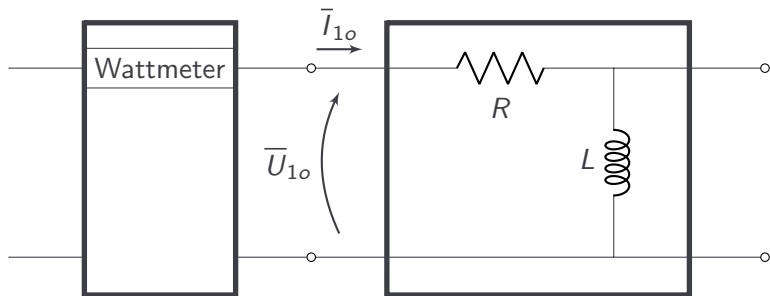


Figure: 2-Ports under open circuit test with wattmeter

The active power measured would be  $P_{1o} = 9.99392$  [W] and the apparent power  $S_{1o} = U_{1o} I_{1o} = 5 \times 4.472 = 22.36$  [VA].

## Exercise 4 : 2-ports characterization - solution

From the knowledge of the apparent power and the active power (both measured in open circuit for this test), one can deduce the reactive power

$$Q_{1o} = \sqrt{S_{1o}^2 - P_{1o}^2} = 20.002 \text{ [var]} \quad (11)$$

$$P = R I^2 \quad \Rightarrow \quad R = \frac{P_{1o}}{I_{1o}^2} = \frac{9.99392}{4.472^2} = 0.5 \text{ } [\Omega]$$

$$Q = X I^2 \quad \Rightarrow \quad X = \frac{Q_{1o}}{I_{1o}^2} = \frac{20.002}{4.472^2} = 1 \text{ } [\Omega]$$

## Exercise 5 : electric heater

Consider an electrical heater that dissipates 15 kW of power when connected to a three-phase power system of 208 V. As a first approximation, the heater is modelled as a purely resistive three-phase load.

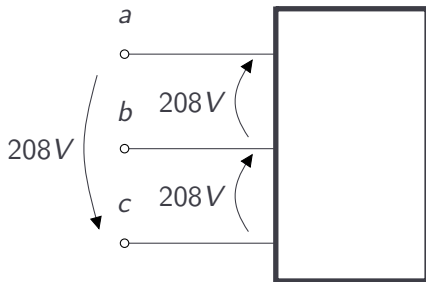


Figure: Three-phase Electrical Heater




## Exercise 5 : electric heater

1. If no additional information is provided about the voltage, does the 208 V correspond to the peak or the RMS value ?
2. Compute the line current if the resistive loads are connected in  $\mathbf{Y}$ .
3. If the resistors are connected in  $\mathbf{Y}$ , compute the resistance of each.
4. Compute the line current if the resistive loads are connected in  $\Delta$ .
5. If the resistors are connected in  $\Delta$ , compute the resistance of each.

## Exercise 5 : electric heater - solution

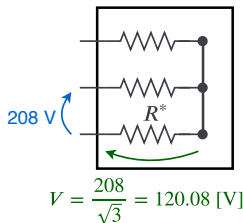1. The value of 208 V corresponds to an RMS value of the line voltages (phase-to-phase). The peak value is  $\sqrt{2} \times 208 = 294.1 \text{ V}$
2. The power of the three-phase system is  $P_{3\varphi} = 15 \text{ kW}$ , then, the power of one phase is  $P_{1\varphi} = \frac{P_{3\varphi}}{3} = 5 \text{ kW}$ . The line current is

$$I = \frac{P_{1\varphi}}{V} = \frac{5000}{120.08} = 41.635 \text{ [A]} \quad (12)$$



$$V = \frac{208}{\sqrt{3}} = 120.08 \text{ [V]}$$

## Exercise 5 : electric heater - solution

3. If the resistors are connected in star configuration, their value must be

$$R^* = \frac{V_{a,b,c}}{I_{a,b,c}} = \frac{120.08}{41.635} = 2.884 \quad [\Omega] \quad (13)$$

4. Even if the resistors are connected in  $\Delta$ , in this case, the line currents remain the same because the power consumption and voltages are kept constant :  $I = 41.635$  [A]

Remark that the current through the loads is different now :

$$J = \frac{I}{\sqrt{3}} = 24.038 \text{ [A]}$$

## Exercise 5 : electric heater - solution

5. If the resistors are known to be connected in  $\Delta$ , the resistance of each is

$$R^{\Delta} = \frac{U}{J} = \frac{208}{24.038} = 8.6528 \quad [\Omega] \quad (14)$$

Also remark that  $Z^{\Delta} = 3 Z^*$  which is the expected results if the two loads consume the same amount of power.

