



# Electromagnetic Energy Conversion

## ELEC0431

### Exercise session 2: Reminders of balanced three-phase systems

18 February 2022

Florent Purnode ([florent.purnode@uliege.be](mailto:florent.purnode@uliege.be)) – Nicolas Davister ([ndavister@uliege.be](mailto:ndavister@uliege.be))

Montefiore Institute, Department of Electrical Engineering and Computer Science,  
University of Liège, Belgium

# Looking back

---

Clarifications on exercise session 1

# Exercise 1: manually computing $\bar{I}$

$$\bar{I} = \frac{\bar{V}}{R + jX} \quad ???$$



Option 1: use your calculator

(win time)

Option 2: have fun with maths!

(personal challenge → happiness)


$$\bar{I} = \frac{\bar{V}}{R + jX} = \frac{\bar{V}}{R + jX} \frac{R - jX}{R - jX} = \frac{R}{R^2 + X^2} \bar{V} - j \frac{X}{R^2 + X^2} \bar{V}$$

$$|\bar{I}| = \sqrt{\left(\frac{R}{R^2 + X^2}\right)^2 + \left(\frac{X}{R^2 + X^2}\right)^2} V = 9.044 \text{ A}$$


$$\varphi = \arctan \frac{\frac{X}{R^2 + X^2}}{\frac{R}{R^2 + X^2}} = \arctan \frac{X}{R} = 38.146^\circ$$

$$\varphi = \theta - \psi \Leftrightarrow \psi = \theta - \varphi = 20 - 38.146 = -18.146^\circ$$

$$\bar{I} = 9.044 \angle -18.146^\circ$$

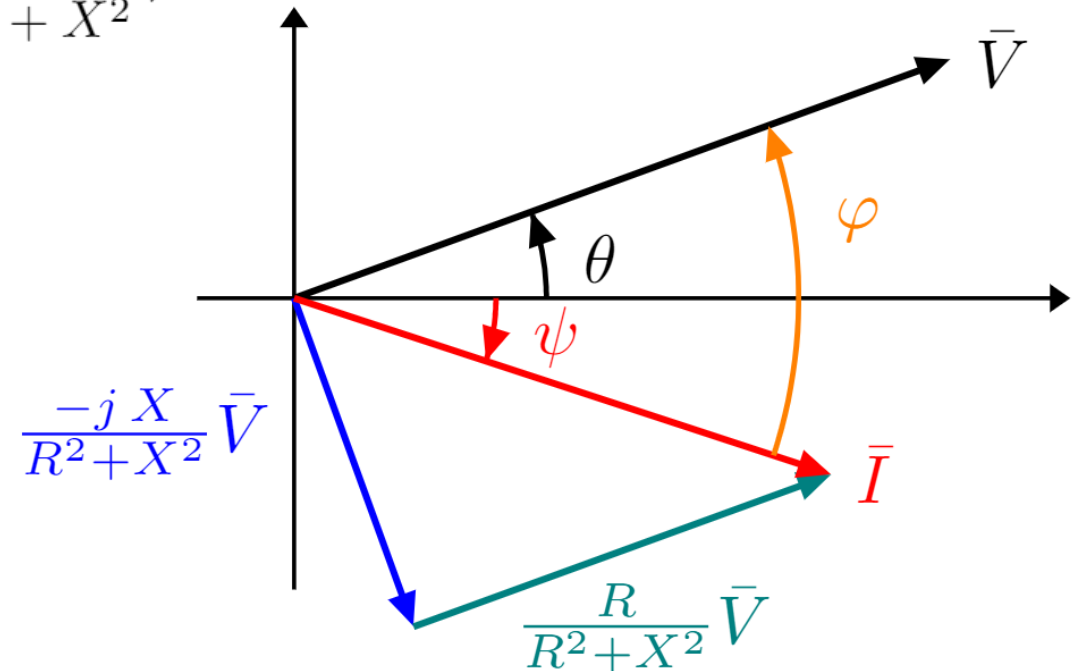
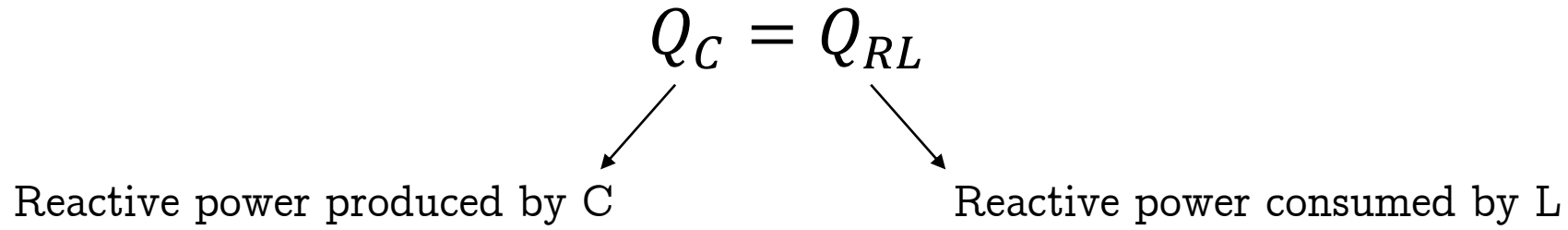
# Exercise 2: Matching the reactive powers



➔ Ok if we consider both the motor and generator convention

---

In case only the motor convention is used (usual convention)

$$Q_C = -Q_{RL}$$

# Correction ex. 3


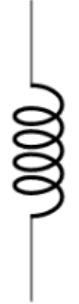
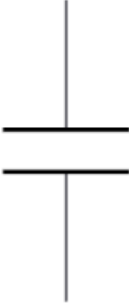
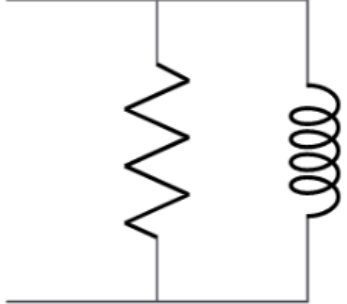
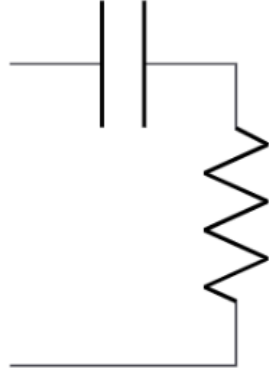
---

One port small quiz

# Exercise 3: one-port small quiz

Fill the cells of the table below with the most appropriate answer among :

$=0$        $<0$        $>0$        $=1$        $<1$        $+\infty$        $-\infty$


one-port:					
active power consumed					
reactive power produced					
$\cos \phi$					
$\tan \phi$					

# Exercise 3: R

$$\bar{V} = Z \bar{I}$$

$$Z = R$$


$$\bar{V} = R \bar{I}$$

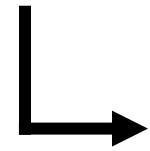

$$\cos(\varphi) = 1$$

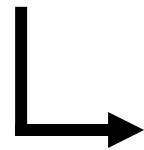
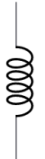
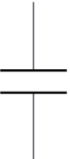
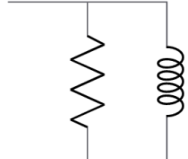

$$\tan(\varphi) = 0$$

$$S = \bar{V} \bar{I}^* = RI^2$$



$$P > 0$$

$$Q = 0$$

one-port:					
active power consumed					
reactive power produced					
$\cos \phi$					
$\tan \phi$					

# Exercise 3: L



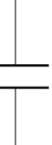
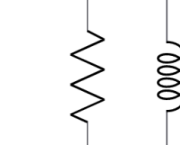

$$\begin{aligned}\bar{V} &= Z \bar{I} \\ Z &= j\omega L \\ \bar{V} &= j\omega L \bar{I}\end{aligned}$$



$$\begin{aligned}\cos(\varphi) &= 0 \\ \tan(\varphi) &= +\infty\end{aligned}$$

$$S = \bar{V} \bar{I}^* = j\omega L I^2$$

$$\begin{aligned}P &= 0 \\ Q &> 0 \Rightarrow \text{reactive power produced} < 0\end{aligned}$$

one-port:					
active power consumed	> 0				
reactive power produced	0				
$\cos \phi$	1				
$\tan \phi$	0				



# Exercise 3: C

$$\bar{V} = Z \bar{I}$$

$$Z = \frac{-j}{\omega C}$$

$$\bar{V} = \frac{-j}{\omega C} \bar{I}$$








$$\cos(\varphi) = 0$$

$$\tan(\varphi) = -\infty$$

$$S = \bar{V} \bar{I}^* = \frac{-j}{\omega C} I^2$$

$$P = 0$$

$$Q < 0 \rightarrow \text{reactive power produced} > 0$$

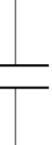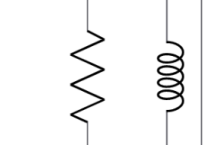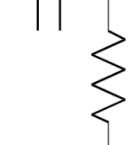one-port:					
active power consumed	> 0	0			
reactive power produced	0	< 0			
$\cos \phi$	1	0			
$\tan \phi$	0	$+\infty$			


# Exercise 3: R // L

$$\bar{V} = Z \bar{I}$$

$$Z = \left( \frac{1}{R} + \frac{1}{jX} \right)^{-1} = \frac{RX^2}{R^2 + X^2} + j \frac{R^2 X}{X^2 + R^2}$$



$$\bar{V} = \frac{RX^2}{R^2 + X^2} \bar{I} + j \frac{R^2 X}{X^2 + R^2} \bar{I}$$
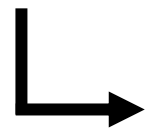
$$S = \bar{V} \bar{I}^* = \frac{RX^2}{R^2 + X^2} I^2 + j \frac{R^2 X}{X^2 + R^2} I^2$$








$$P > 0$$
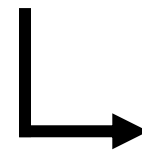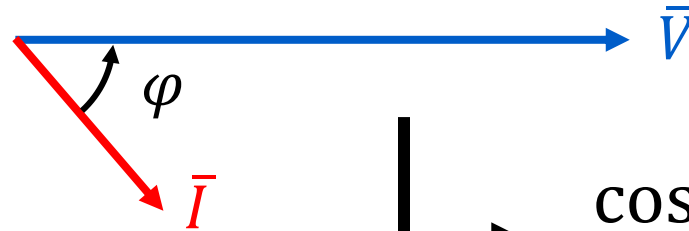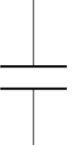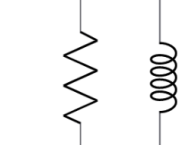
$$Q > 0 \Rightarrow \text{reactive power produced} < 0$$



$$\cos(\varphi) \in ]0,1[$$

$$\tan(\varphi) \in ]0, +\infty[$$


one-port:					
active power consumed	> 0	0	0		
reactive power produced	0	< 0	> 0		
cos φ	1	0	0		
tan φ	0	+∞	-∞		



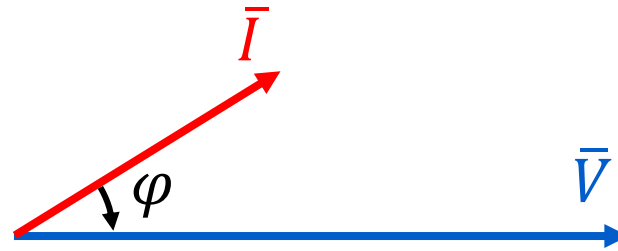
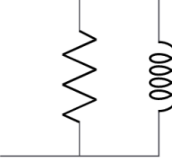

# Exercise 3: RC


$$\bar{V} = Z \bar{I}$$

$$Z = R + \frac{-j}{\omega C}$$

$$\bar{V} = R \bar{I} - \frac{j}{\omega C} \bar{I}$$




one-port:					
active power consumed	$> 0$	$0$	$0$	$> 0$	
reactive power produced	$0$	$< 0$	$> 0$	$< 0$	
$\cos \phi$	$1$	$0$	$0$	$\in ]0,1[$	
$\tan \phi$	$0$	$+\infty$	$-\infty$	$\in ]0, +\infty[$	

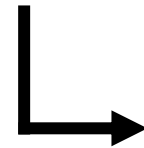

$$\cos(\phi) \in ]0,1[$$

$$\tan(\phi) \in ]-\infty, 0[$$

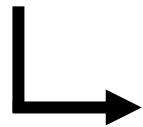
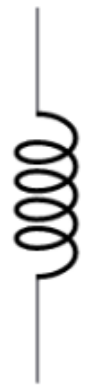
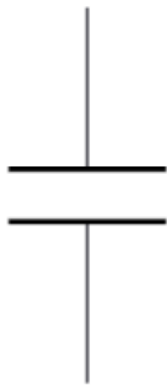
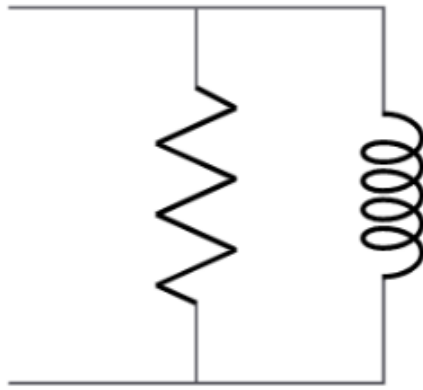
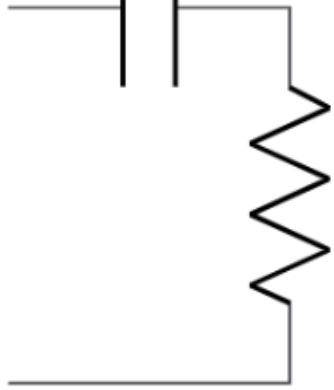
$$S = \bar{V} \bar{I}^* = R I^2 - \frac{j}{\omega C} I^2$$



$$P > 0$$

$$Q < 0 \Rightarrow \text{reactive power produced} > 0$$

# Exercise 3: summary

one-port:					
active power consumed	$> 0$	$= 0$	$= 0$	$> 0$	$> 0$
reactive power produced	$= 0$	$< 0$	$> 0$	$< 0$	$> 0$
$\cos \phi$	$= 1$	$0$	$0$	$\in ]0,1[$	$\in ]0,1[$
$\tan \phi$	$= 0$	$+\infty$	$= -\infty$	$\in ]0, +\infty[$	$\in ]-\infty, 0[$


# Reminders

---




synchronous machine and three-phase systems
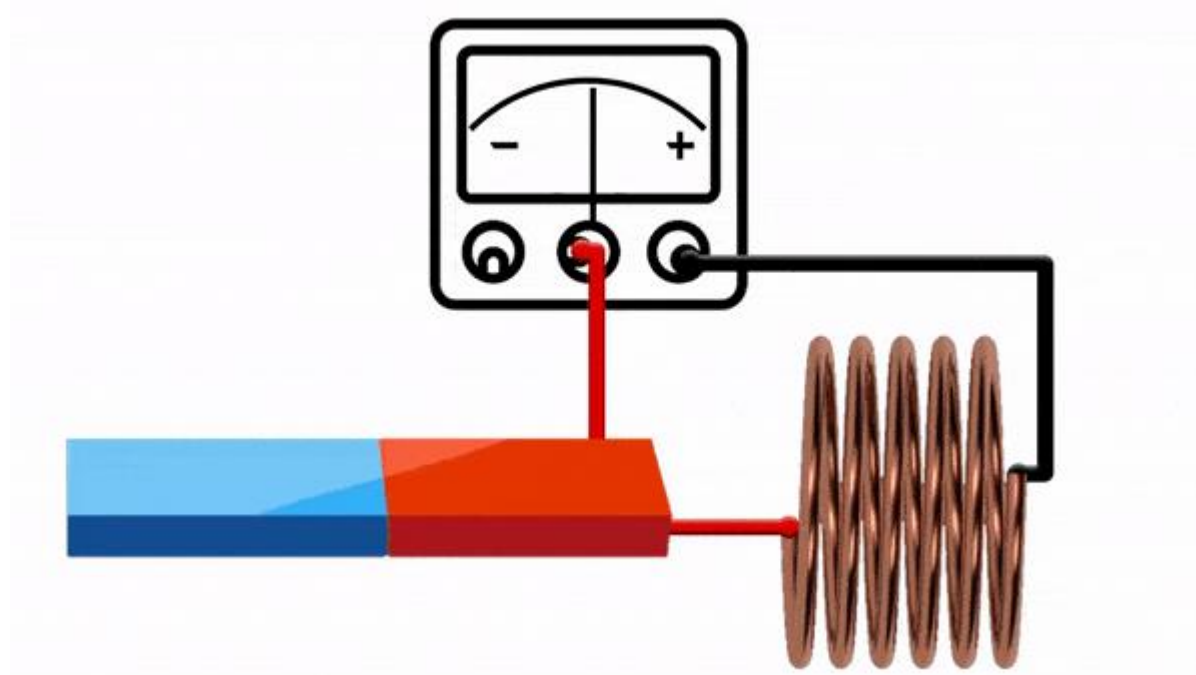
# Faraday's law

$$\varepsilon = - \frac{\partial \phi_B}{\partial t}$$





# One phase generator

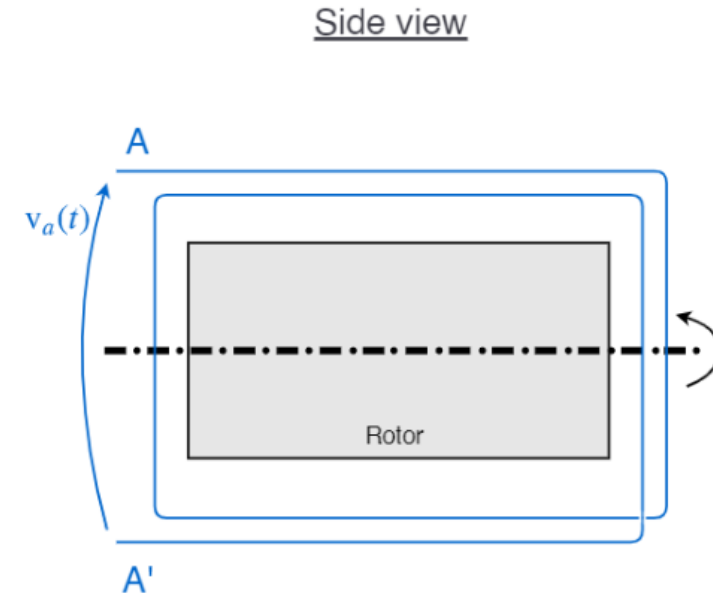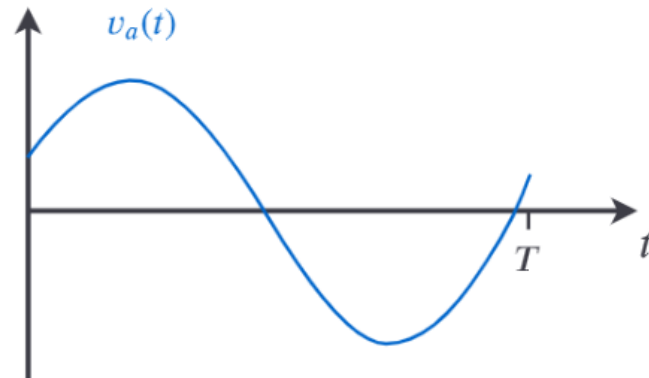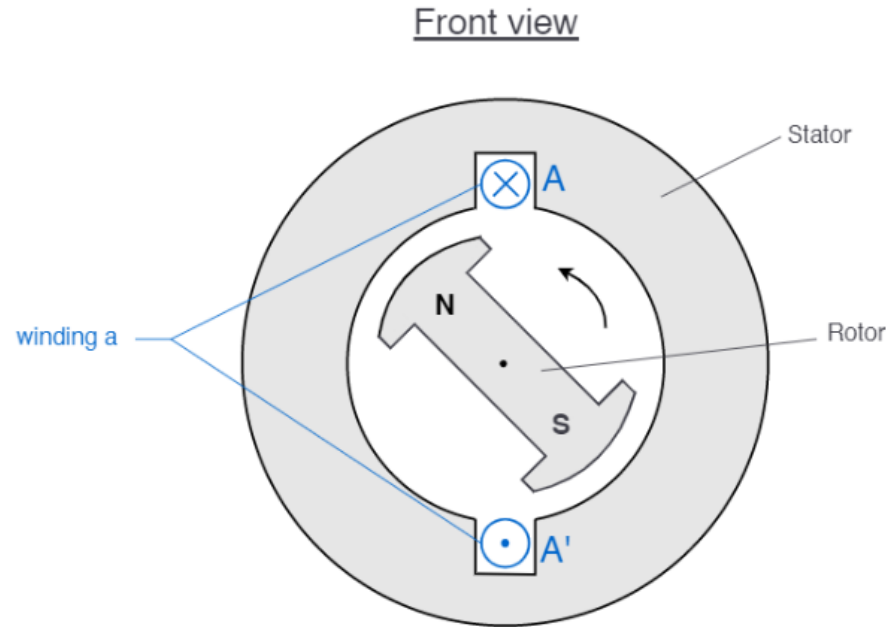


The voltage  $v_a(t)$  is induced in the winding as the magnetic flux created by the rotor varies over time :

$$v_a(t) = -n_a \underbrace{\frac{d\phi(t)}{dt}}_{\text{varying flux}} \quad (3)$$

# One phase generator – power

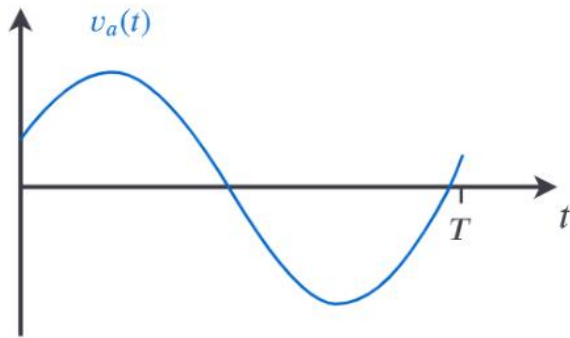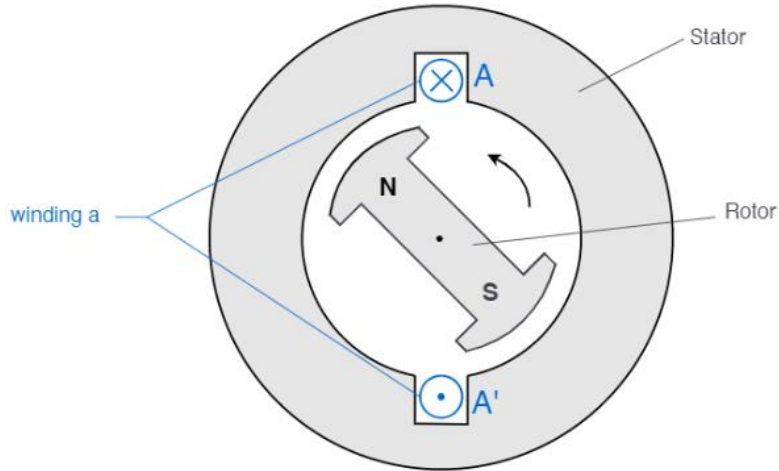



Output power

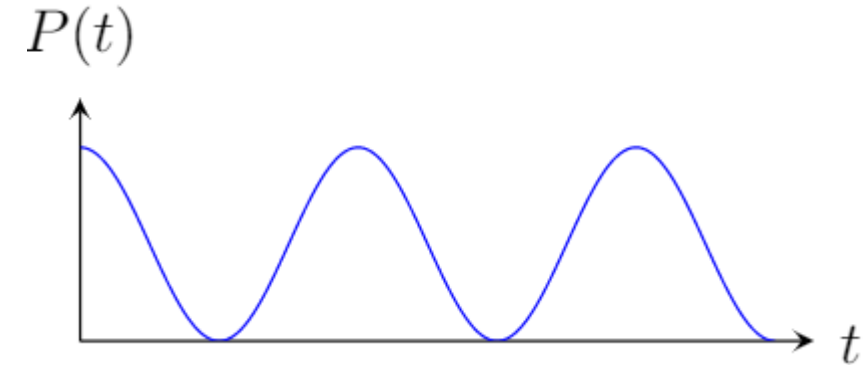

➡ The total output power fluctuates ➡ the input torque fluctuates ☹




# Two phase generator

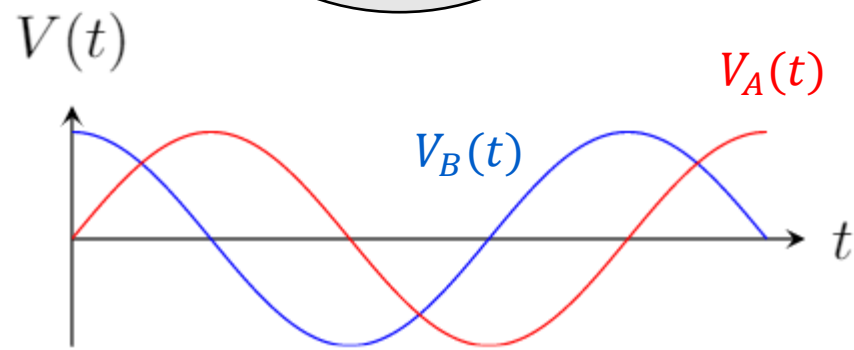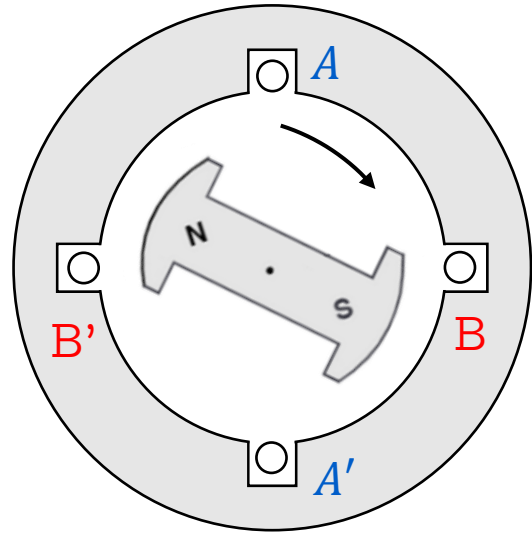




Output power

In case loads are the same


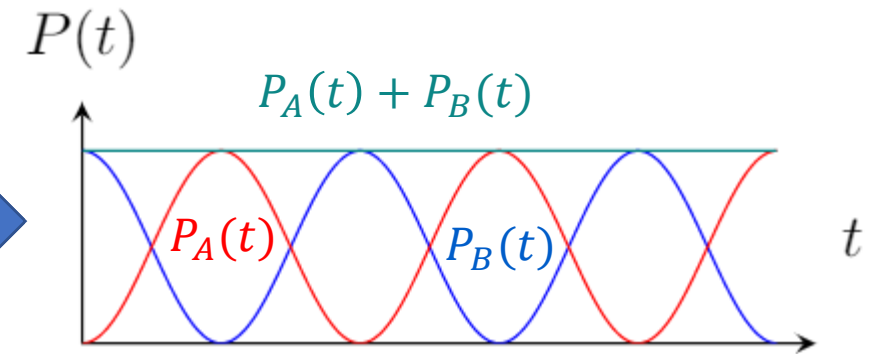


➡ The total output power is constant ➡ the input torque is constant 😊

# Three phase generator

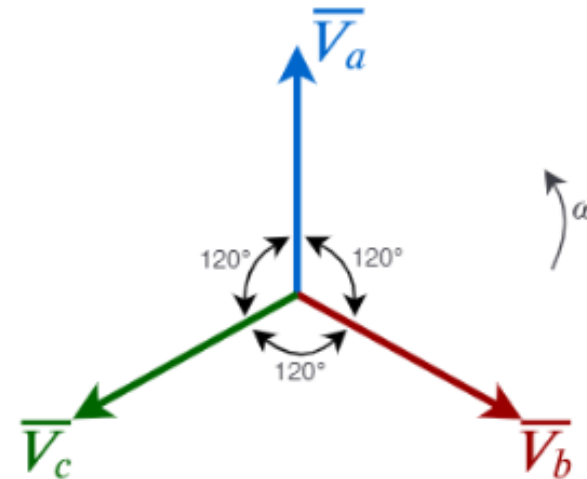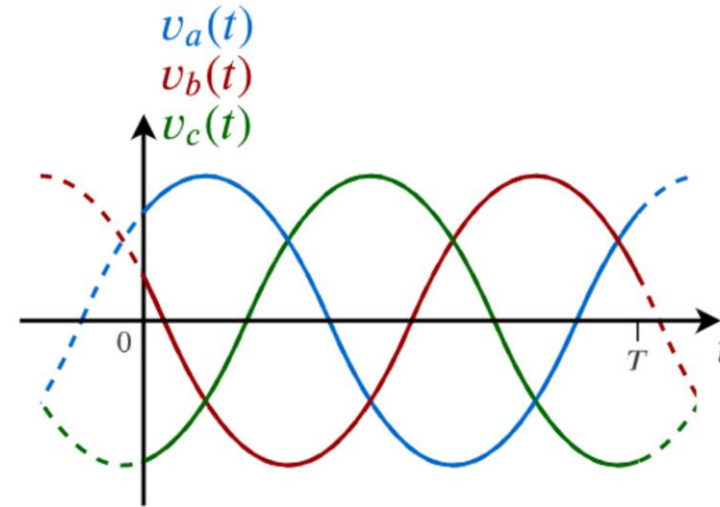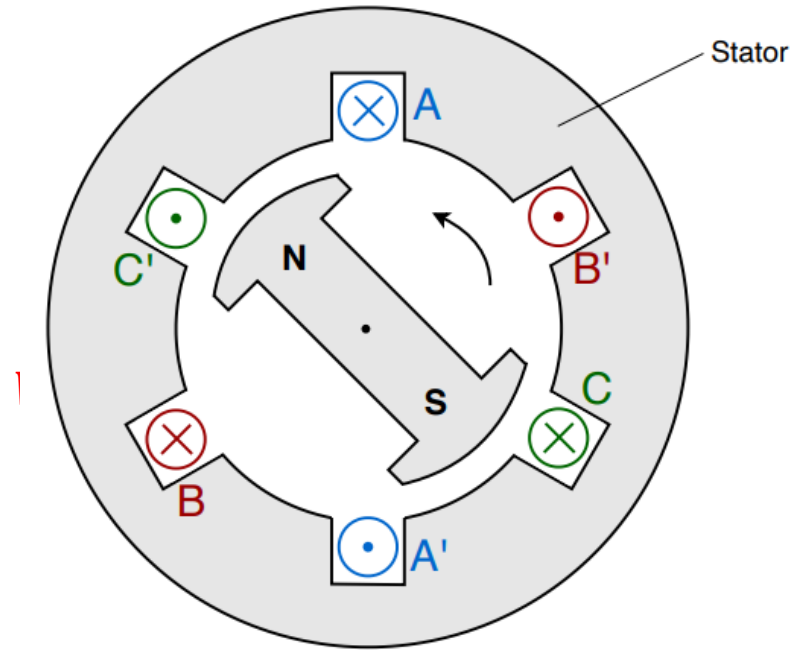


# Three phase circuit

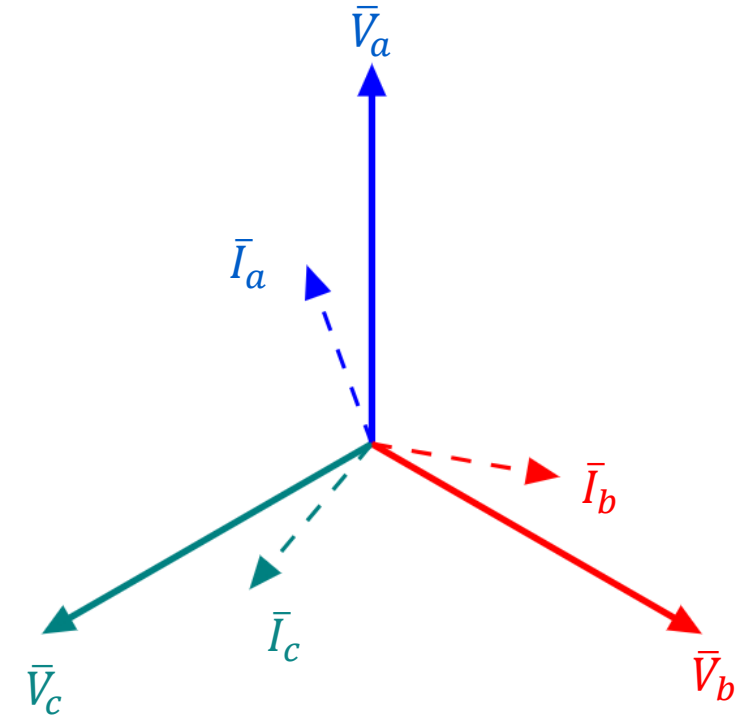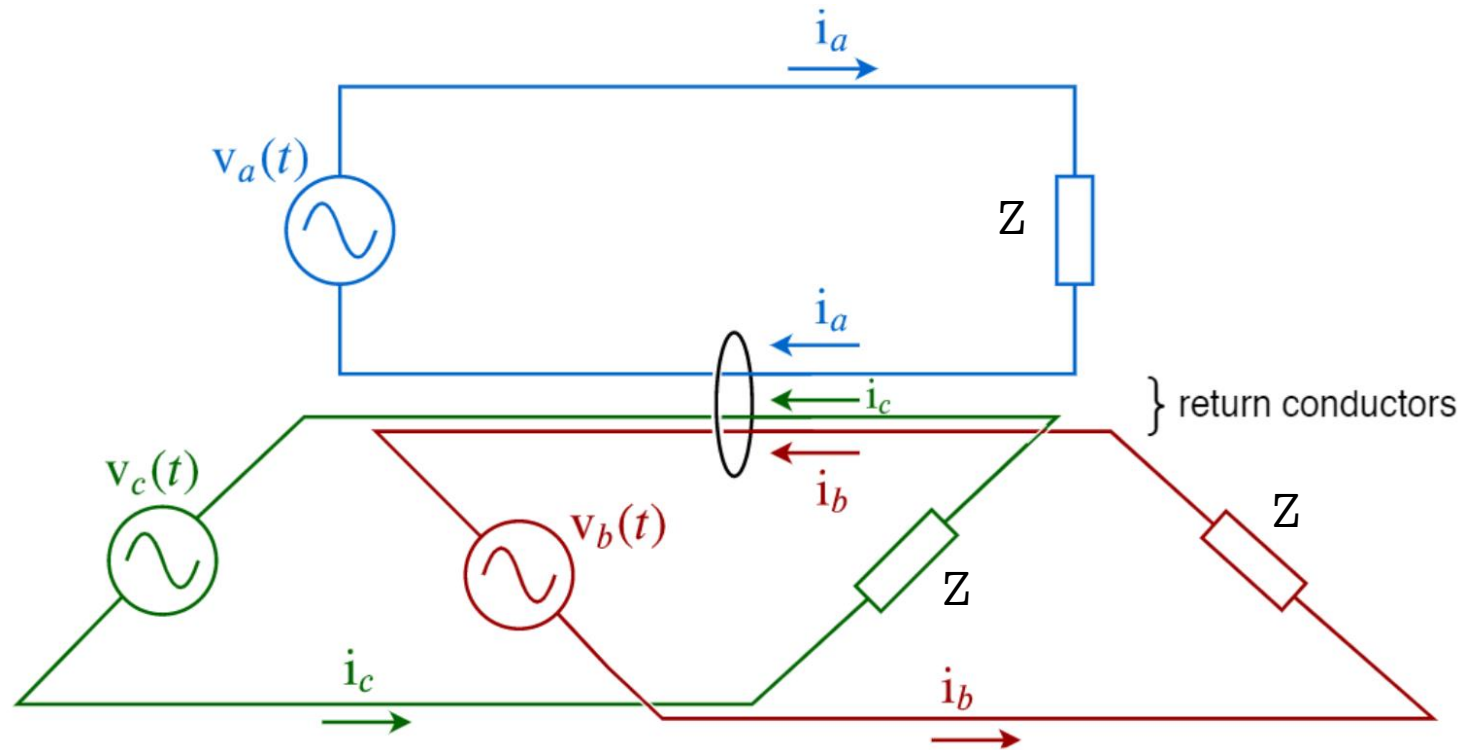

$$\bar{I}_a + \bar{I}_b + \bar{I}_c = 0 \text{ (for identical load } Z\text{)}$$

➔ The 3 return conductors can be removed ☺☺☺

# Balanced three phase circuit

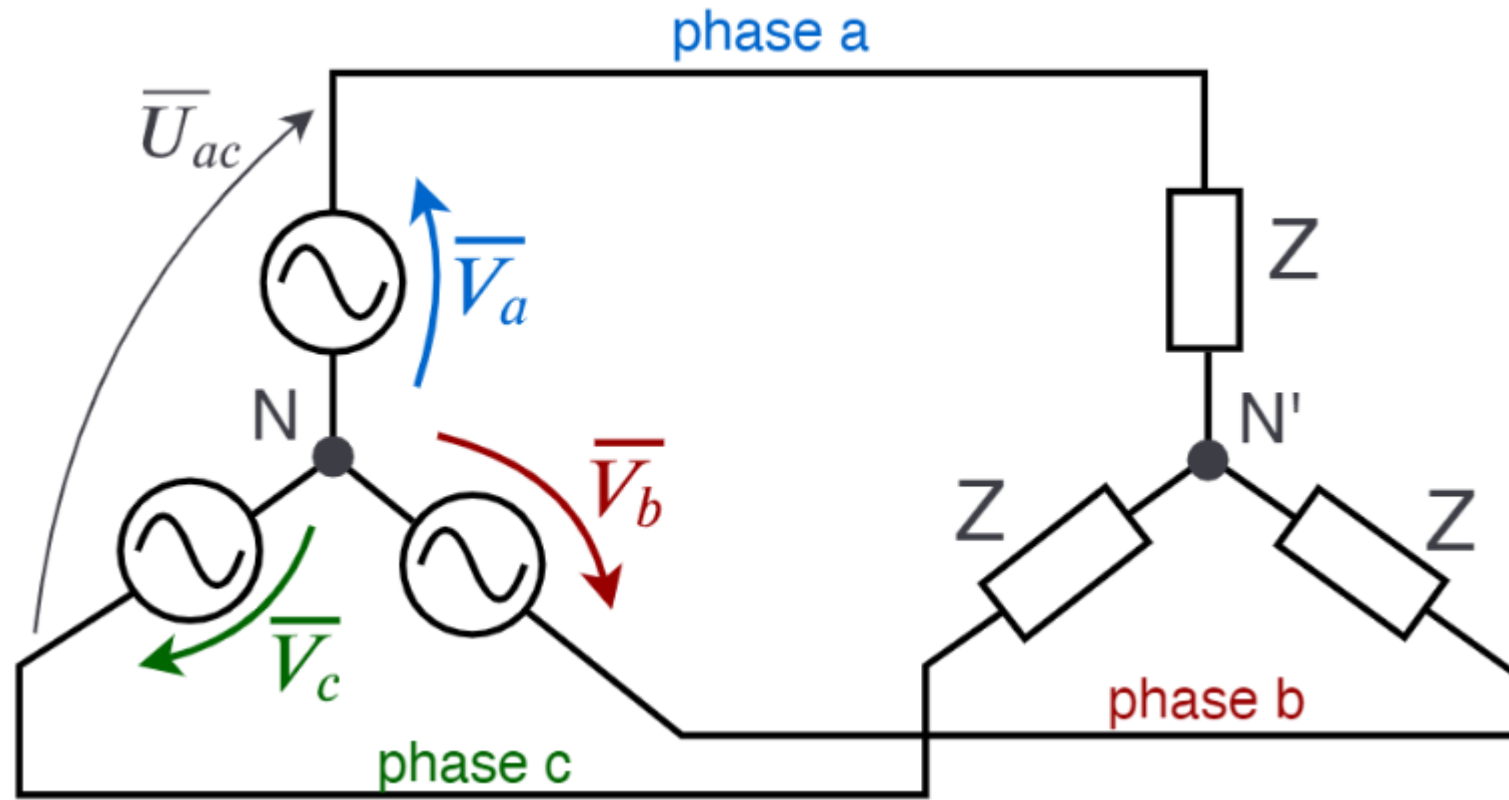


The balanced three-phase circuit is the assembly of three **identical** circuits called phases. The 3 signals are dephased by  $120^\circ$ .
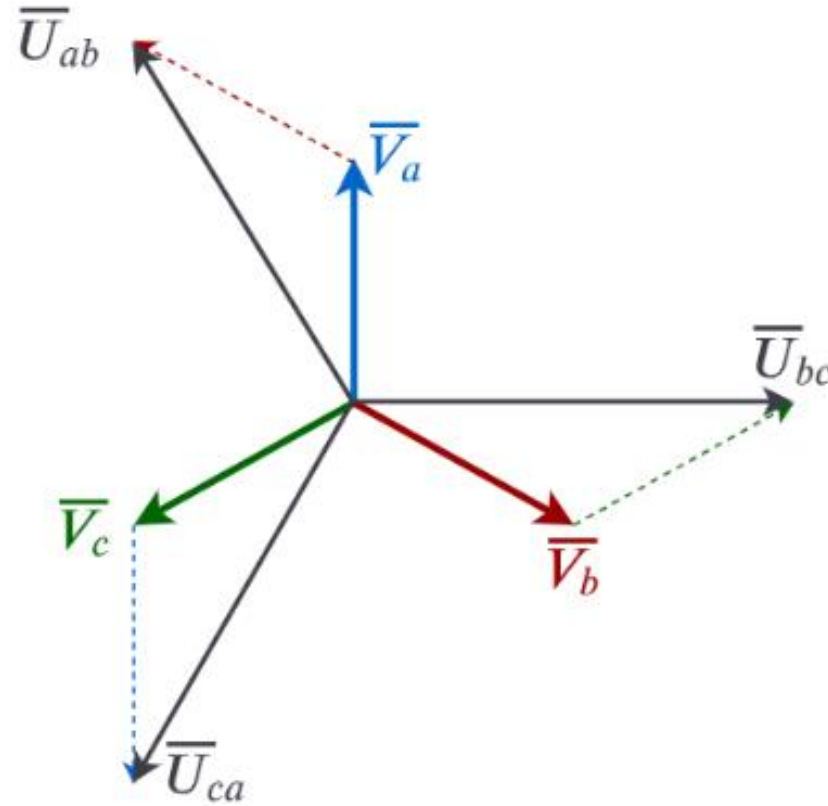
# Line and phase voltages

Line voltages

$$\begin{aligned}\overline{U}_{ab} &= \overline{V}_a - \overline{V}_b \\ \overline{U}_{bc} &= \overline{V}_b - \overline{V}_c \\ \overline{U}_{ca} &= \overline{V}_c - \overline{V}_a\end{aligned}$$





$\overline{V}_a$ ,  $\overline{V}_b$  and  $\overline{V}_c$  are the phase voltages, measured between a phase and the neutral N.

$\overline{U}_{ab}$ ,  $\overline{U}_{bc}$  and  $\overline{U}_{ca}$  are the line voltages (or phase-to-phase voltages), measured between two phases.
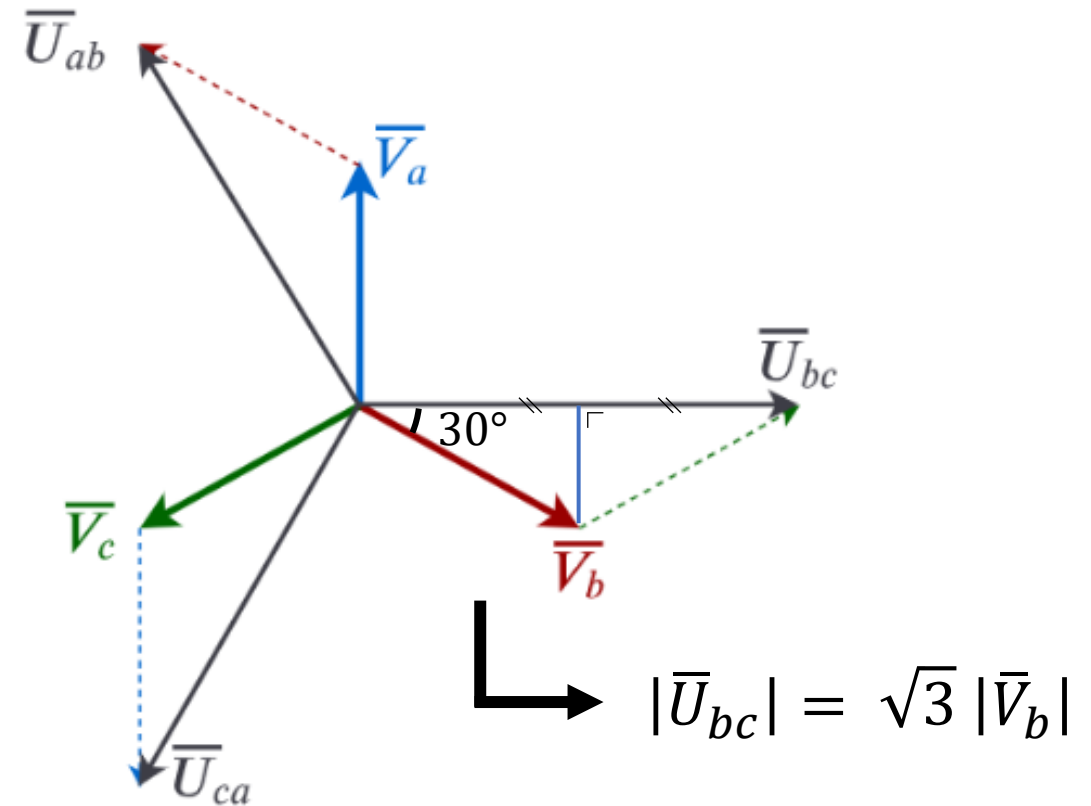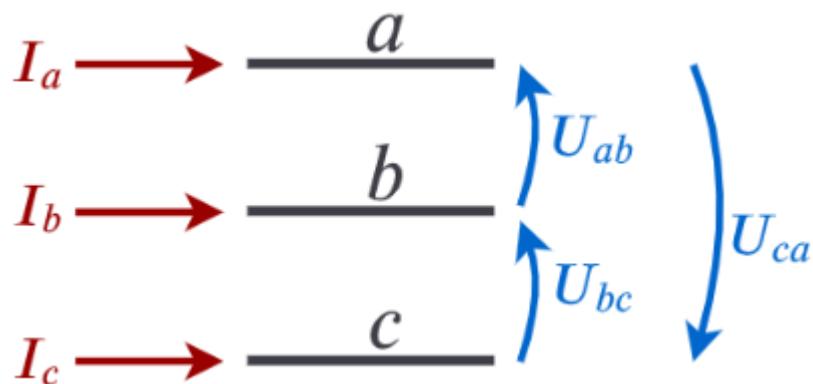
# Line and phase voltages


On a three-phase network without the neutral conductor, one can only measure the line voltages and the line currents.




# Star and triangle connections

Three-phase loads can be arranged either in star (Y) or in triangle ( $\Delta$ )


Y

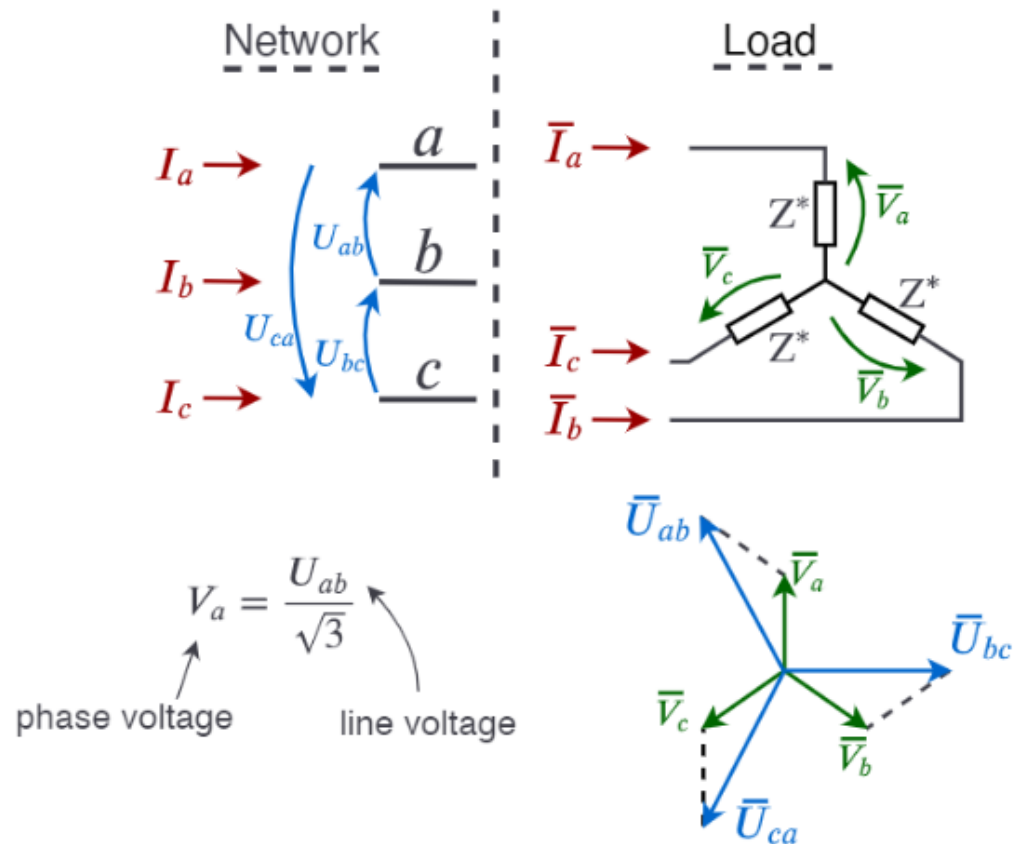

$\Delta$

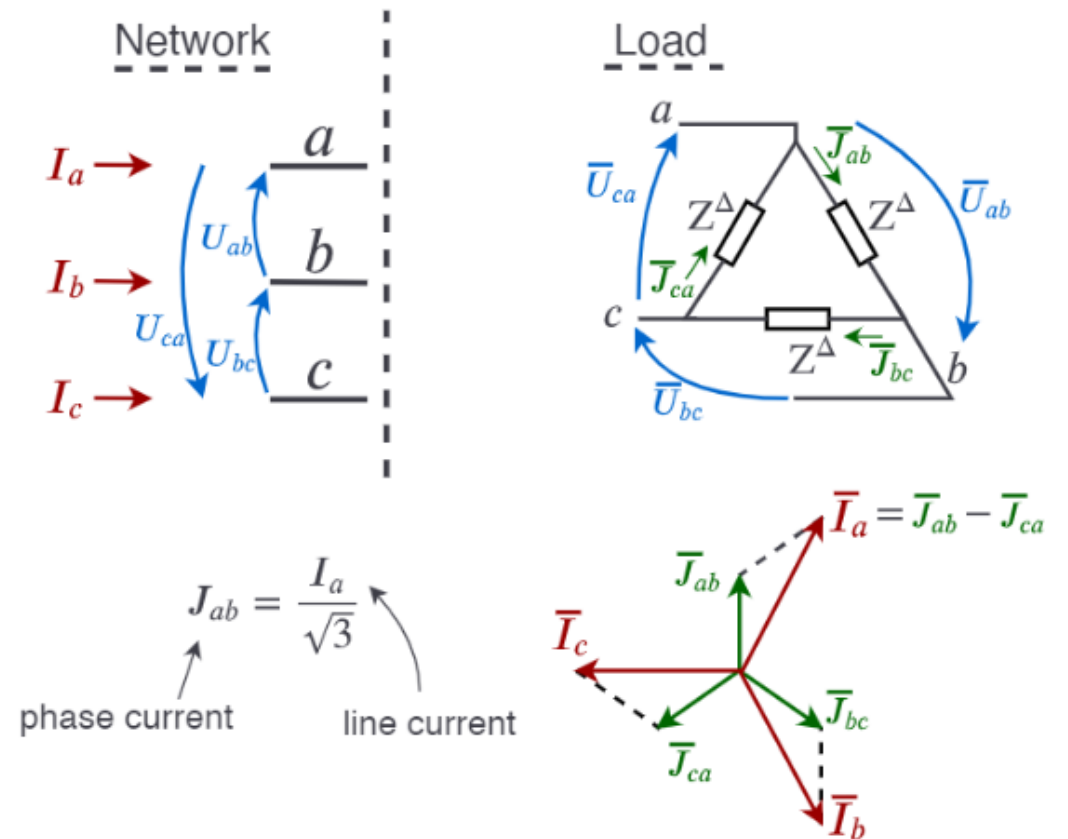

# Line and phase voltages

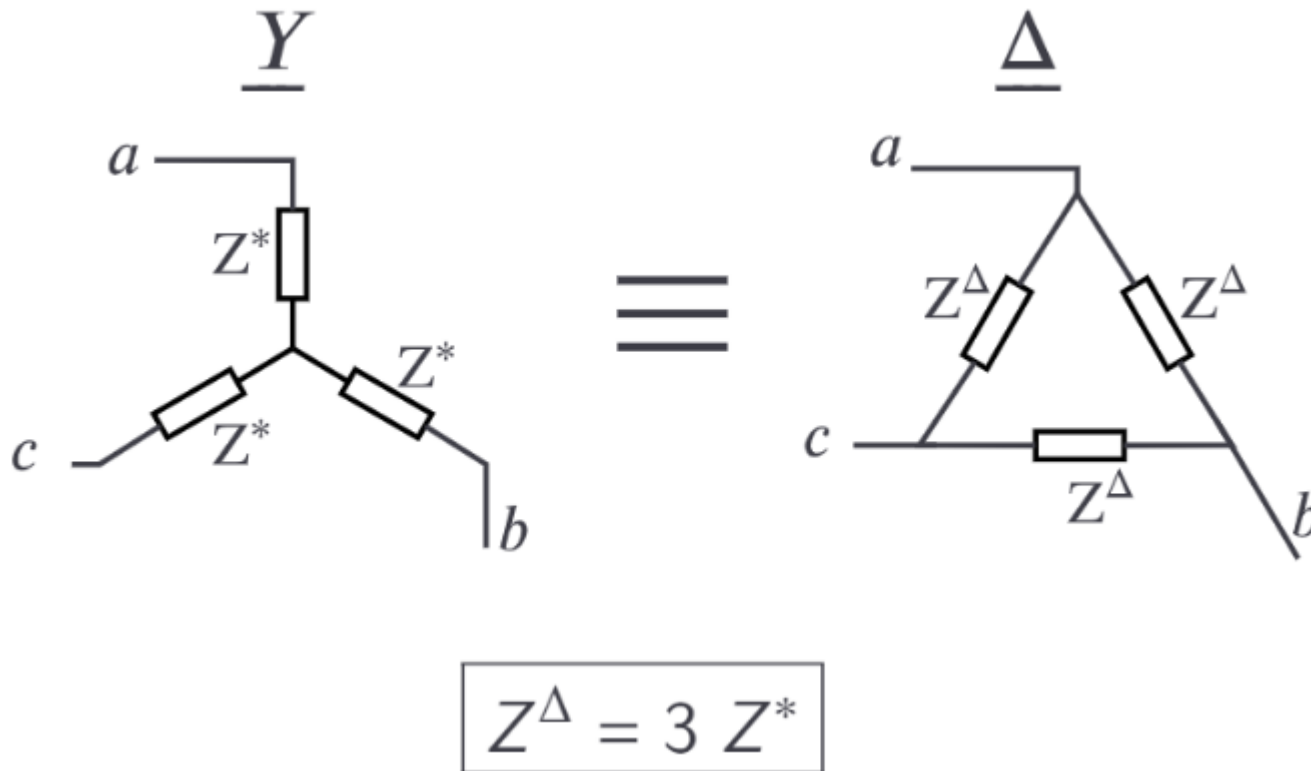

From the network perspective, the Y and  $\Delta$  arrangements are equivalent as long as they provide the same line voltages and current. This is achieved in case  $Z^\Delta = 3 Z^*$ .



# Exercises

---


Exercise 4: Two-ports characterization

Exercise 5: Electric heater
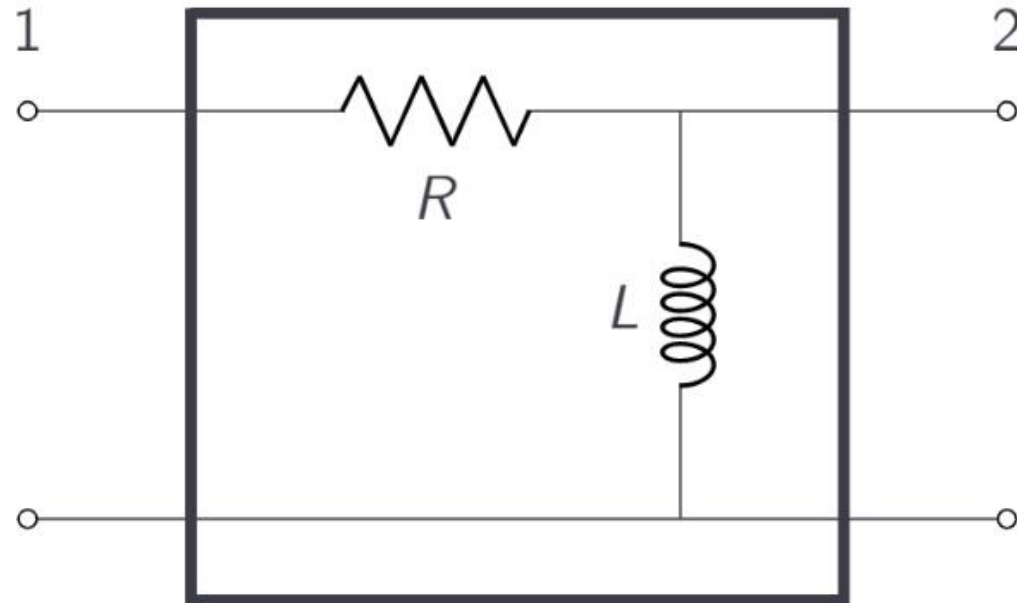
# Exercise 4: Two-ports characterization

Characterize the 2-ports of Figure 1. In that context, two tests have been performed: a short circuit test and an open circuit test.

- 559 mV and 1.118 A are measured at the access 1 while the access 2 is shorted (short circuit test at 50 Hz).
- 5 V and 4.472 A are measured at the access 1 while the access 2 is left open (open circuit test at 50 Hz).




# Exercise 4: Two-ports characterization

Consider that the tests are performed at 50 Hz. The 2-ports could be fully characterized by only one of the two tests if the active power was measured during the tests. The active power can be measured with a wattmeter.

1. Determine the value of  $R$  and  $L$  with the information above.
2. Which test would be necessary ?
3. During that test, an active power of 9.99392 W has been measured. Prove that it gives the correct value of  $R$  and  $L$ .
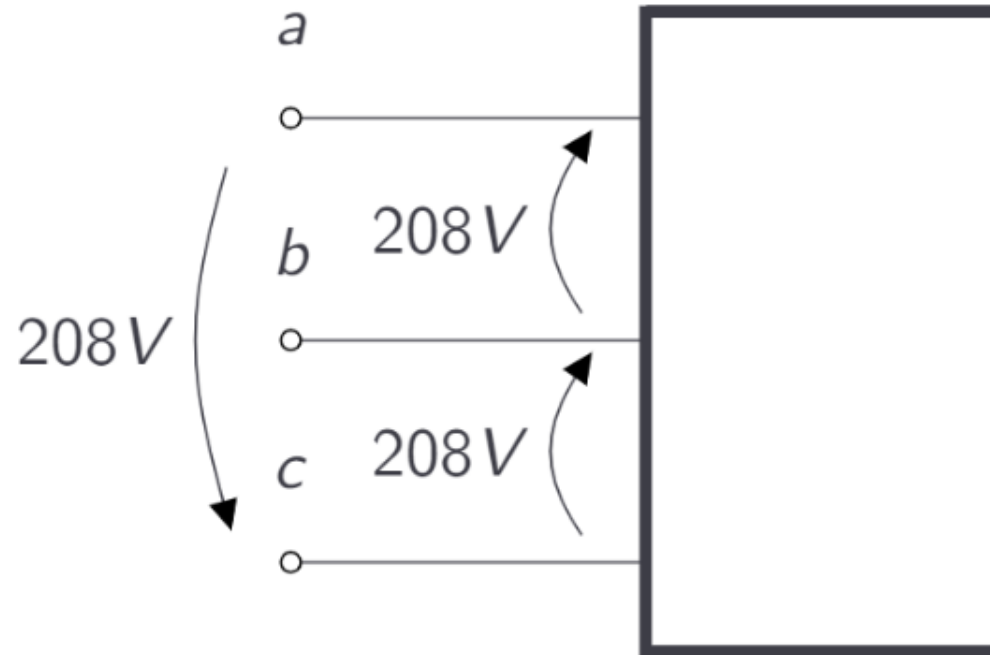
# Exercise 5: Electric heater

Consider an electrical heater that dissipates 15 kW of power when connected to a three-phase power system of 208 V. As a first approximation, the heater is modelled as a purely resistive three-phase load.



# Exercise 5: Electric heater

1. If no additional information is provided about the voltage, does the 208 V correspond to the peak or the RMS value ?
2. Compute the line current if the resistive loads are connected in  $\mathbf{Y}$ .
3. If the resistors are connected in  $\mathbf{Y}$ , compute the resistance of each.
4. Compute the line current if the resistive loads are connected in  $\Delta$ .
5. If the resistors are connected in  $\Delta$ , compute the resistance of each.