



Electromagnetic Energy Conversion

ELEC0431

Exercise session 2: Balanced three-phase systems

17 February 2023

Florent Purnode (florent.purnode@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,
University of Liège, Belgium

In this class...


- Producer or consumer ?
- Exercise 3
- Introduction to three-phase systems
- Star and Delta configurations
- Exercise 6
- Exercise 4

Producer or consumer ?

Using the **passive convention**, we consider a one-port crossed by a current $\bar{I} = I e^{j\psi}$ with a voltage $\bar{V} = V e^{j\theta}$.

The associated **complex power** is
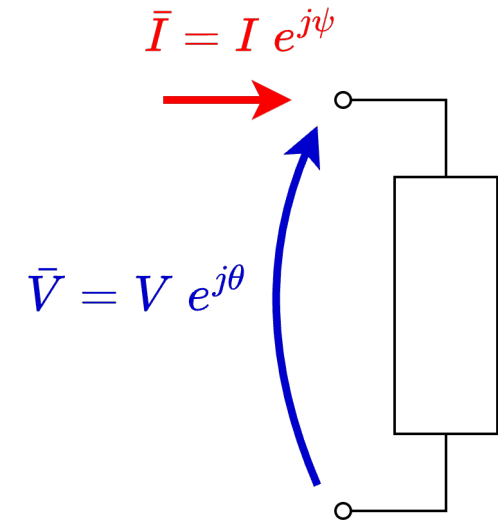
$$\begin{aligned} S &= \bar{V} \bar{I}^* = VI e^{j(\theta - \psi)} \\ &= VI \cos(\theta - \psi) + j VI \sin(\theta - \psi) \\ &= P + j Q \end{aligned}$$



In case P is **positive**, we say that the one-port **consumes** active power.


In case P is **negative**, we say that the one-port **produces** active power.

In case Q is **positive**, we say that the one-port **consumes** reactive power.

In case Q is **negative**, we say that the one-port **produces** reactive power.

Producer or consumer ?

Taking \bar{I} as reference:

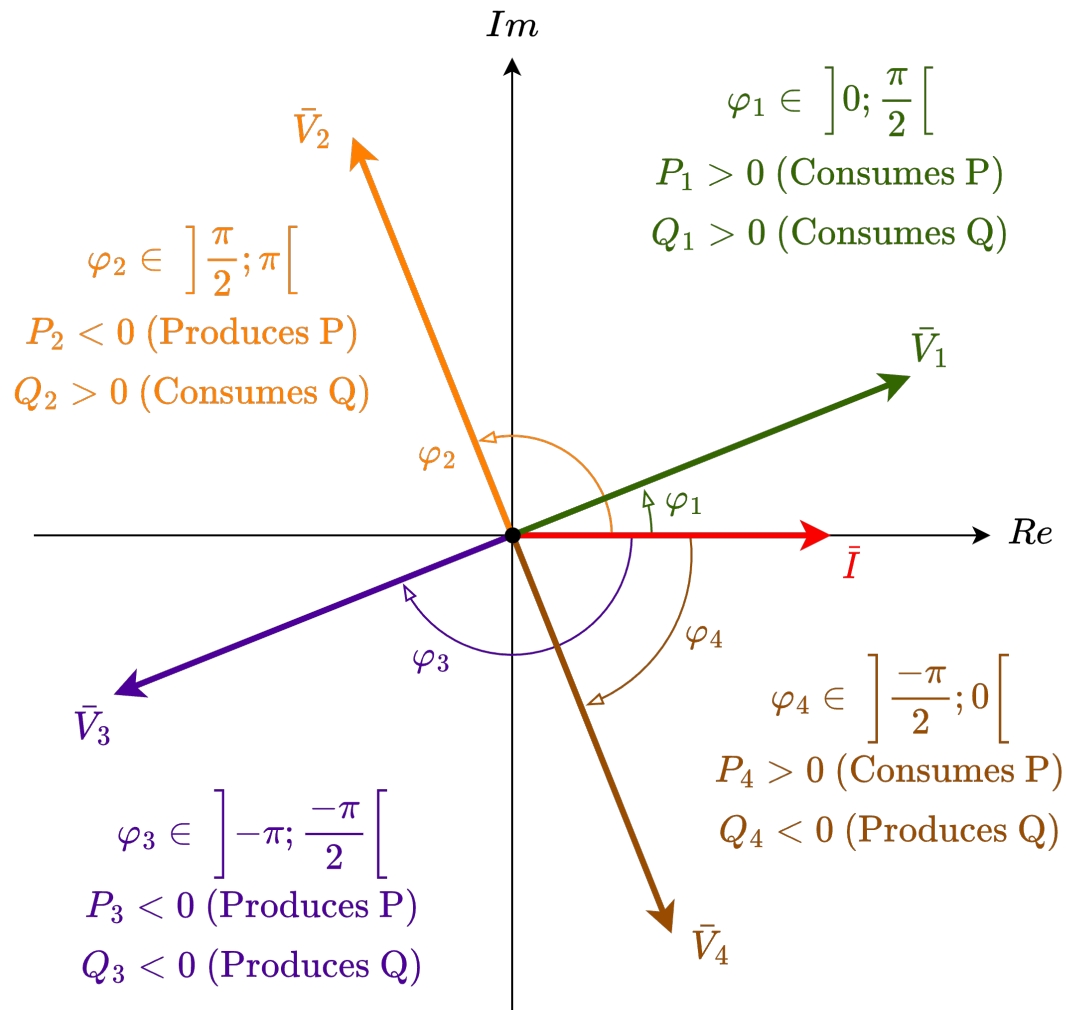

$$P = VI \cos(\theta - \psi) = VI \cos(\varphi)$$

$$Q = VI \sin(\theta - \psi) = VI \sin(\varphi)$$

➤ If $\varphi > 0$

The **voltage leads** the **current**

The one-port consumes **reactive power**

➤ If $\varphi < 0$

The **voltage lags** the **current**

The one-port produces **reactive power**

➤ If $|\varphi| < \frac{\pi}{2}$

The one-port consumes **active power**






➤ If $|\varphi| > \frac{\pi}{2}$

The one-port produces **active power**

Exercise 3


Fill the cells of the table below with the most appropriate answer among

$= 0$ < 0 > 0 $= 1$ < 1 $+\infty$ $-\infty$

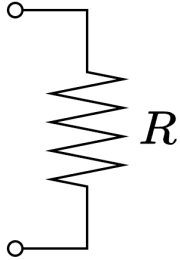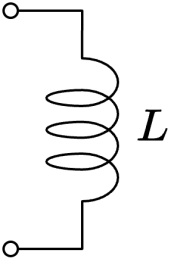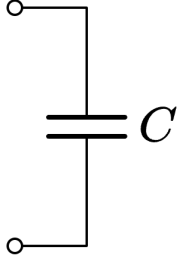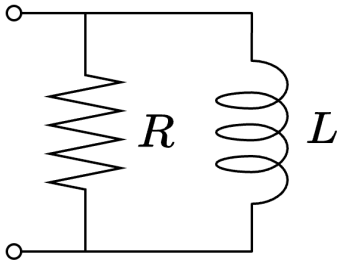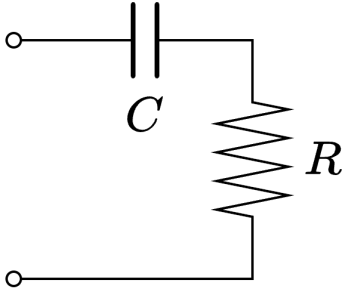					
Active power consumed	> 0	$= 0$	$= 0$	> 0	> 0
Reactive power produced	$= 0$	< 0	> 0	< 0	> 0
$\cos(\varphi)$	$= 1$	$= 0$	$= 0$	> 0	> 0
$\tan(\varphi)$	$= 0$	$+\infty$	$-\infty$	> 0	< 0

One-phase generator

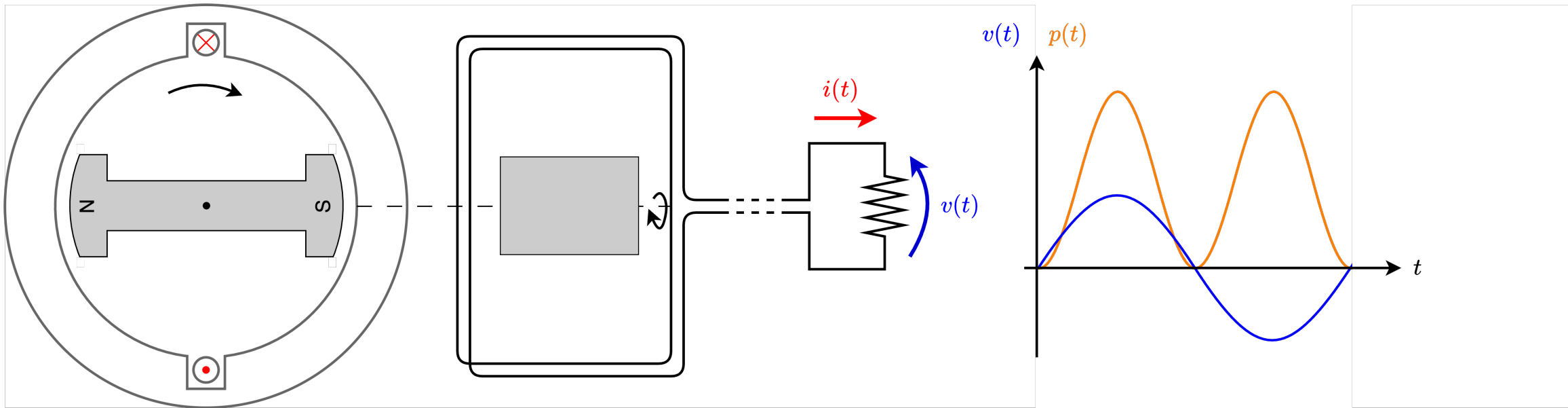
To build an AC generator, one could spin a magnet in a coil. A voltage $v(t)$ is induced in the winding as it perceives a magnetic flux varying over time (Lenz).






The output power $p(t)$ fluctuates so that the input torque fluctuates as well. However, we would like to have a constant input torque.

Two-phase generator

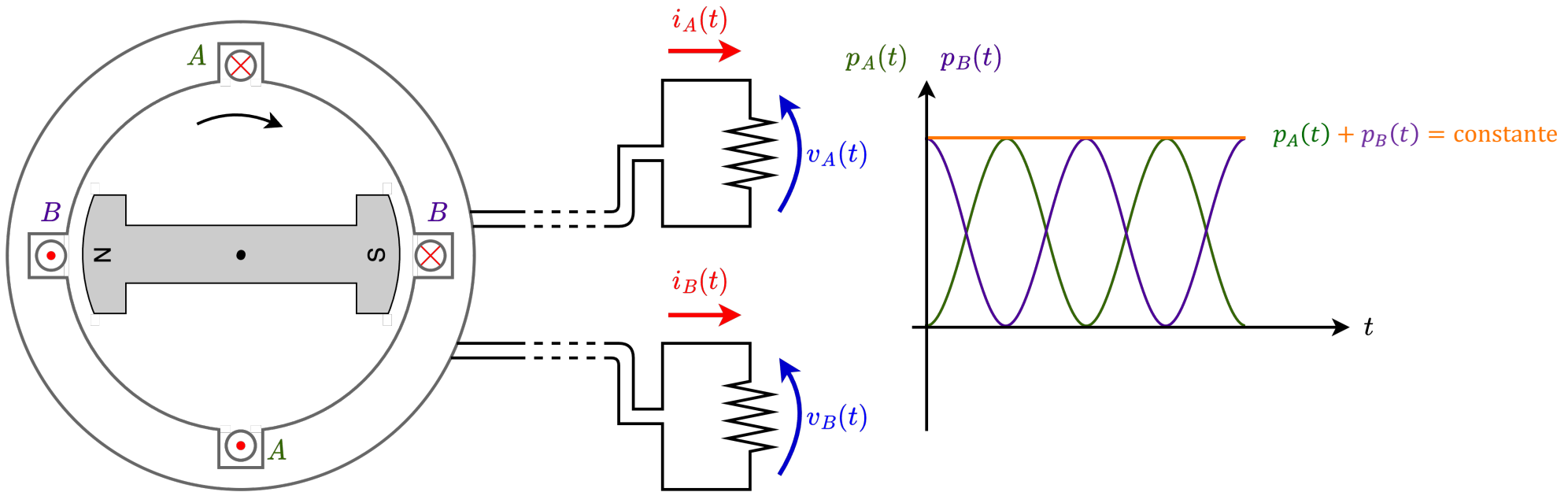Using a second winding connected to an **identical** load, a constant input torque can be obtained.



Three-phase generator

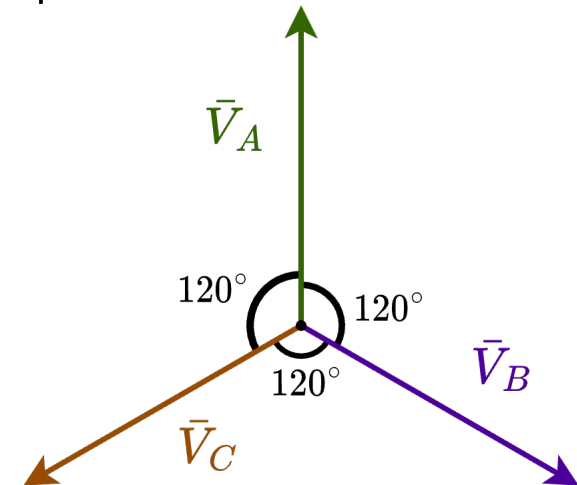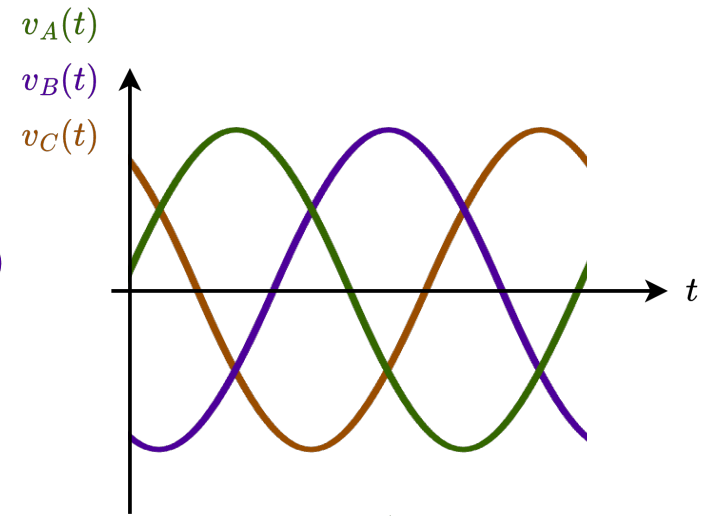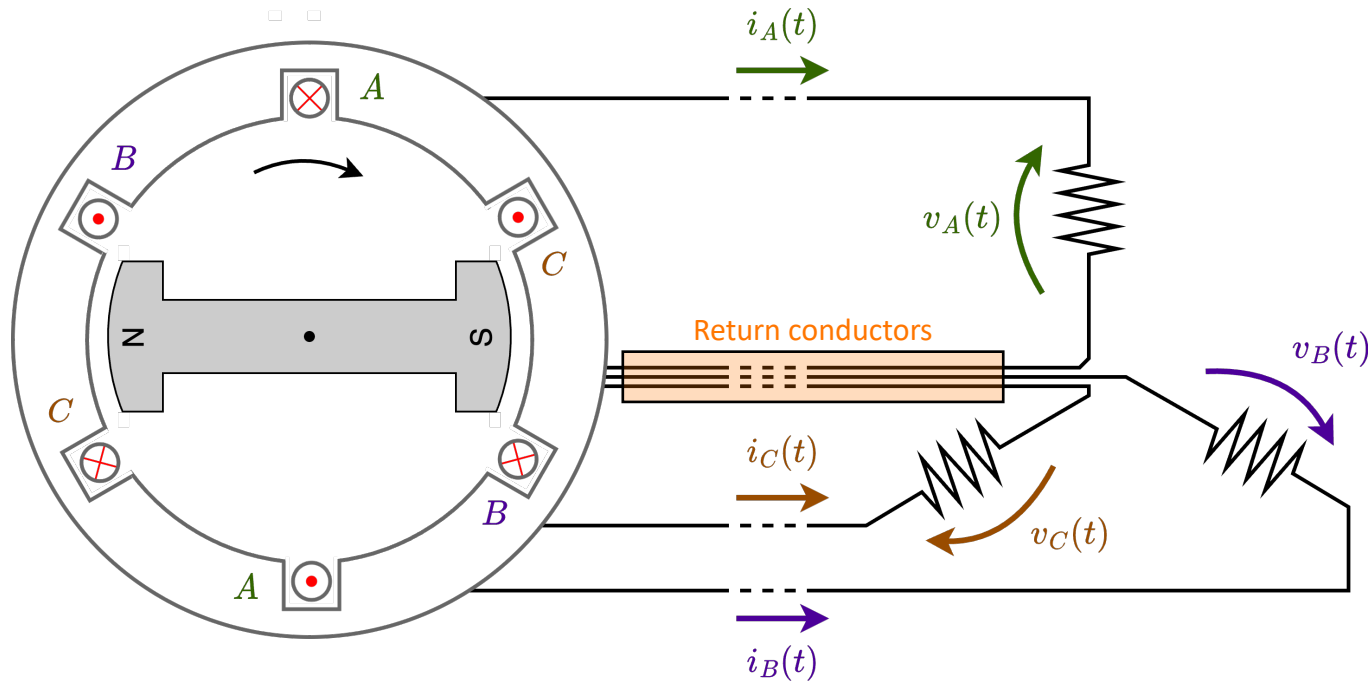


Using identical loads, the input torque also remains constant when using three phases. Moreover, plotting the current phase diagram, it appears that the sum of the currents is zero. The return wires can thus be removed.

Balanced three phase circuit


A balanced three-phase circuit is the assembly of three identical circuits. From one circuit to the other, currents and voltages are out of phase by 120° .

Loads are typically connected in either a **star** (\star or Y) configuration or in a **delta** (Δ) configuration:

Star configuration:

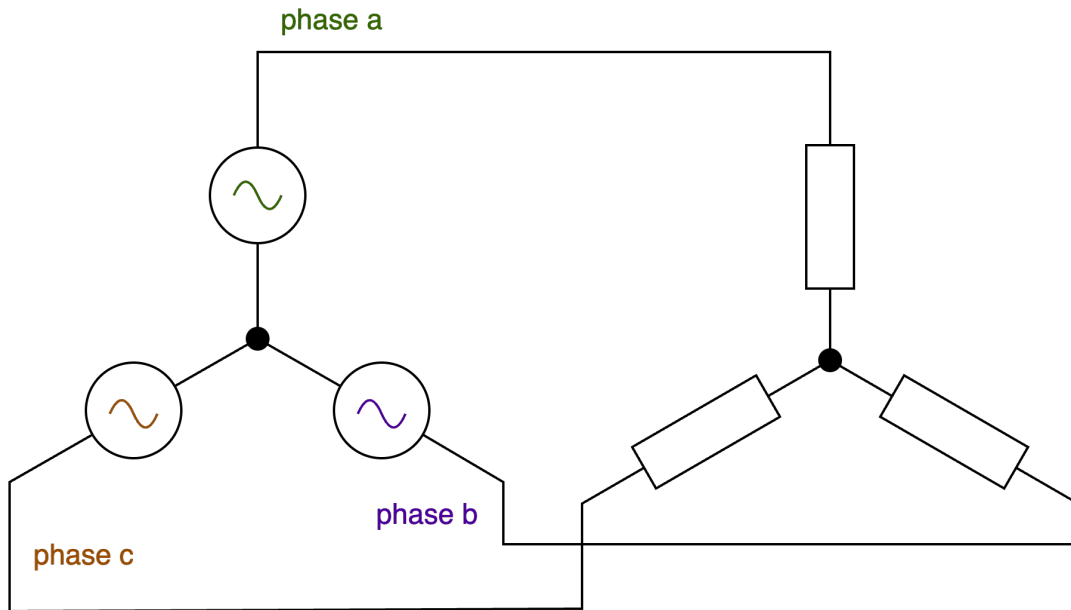

Delta configuration:

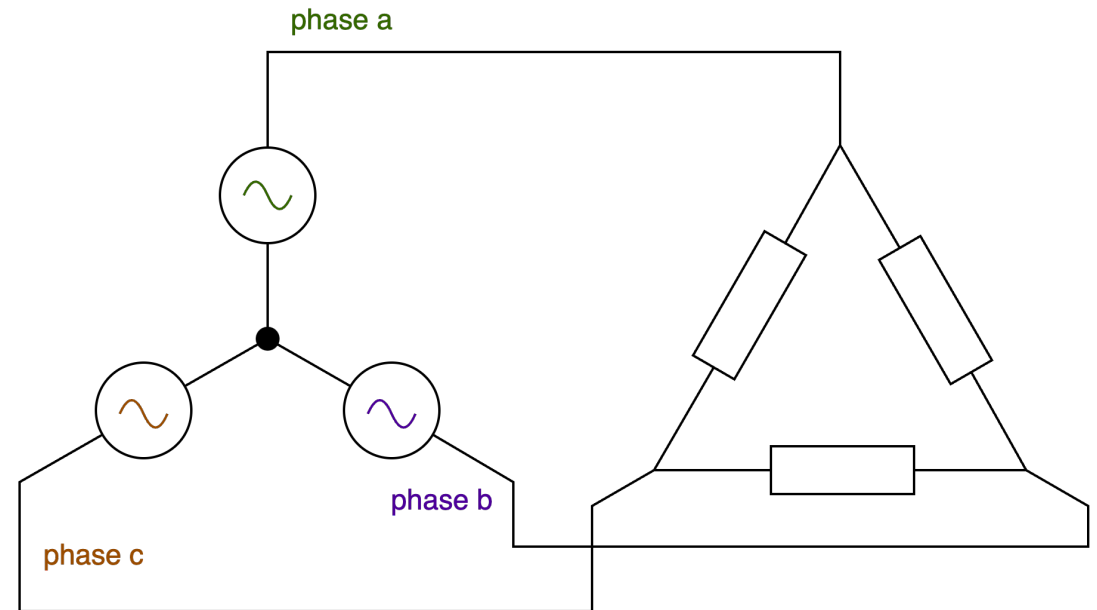


Star configuration

In a star configuration, the current flowing in the transmission line z is the current flowing through the load z .

However, we differentiate:

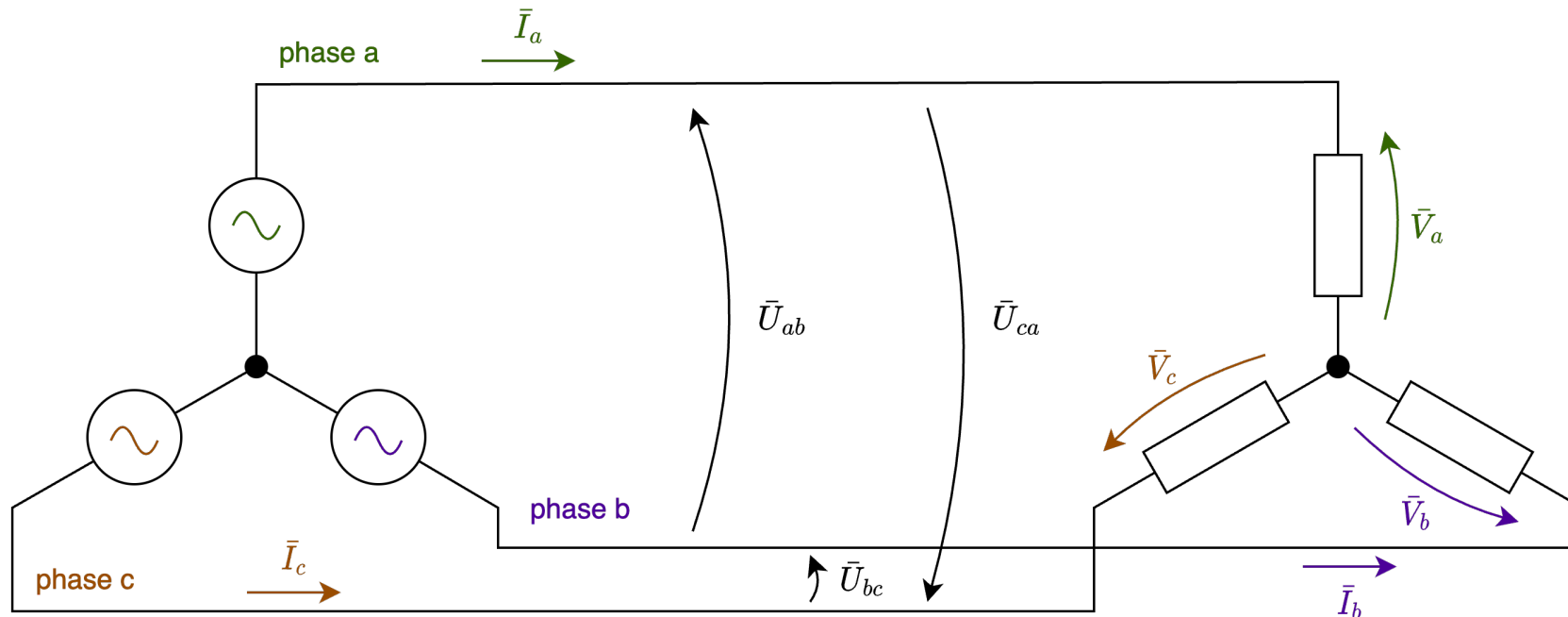- The **line voltage** \bar{U}_{xy} which is the voltage between the phase x and the phase y .
- The **phase voltage** \bar{V}_z which is the voltage across the load z .




$$\bar{U}_{ab} = \bar{V}_a - \bar{V}_b$$

$$\bar{U}_{bc} = \bar{V}_b - \bar{V}_c$$

$$\bar{U}_{ca} = \bar{V}_c - \bar{V}_a$$

Star configuration
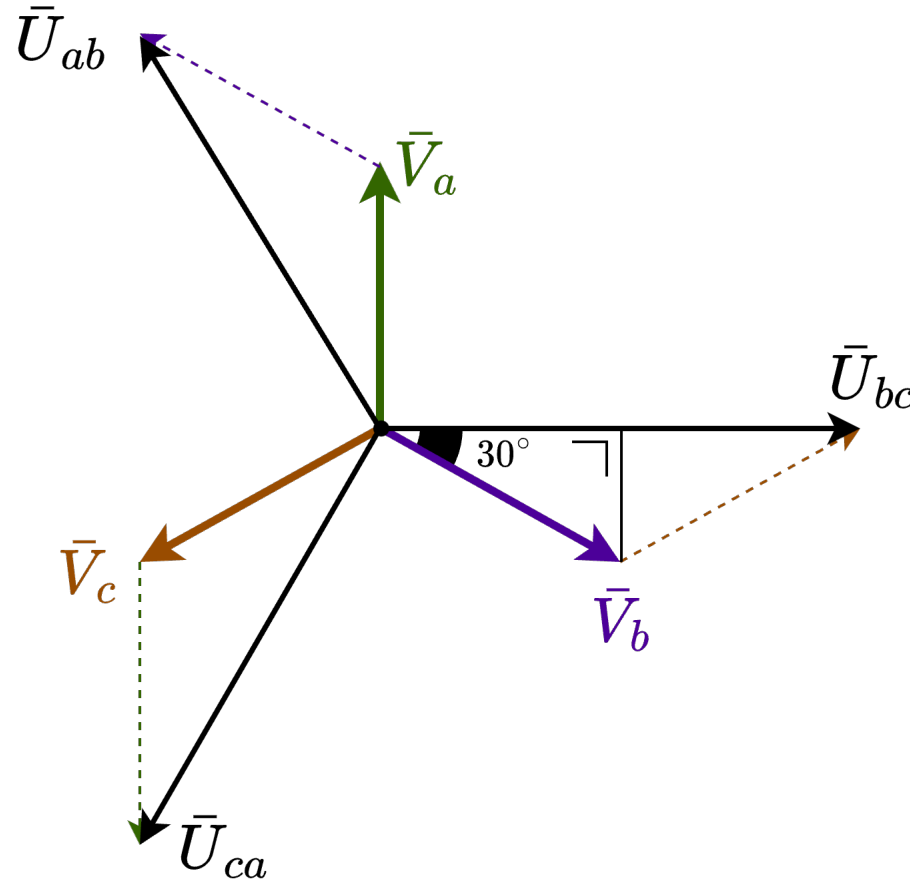
$$\begin{aligned}\bar{U}_{ab} &= \bar{V}_a - \bar{V}_b \\ \bar{U}_{bc} &= \bar{V}_b - \bar{V}_c \\ \bar{U}_{ca} &= \bar{V}_c - \bar{V}_a\end{aligned}$$



$$\begin{aligned}\frac{U_{bc}}{2} &= \cos(30^\circ) V_b = \frac{\sqrt{3}}{2} V_b \\ \Rightarrow U_{bc} &= \sqrt{3} V_b\end{aligned}$$


In a star configuration, the line voltage is $\sqrt{3}$ the phase voltage.

Delta configuration

In a star configuration, the voltage between the phase x and the phase y is the voltage across the load xy .

However, we differentiate:

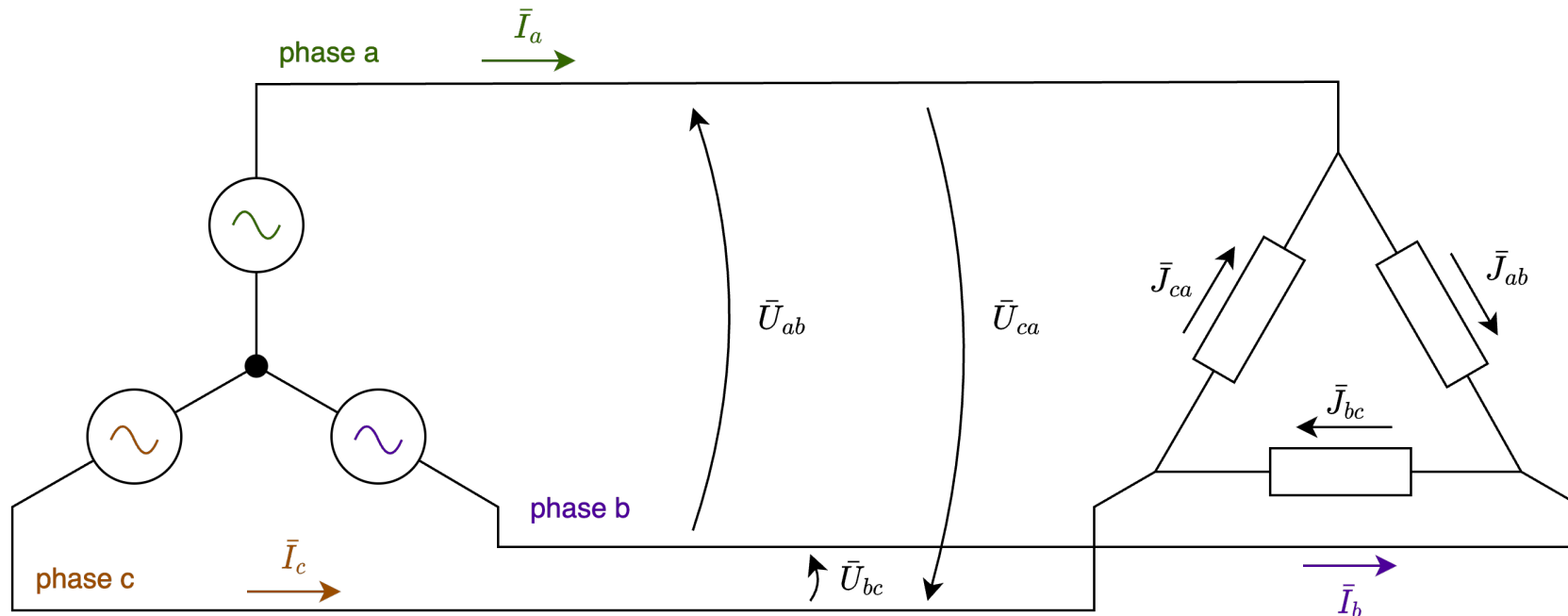- The **line current** \bar{I}_z which is the current flowing in the transmission line z .
- The **phase current** \bar{J}_{xy} which is the current flowing in the load xy .



$$\bar{I}_a = \bar{J}_{ab} - \bar{J}_{ca}$$

$$\bar{I}_b = \bar{J}_{bc} - \bar{J}_{ab}$$


$$\bar{I}_c = \bar{J}_{ca} - \bar{J}_{bc}$$

Star configuration

$$\bar{I}_a = \bar{J}_{ab} - \bar{J}_{ca}$$

$$\bar{I}_b = \bar{J}_{bc} - \bar{J}_{ab}$$
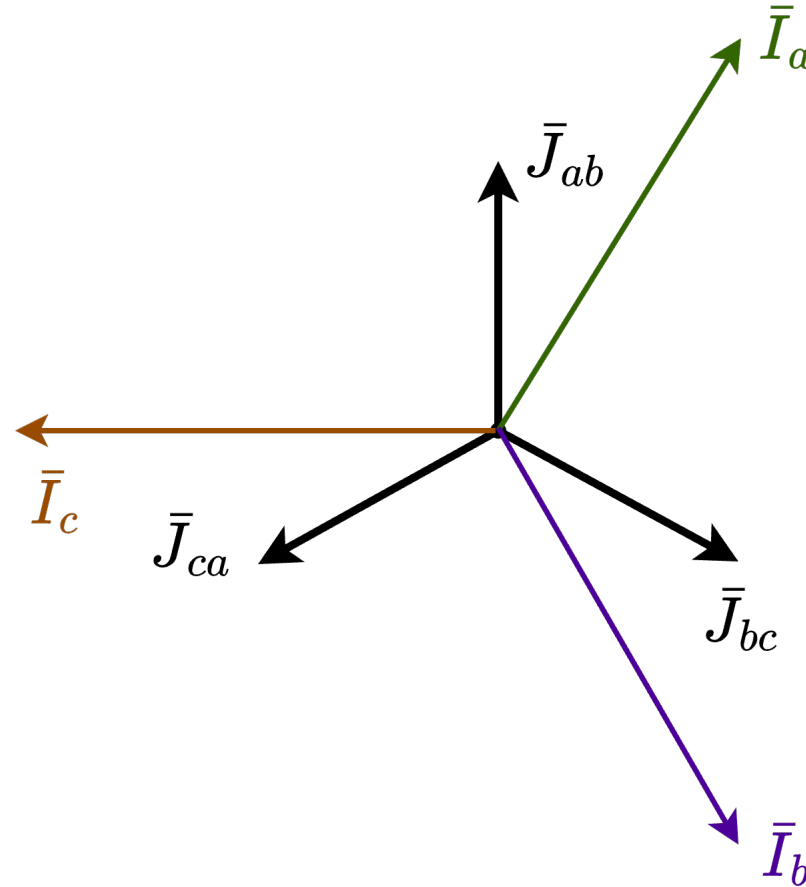
$$\bar{I}_c = \bar{J}_{ca} - \bar{J}_{bc}$$




$$\frac{I_b}{2} = \cos(30^\circ) J_{bc} = \frac{\sqrt{3}}{2} J_{bc}$$
$$\Rightarrow I_b = \sqrt{3} J_{bc}$$

In a delta configuration, the line current is $\sqrt{3}$ the phase current.


Star and Delta configurations: recap

Y


Network

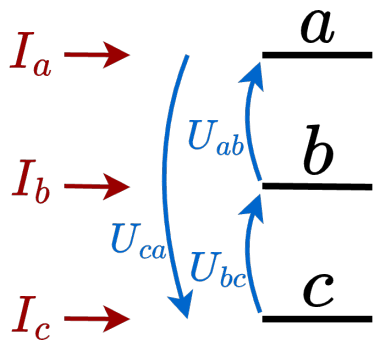

Load

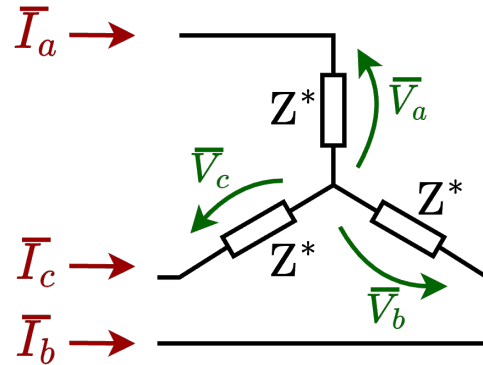

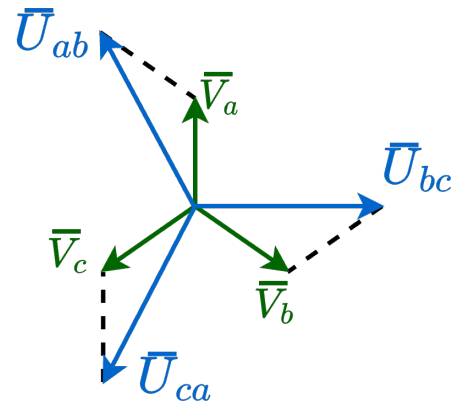
$$V_a = \frac{U_{ab}}{\sqrt{3}}$$
 phase voltage line voltage




Δ


Network

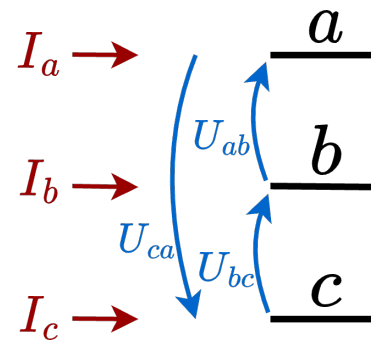

Load

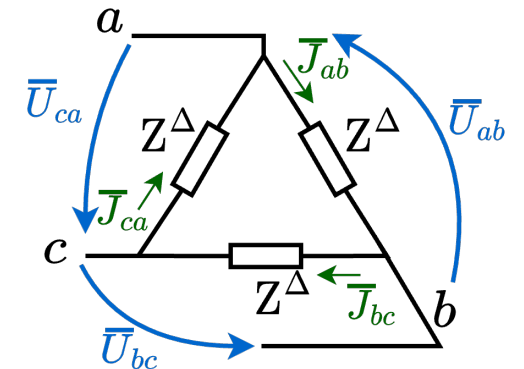


$$J_{ab} = \frac{I_a}{\sqrt{3}}$$
 phase current line current

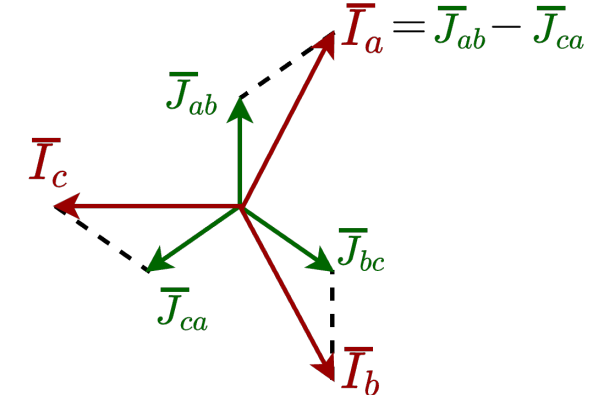

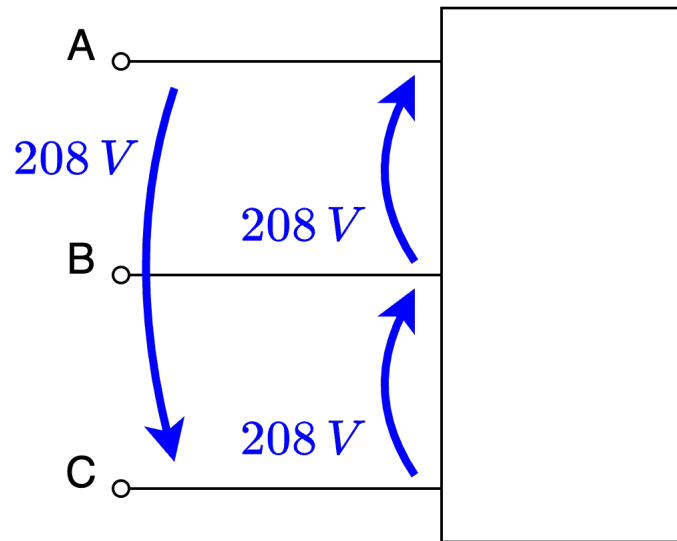Exercise 6


Consider an electrical heater that dissipates 15 kW of power when connected to a three-phase power system of 208 V . As a first approximation, the heater is modelled as a purely resistive three-phase load.



1. If no additional information is provided about the voltage, does the 208 V correspond to the peak or to the RMS value ?
2. Compute the line current if the resistive loads are connected in \star .
3. If the resistors are connected in \star , compute the resistance of each.
4. Compute the line current if the resistive loads are connected in Δ .
5. If the resistors are connected in Δ , compute the resistance of each.

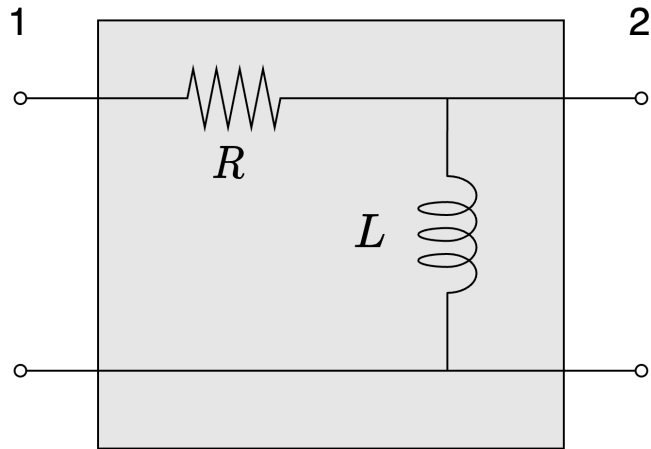Exercise 4

Characterize the 2-port hereunder. Two tests have been performed: a short circuit test and an open circuit test:



- 559 mV and 1.118 A are measured at the access 1 while the access 2 is shorted (short circuit test at 50 Hz).
- 5 V and 4.472 A are measured at the access 1 while the access 2 is left open (open circuit test at 50 Hz).

The 2-port could be fully characterized by only one of the two tests if the active power was measured during the tests. The active power can be measured with a wattmeter.

1. Determine the value of R and L with the information above.
2. Which test would be necessary ?
3. During that test, an active power of 9.99392 W has been measured. Prove that it gives the correct value R and L .