



# Electromagnetic Energy Conversion

## ELEC0431

### Exercise session 3: Magnetic circuits and transformers

21 February 2025

Florent Purnode (florent.purnode@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,  
University of Liège, Belgium

# Laboratories – Schedule and groups

To create the lab schedule, you are required to fill **by group** the doodle <https://framadate.org/LabsELEC0431>:

- By group of **4 students**, select **6** available time slots  
(**you may be given random sessions if less than 6 time slots were selected**).
- In the space provided for names, write the **STUDENT ID NUMBERS** of all **4 MEMBERS** of the group  
(for example: “s161514, s171856, s164442, s179088”).
- A time slot can be selected by maximum six groups, **do not delay in completing this Doodle**.
- In addition to your selected time slots, your schedule could include laboratory sessions on the 18/04, 25/04, 9/05 and 16/05 mornings (Friday mornings in place of the traditional classes).

**IF AND ONLY IF** it is impossible for you to create a group of four students meeting the requirements, send me an email ([florent.purnode@uliege.be](mailto:florent.purnode@uliege.be)) without delay.

Make sure to complete the doodle by **23:59 on Friday, February 28<sup>th</sup>**,  
(Students who would not have given their availabilities by this time will be given random time slots).

Quick reminder: Laboratories are **mandatory**  
(In case of unexcused absence, an absence grade will be given for the entire course).

# In this class...

- Magnetic circuits
- Exercise 6
- Transformers
- Exercise 7


# Magnetic circuits

---

Ampere's law and magnetomotive force  
Magnetic permeability and magnetic flux  
Ferromagnetic materials  
Reluctance and magnetic circuit  
Exercise 6
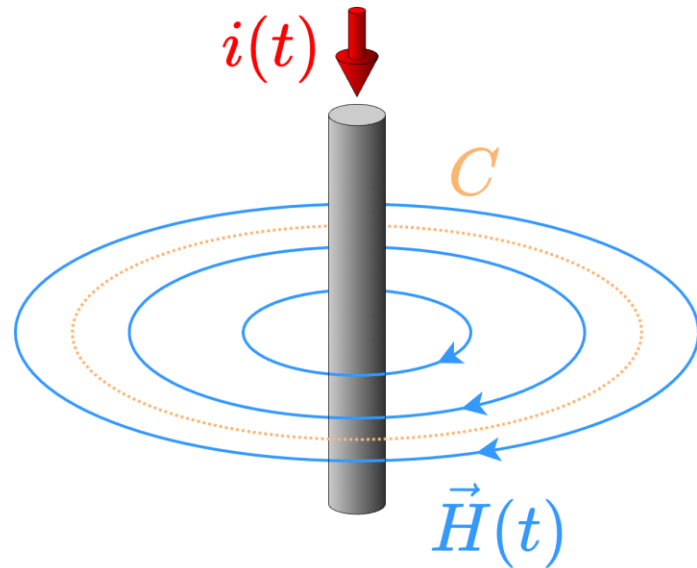
# Ampere's law and magnetomotive force


A current flowing into a wire generates a magnetic field  $H$ .



**Ampere's law** relates the magnetic field  $\vec{H}(t)$  circulating around a closed loop  $C$  to the current  $i(t)$  passing through that loop:

$$\oint_C \vec{H}(t) \cdot d\vec{l} = i(t)$$

A solenoid is a coil of wires.

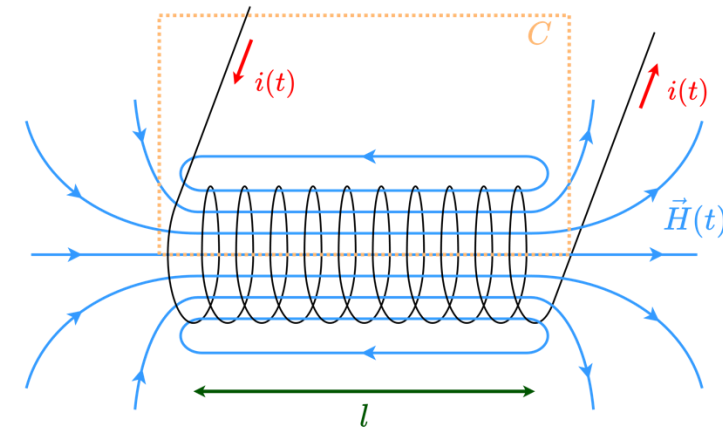

Considering  $N$  turns, the magnetic field  $\vec{H}(t)$  generated is  $N$  times the magnetic field for a single wire:


$$\oint_C \vec{H}(t) \cdot d\vec{l} = N i(t)$$

Inside of the coil, considering RMS values, it simplifies to:

$$H l = N I = \mathcal{F}$$

$\mathcal{F}$  is the **magnetomotive force**.
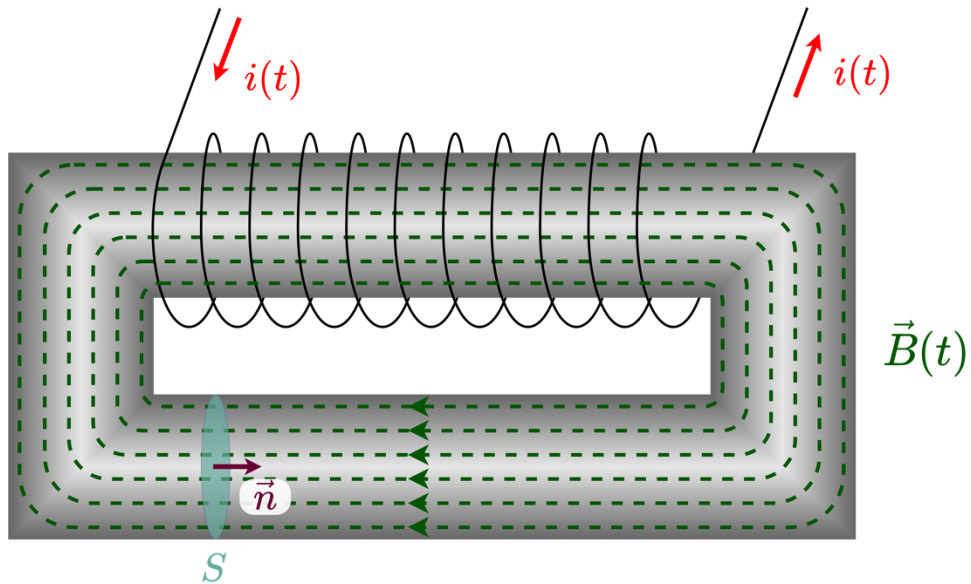
# Magnetic permeability and magnetic flux



The magnetic permeability  $\mu$  links Magnetic flux  $\vec{H}$  and magnetic flux density  $\vec{B}$ :

$$\vec{B} = \mu \vec{H} = \mu_0 \mu_r \vec{H}$$

- $\mu_0 = 4\pi 10^{-7} H/m$  is the permeability of vacuum
- $\mu_r$  is the relative permeability. It varies from one material to the other ( $\mu_r = 1$  for air).

The magnetic flux  $\phi(t)$  is the quantity of magnetic flux density  $\vec{B}(t)$  crossing a surface  $S$ :


$$\phi(t) = \int_S \vec{B}(t) \cdot \vec{n} \, ds.$$

With  $\vec{B}(t)$  uniform over  $S$  and considering the RMS values:

$$\phi = B S = \mu H S$$
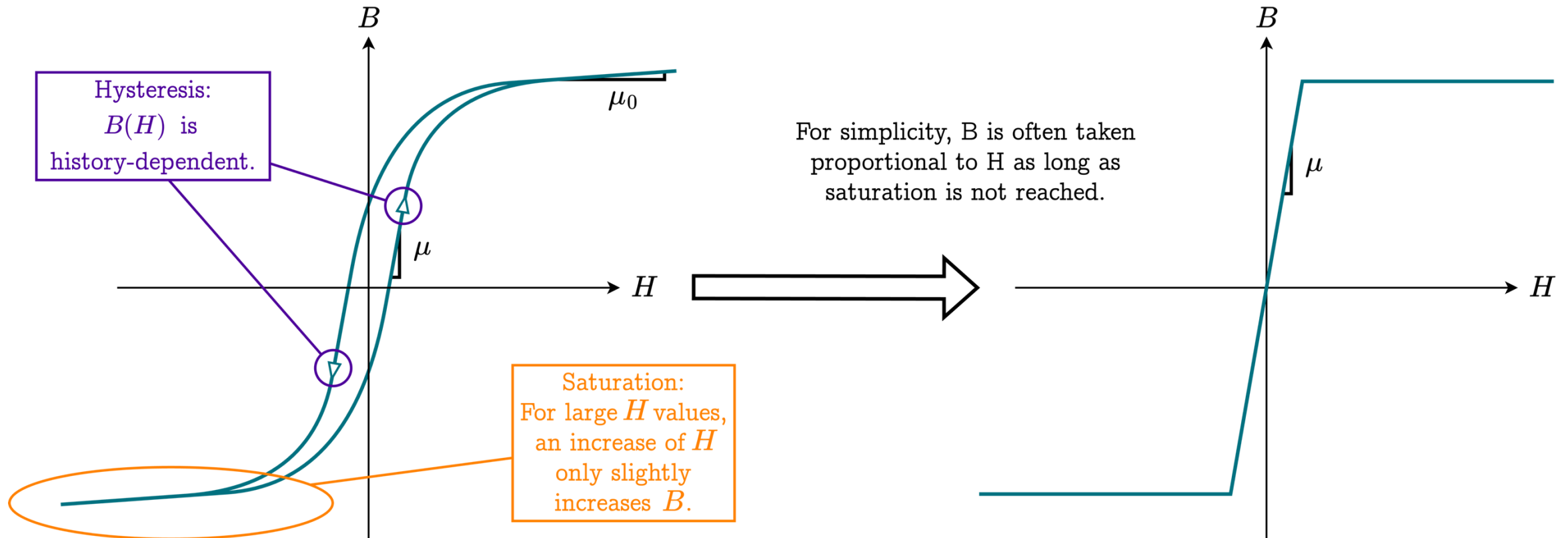
# Ferromagnetic materials

Ferromagnetic materials have a large magnetic permeability  $\mu$ . For this reason, they are often used to handle high magnetic fluxes. They however exhibit hysteresis and saturation:



# Reluctance and magnetic circuit

From Ampere's law (slide 5):

$$Hl = NI = \mathcal{F}$$

From magnetic constitutive law (slide 6):

$$\phi = \mu HS$$

$$\mathcal{F} = NI = \frac{l}{\mu S} \phi = \mathcal{R} \phi$$

Magnetomotive force

Reluctance

Magnetic flux

The relation linking magnetomotive force, reluctance and magnetic flux is similar to the Ohm's law linking voltage, resistance and current:

Ohm's law:  $V = RI$

Pouillet's law:  $R = \frac{l}{\sigma S}$

$\sigma$  is the conductivity  $\left[\frac{S}{m}\right]$

Magnetic circuit equation:  $\mathcal{F} = \mathcal{R} \phi$


Magnetic reluctance formula:  $\mathcal{R} = \frac{l}{\mu S}$

$\mu$  is the permeability  $\left[\frac{H}{m}\right]$


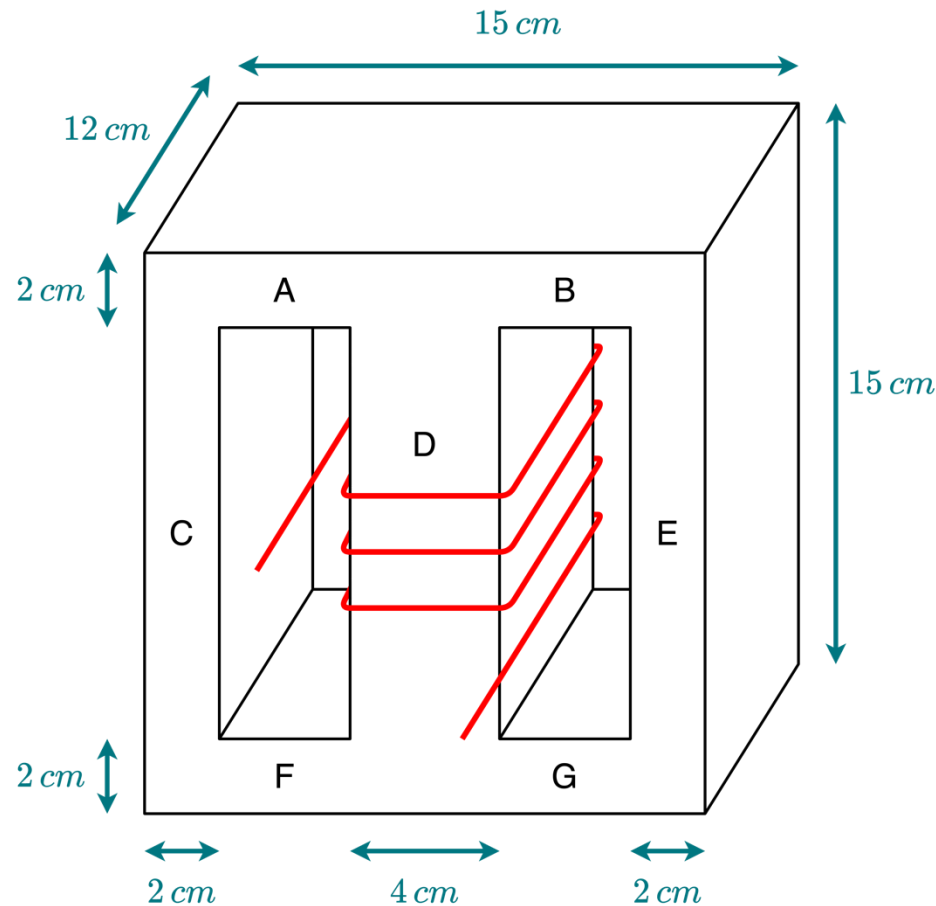
# Exercise 6

Consider an inductor made of an iron core as depicted hereunder and a 60-turn winding, wound around the central leg.



1. Draw an equivalent magnetic circuit of the inductor.
2. Compute the total reluctance of this circuit, considering a relative permeability  $\mu_r$  of 1500 for the iron. Deduce the inductance from it.
3. Do the same computation as in the previous steps, but now considering a constant air gap of 0.1 mm in each leg.

# Transformers

---

The ideal transformer

The real transformer


Shifting impedances

Open-circuit and short-circuit tests

Exercise 7
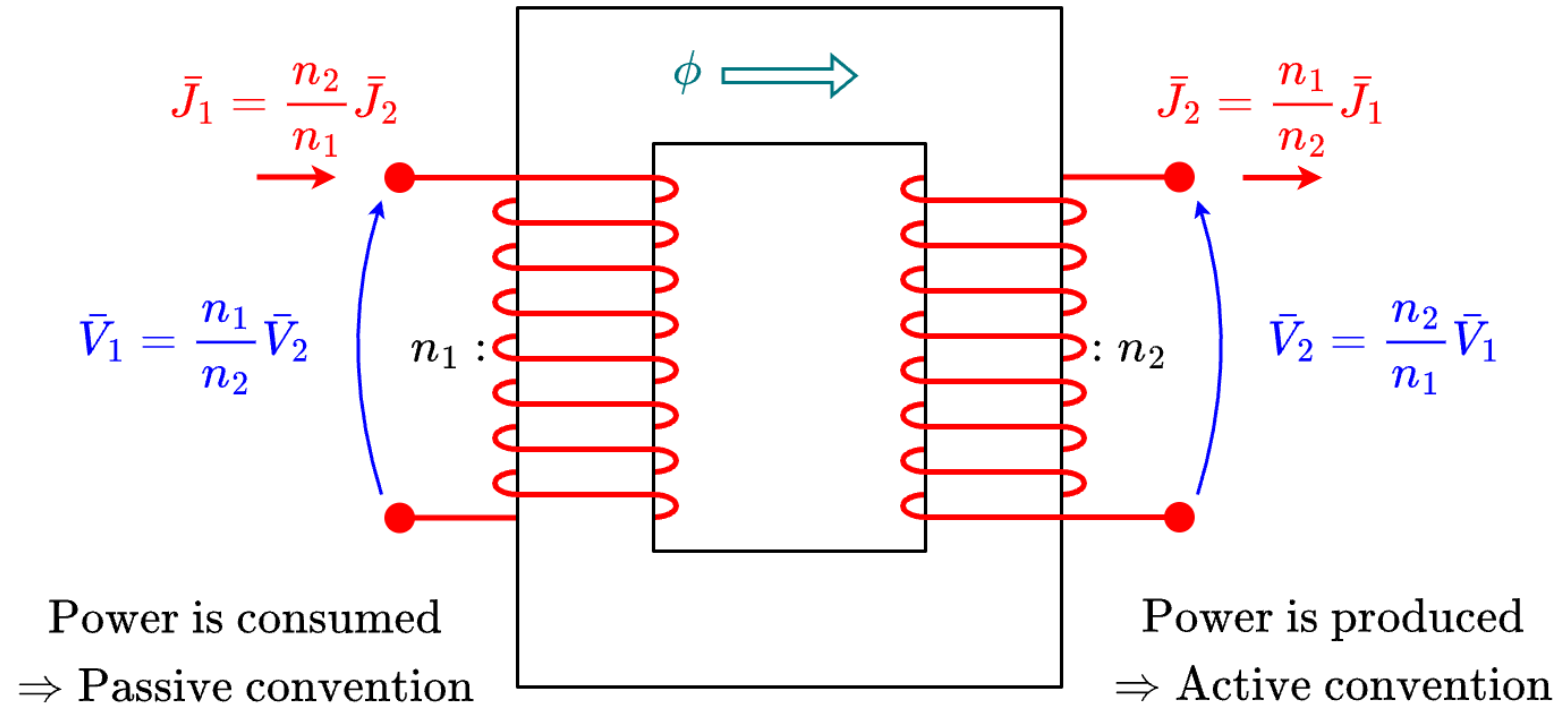
# The ideal transformer


A transformer consists of two or more coils wrapped around a magnetic core, used to increase or decrease an AC voltage/current:



In an ideal transformer:


$$n_2 \bar{V}_1 = n_1 \bar{V}_2 \quad \text{and} \quad n_1 \bar{J}_1 = n_2 \bar{J}_2$$

# The real transformer

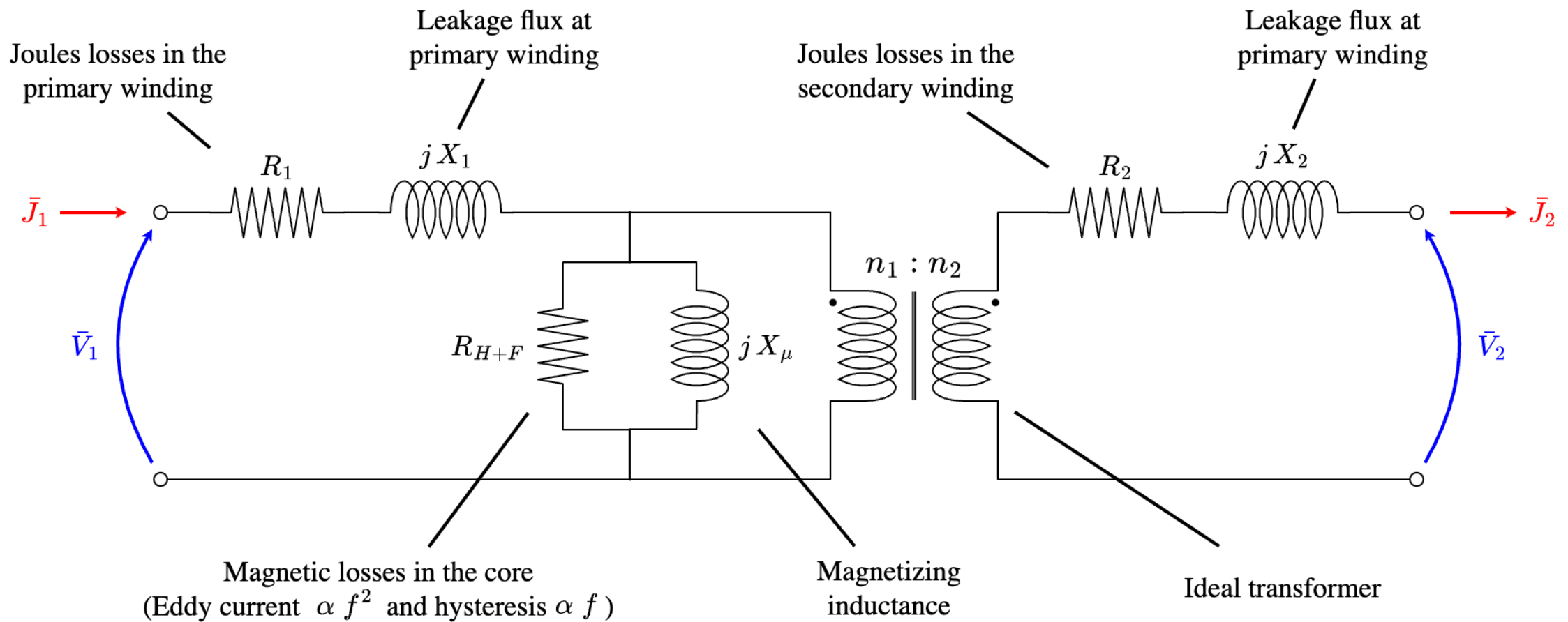

In practice, transformers are built to minimize the losses  $\rightarrow R_1, R_2, X_1, X_2 \ll R_{H+F}, X_\mu$

# Shifting impedances

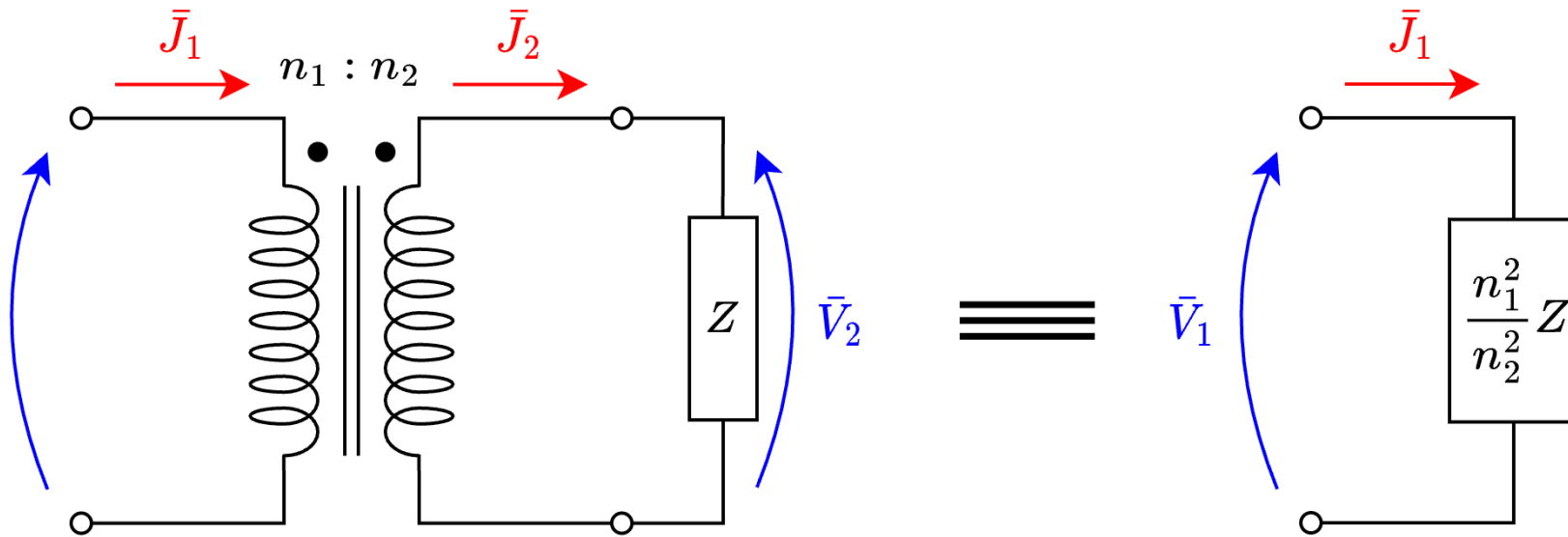

$$n_2 \bar{V}_1 = n_1 \bar{V}_2$$

$$n_1 \bar{J}_1 = n_2 \bar{J}_2$$


Seen from the secondary, the impedance is  $Z = \frac{\bar{V}_2}{\bar{J}_2}$

Seen from the primary, the impedance is  $Z' = \frac{\bar{V}_1}{\bar{J}_1} = \frac{\bar{V}_2 \left(\frac{n_1}{n_2}\right)}{\bar{J}_2 \left(\frac{n_2}{n_1}\right)} = \frac{n_1^2}{n_2^2} \frac{\bar{V}_2}{\bar{J}_2} = \frac{n_1^2}{n_2^2} Z$
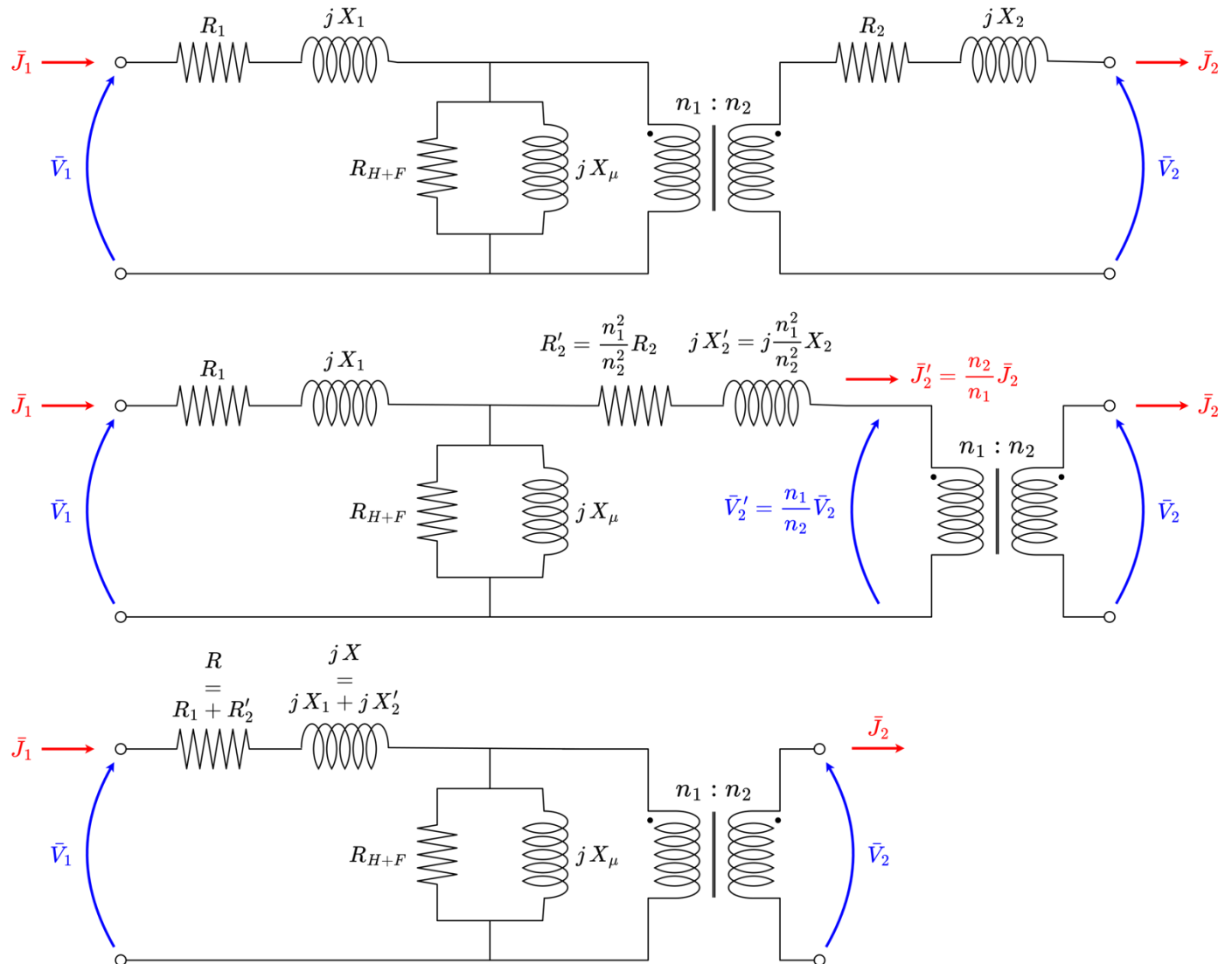
# The real transformer – impedances gathered at primary

One can shift the impedances from the secondary to primary side of the ideal transformer


$R'_2$  and  $jX'_2$  can pass on the other side of the magnetizing branch since  $R'_2, X'_2 \ll R_{H+F}, X_\mu$



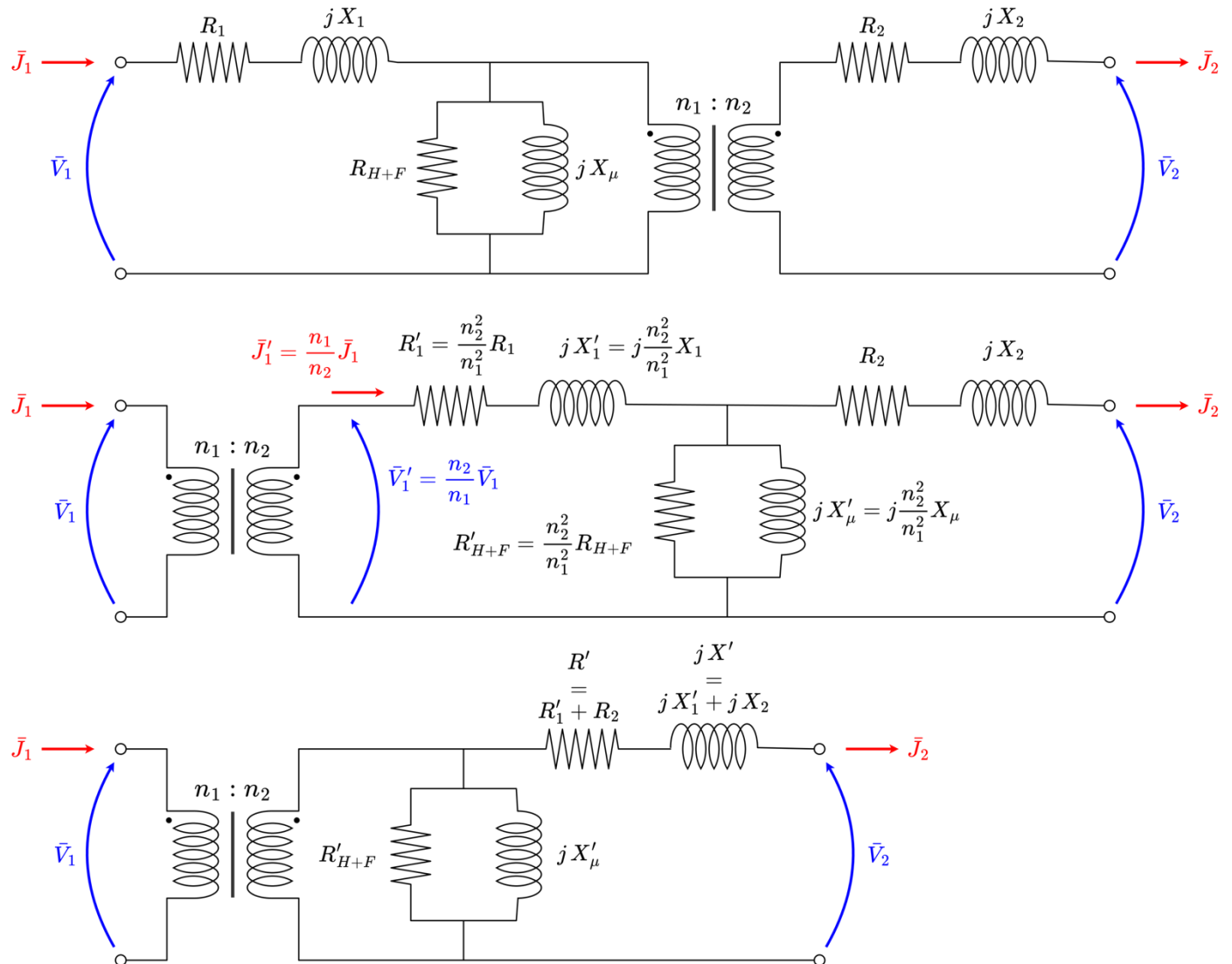
# The real transformer – impedances gathered at secondary

One can shift the impedances from the primary to secondary side of the ideal transformer

$R'_1$  and  $jX'_1$  can pass on the other side of the magnetizing branch since  $R'_1, X'_1 \ll R_{H+F}, X_\mu$



# Open circuit test

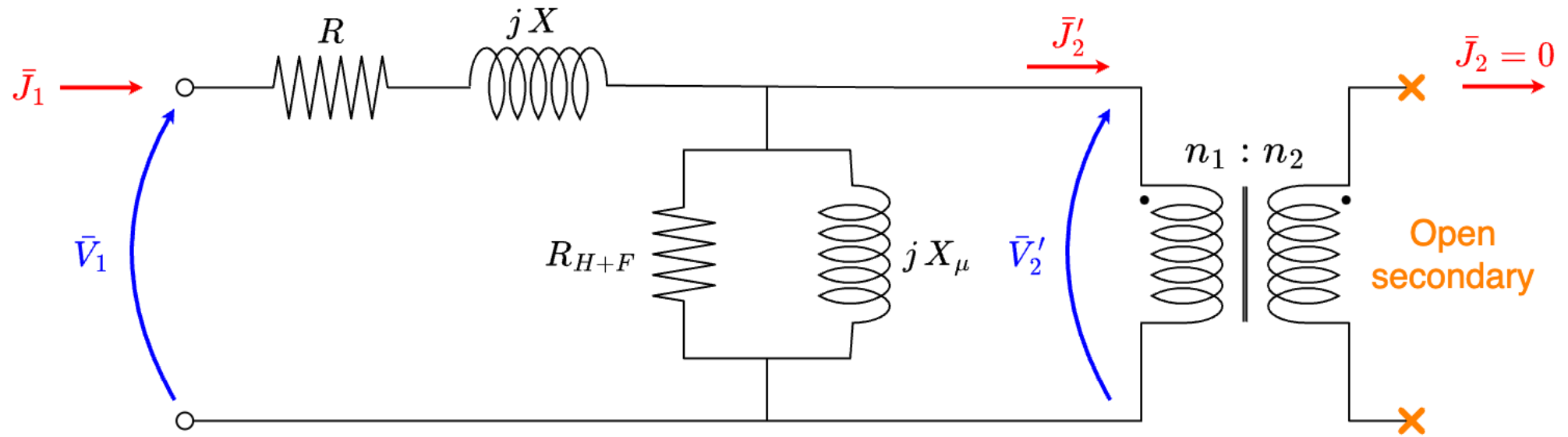


$$\bar{J}_2 = 0 \rightarrow \bar{J}'_2 = 0$$

$$R, X \ll R_{H+F}, X_\mu$$

$$\rightarrow \bar{V}'_2 \gg (R + jX) \bar{J}_1$$

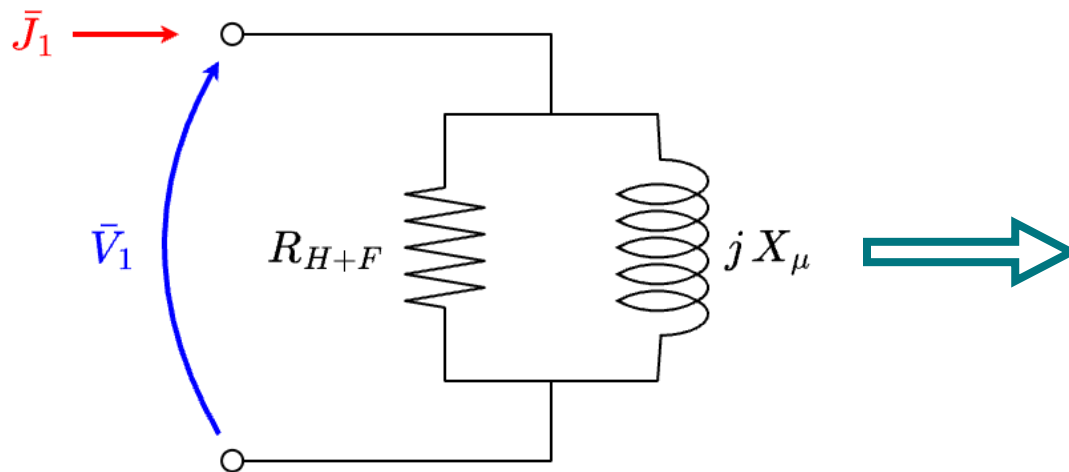$\rightarrow R$  and  $X$  can be neglected




$$P \approx \frac{V_1^2}{R_{H+F}}$$

$$Q \approx \frac{V_1^2}{X_\mu}$$




# Short-circuit test

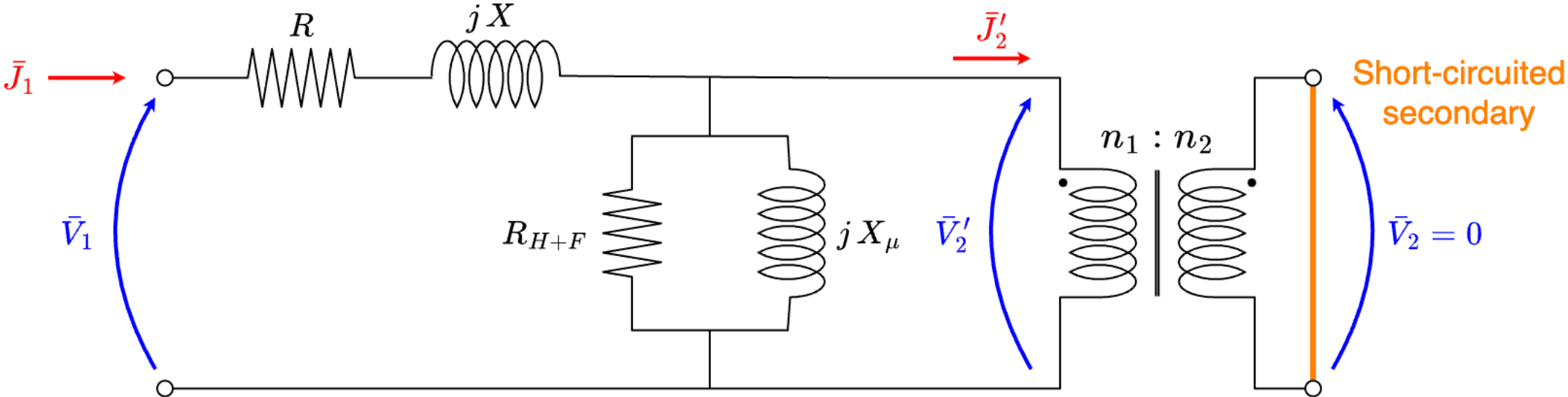

$\bar{V}_2 = 0 \rightarrow \bar{V}'_2 = 0$


→ Voltage drop only for R and X

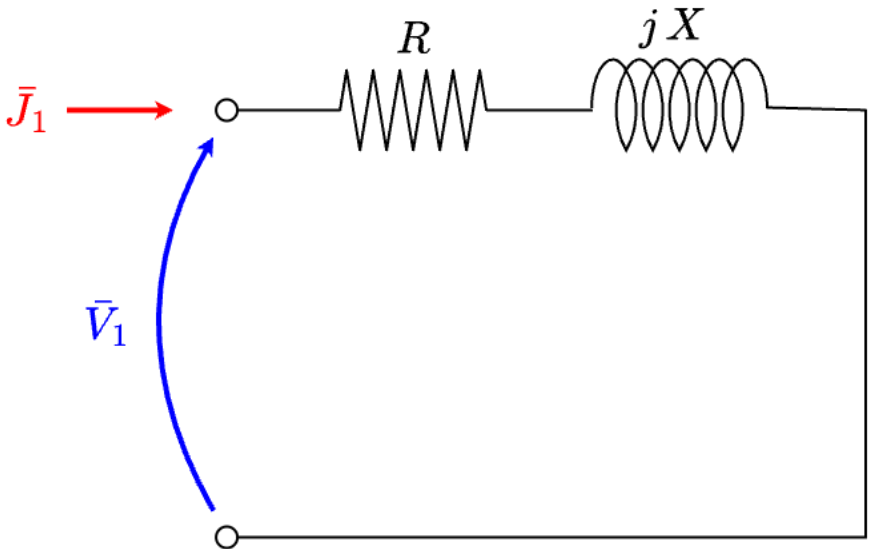

$P \approx R J_1^2$   
 $Q \approx X J_1^2$
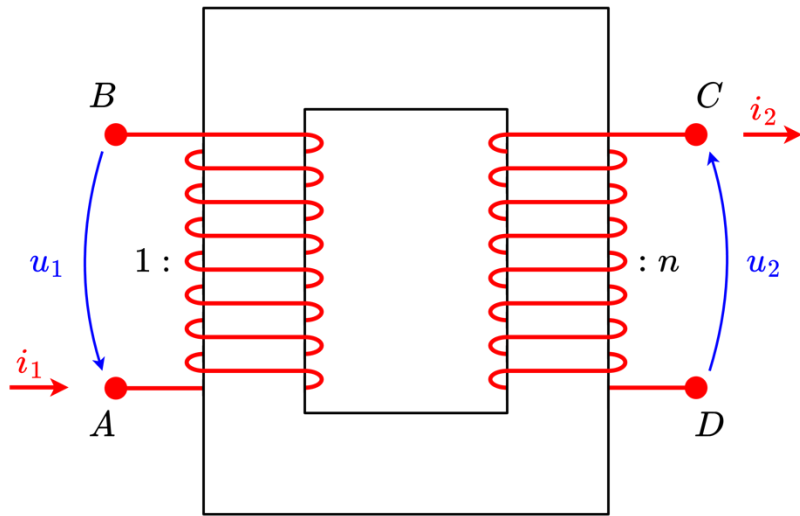
# Exercise 7

Two tests are performed on the transformer illustrated hereunder:



- Using open secondary winding, the transformer generates a voltage of RMS value  $U_{2o} = 100 \text{ V}$  at the secondary winding, for an applied voltage of RMS value  $U_{1o} = 20 \text{ V}$  with a drawn current intensity of RMS value  $I_{1o} = 3.2 \text{ A}$  and a consumed power  $P_{1o} = 8 \text{ W}$ .
- Using short-circuited secondary winding, a voltage of RMS value  $U_{1s} = 0.8 \text{ V}$  for a total power of  $P_{1s} = 24 \text{ W}$  is measured, causing a current flow of RMS value  $I_{2s} = 10 \text{ A}$  through the secondary winding.

Considering a simplified equivalent model of the transformer (resistances and inductances gathered and moved to the secondary winding) and a frequency of 50 Hz:

1. Calculate the transformer ratio  $n$ .
2. Calculate the resistance  $R'_{H+F}$  and the magnetizing inductance  $L'_{\mu}$ .
3. Compute the resistance  $R'$  and the inductance  $L'$ .

# Exercise 7

Using the transformer connected to a load on the secondary side drawing a current of RMS value  $I_2 = 12 \text{ A}$  with a power factor  $\cos(\varphi) = 0.8$  (the current is lagging the voltage), an RMS voltage  $U_1 = 20 \text{ V}$  is applied to the primary winding.

4. Calculate the RMS voltage  $U_2$  appearing across the secondary winding.  
(What wise approximation can be made here?)
5. Deduce the active power  $P_2$  provided to the load.
6. Calculate the RMS current  $I_1$  on the primary side.
7. Compute the transformer efficiency  $\eta$ .