



Electromagnetic Energy Conversion

ELEC0431

Exercise session 3: Magnetic circuits and transformers

20 February 2026

Florent Purnode (florent.purnode@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,
University of Liège, Belgium

Reminder: Laboratories – Schedule and groups

To create the lab schedule, you are required to fill **by group** the doodle <https://beta.framadate.org/polls/465a07d3b8361e104f3d>:

- By group of **4 students**, select **6** available time slots
(you may be given random sessions if less than 6 time slots were selected).
- In the space provided for names, write the **STUDENT ID NUMBERS** of all **4 MEMBERS** of the group
(for example: “s161514, s171856, s164442, s179088”).
- A time slot can be selected by maximum six groups, **do not delay in completing this Doodle.**
- In addition to your selected time slots, your schedule could include laboratory sessions on the 17/04, 24/04, 8/05 and 15/05 mornings (Friday mornings in place of the traditional classes).

IF AND ONLY IF it is impossible for you to create a group of four students meeting the requirements, send me an email (florent.purnode@uliege.be) without delay.

Make sure to complete the doodle by 23:59 on Friday, February 20, (**That's tonight!**)
(Students who would not have given their availabilities by this time will be given random time slots).

Quick reminder: Laboratories are **mandatory**

In case of unexcused absence, an absence grade will be given for the entire course.

In this class...


- Magnetic circuits
- Exercise 6
- Transformers
- Exercise 7

Magnetic circuits

Ampere's law and magnetomotive force
Magnetic permeability and magnetic flux
Ferromagnetic materials
Reluctance and magnetic circuit
Exercise 6

Ampere's law and magnetomotive force

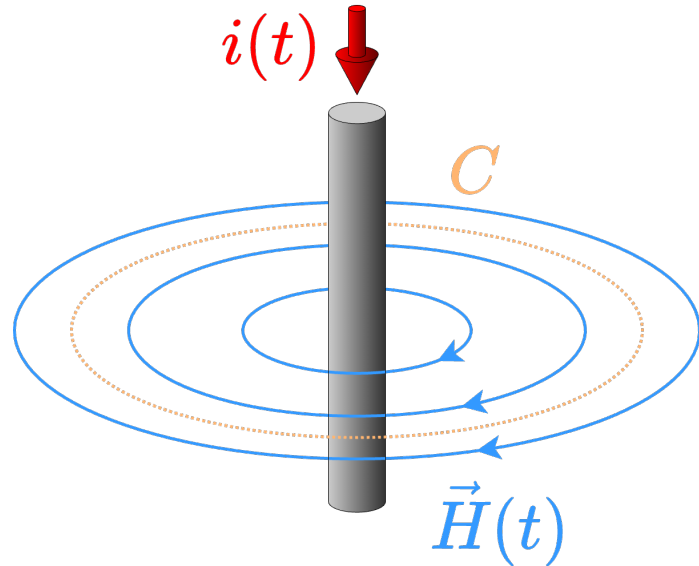
A current flowing into a wire generates a magnetic field H .



Ampere's law relates the magnetic field $\vec{H}(t)$ circulating around a closed loop C to the current $i(t)$ passing through that loop:

$$\oint_C \vec{H}(t) \cdot d\vec{l} = i(t)$$

A solenoid is a coil of wires.

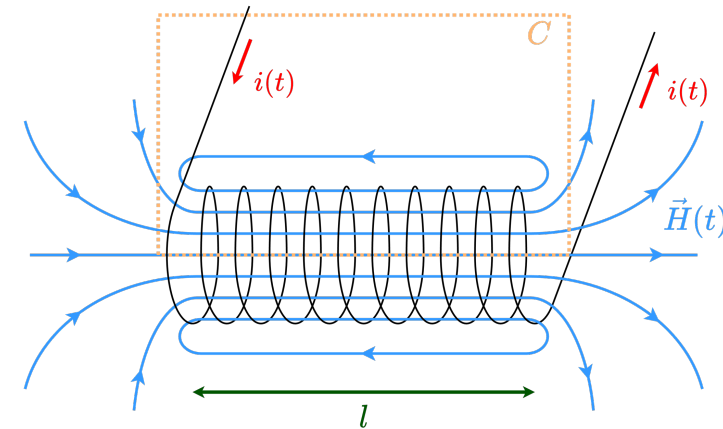

Considering N turns, the magnetic field $\vec{H}(t)$ generated is N times the magnetic field for a single wire:


$$\oint_C \vec{H}(t) \cdot d\vec{l} = N i(t)$$

Inside of the coil, considering RMS values, it simplifies to:

$$H l = N I = \mathcal{F}$$

\mathcal{F} is the **magnetomotive force**.

Magnetic permeability and magnetic flux

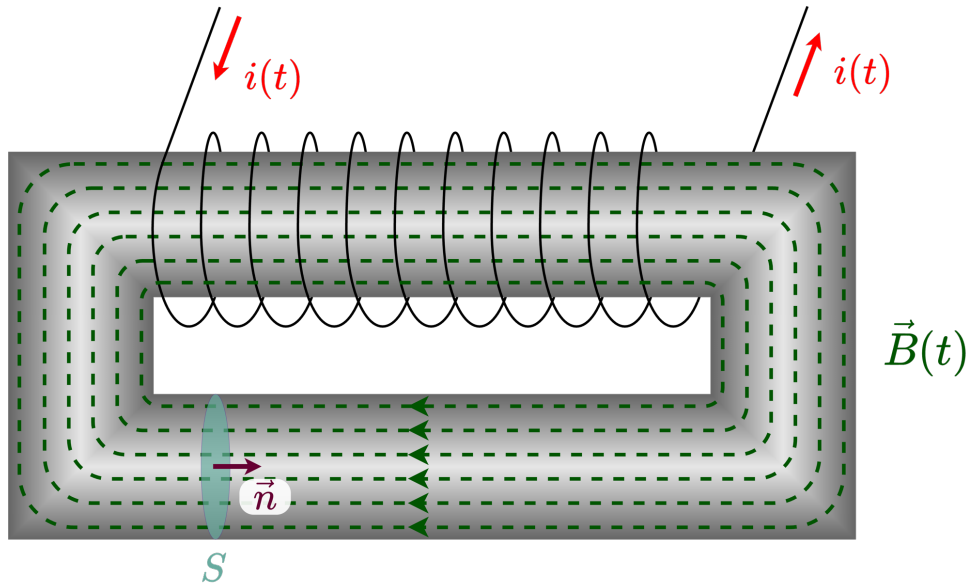

The magnetic permeability μ links Magnetic flux \vec{H} and magnetic flux density \vec{B} :

$$\vec{B} = \mu \vec{H} = \mu_0 \mu_r \vec{H}$$

- $\mu_0 = 4\pi 10^{-7} H/m$ is the permeability of vacuum
- μ_r is the relative permeability. It varies from one material to the other ($\mu_r = 1$ for air).

The magnetic flux $\phi(t)$ is the quantity of magnetic flux density $\vec{B}(t)$ crossing a surface S :


$$\phi(t) = \int_S \vec{B}(t) \cdot \vec{n} \, ds.$$

With $\vec{B}(t)$ uniform over S and considering the RMS values:

$$\phi = B S = \mu H S$$

Ferromagnetic materials

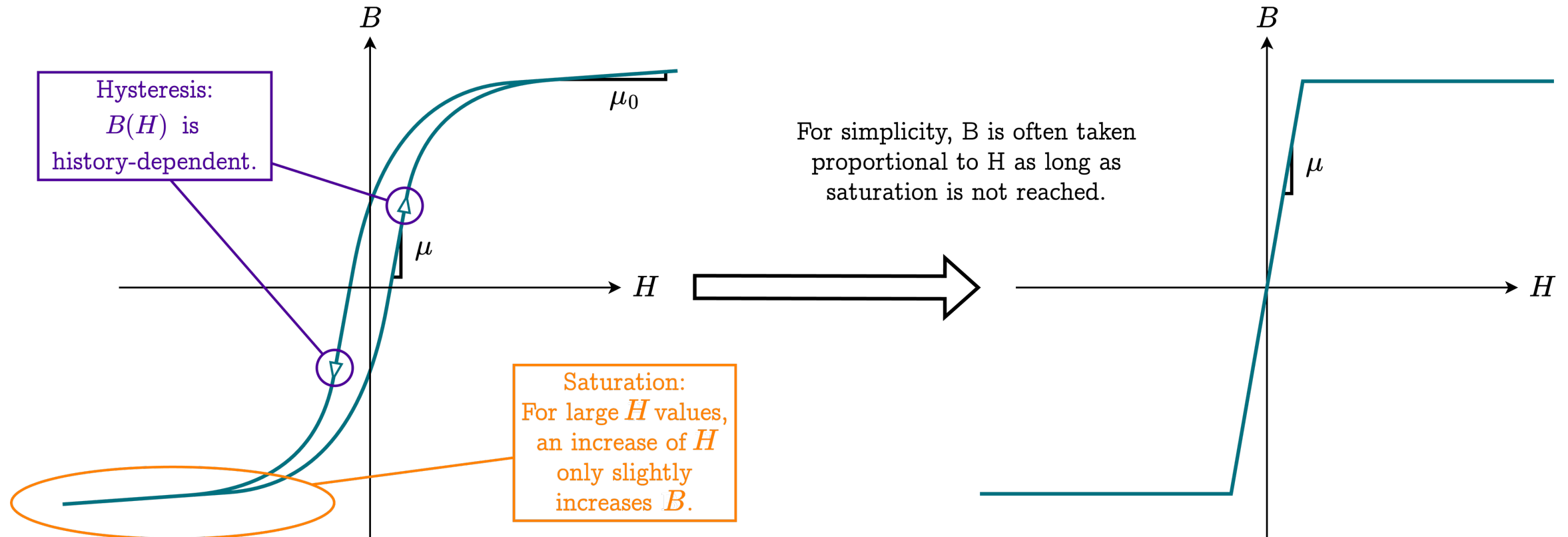Ferromagnetic materials have a large magnetic permeability μ . For this reason, they are often used to carry high magnetic fluxes. They however exhibit hysteresis and saturation:



Reluctance and magnetic circuit

From Ampere's law (slide 5):

$$Hl = NI = \mathcal{F}$$

From magnetic constitutive law (slide 6):

$$\phi = \mu HS$$

$$\mathcal{F} = NI = \frac{l}{\mu S} \phi = \mathcal{R} \phi$$

Magnetomotive force

Reluctance

Magnetic flux

The relation linking magnetomotive force, reluctance and magnetic flux is similar to the Ohm's law linking voltage, resistance and current:

Ohm's law: $V = RI$

Pouillet's law: $R = \frac{l}{\sigma S}$

σ is the conductivity $\left[\frac{S}{m}\right]$


Magnetic circuit equation: $\mathcal{F} = \mathcal{R} \phi$

Magnetic reluctance formula: $\mathcal{R} = \frac{l}{\mu S}$

μ is the permeability $\left[\frac{H}{m}\right]$

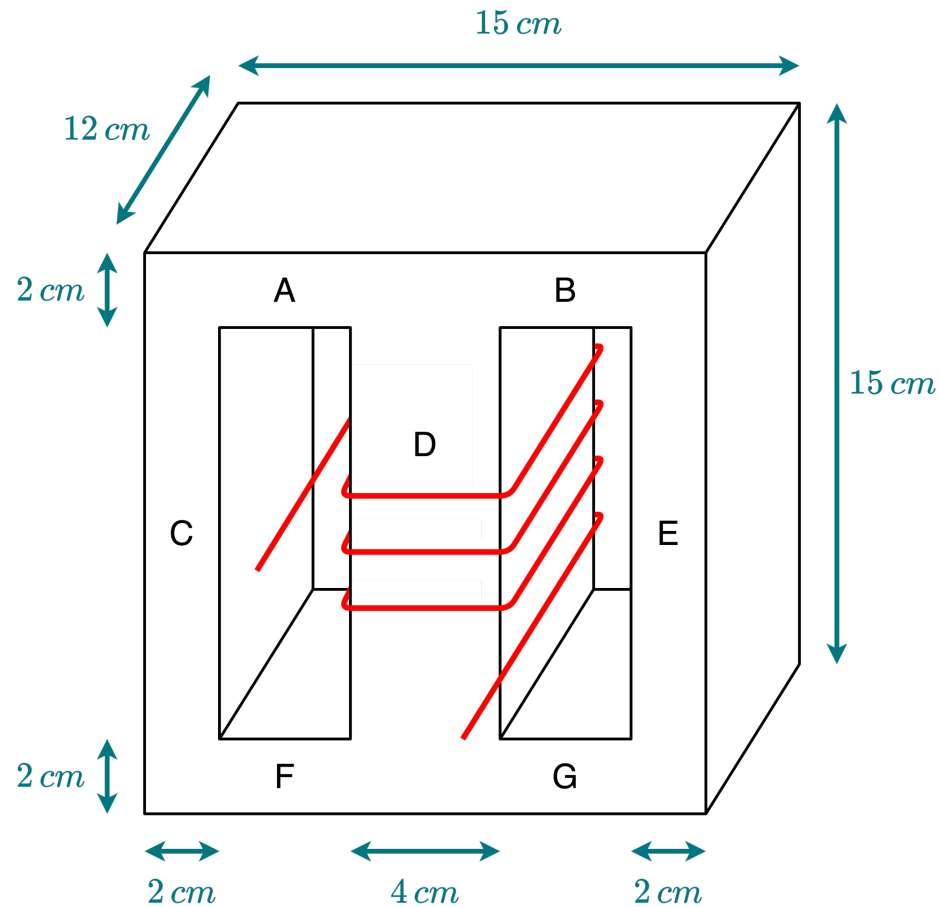Exercise 6

Consider an inductor made of an iron core as depicted hereunder and a 60-turn winding, wound around the central leg.



1. Draw an equivalent magnetic circuit of the inductor.
2. Compute the total reluctance of this circuit, considering a relative permeability μ_r of 1500 for the iron. Deduce the inductance from it.
3. Do the same computation as in the previous steps, but now considering a constant air gap of 0.1 mm in each leg.

Transformers

The ideal transformer

The real transformer


Shifting impedances

Open-circuit and short-circuit tests

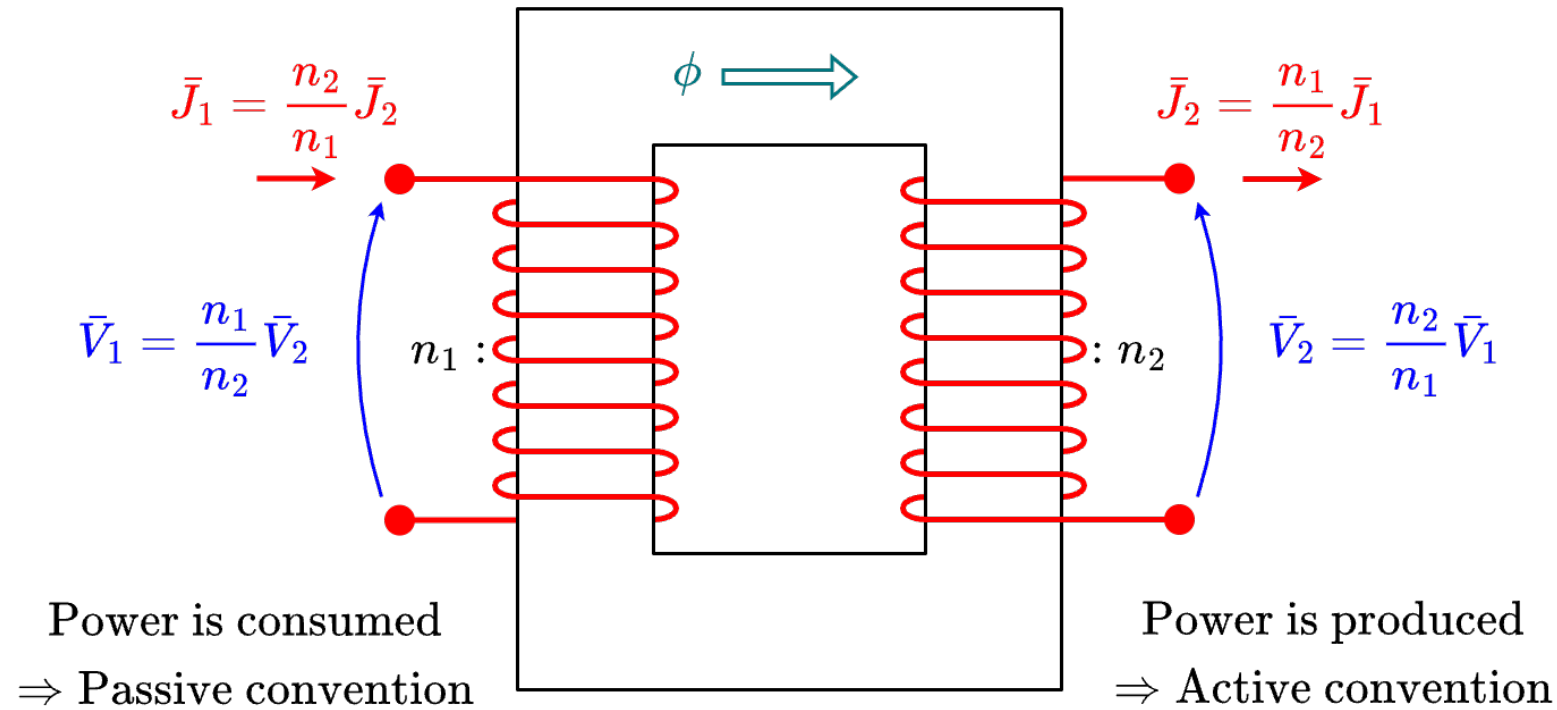Exercise 7

The ideal transformer


A transformer consists of two or more coils wrapped around a magnetic core, used to increase or decrease an AC voltage/current:



In an ideal transformer:


$$n_2 \bar{V}_1 = n_1 \bar{V}_2 \quad \text{and} \quad n_1 \bar{J}_1 = n_2 \bar{J}_2$$

The real transformer

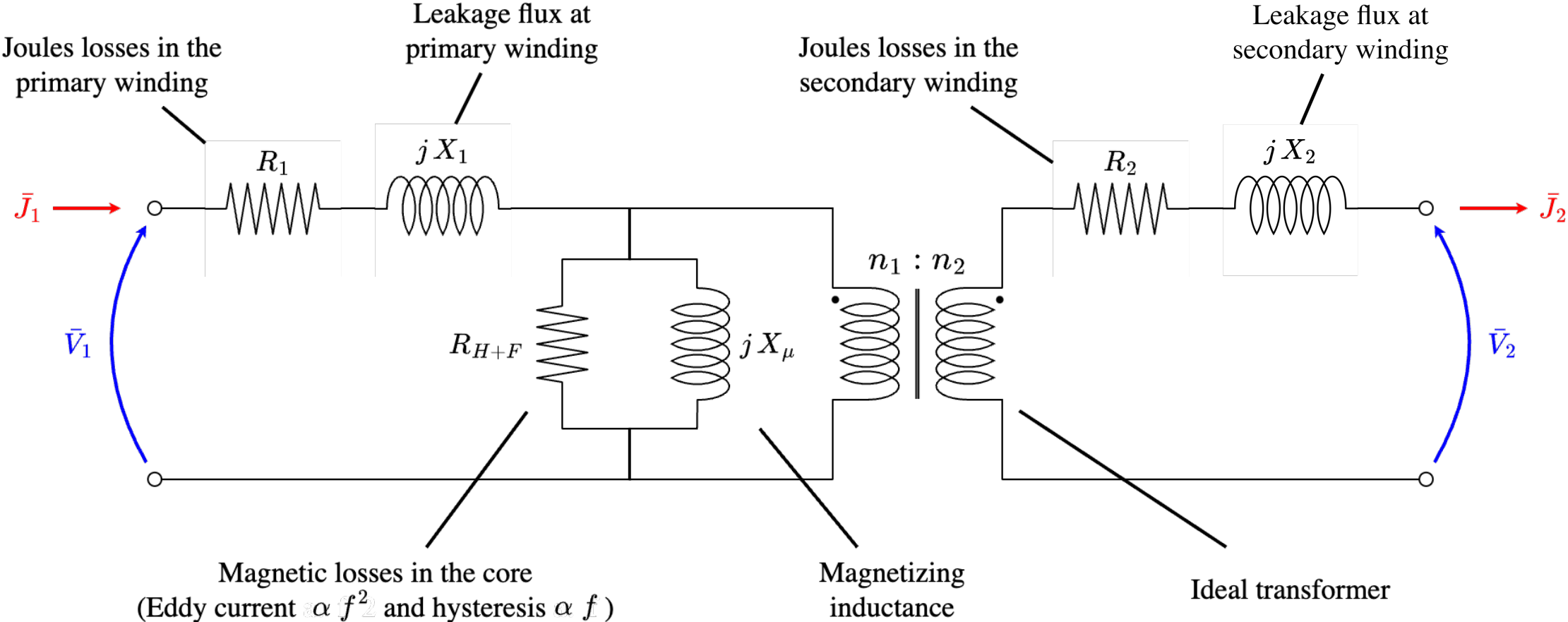

In practice, transformers are built to minimize the losses $\rightarrow R_1, R_2, X_1, X_2 \ll R_{H+F}, X_\mu$

Shifting impedances

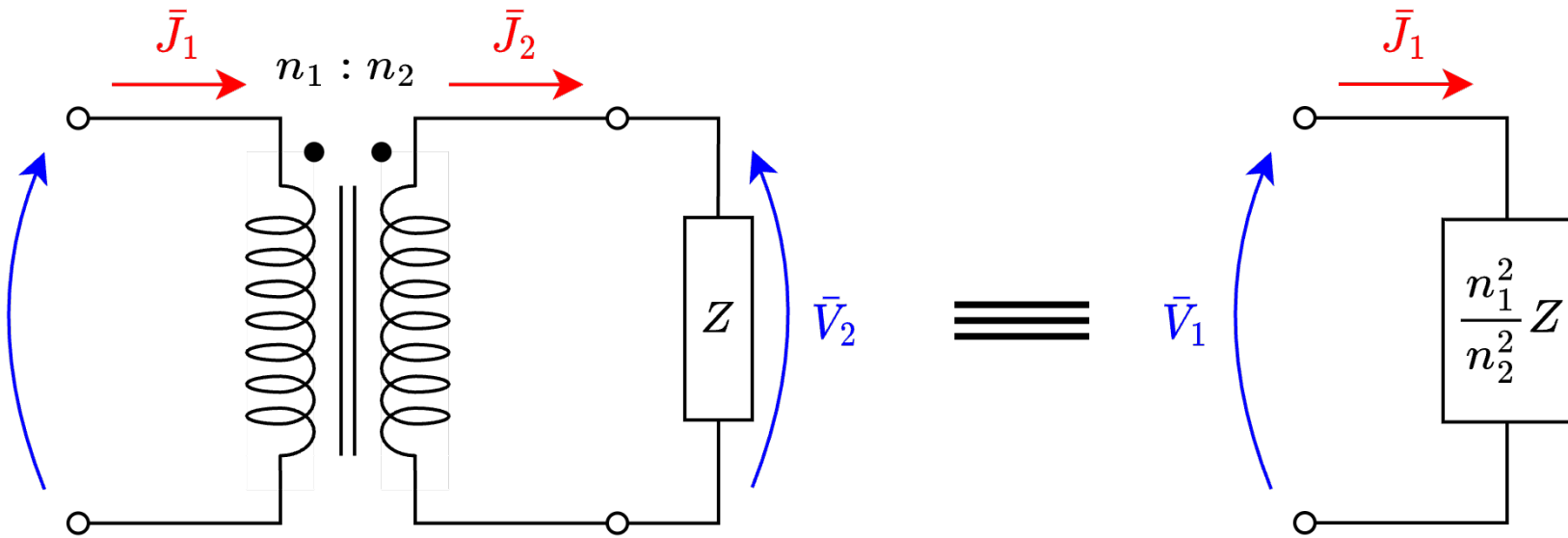

$$n_2 \bar{V}_1 = n_1 \bar{V}_2$$

$$n_1 \bar{J}_1 = n_2 \bar{J}_2$$


Seen from the secondary, the impedance is $Z = \frac{\bar{V}_2}{\bar{J}_2}$

Seen from the primary, the impedance is $Z' = \frac{\bar{V}_1}{\bar{J}_1} = \frac{\bar{V}_2 \left(\frac{n_1}{n_2}\right)}{\bar{J}_2 \left(\frac{n_2}{n_1}\right)} = \frac{n_1^2}{n_2^2} \frac{\bar{V}_2}{\bar{J}_2} = \frac{n_1^2}{n_2^2} Z$

The real transformer – impedances gathered at primary

One can shift the impedances from the secondary to primary side of the ideal transformer



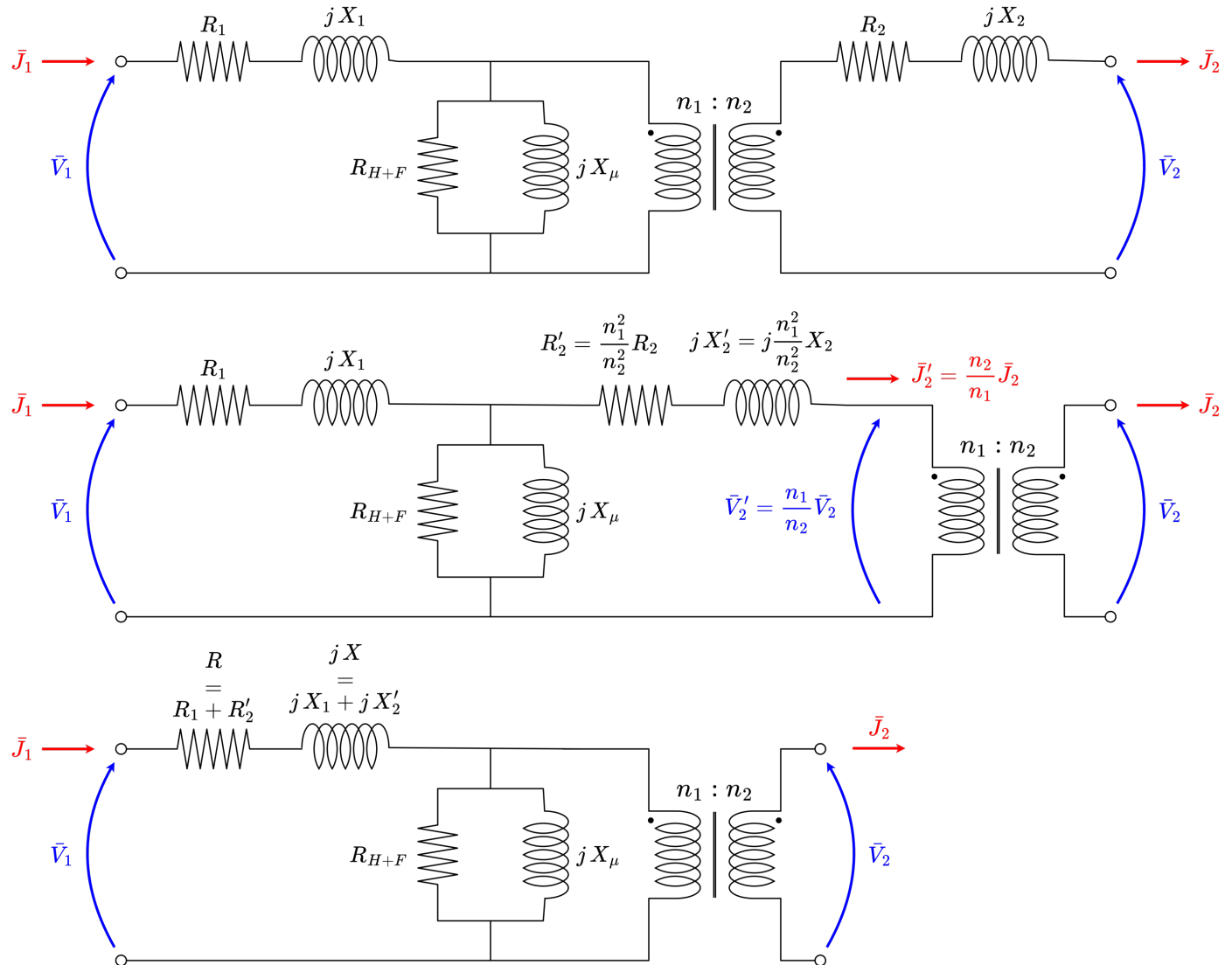
R'_2 and jX'_2 can pass on the other side of the magnetizing branch since $R'_2, X'_2 \ll R_{H+F}, X_\mu$




The real transformer – impedances gathered at secondary

One can shift the impedances from the primary to secondary side of the ideal transformer

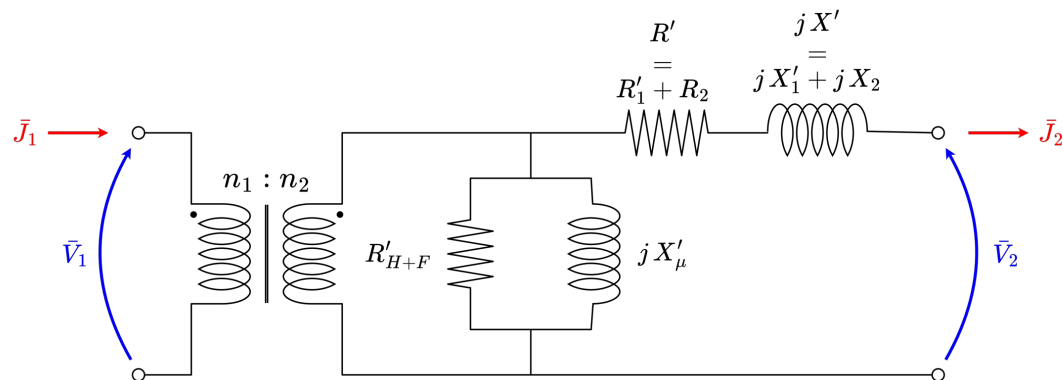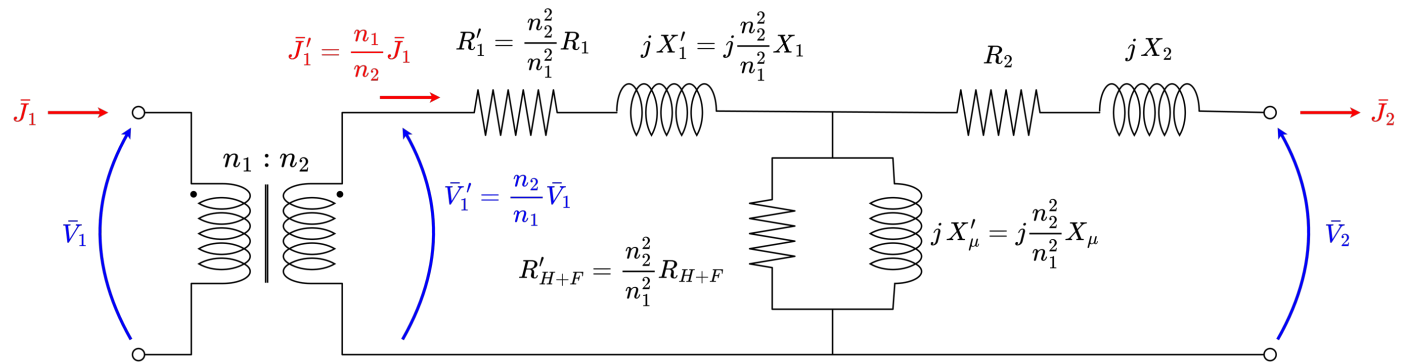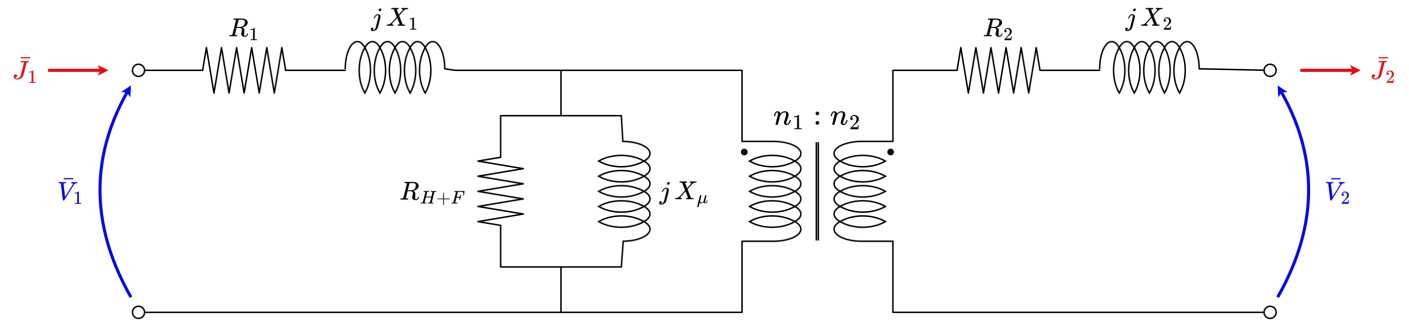R'_1 and jX'_1 can pass on the other side of the magnetizing branch since $R'_1, X'_1 \ll R_{H+F}, X_\mu$



Open circuit test

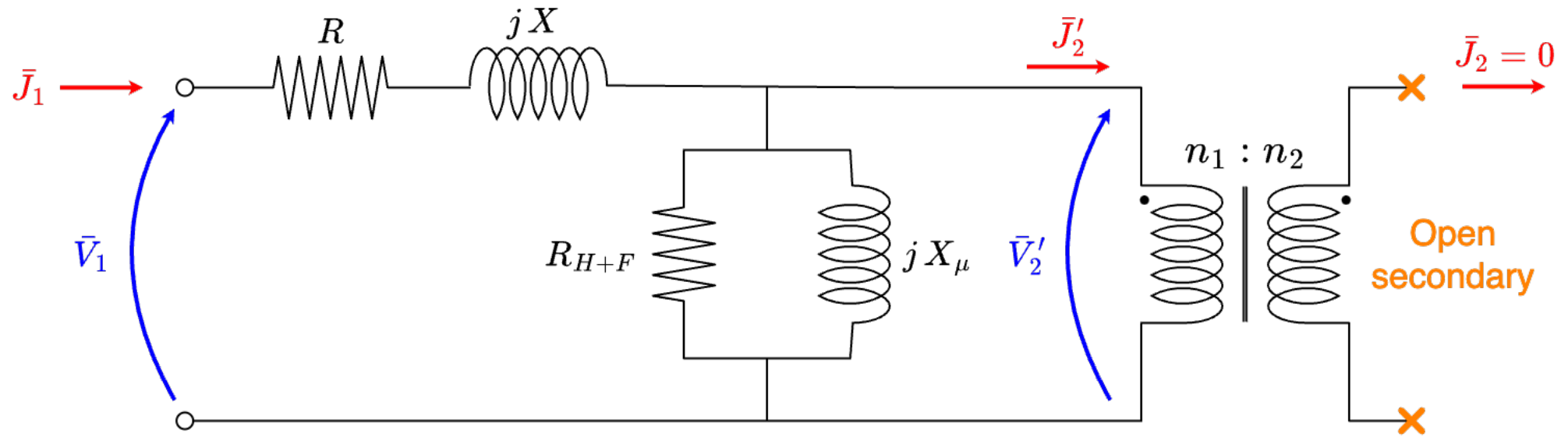


$$\bar{J}_2 = 0 \rightarrow \bar{J}'_2 = 0$$

$$R, X \ll R_{H+F}, X_\mu$$

$$\rightarrow \bar{V}'_2 \gg (R + jX) \bar{J}_1$$


→ R and X can be neglected

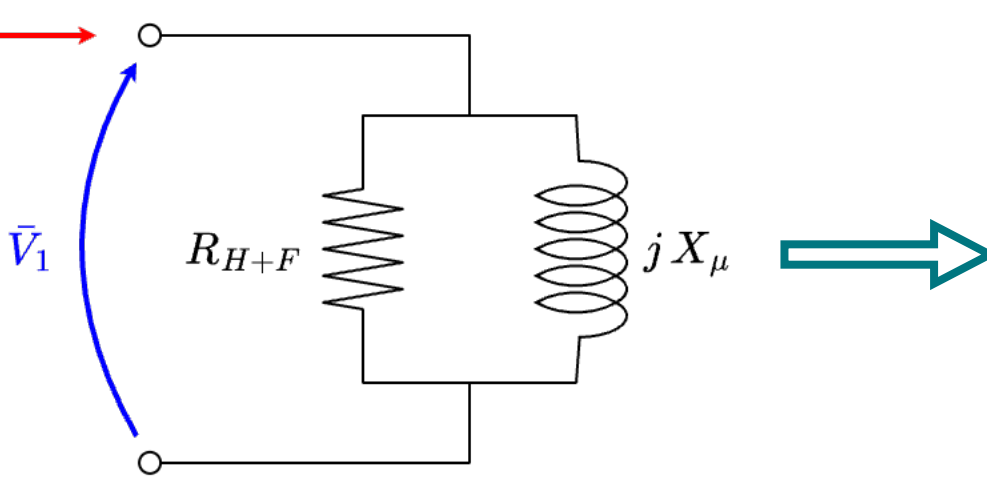

$$P \approx \frac{V_1^2}{R_{H+F}}$$



$$Q \approx \frac{V_1^2}{X_\mu}$$

Short-circuit test

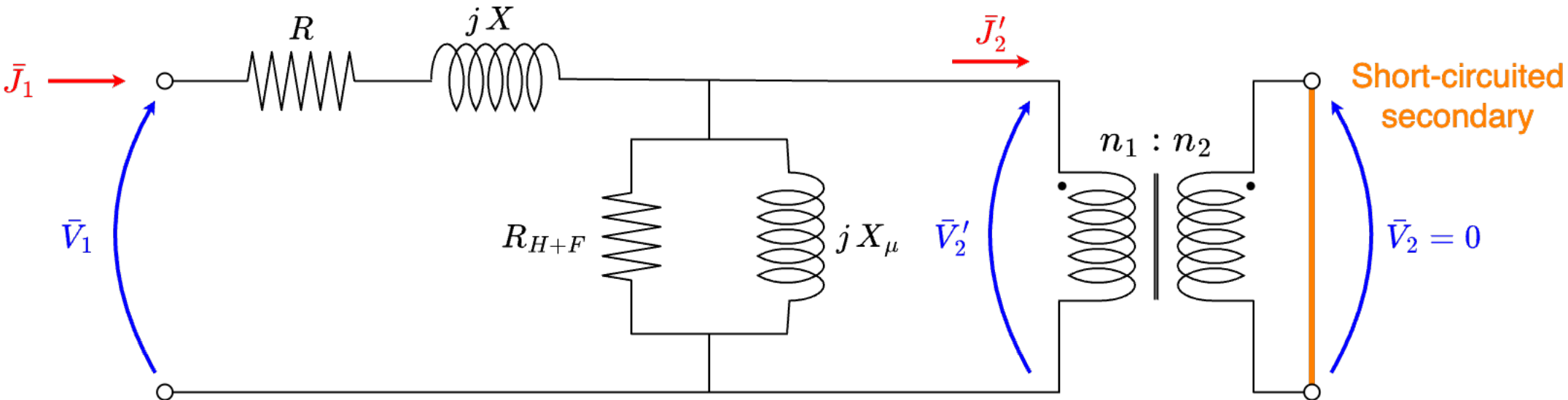

$\bar{V}_2 = 0 \rightarrow \bar{V}'_2 = 0$


→ Voltage drop only for R and X

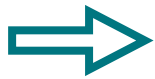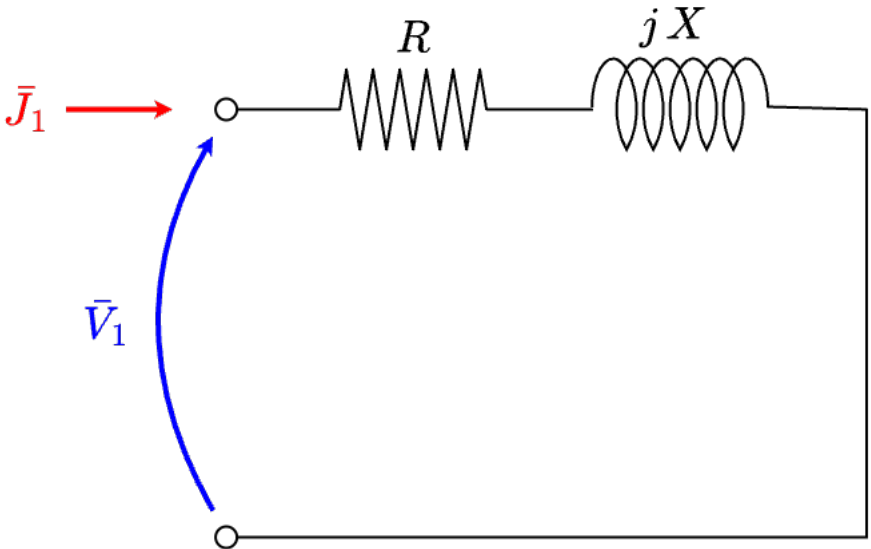

$P \approx R J_1^2$
 $Q \approx X J_1^2$

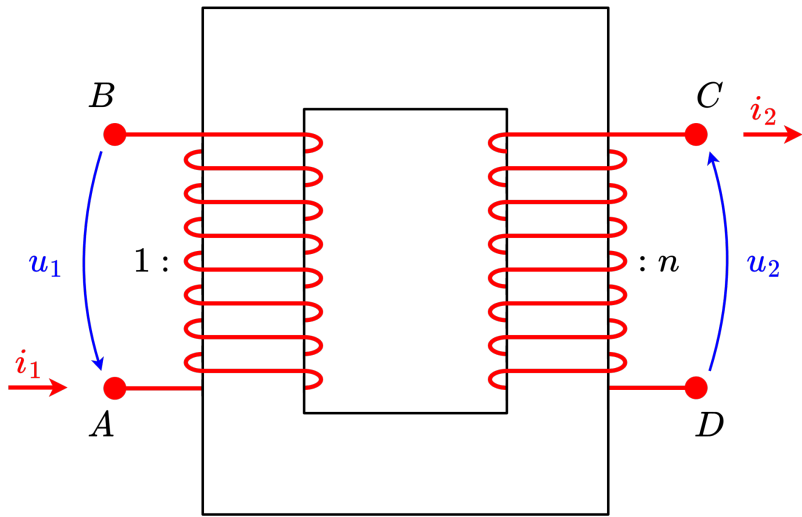Exercise 7

Two tests are performed on the transformer illustrated hereunder:



- Using open secondary winding, the transformer generates a voltage of RMS value $U_{2o} = 100\text{ V}$ at the secondary winding, for an applied voltage of RMS value $U_{1o} = 20\text{ V}$ with a drawn current intensity of RMS value $I_{1o} = 3.2\text{ A}$ and a consumed power $P_{1o} = 8\text{ W}$.
- Using short-circuited secondary winding, a voltage of RMS value $U_{1s} = 0.8\text{ V}$ for a total power of $P_{1s} = 24\text{ W}$ is measured, causing a current flow of RMS value $I_{2s} = 10\text{ A}$ through the secondary winding.

Considering a simplified equivalent model of the transformer (resistances and inductances gathered and moved to the secondary winding) and a frequency of 50 Hz:

1. Calculate the transformer ratio n .
2. Calculate the resistance R'_{H+F} and the magnetizing inductance L'_μ .
3. Compute the resistance R' and the inductance L' .

Exercise 7

Using the transformer connected to a load on the secondary side drawing a current of RMS value $I_2 = 12\text{ A}$ with a power factor $\cos(\varphi) = 0.8$ (the current is lagging the voltage), an RMS voltage $U_1 = 20\text{ V}$ is applied to the primary winding.

4. Calculate the RMS voltage U_2 appearing across the secondary winding.
(What wise approximation can be made here?)
5. Deduce the active power P_2 provided to the load.
6. Calculate the RMS current I_1 on the primary side.
7. Compute the transformer efficiency η .