

ELEC0431 : Exercise session 4

Three-Phase transformers


26 February 2021



Nicolas Davister

Montefiore Institute, Department of Electrical Engineering and Computer Science, University of Liège, Belgium

Exercises

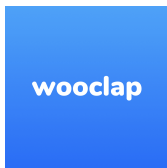

Exercises of session 4

Wooclap code : NSATKE

Exercise 9 : three-phase transformer

The three-phase transformer, described by the normalized scheme, is connected to a balanced three-phase network of composed voltages u_{AB} , u_{BC} , u_{CA} of RMS voltage U_1 on the primary side, whereas on the secondary side, a three-phase balanced system of composed voltages u_{ab} , u_{bc} , u_{ca} of RMS voltage U_2 is obtained.

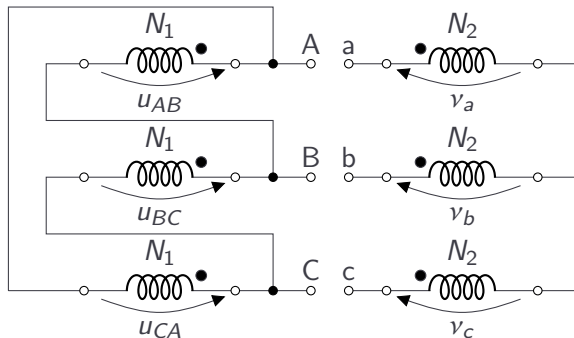


Figure: Three-phase transformer.

Exercise 9 : three-phase transformer

The line current intensities in the primary and secondary windings are respectively denoted I_1 and I_2 . The transformer has the following characteristics:

- Apparent nominal power $S_n = 250$ kVA;
- Composed primary winding RMS voltages $U_{1n} = 5.2$ kV;
- Nominal frequency $f_n = 50$ Hz;

and ferromagnetic losses are neglected. To characterize the transformer two tests have been performed:

- Using open secondary windings, the transformer generates a composed voltage of RMS value $U_{2o} = 400$ V at each secondary winding, for an applied composed nominal voltage of RMS value U_{1n} ;
- Using short-circuited secondary windings, a composed voltage of RMS value $U_{1s} = 600$ V is applied at each primary winding for a total primary power $P = 7.35$ kW, producing line current of RMS intensity $I_{2s} = 350$ A.

Exercise 9 : three-phase transformer

1. Calculate the transformer ratio n so that it is greater than 1;

Exercise 9 : three-phase transformer - solution

The transformer ratio is


$$n = \frac{U_{AB}}{U_{ab}} = \frac{U_{1n}}{U_{2o}} = \frac{5\,200}{400} = 13$$

Exercise 9 : three-phase transformer

2. For the first test condition (open secondary windings), draw a Fresnel diagram including the primary composed voltages u_{AB} , u_{BC} , u_{CA} , the direct secondary voltage v_a , v_b , v_c and the secondary composed voltages u_{ab} , u_{bc} , u_{ca} ;

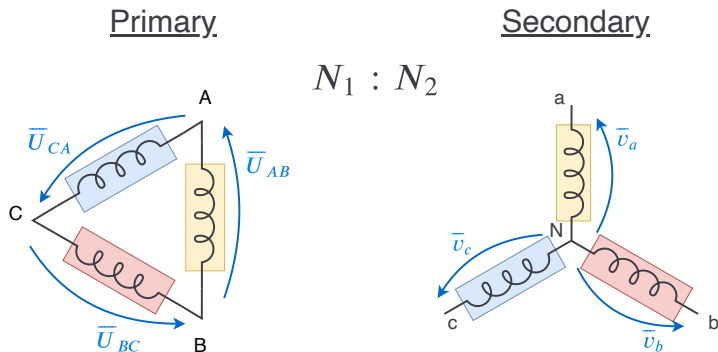Exercise 9 : three-phase transformer - solution

The primary windings are connected in Δ (delta) configuration while secondary windings are connected in star.



N_1 and N_2 are respectively the number of turns in the primary and the secondary.


Exercise 9 : three-phase transformer - solution

$$\bar{v}_a = \frac{N_2}{N_1} \cdot \bar{U}_{AB}$$


$$\bar{v}_b = \frac{N_2}{N_1} \cdot \bar{U}_{BC}$$

$$\bar{v}_c = \frac{N_2}{N_1} \cdot \bar{U}_{CA}$$

Primary.

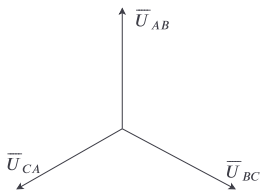

Secondary.

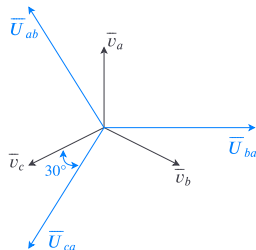

Exercise 9 : three-phase transformer

- Express and compute the column ratio $n_c = \frac{N_1}{N_2}$ according to n ;

Exercise 9 : three-phase transformer - solution

The column ratio can be obtained from

$$n_c = \frac{N_1}{N_2} = \frac{U_{AB}}{v_a} \quad (1)$$

As

$$n = \frac{U_{AB}}{\sqrt{3} v_a}$$

$$n_c = \sqrt{3} n = 22.517$$

Exercise 9 : three-phase transformer

- Given that the transformer is composed of 3 cores of section $A_c = 5 \text{ dm}^2$, and that the magnetic field amplitude is $B_m = 1.2 \text{ T}$, compute the number of turns N_1 of each primary winding and deduce the value of the number of turns of each winding N_2 ;

Exercise 9 : three-phase transformer - solution

The maximum magnetic flux in the transformer as

$$\phi_m = B_m A_c \quad (2)$$

and according to Lenz law,

$$U_1(t) = -N_1 \frac{d}{dt}(\phi_1(t))$$

$$U_{AB} \sqrt{2} \cos(\omega t) = -N_1 \frac{d}{dt}(\phi_m \cos(\omega t + \frac{\pi}{2}))$$

$$U_{AB} \sqrt{2} \cos(2\pi f t) = N_1 2\pi f \phi_m \cos(2\pi f t)$$

where U_{AB} is the RMS value of the voltage and B_m is the peak value of the magnetic induction.

Exercise 9 : three-phase transformer - solution

$$N_1 = \frac{\sqrt{2} U_{AB}}{2\pi f B_m A_c} = \frac{\sqrt{2} \cdot 5200}{2\pi \cdot 50 \cdot 1.2 \cdot 0.05} = 390 \quad (3)$$

Then, as the column ratio n_c is equal to $\frac{N_1}{N_2}$,

$$N_2 = \frac{N_1}{n_c} = \frac{390}{22.517} = 17 \quad (4)$$

Remark that

$$B_m = \frac{\sqrt{2} U}{2\pi f N A_c} \quad (5)$$


the magnetic induction is directly proportional to the voltage and is inversely proportional to the frequency, number of turns and the cross-section area.

Exercise 9 : three-phase transformer

- Using a simple single-phase equivalent model (leak resistance and inductance moved to the secondary windings), provide the Thévenin's model seen from a secondary winding and calculate the resistance R_{eq} (R') and the reactance X_{eq} (X') of this model;


Exercise 9 : three-phase transformer - solution

Considering the Thévenin equivalent in which, V_{th} is equal to the voltage at no load of the circuit while Z_{th} is the circuit impedance when all voltage sources are shorted.

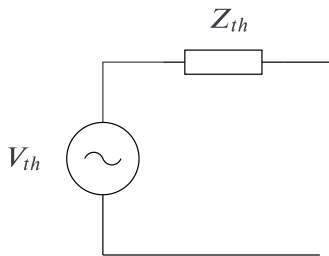

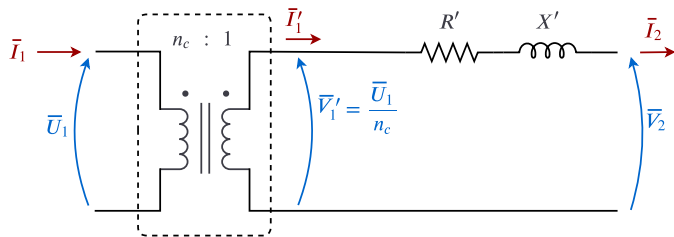Exercise 9 : three-phase transformer - solution

And considering the transformer equivalent circuit.



By definition of the Thevenin equivalent circuit,

$$V_{th} = V_2 = \frac{U_2}{\sqrt{3}} = 230.94 \text{ V} \quad (6)$$

Exercise 9 : three-phase transformer - solution

$$Z_{th} = R' + jX'$$

where R' and X' are obtained from the short circuit measurements :

$$R' = \frac{P_{2s}}{I_{2s}^2} = \frac{\frac{7350}{3}}{350^2} = 20 \text{ m}\Omega \quad (7)$$

$$U_{2s} = \frac{U_{1s}}{n} = \frac{600}{13} = 46.15 \text{ V}$$

$$S_{2s} = V_{2s} I_{2s} = \frac{U_{2s}}{\sqrt{3}} I_{2s} = 9\,326.26 \text{ VA}$$

$$\rightarrow Q_{2s} = \sqrt{S_{2s}^2 - P_{2s}^2} = 8\,998.7 \text{ var}$$

which finally leads to

$$X' = \frac{Q_{2s}}{I_{2s}^2} = 73.4 \text{ m}\Omega \quad (8)$$

Exercise 9 : three-phase transformer

The nominal regime is now considered by applying the composed nominal voltage U_{1n} at the primary windings and connecting a three-phase balanced load on the secondary side (detailed in 2). Each branch is composed of a resistor of value $R^* = 554 \text{ m}\Omega$ in series with a coil of value $L^* = 3.05 \text{ mH}$.


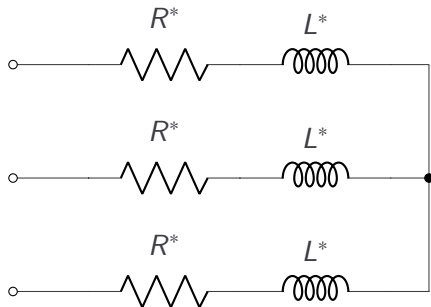


Figure: First load connected to the secondary side of the three-phase transformer.

6. Calculate the power factor $\cos \varphi_2$ of this load;

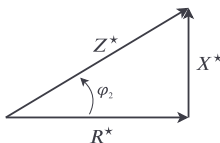Exercise 9 : three-phase transformer - solution

$$X^* = 2\pi f L^* = 958.2 \text{ m}\Omega \quad (9)$$



$$\varphi_2 = \arctan\left(\frac{X^*}{R^*}\right) = 59.96^\circ$$

$$\boxed{\cos(\varphi_2) = 0.5005}$$

$$(10)$$

An other solution is :


$$\cos(\varphi_2) = \frac{R^*}{\sqrt{(R^*)^2 + (X^*)^2}}$$

Exercise 9 : three-phase transformer

7. Draw the Fresnel diagram corresponding to the balanced single-phase equivalent model. Deduce the RMS values of the current intensities I_2 and the composed voltages U_2 ;

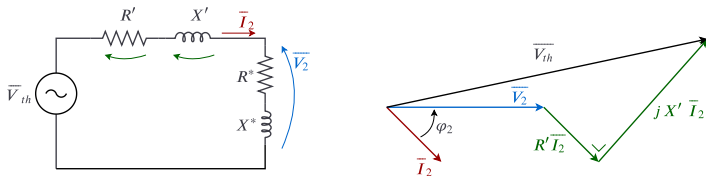Exercise 9 : three-phase transformer - solution

In nominal regime, when the three-phase load is connected to the secondary of the transformer, the Fresnel diagram is as following :



From this diagram, the current \bar{I}_2 and voltage \bar{V}_2 can be calculated as

$$\bar{I}_2 = \frac{V_{th}}{Z_{th} + R^* + jX^*}$$

$$I_2 = \frac{V_{th}}{\sqrt{(R' + R^*)^2 + (X' + X^*)^2}} = 195.7 \text{ A} \quad (11)$$

and the voltage is

$$\overline{V}_2 = (R^* + jX^*) \overline{I}_2$$

$$\boxed{V_2 = \sqrt{(R^*)^2 + (X^*)^2} I_2 = 216.58 \text{ V}} \quad (12)$$

Exercise 9 : three-phase transformer

8. Compute the power P_2 flowing from the transformer to the load;

Exercise 9 : three-phase transformer - solution

The active power consumed by the load is

$$P_2 = V_2 I_2 \cos \varphi_2 = 216.58 \cdot 195.7 \cdot 0.5 = 21.219 \text{ kW} \quad (13)$$

Exercise 9 : three-phase transformer

9. Calculate the transformer efficiency η ;

Exercise 9 : three-phase transformer - solution

In order to compute the transformer efficiency, one can first compute the losses in the transformer, noted P_{loss}

$$P_{\text{loss}} = R' I_2^2 = 0.02 \cdot 195.7^2 = 765.97 \text{ W} \quad (14)$$

Then, the efficiency can be computed as

$$\eta = \frac{P_2}{P_2 + P_{\text{loss}}} = \frac{21\,219}{21\,984} = 0.9651 \% \quad (15)$$

Exercise 9 : three-phase transformer

10. Another load is used, compute the value of the resistance R° and the inductance L° such that this load is equivalent to the one detailed in next figure.

Exercise 9 : three-phase transformer

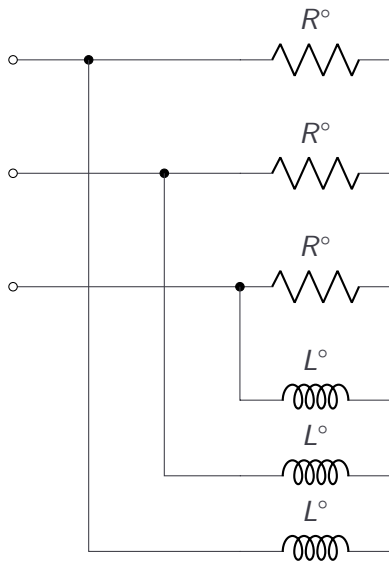


Figure: Second load connected to the secondary side of the three-phase

Exercise 9 : three-phase transformer - solution

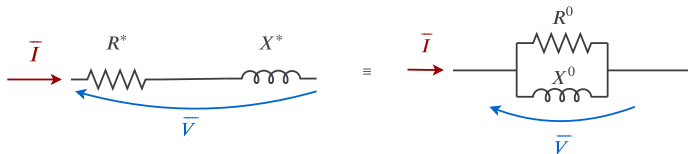


Figure: Equivalence between the two loads.

With the following equations,

$$V = \sqrt{R^{*2} + X^{*2}} I \quad (16)$$

$$P = R^* I^2 = \frac{V^2}{R^0} \quad (17)$$

$$Q = X^* I^2 = \frac{V^2}{X^0} \quad (18)$$

Exercise 9 : three-phase transformer - solution

one can obtain

$$R^0 = \frac{V^2}{I^2} \cdot \frac{1}{R^*} = \frac{R^{*2} + X^{*2}}{R^*} \quad (19)$$

$$X^0 = \frac{V^2}{I^2} \cdot \frac{1}{X^*} = \frac{R^{*2} + X^{*2}}{X^*} \quad (20)$$

$$(21)$$