



Electromagnetic Energy Conversion

ELEC0431

Exercise session 7: Asynchronous machines

25 March 2022

Florent Purnode (florent.purnode@uliege.be) – Nicolas Davister (ndavister@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,
University of Liège, Belgium

Reminders

The asynchronous machine

The asynchronous machine – working principle



1. The stator generates a rotating magnetic field.
2. Closed loop wire in the varying magnetic flux
→ Faraday's law: e.m.f.
1. The e.m.f. leads to a current.
2. Current in a magnetic flux
→ Laplace: $\vec{F} = q\vec{v} \wedge \vec{B}$.
1. \vec{F} makes the rotor rotate.

✓ Self starting

✓ brushless & no permanent magnet → easy to build

The asynchronous machine – rotation speed



→ The rotor doesn't move → high varying fluxes
→ high current → big acceleration

No rotation → The rotor accelerate

→ The rotor rotates at the same speed as the magnetic field → no varying fluxes → no force on the rotor → deceleration due to mechanical losses

Rotor too fast → The rotor decelerate



The rotor will rotate at a speed lower than the one of the magnetic field
(Asynchronous)

The asynchronous machine – slip

→ Speed of the magnetic flux = $\dot{\theta}_s$ = synchronous speed

→ Speed of the rotor = $\dot{\theta}$

The slip g (“glissement” in French) links the two speeds:


$$g = \frac{\dot{\theta}_s - \dot{\theta}}{\dot{\theta}_s}$$

Note:

- If the stator doesn't move → $\dot{\theta} = 0$ → $g = 1$
- if the stator moves at the synchronous speed → $\dot{\theta} = \dot{\theta}_s$ → $g = 0$


The asynchronous machine – slip and torque

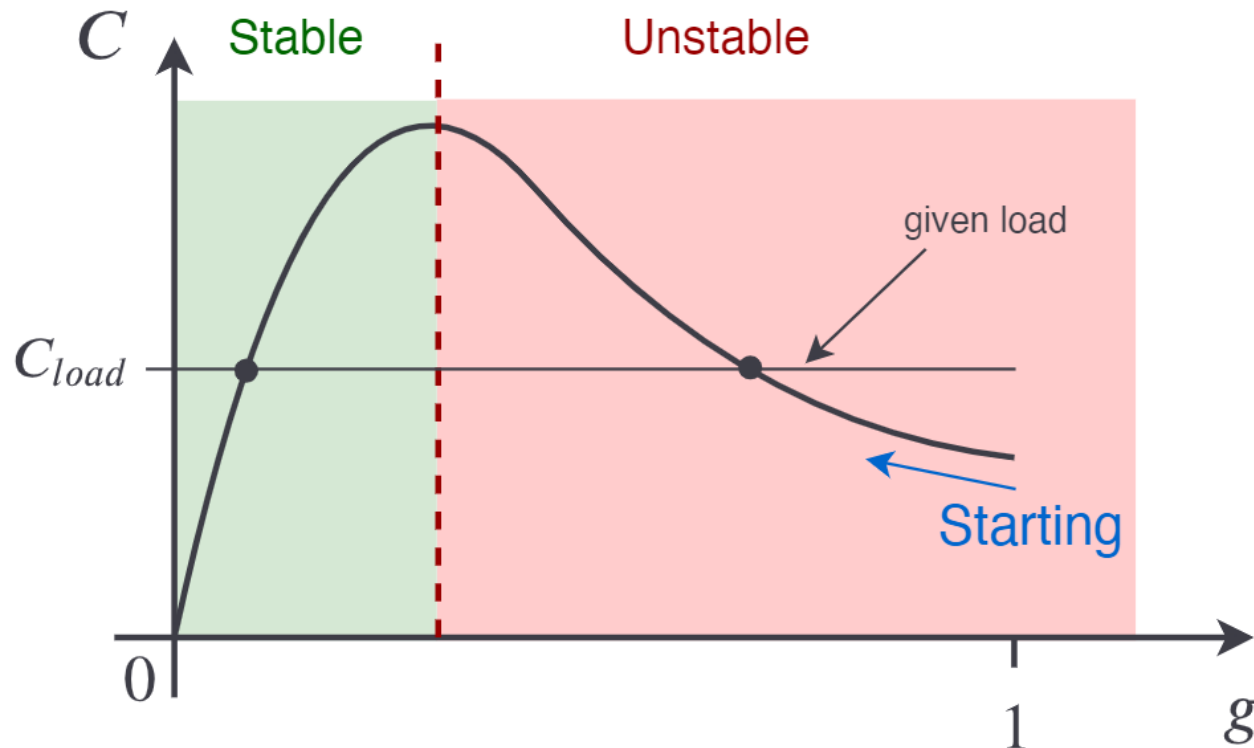The relationship between the torque C and the slip g leads to the stable and unstable behaviours of the asynchronous machine.




The asynchronous machine – equivalent model

Joule losses in the stator winding

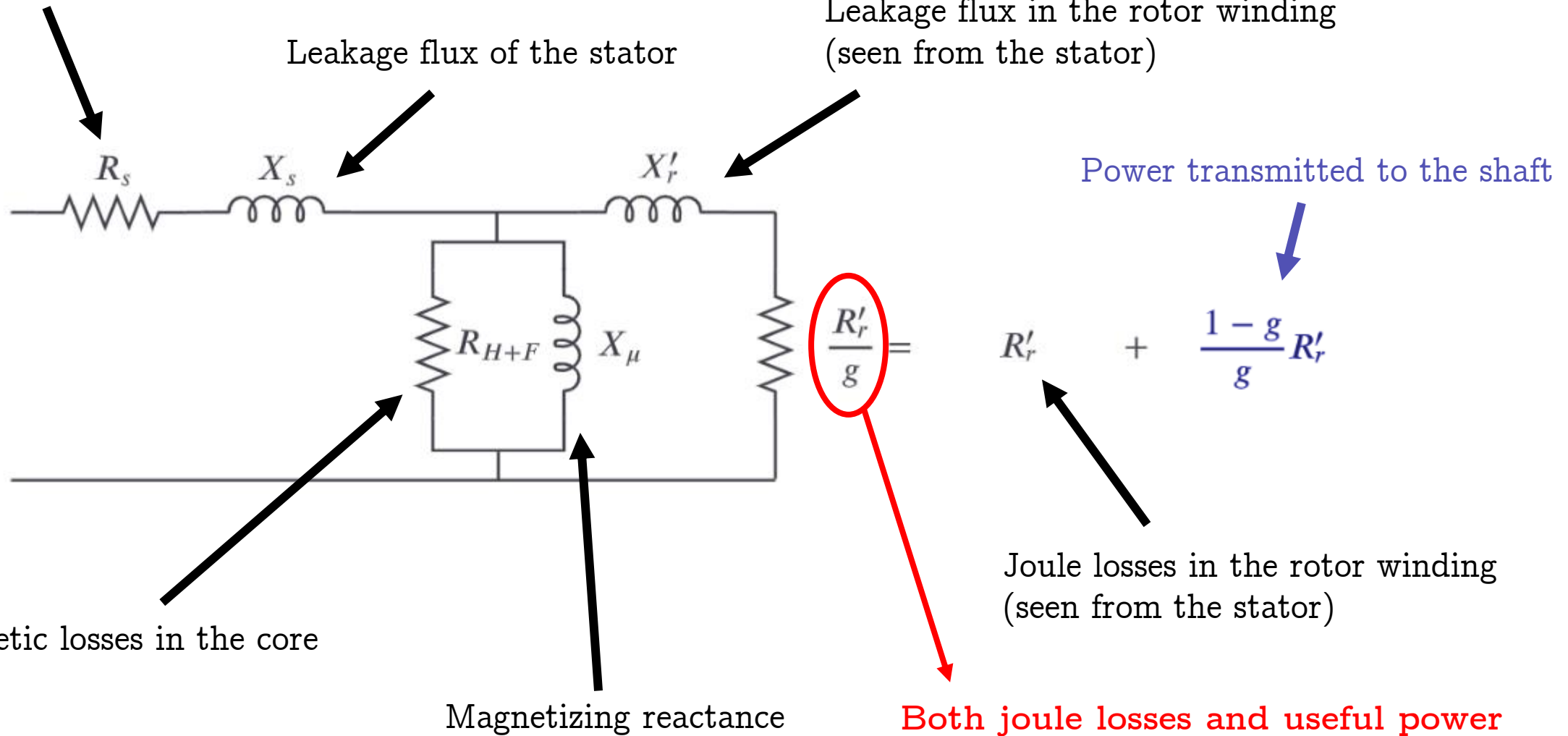


The asynchronous machine – equivalent model

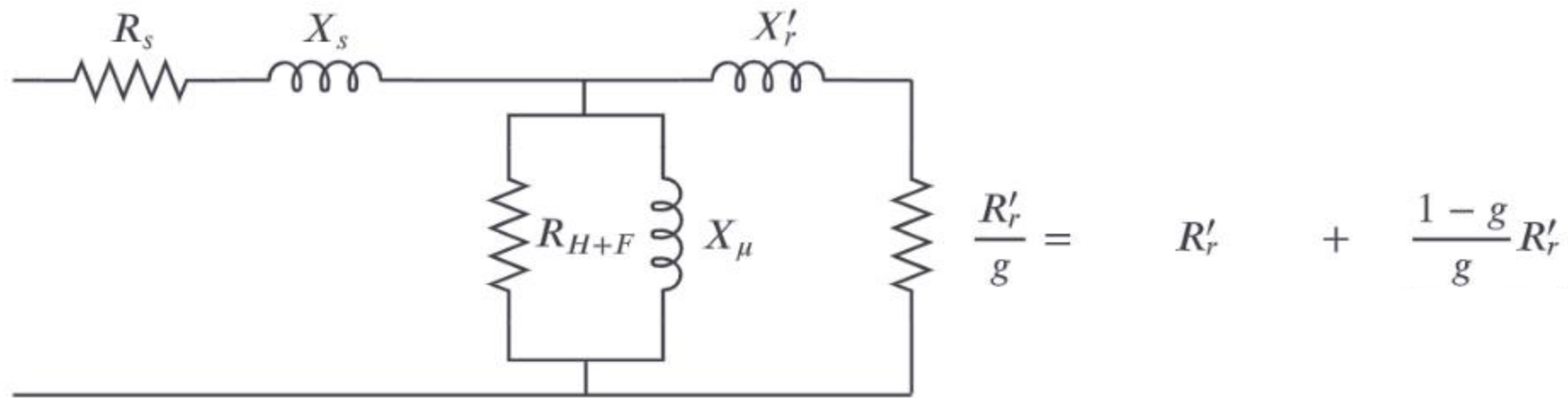The equivalent circuit of the asynchronous machine is close to the circuit of the transformer.



Indeed, the induction machine behaves as a transformer with its secondary short-circuited. The important difference is that the rotor, as it is a moving part of the machine, sees a frequency $g \cdot f$ different than the stator nominal frequency f .

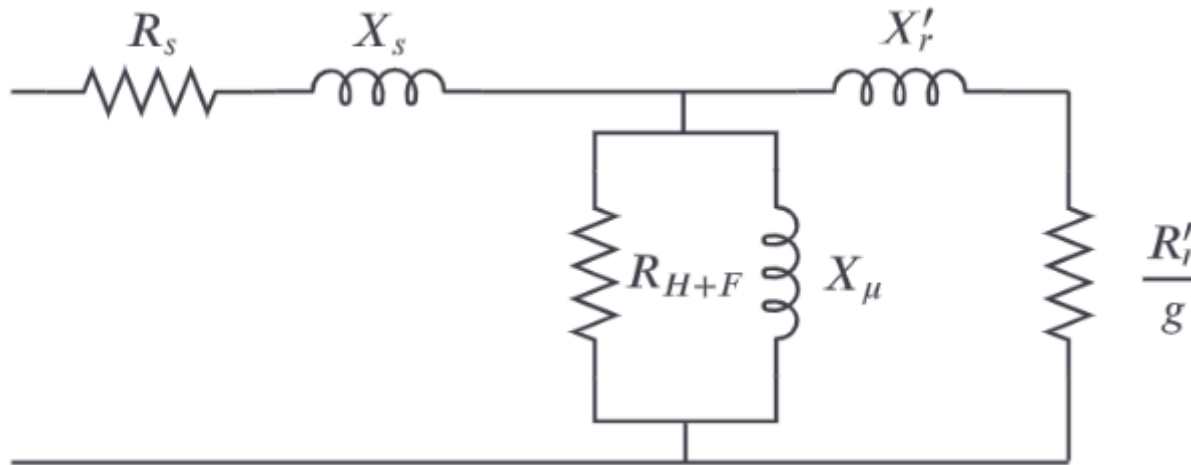The asynchronous machine – equivalent model



The asynchronous machine is built to minimize the losses

$$\rightarrow R_s, R'_r \ll R_{H+F}$$

$$\rightarrow X_s, X'_r \ll X_\mu$$


(same as for the transformer)

The parameters R, X, R_{H+F} and X_μ can be determined in the same way as for the transformer: short circuit and open circuit tests.

→ Short circuit obtained by taking $g = 1$ → the rotor is set to the synchronous speed.

→ Open circuit obtained by taking $g = 0$ → the rotor is forced not to move.

The asynchronous machine – Power balance

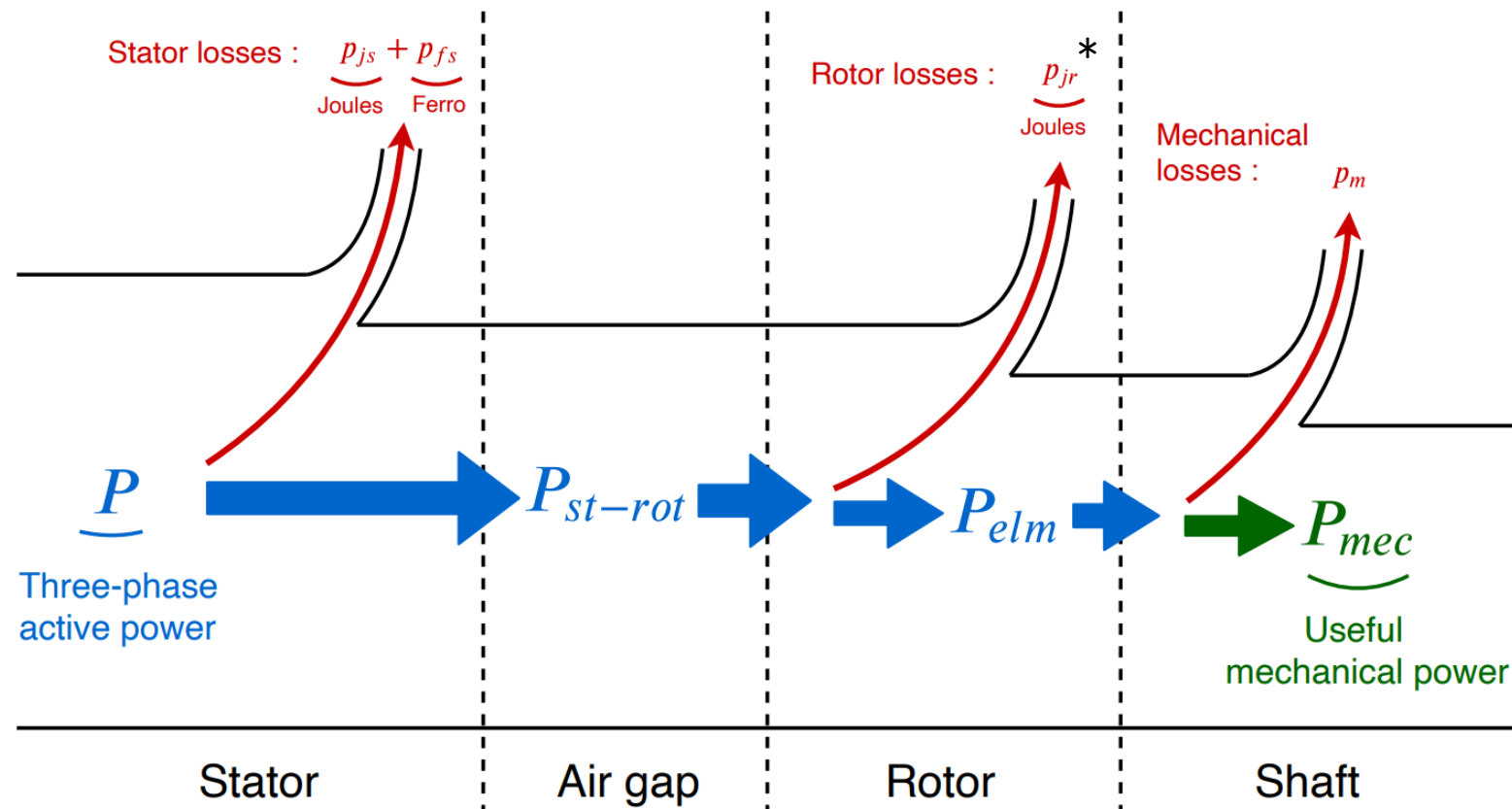

* Ferromagnetic losses in the rotor can be neglected since the rotor current frequency is much smaller than the grid frequency

Exercises

Exercise 19: Asynchronous motor for washer cleaner

Exercise 19: Asynchronous motor for washer cleaner

A star-shaped asynchronous motor of a high-pressure washer cleaner has the following nominal characteristics:

- Power $P_n = 5.5$ kW,
- RMS composed voltage value $U_{sn} = 400$ V,
- Frequency $f_n = 50$ Hz,
- RMS line current intensities $I_{sn} = 11$ A,
- Speed of rotation $\dot{\theta}_n = 1460$ RPM.

Assume that the stator reactance X_s is equal to the stator resistance R_s . Using a single-phase equivalent model of the asynchronous motor when needed,

1. Calculate the synchronous speed of rotation $\dot{\theta}_s$, the number of pair of poles of the motor and the nominal slip g_n ;
2. Determine the value of the stator resistance R_s given that a current of RMS value $I_0 = 10$ A flows when a voltage of RMS value $U_0 = 20.6$ V is applied;

Exercise 19: Asynchronous motor for washer cleaner

3. At the nominal operating point, without mechanical load, the motor draws a current of RMS value $I_{s0} = 3.07 \text{ A}$ for an active power $P_{s0} = 245 \text{ W}$. Calculate the overall losses and calculate the resistance modelling ferromagnetic losses R_{HF} and the magnetizing inductance L_{μ} , assuming that mechanical losses equal ferromagnetic losses;

Consider that the machine operates at nominal speed and produces the nominal mechanical power P_n to the mechanical load. The nominal mechanical power can also be denoted P_{mec} .

4. At the nominal operating point, calculate the transmitted power from the stator to the rotor and the Joules losses in the stator p_{js} and deduce the total consumed power P ;
5. Calculate the rotoric resistance R'_r and the leak inductance L'_r seen from the stator;
6. At the nominal operating point, calculate the mechanical torque Γ_{un} and the electromagnetic torque Γ_n , the power factor $\cos \phi_n$ and the efficiency η_n ;
7. Compute the RMS value I_s of the line currents, and the power factor $\cos \varphi$ at a rotation speed of 0 RPM.