



# Electromagnetic Energy Conversion

## ELEC0431

### Exercise session 8: Asynchronous machines

1 April 2022

Florent Purnode ([florent.purnode@uliege.be](mailto:florent.purnode@uliege.be)) – Nicolas Davister ([ndavister@uliege.be](mailto:ndavister@uliege.be))

Montefiore Institute, Department of Electrical Engineering and Computer Science,  
University of Liège, Belgium

# Reminders

---

The asynchronous machine

# The asynchronous machine – working principle



start-up:

3-phase currents in stator windings  $\rightarrow$  rotating magnetic field  $\rightarrow$  variational magnetic field through rotor closed loop windings  $\rightarrow$  e.m.f.  $\rightarrow$  currents in closed loop rotor windings (eddy currents)  $\rightarrow$  torque due to Laplace:  $\vec{F} = q\vec{v} \wedge \vec{B}$   $\rightarrow$  the rotor starts moving.


Rotation speed:

- $\dot{\theta}$   $\rightarrow$  Speed of rotation of the rotor
- $\dot{\theta}_s$   $\rightarrow$  Speed of rotation of the magnetic field
- $g = \frac{\dot{\theta}_s - \dot{\theta}}{\dot{\theta}_s}$  = the slip (glissement in French)

$\rightarrow \dot{\theta} \leq \dot{\theta}_s \rightarrow g \in [0; 1]$

# The asynchronous machine – equivalent model

Joule losses in the stator winding

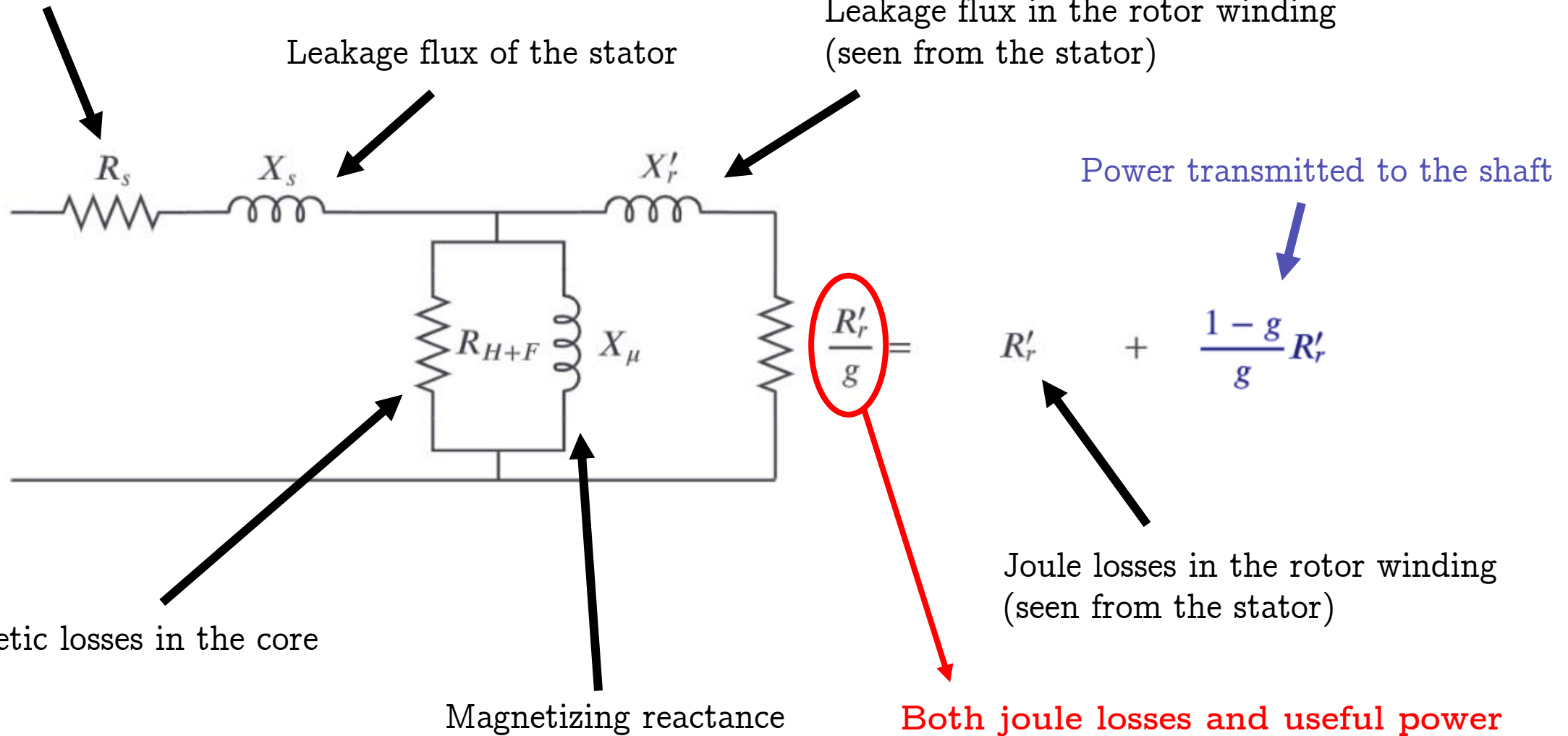

Leakage flux of the stator

Leakage flux in the rotor winding  
(seen from the stator)

Power transmitted to the shaft


Magnetic losses in the core

Magnetizing reactance

Joule losses in the rotor winding  
(seen from the stator)

Both joule losses and useful power
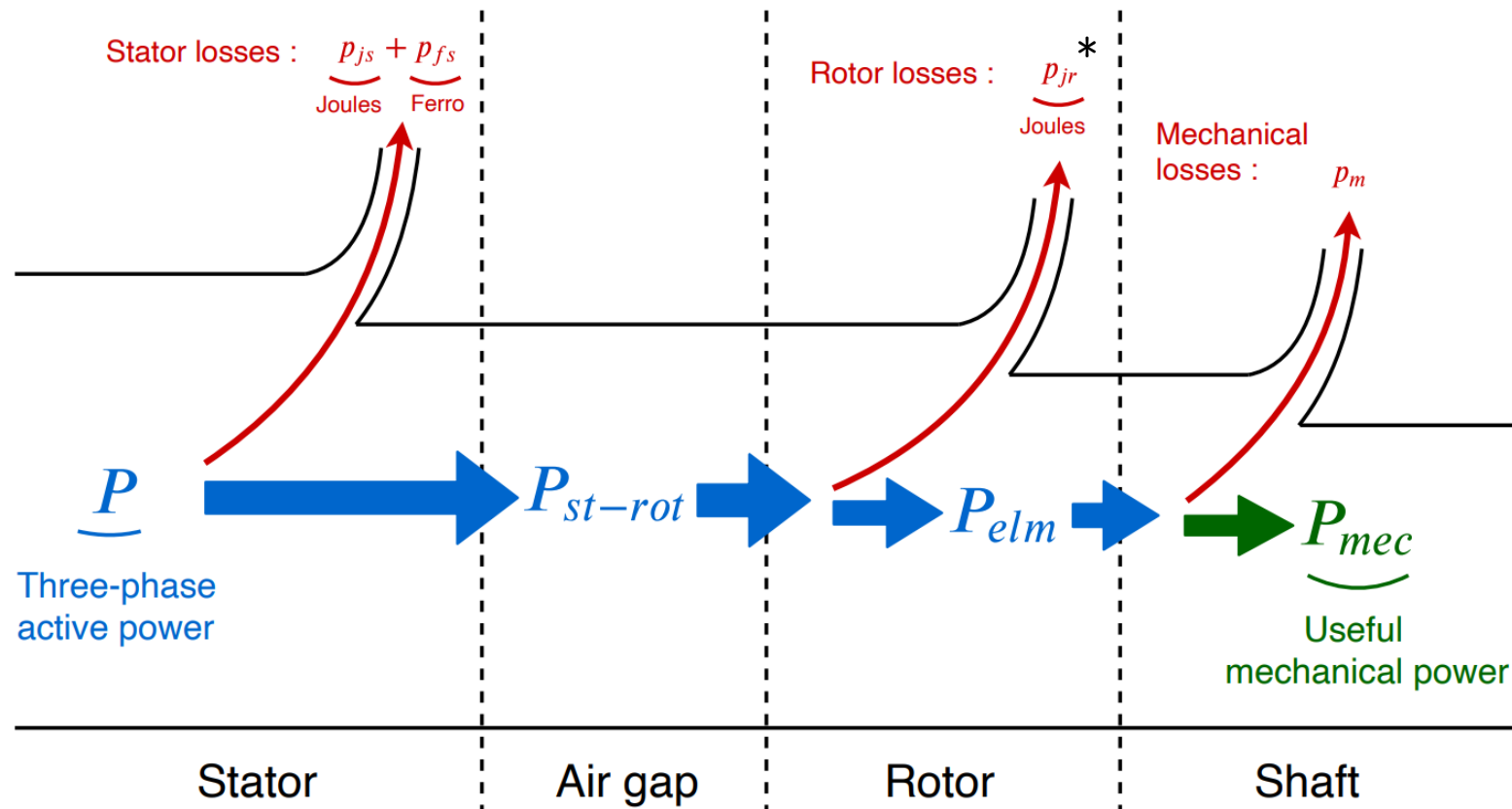
# The asynchronous machine – Power balance



\* Ferromagnetic losses in the rotor can be neglected since the rotor current frequency is much smaller than the grid frequency

# Exercises

---

Exercise 19: Asynchronous motor for washer cleaner

Exercise 20: Asynchronous motor of a fan

# Exercise 19: Asynchronous motor for washer cleaner

A star-shaped asynchronous motor of a high-pressure washer cleaner has the following nominal characteristics:

- $P_n = 5.5 \text{ kW}$
- RMS composed voltage value  $U_{sn} = 400 \text{ V}$
- Frequency  $f_n = 50 \text{ Hz}$
- RMS line current intensities  $I_{sn} = 11 \text{ A}$
- Speed of rotation  $\dot{\theta}_n = 1460 \text{ RPM}$

Assume that the stator reactance  $X_s$  is equal to the stator resistance  $R_s$ . Use a single-phase equivalent model of the asynchronous motor when needed.

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$

# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$

1. Calculate the synchronous speed of rotation  $\dot{\theta}_s$ , the number of pair of poles of the motor and the nominal slip  $g_n$ .
2. Determine the value of the stator resistance  $R_s$  given that a current of RMS value  $I_0 = 10 \text{ A}$  flows when a voltage of RMS value  $U_0 = 20.6 \text{ V}$  is applied.
3. At the nominal operating point, without mechanical load, the motor draws a current of RMS value  $I_{s0} = 3.07 \text{ A}$  for an active power  $P_{s0} = 245 \text{ W}$ . Calculate the overall losses and calculate the resistance modelling ferromagnetic losses  $R_{H+F}$  and the magnetizing inductance  $L_\mu$ , assuming that mechanical losses equal ferromagnetic losses;

Consider that the machine operates at nominal speed and produces the nominal mechanical power  $P_n$  to the mechanical load. The nominal mechanical power can also be denoted  $P_{mec}$ .

4. At the nominal operating point, calculate the transmitted power from the stator to the rotor and the Joules losses in the stator  $P_{js}$  and deduce the total consumed power  $P$ .
5. Calculate the rotoric resistance  $R'_r$  and the leak inductance  $L'_r$  seen from the stator.
6. At the nominal operating point, calculate the mechanical torque  $\Gamma_{un}$  and the electromagnetic torque  $\Gamma_n$ , the power factor  $\cos \varphi_n$  and the efficiency  $\eta_n$ .
7. Compute the RMS value  $I_s$  of the line currents, and the power factor  $\cos \phi$  at a rotation speed of 0 RPM.




# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$

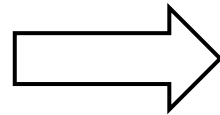
1. Calculate the synchronous speed of rotation  $\dot{\theta}_s$ , the number of pair of poles of the motor and the nominal slip  $g_n$ .

$$\begin{aligned} f_n &= 50 \text{ Hz} \\ &= 50 \cdot 60 = 3000 \text{ RPM} \\ &= p * \dot{\theta}_s \end{aligned}$$



$p$	$\dot{\theta}_s = 3000/p$
1	3000
2	1500
3	1000
4	750

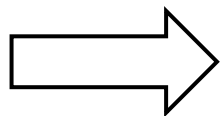$\dot{\theta}_s$  closed from  $\dot{\theta}_n$  and higher



Two pairs of poles and synchronous speed of  $\dot{\theta}_s = 1500 \text{ RPM}$ .


$$g_n = \frac{\dot{\theta}_s - \dot{\theta}_n}{\dot{\theta}_s} = \frac{1500 - 1460}{1500} = 0.0267$$

# Exercise 19: Asynchronous motor for washer cleaner



**Star configuration** -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$   
 $\dot{\theta}_s = 1500 \text{ RPM}$

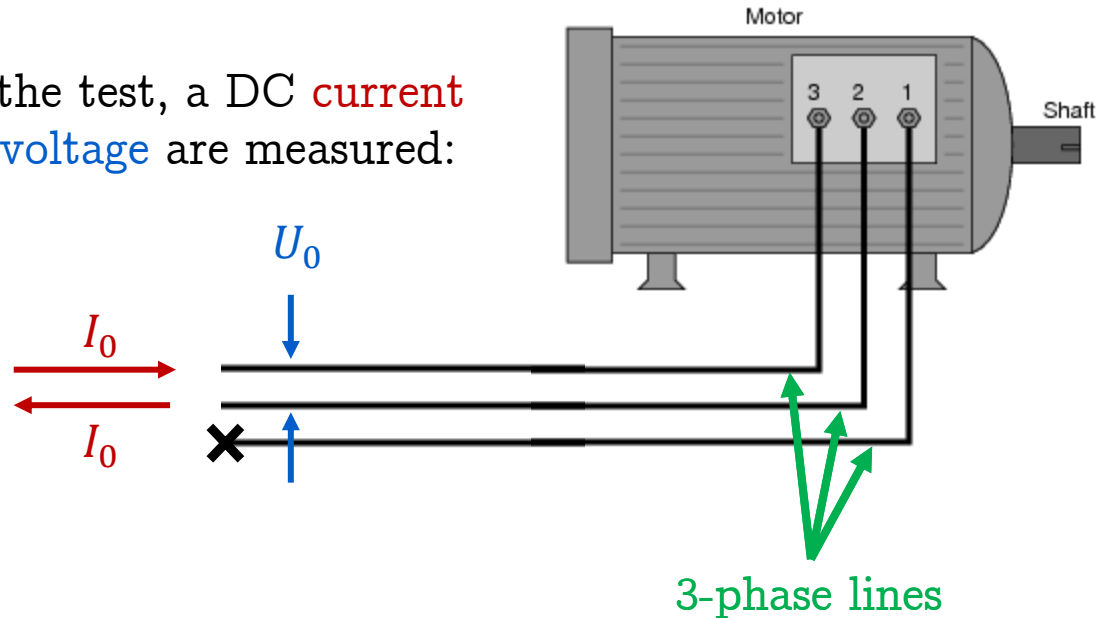2. Determine the value of the stator resistance  $R_s$  given that a current of RMS value  $I_0 = 10 \text{ A}$  flows when a voltage of RMS value  $U_0 = 20.6 \text{ V}$  is applied.

For the test, a DC **current** and **voltage** are measured:



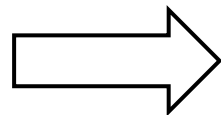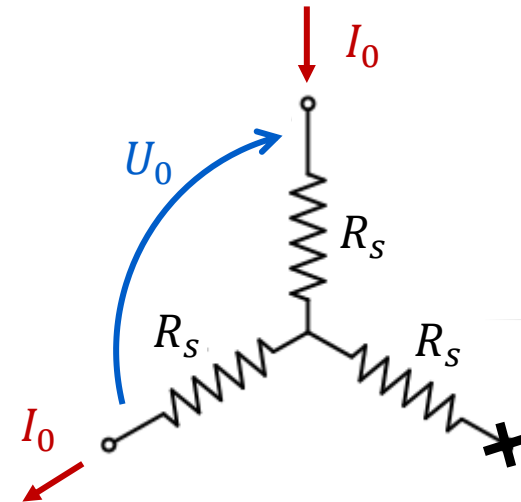The voltage drop is due only to the resistance of the stator windings  $R_s$




$$U_0 = (2 \cdot R_s) \cdot I_0 \Leftrightarrow R_s = \frac{U_0}{2 I_0} = 1,03 \Omega$$

# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$   
 $\dot{\theta}_s = 1500 \text{ RPM}$  -  $R_s = 1,03\Omega$

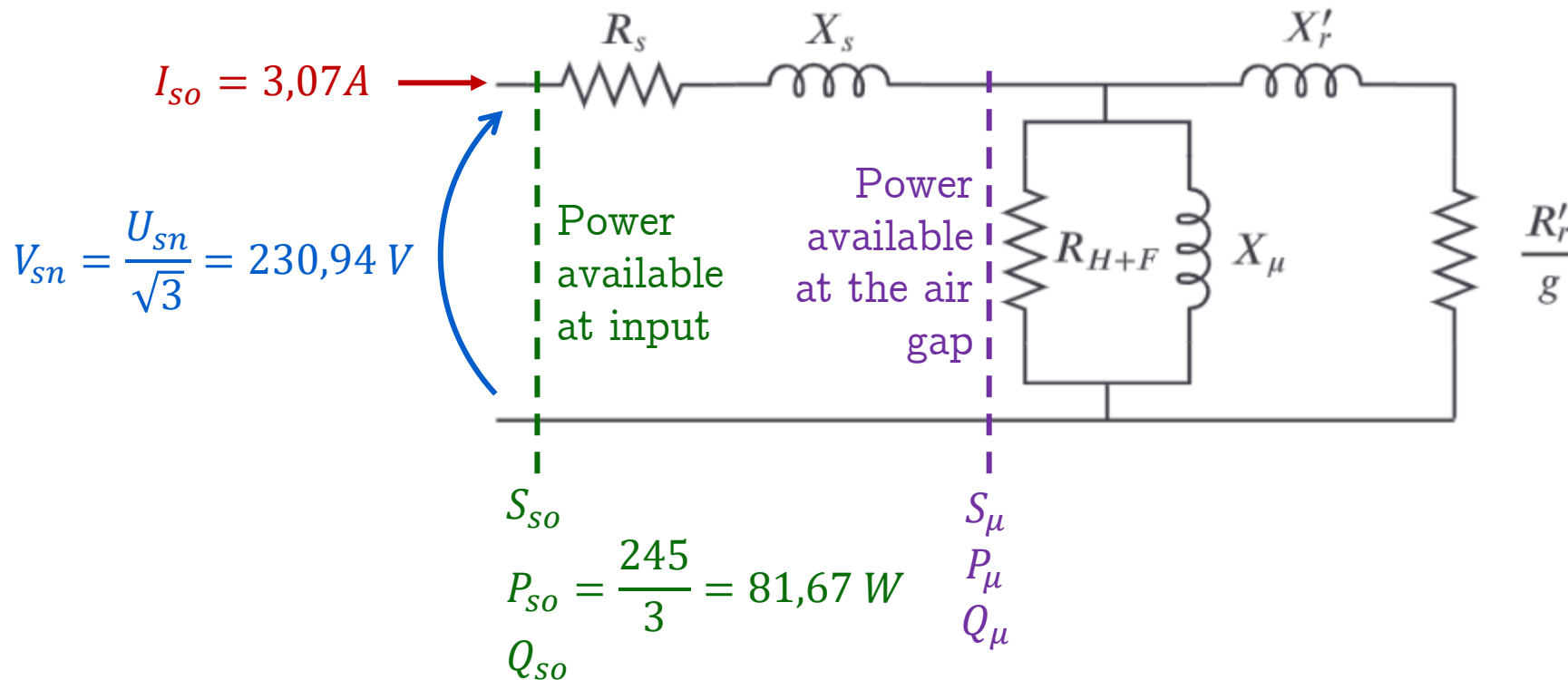3. At the nominal operating point, without mechanical load, the motor draws a current of RMS value  $I_{s0} = 3.07 \text{ A}$  for an active power  $P_{s0} = 245 \text{ W}$ . Calculate the overall losses and calculate the resistance modelling ferromagnetic losses  $R_{H+F}$  and the magnetizing inductance  $L_\mu$ , assuming that mechanical losses equal ferromagnetic losses




1.  $S_{s0} = V_{sn} I_{s0}$
2.  $Q_{s0} = \sqrt{S_{s0}^2 - P_{s0}^2}$
3.  $P_\mu = P_{s0} - R_s I_{s0}^2$
4.  $Q_\mu = Q_{s0} - X_s I_{s0}^2$
5.  $S_\mu = \sqrt{P_\mu^2 + Q_\mu^2}$
6.  $V_\mu = \frac{S_\mu}{I_{s0}}$

# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$   
 $\dot{\theta}_s = 1500 \text{ RPM}$  -  $R_s = 1,03 \Omega$

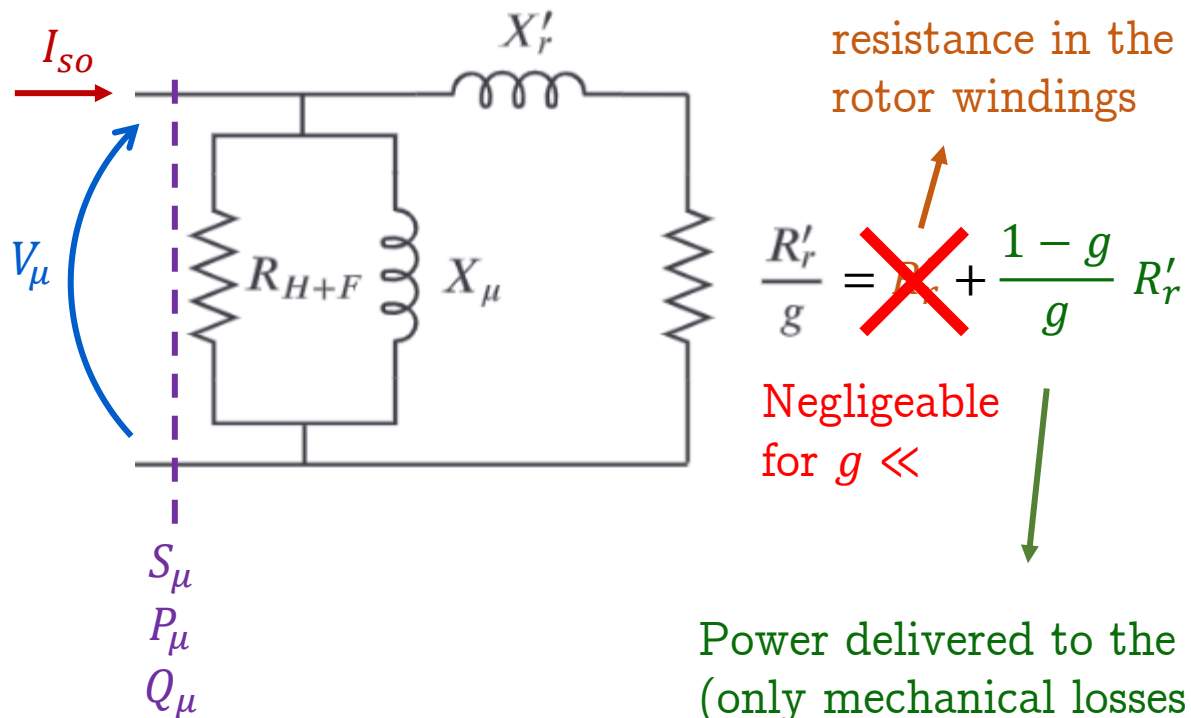3. At the nominal operating point, without mechanical load, the motor draws a current of RMS value  $I_{s0} = 3.07 \text{ A}$  for an active power  $P_{s0} = 245 \text{ W}$ . Calculate the overall losses and calculate the resistance modelling ferromagnetic losses  $R_{H+F}$  and the magnetizing inductance  $L_\mu$ , assuming that **mechanical losses equal ferromagnetic losses**



All the active power available at the air gap is lost either with  $R_{H+F}$  (ferromagnetic losses) or with  $\frac{1-g}{g} R_r'$  (mechanical losses)


$$\begin{aligned} P_\mu &= P_f + P_m \\ &= 2 P_{ferro} \\ &= 2 \frac{V_\mu^2}{R_{H+F}} \end{aligned}$$

$$R_{H+F} = \frac{2 V_\mu^2}{P_\mu} = 1437,88 \Omega$$

# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$   
 $\dot{\theta}_s = 1500 \text{ RPM}$  -  $R_s = 1,03 \Omega$  -  $R_{H+F} = 1437,88 \Omega$

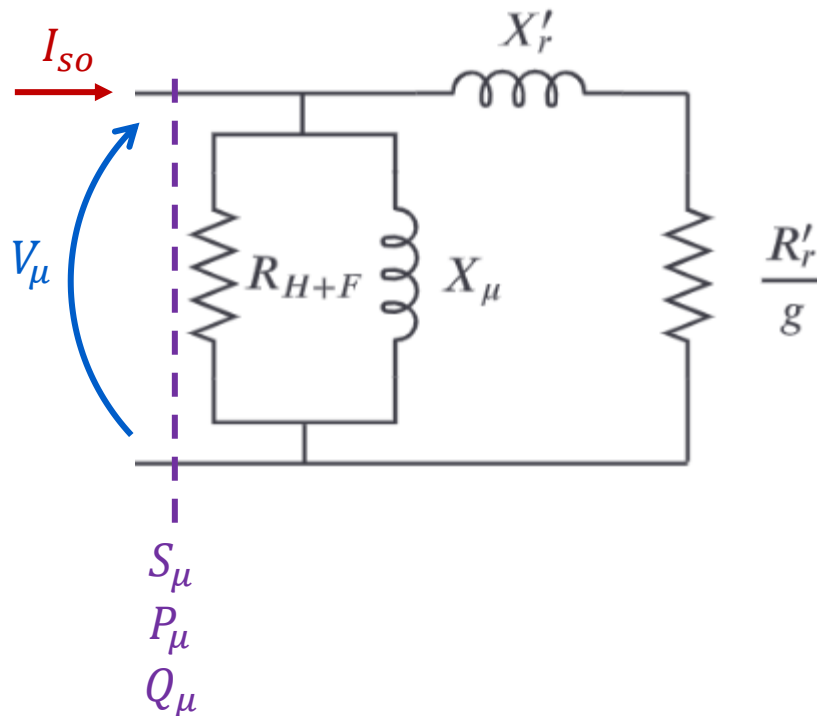3. At the nominal operating point, without mechanical load, the motor draws a current of RMS value  $I_{s0} = 3.07 \text{ A}$  for an active power  $P_{s0} = 245 \text{ W}$ . Calculate the overall losses and calculate the resistance modelling ferromagnetic losses  $R_{H+F}$  and the magnetizing inductance  $L_\mu$ , assuming that mechanical losses equal ferromagnetic losses




By considering  $X_r' \ll X_\mu$ , all the reactive power available at the air gap can be considered to be lost in  $X_\mu$ :

$$Q_\mu = \frac{V_\mu^2}{X_\mu} \Leftrightarrow X_\mu = \frac{V_\mu^2}{Q_\mu} = 74,84 \Omega$$

# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$   
 $\dot{\theta}_s = 1500 \text{ RPM}$  -  $R_s = 1,03 \Omega$  -  $R_{H+F} = 1437,88 \Omega$  -  $X_\mu = 74,84 \Omega$

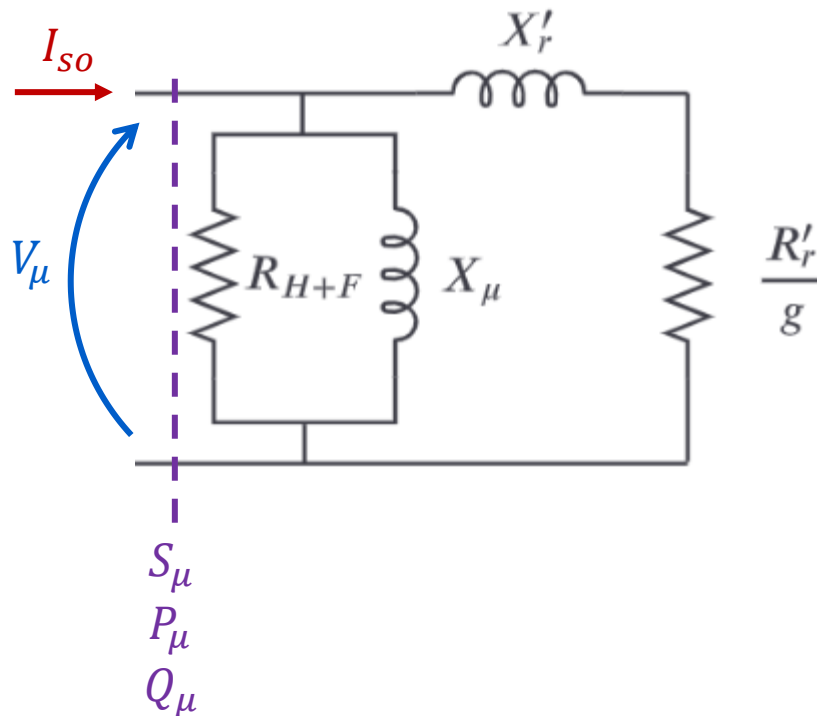3. At the nominal operating point, without mechanical load, the motor draws a current of RMS value  $I_{s0} = 3.07 \text{ A}$  for an active power  $P_{s0} = 245 \text{ W}$ . Calculate the overall losses and calculate the resistance modelling ferromagnetic losses  $R_{H+F}$  and the magnetizing inductance  $L_\mu$ , assuming that mechanical losses equal ferromagnetic losses



Half  $P_\mu$  is for the mechanical losses, the other half is for the ferromagnetic losses → Considering three phases:


$$P_m = 3 \frac{P_\mu}{2} = 107,94 \text{ W}$$

$$P_f = 3 \frac{P_\mu}{2} = 107,94 \text{ W}$$

# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$   
 $\dot{\theta}_s = 1500 \text{ RPM}$  -  $R_s = 1,03 \Omega$  -  $R_{H+F} = 1437,88 \Omega$  -  $X_\mu = 74,84 \Omega$  -  $P_m = P_f = 107,94 \text{ W}$

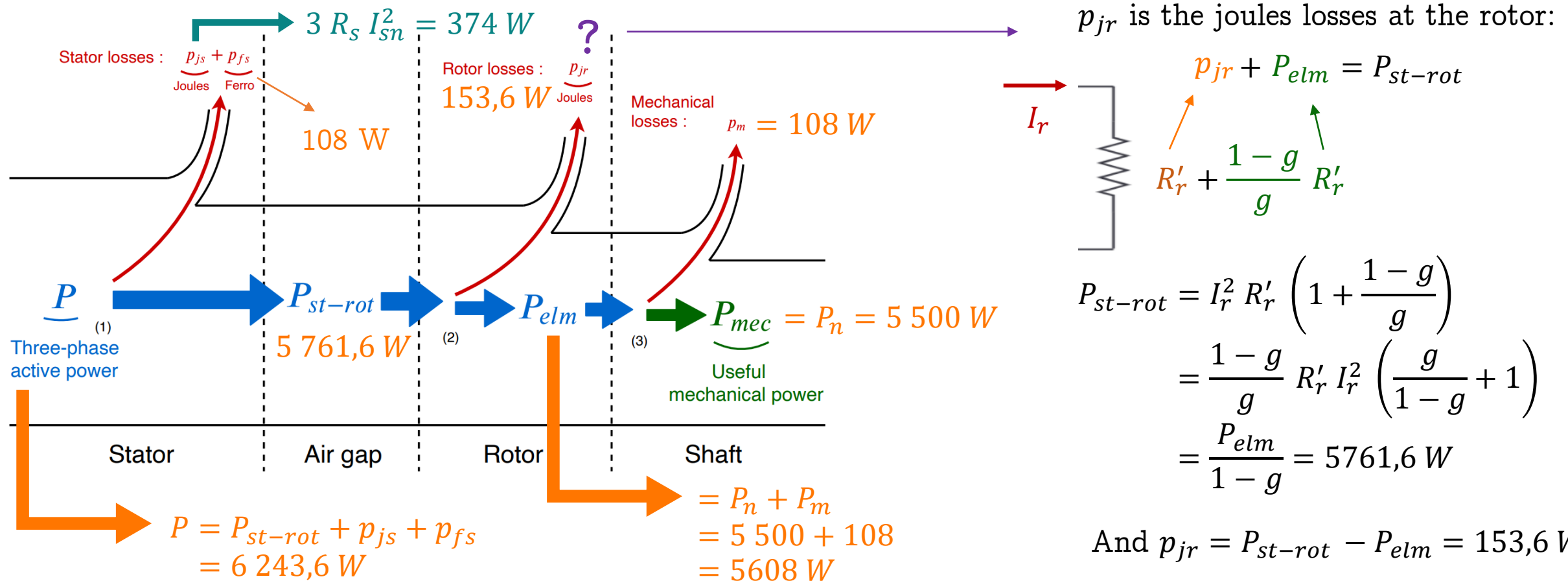4. At the nominal operating point, calculate the transmitted power from the stator to the rotor and the Joules losses in the stator  $P_{js}$  and deduce the total consumed power  $P$ .



# Exercise 19: Asynchronous motor for washer cleaner

Star configuration -  $P_n = 5,5 \text{ kW}$  -  $U_{sn} = 400 \text{ V}$  -  $f_n = 50 \text{ Hz}$  -  $I_{sn} = 11 \text{ A}$  -  $\dot{\theta}_n = 1460 \text{ RPM}$  -  $X_s = R_s$   
 $\dot{\theta}_s = 1500 \text{ RPM}$  -  $R_s = 1,03 \Omega$  -  $R_{H+F} = 1437,88 \Omega$  -  $X_\mu = 74,84 \Omega$  -  $P_m = P_f = 107,94 \text{ W}$  -  $P = 6\,244 \text{ W}$

5. Calculate the rotor resistance  $R'_r$  and the leak inductance  $L'_r$  seen from the stator.
6. At the nominal operating point, calculate the mechanical torque  $\Gamma_{un}$  and the electromagnetic torque  $\Gamma_n$ , the power factor  $\cos \varphi_n$  and the efficiency  $\eta_n$ .
7. Compute the RMS value  $I_s$  of the line currents, and the power factor  $\cos \phi$  at a rotation speed of 0 RPM.



# Exercise 20: Asynchronous motor of a fan

On the nameplate of an asynchronous motor of a fan used in an air handling unit, the following characteristics are read:

4.4 kW; 230/400 V; 15.5/9 A; 50 Hz; 4 poles

Using a single-phase equivalent model of the asynchronous motor:

1. Explain the meaning of each element on the nameplate;
2. The motor is used on a 230 V network, explain which winding coupling should be used for the stator;
3. Calculate the synchronous speed of rotation  $\dot{\theta}_s$ ;
4. Given that the (DC) resistance value measured between two stator terminals is  $R_a = 0.654 \Omega$ , compute the value of the statoric resistance  $R_s$  of the equivalent single-phase model;
5. A calibrated motor is used to rotate the shaft of the unpowered considered motor, upto reaching the synchronous speed, at which the calibrated motor consumes 86 W. Calculate the mechanical losses of the motor and explain why assuming that these mechanical losses remain constant is a good approximation;
6. At the nominal operating point, without mechanical load, the motor draws a current of RMS value  $I_{s0} = 3.82 \text{ A}$  for an active power  $P_{s0} = 300 \text{ W}$ . Calculate the resistance modelling ferromagnetic losses  $R_{H+F}$  and the statoric inductance  $L_\mu$ ;

# Exercise 20: Asynchronous motor of a fan

7. The rotor shaft of the motor is stalled while a voltage of RMS value  $U_{sc} = 57.5 \text{ V}$  is applied for a consumed three-phase active power  $P_{sc,3\phi} = 374 \text{ W}$  and three-phase reactive power  $Q_{sc,3\phi} = 1.09 \text{ kvar}$ . Calculate the rotoric resistance  $R'_r$  and the leak inductance  $X'_r$  seen from the stator.

A direct voltage of value  $V_s$  and frequency  $f$  is applied on each phase of the motor.

8. Using single-phase equivalent model of the asynchronous motor, express the RMS current value  $I_s$  in terms of  $V_s$ ,  $R_s$ ,  $R'_r$ ,  $g$  et  $X'_r$ ;
9. Calculate the transmitted power from the stator to the rotor;
10. Calculate the electromagnetic torque  $C_{elm}$  and give the maximal reachable torque  $\Gamma_{\max}$  after showing that  $C_{elm}$  is maximal for a slip value  $g_{\max}$ ;
11. Plot  $C$  with respect to  $g$  for an applied voltage  $V_s$  equal to  $V_n$ ,  $\frac{V_n}{\sqrt{2}}$  and  $\frac{V_n}{2}$ ;
12. Explain why a control on the rotor voltages is not suitable for speed variation for load having constant resistive torque;
13. To limit the peak current when starting the motor, a star/delta starter is frequently used. Assuming that this transient mode is much more longer compared to period corresponding to the frequency  $f$  of the applied voltages, calculate the RMS current values of the line currents compared to those drawn by using a star/delta starter.