



Electromagnetic Energy Conversion

ELEC0431

Exercise session 8: Asynchronous machines

31 March 2023

Florent Purnode (florent.purnode@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,
University of Liège, Belgium

Exercise 16: Three-phase turbo-alternator

On the nameplate of an asynchronous motor of a fan used in an air handling unit, the following characteristics are read:

4.4 kW; 230/400 V; 15.5/9 A; 50 Hz; 4 poles

Using a single-phase equivalent model of the asynchronous motor and neglecting the statoric leak inductance X_s :

1. Explain the meaning of each element on the nameplate.
2. The motor is used on a 230 V network, explain which winding coupling should be used for the stator.
3. Calculate the synchronous speed of rotation $\dot{\theta}_s$.
4. Given that the (DC) resistance value measured between two stator terminals is $R_a = 0.654 \Omega$, compute the value of the statoric resistance R_s of the equivalent single-phase model.
5. A calibrated motor is used to rotate the shaft of the unpowered considered motor, upto reaching the synchronous speed, at which the calibrated motor consumes 86 W. Calculate the mechanical losses of the motor and explain why assuming that these mechanical losses remain constant is a good approximation.
6. At the nominal operating point, without mechanical load, the motor draws a current of RMS value $I_{s0} = 3.82 A$ for an active power $P_{s0} = 300 W$. Calculate the resistance modelling ferromagnetic losses R_{H+F} and the statoric inductance L_μ .
7. The rotor shaft of the motor is stalled while a voltage of RMS value $U_{sc} = 57.5 V$ is applied for a consumed three-phase active power $P_{sc,3\phi} = 374 W$ and three-phase reactive power $Q_{sc,3\phi} = 1.09 kvar$. Calculate the rotoric resistance R'_r and the leak inductance X'_r seen from the stator.


Exercise 16: Three-phase turbo-alternator

A direct voltage of value V_S and frequency f is applied on each phase of the motor. Neglecting the magnetizing branch:

8. Using the single-phase equivalent model of the asynchronous motor, express the RMS phase current value J_S in terms of V_S , R_S , R'_r , g and X'_r .
9. Calculate the transmitted power from the stator to the rotor.
10. Calculate the electromagnetic torque C_{elm} and give the maximal reachable torque Γ_{max} after showing that C_{elm} is maximal for a slip value g_{max} .


Exercise 16: Three-phase turbo-alternator

11. Plot C with respect to g for an applied voltage V_s equal to V_n , $\frac{V_n}{\sqrt{2}}$ and $\frac{V_n}{2}$.

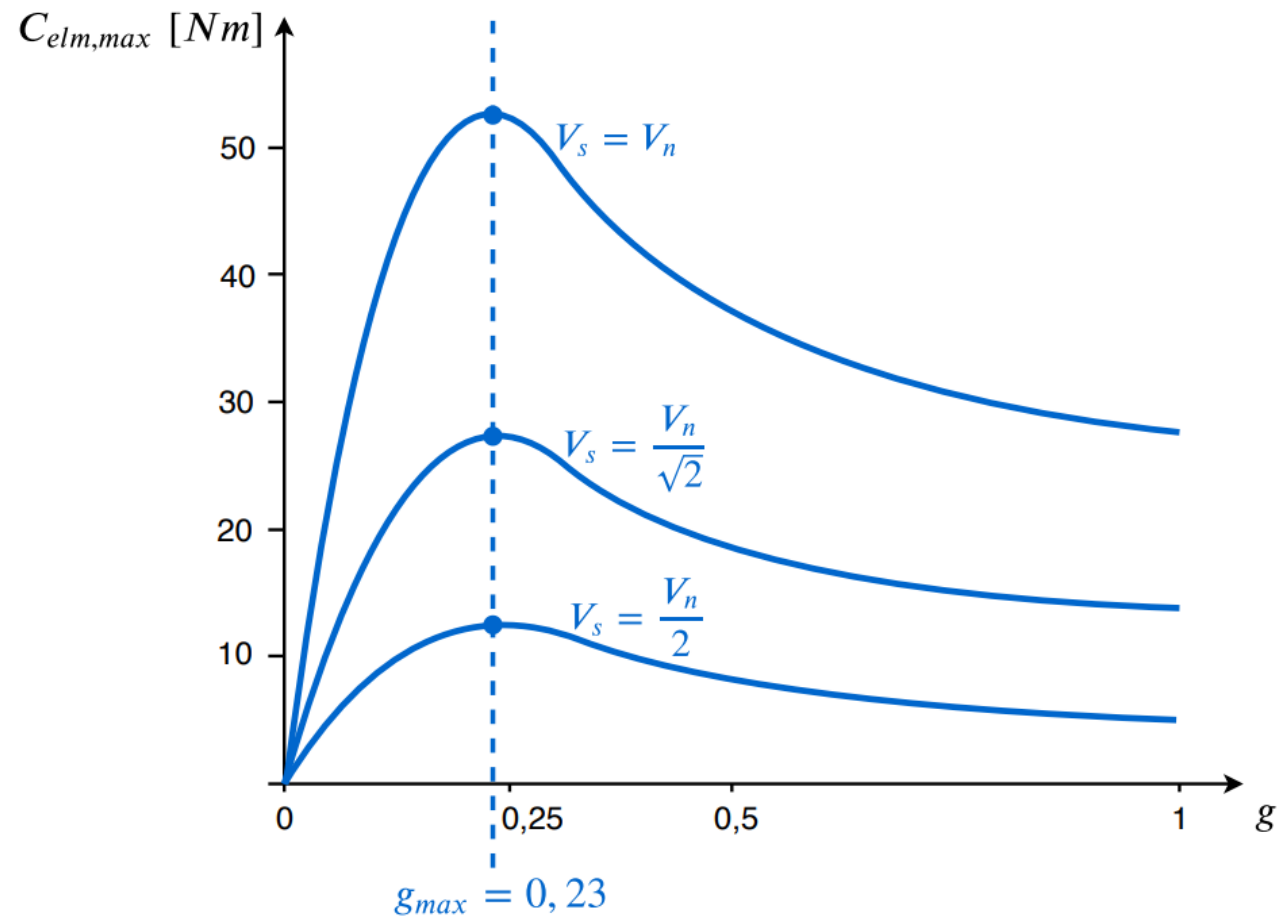

Exercise 16: Three-phase turbo-alternator

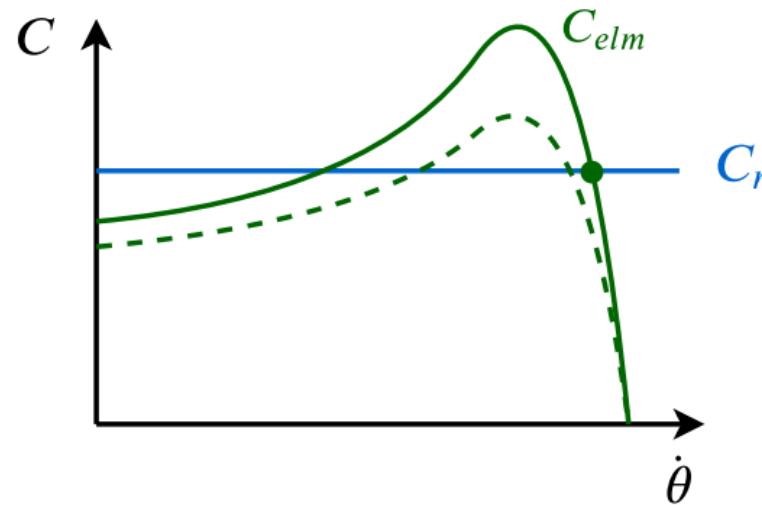12. Explain why a control on the rotor voltages is not suitable for speed variation for load having constant resistive torque.



- ➔ Modifying the voltage has a very small impact on the rotation speed.
 - ➔ the machine must remain in the stable region which is narrow.
13. To limit the peak current when starting the motor, a star/delta starter is frequently used. Assuming that this transient mode is much longer compared to the period corresponding to the frequency f of the applied voltages, calculate the RMS current values of the line currents compared to those drawn by using a star/delta starter.