



Electromagnetic Energy Conversion

ELEC0431

Exercise session 10: Electronic control systems

29 April 2022

Florent Purnode (florent.purnode@uliege.be) – Nicolas Davister (ndavister@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,
University of Liège, Belgium

Reminders

The DC converters


The DC converters – problematic

You want to build a drone. For this, you use DC motors running at 20 V and a 20 V battery. However, the camera and the control part work at 5 V. When the drone is waiting to take off, the control part is in standby and takes only 3 V. **How to obtain 5 or 3 V from the 20 V battery** to supply the control part?



The DC converters – resistive voltage divider

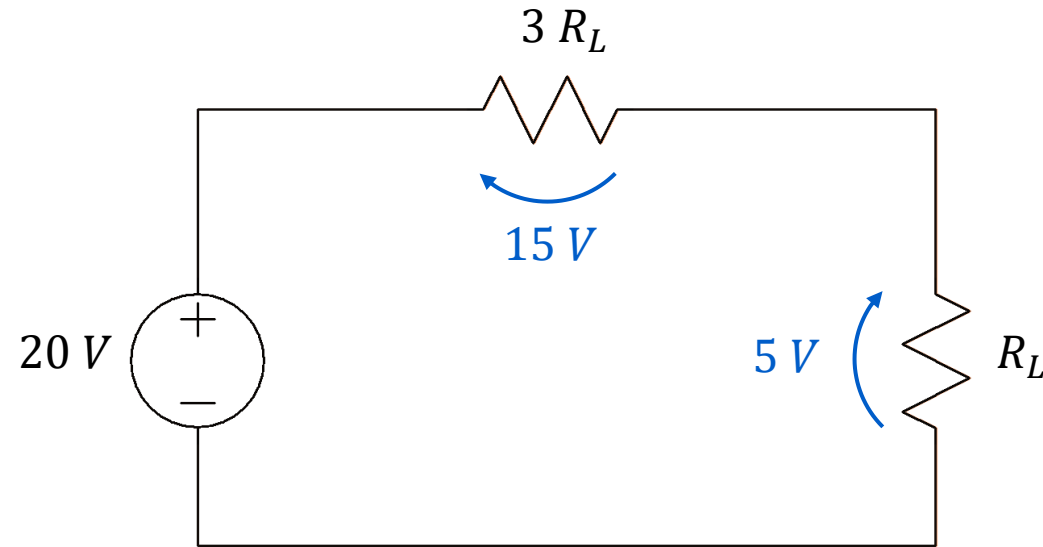
How to obtain 5 or 3 V from the 20 V battery ?



- ☺ We have the 5 V to power the control part.
- ☹ No possible to get the 3 V.
- ☹ Huge power losses

The DC converters – series pass regulator

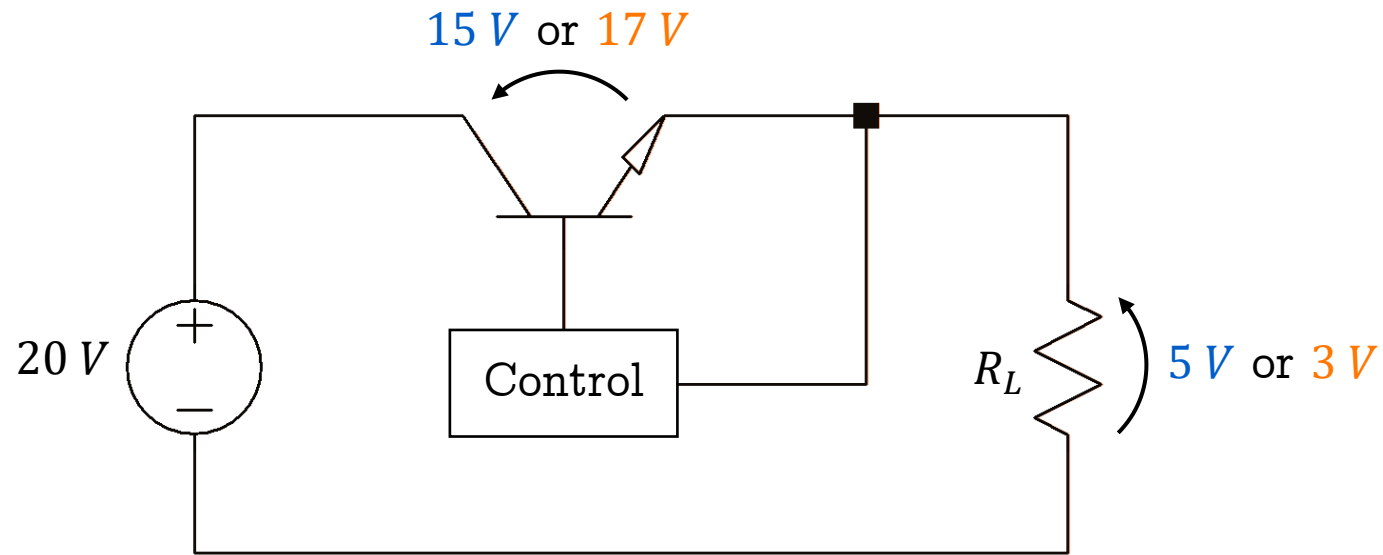
How to obtain 5 or 3 V from the 20 V battery ?



- ☺ We have the 5 V to power the control part.
- ☺ Possible to get the 3 V.
- ☹ Huge power losses

The DC converters – buck converter

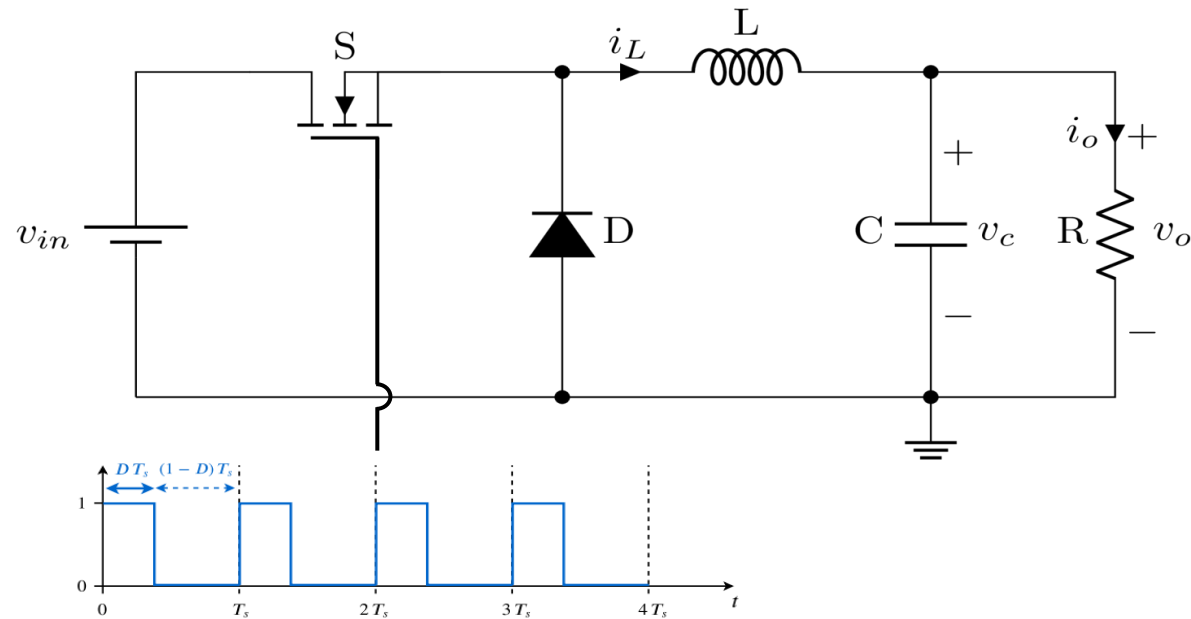
How to obtain 5 or 3 V from the 20 V battery ?



- ☺ We have the 5 V to power the control part.
- ☺ Possible to get the 3 V.
- ☺ Good efficiency

The DC converters – buck converter analysis

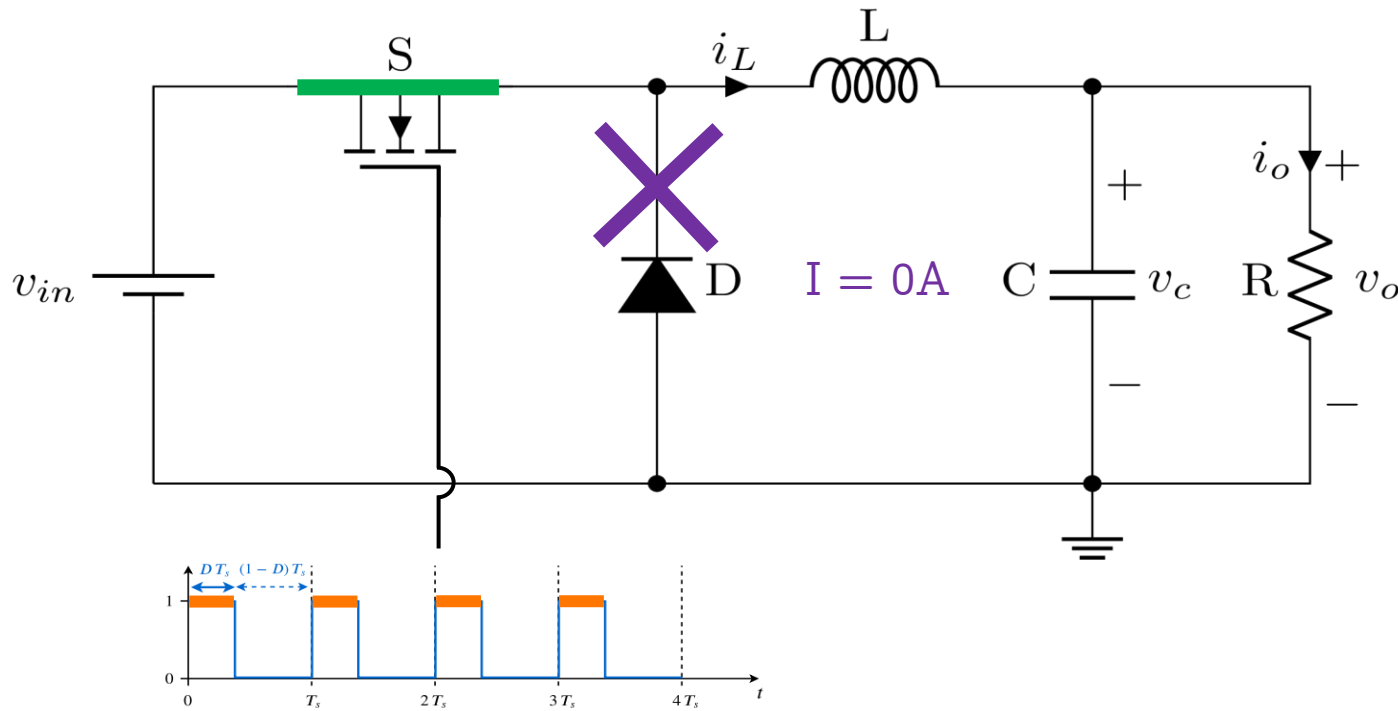
First case: There is a high voltage on the mosfet grid.



➤ The mosfet conducts.


➤ The diode blocks.

Equivalent circuit

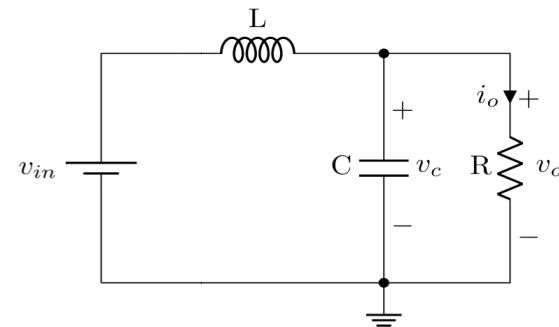


The DC converters – buck converter analysis

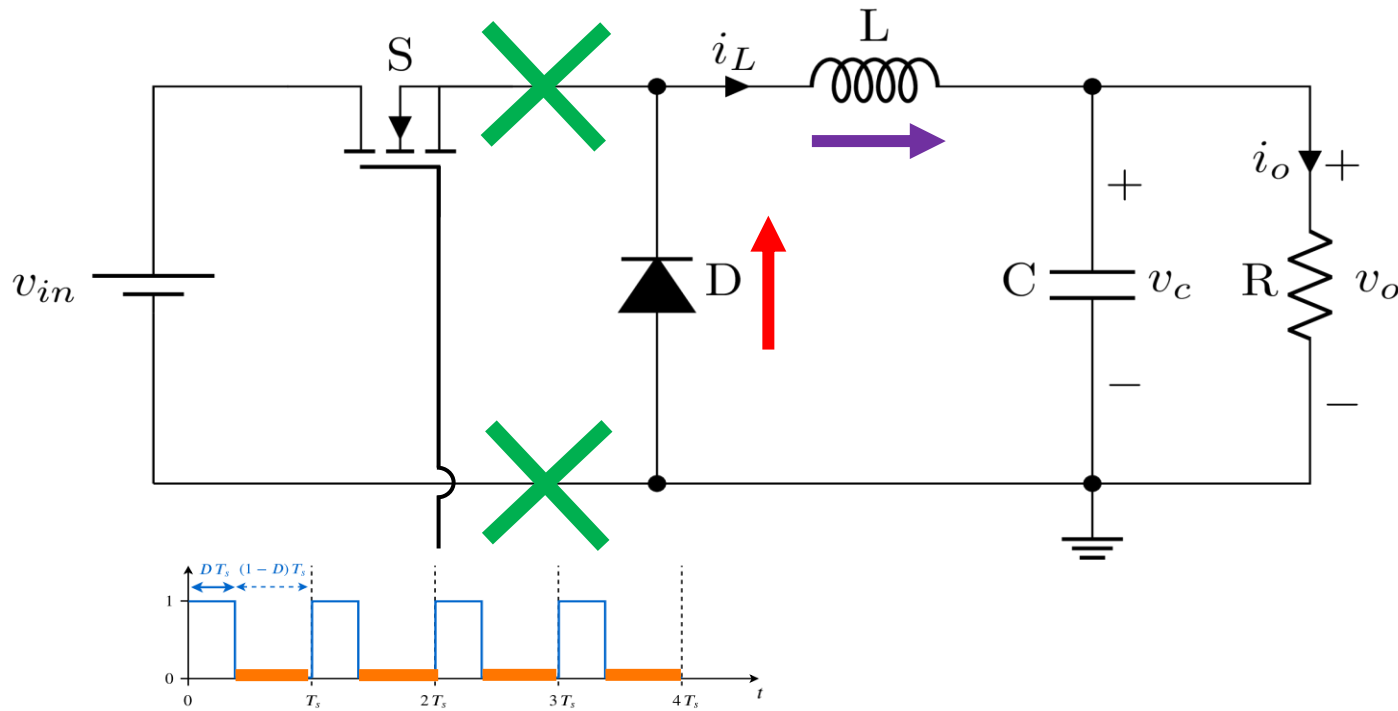Second case: There is a low voltage on the mosfet grid.



- The mosfet blocks
- ➔ The battery is disconnected.
- The Inductance forces current to keep flowing.
- The diode conducts.


Equivalent circuit

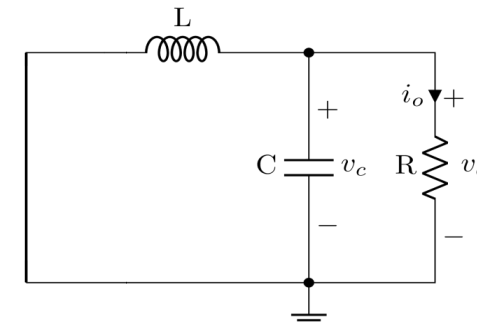

The DC converters – perfect components hypothesis


The equivalent circuits are obtained with the assumption that components are perfect (mosfet and diode), which is not the case in practice:

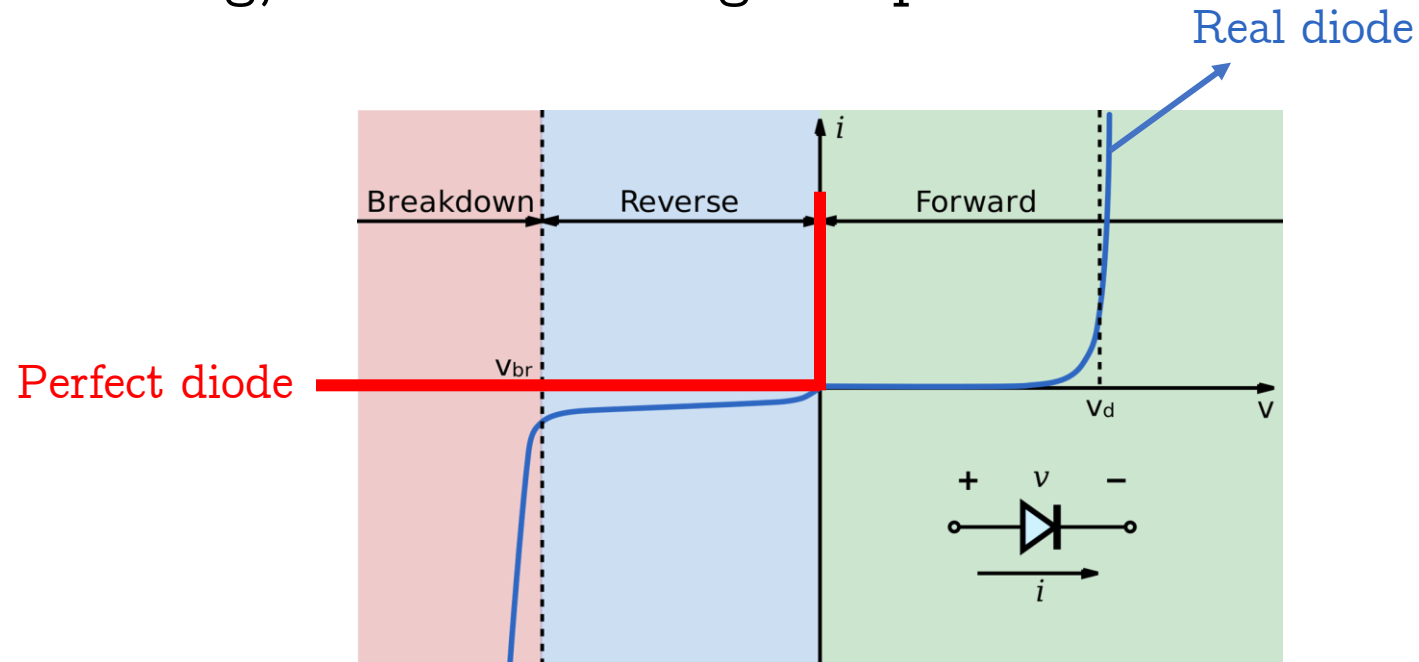- Mosfets have a resistance.
- When blocking, diodes let pass a small current and, when conducting, there is a voltage drop:



The DC converters – duty cycle

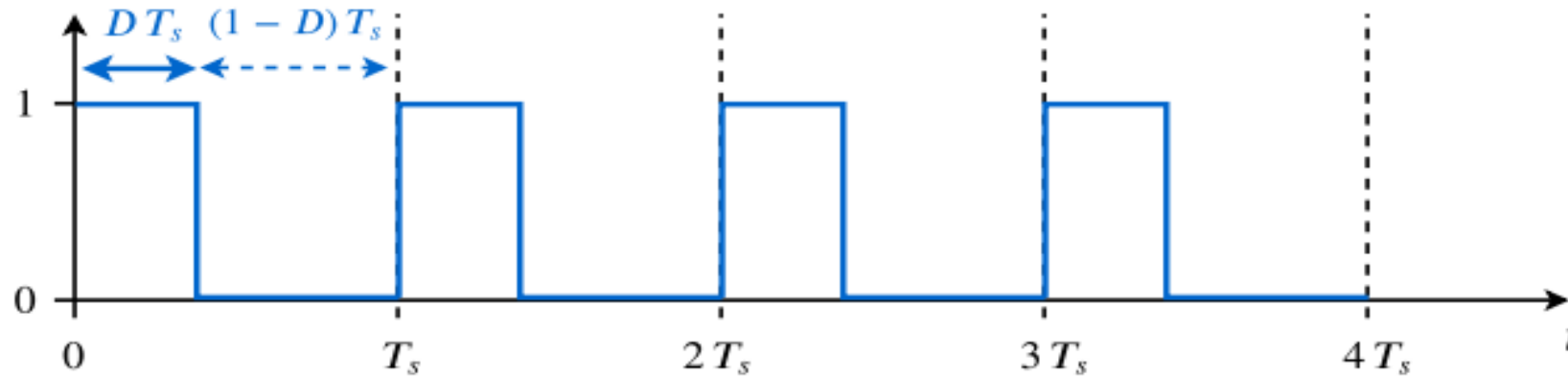The mosfet is all the time turned OFF and ON again using the control signal:



Each period of time T_s (the switching period) is divided in two:

- During a time $D \cdot T_s$, the mosfet conducts.
 - During a time $(1 - D) \cdot T_s$, the mosfet blocks.
- } D is the “duty cycle”. It is the proportion of time during which the switch is closed.
($0 < D < 1$)

The DC converters – The inductor volt-second balance

Governing equation for inductors:

$$v_L(t) = L \frac{di_L(t)}{dt}$$
$$\Rightarrow i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$


In periodic steady state, the net change in the inductor current is zero $\Rightarrow i_L(T_s) = i_L(0)$

$$\Rightarrow \int_0^{T_s} v_L(t) dt$$
$$\Rightarrow \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

\Rightarrow The average inductor voltage is zero in steady state !


The DC converters – buck converter analysis

During D % of the time:

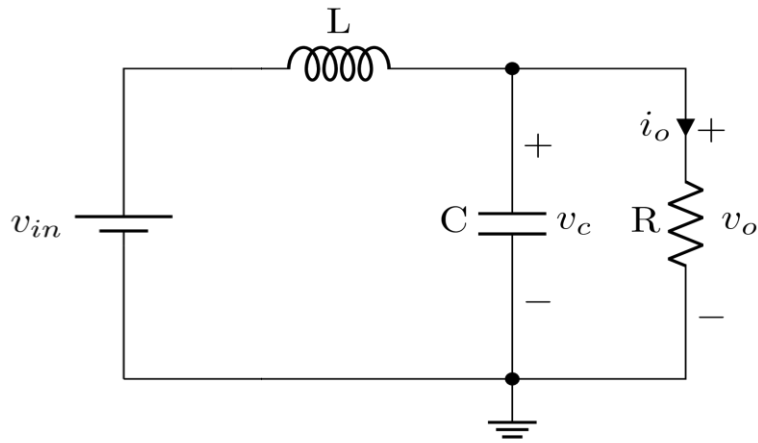

$$\begin{aligned}v_{in} &= v_L(t) + v_o(t) \\ &\approx V_L + V_o\end{aligned}$$

During $(1-D)$ % of the time:

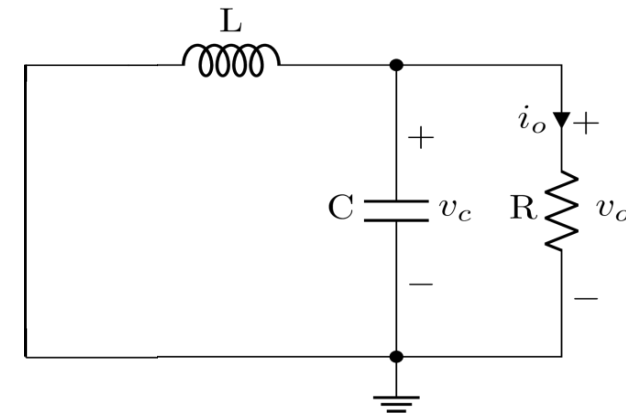

$$\begin{aligned}0 &= v_L(t) + v_o(t) \\ &\approx V_L + V_o\end{aligned}$$

Volt second balance: $\langle v_L \rangle = 0$

$$\rightarrow D(V_{in} - V_o) + (1 - D)(-V_o) = 0$$

$$\rightarrow D V_{in} - D V_o - V_o + D V_o = 0$$

$$\rightarrow V_o = D V_{in}$$

Exercises

Exercise 24: Regenerative braking

Exercise 26: DC-DC buck converter

Exercise 27: DC-DC boost converter

Exercise 24: Regenerative braking

Hybrid electric vehicles are generally provided with regenerative braking, allowing to load onboard battery when the vehicle is braking or when the vehicle acts as a driving load. In this exercise, the DC motor, having an electromotive force E and internal resistance $R = 0.5 \Omega$ is connected (when the regenerative braking is active) to a battery delivering a current I under the voltage $V = 100 \text{ V}$ using a chopper DC-DC converter (Fig. 64).


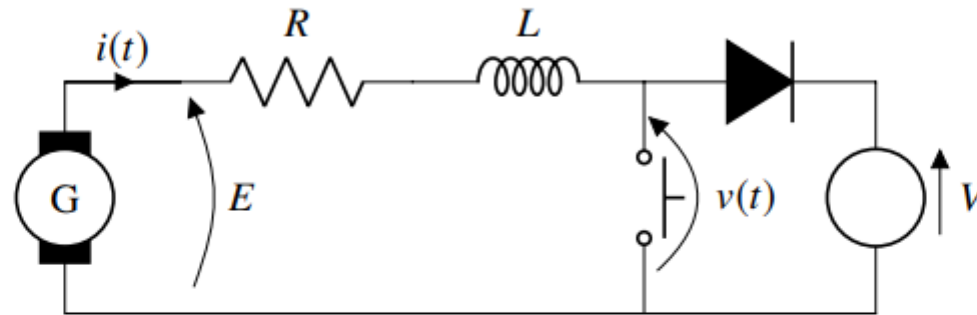


Figure 64: DC-DC converter for regenerative braking.

1. Find the mean value of $v(t)$: V_m ;
2. Find the link between the mean input current I_m and the mean output current I ;
3. Express the voltage V with respect to I_m , E , R and D , the duty cycle;
4. Compute the duty cycle allowing to obtain $V_m = 60 \text{ V}$;
5. Compute the mean braking current I_m when the motor delivers an electromotive force $E = 70 \text{ V}$ for $V_m = 60 \text{ V}$;
6. Calculate the braking power $E I_m$ and the braking torque C_m if the motor speed of rotation is $\dot{\theta} = 955 \text{ RPM}$.

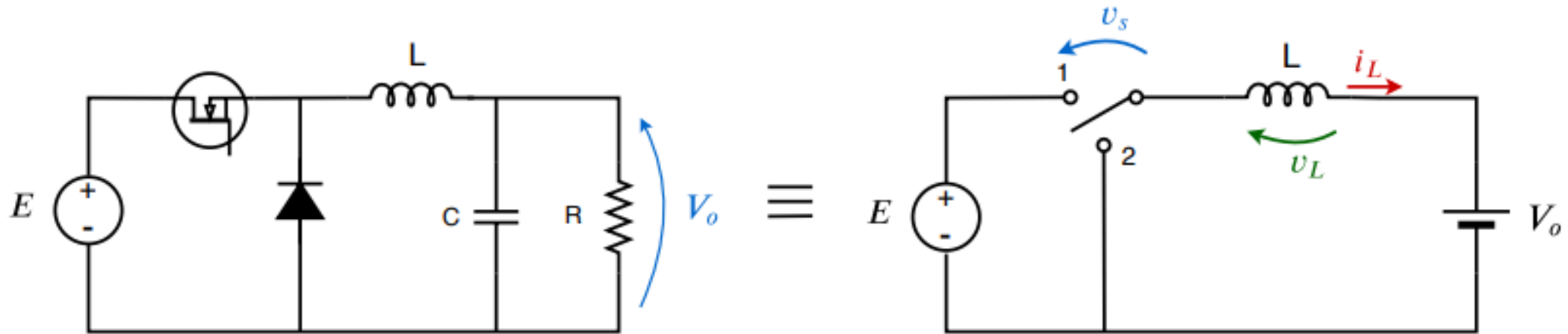Exercise 26: DC-DC buck converter

DC-DC converters are used to adapt two different voltage levels. For instance, in particular model of an electric car, the battery voltage is set to $E = 302$ V, whereas the auxiliaries (lights, cigar lighter, window and wiper motors, ...) are working with $V_o = 12$ V. A DC-DC buck converter is used to reduce the battery high voltage to the lower value (12 V) ensuring high efficiency. The DC-DC buck converter can be modelled by the following circuit.



1. Find the waveforms of the voltage across the ideal switch (v_s) and the voltage across the inductance (v_L).
2. Deduce the inductance current waveform from it.

Exercise 26: DC-DC buck converter

Now, suppose that the average voltage across the inductance is 0 during a switching period (corresponding to a steady-state condition).


3. Express the ratio $\frac{V_o}{E}$ in terms of the duty cycle D .
4. Give the value of D in this situation.

The current ripple Δi is defined as the absolute difference between the maximum of current (during a switching period) and the average current I (over the same switching period).

5. Find the expression of the inductor current ripple Δi_L in terms of V_o , E , D , T_s and L .
6. Estimate the inductor current ripple Δi_L for a switching frequency $f_s = 1000$ Hz and an inductance of 50 mH. Compare the value of the current ripple to the value of the output current if the auxiliaries draw 12 W.

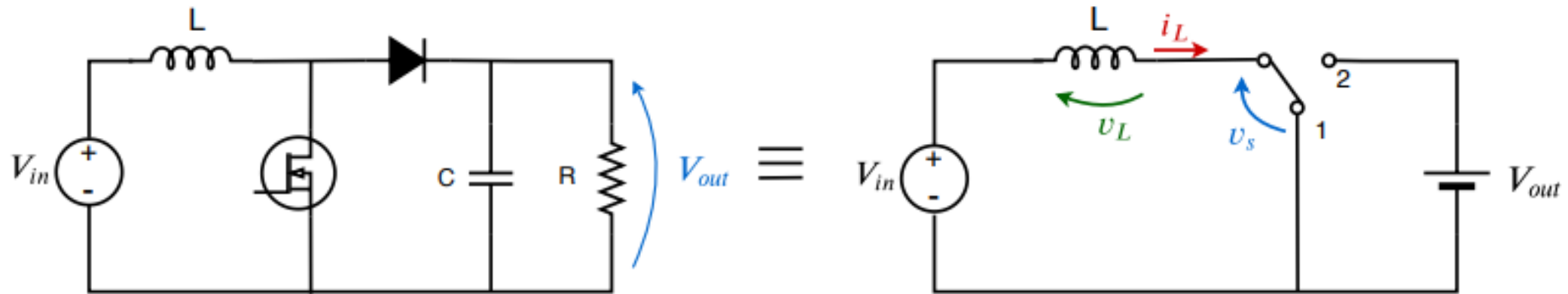Exercise 27: DC-DC boost converter

DC-DC converters are used to adapt two different voltage levels. In some electronic calculator, the battery voltage is set as $V_{in} = 3\text{ V}$, whereas the electronic parts work under $V_{out} = 9\text{ V}$. A DC-DC boost converter is used to increase the battery low voltage to the higher value (9 V) ensuring high efficiency. The DC-DC boost converter can be modelled by the following circuit.



1. Find the waveforms of the voltage across the ideal switch (v_s) and the voltage across the inductance (v_L).
2. Deduce the inductance current waveform from it.

Exercise 27: DC-DC boost converter

Now, suppose that the average voltage across the inductance is 0 during a switching period (corresponding to a steady-state condition).

3. Express the ratio $\frac{V_{out}}{V_{in}}$ in terms of the duty cycle D .
4. Give the value of D in this situation.

The current ripple Δi is defined as the absolute difference between the maximum of current (during a switching period) and the average current I (over the same switching period).

5. Find the expression of the inductor current ripple Δi_L in terms of V_{out} , V_{in} , D , T_s and L .
6. Estimate the inductor current ripple Δi_L for a switching frequency $f_s = 30$ kHz and an inductance of 75 mH. Compare the value of the current ripple to the value of the output current if the system draws 15 mW.