

# Electromagnetic Energy Conversion ELEC0431

## Exercise session 10: Electronic control systems

28 April 2023

Florent Purnode (florent.purnode@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science, University of Liège, Belgium

- Exercise 24: Regenerative braking
- Exercise 26: DC-DC buck converter
- Exercise 27: DC-DC boost converter

You want to build a drone. For this, you use DC motors running at 20 V and a 20 V battery. However, the camera and the control part work at 5 V. When the drone is waiting to take off, the control part is in standby and takes only 3 V. How to obtain 5 or 3 V from the 20 V battery to supply the control part?



#### How to obtain 5 or 3 V from the 20 V battery ?

→ Use a resistive voltage divider



We have the 5 V to power the control part.
Not possible to get the 3 V.
Huge power losses.

#### How to obtain 5 or 3 V from the 20 V battery ?

→ Use a series pass regulator



- $\odot$  We have the 5 V to power the control part.
- $\odot$  Possible to get the 3 V.
- $\otimes$  Huge power losses.

#### How to obtain 5 or 3 V from the 20 V battery ?

→ Use a DC-DC converter



*D* is the "duty cycle". It is the proportion of time during which the MOSFET conducts (0 < D < 1).

We have the 5 V to power the control part.
Possible to get the 3 V.
High efficiency

NB: The analysis is made assuming that components are ideal (mosfet and diode), which is not the case in practice.

### **Exercises**

# Exercise 24: Regenerative braking Exercise 26: DC-DC buck converter Exercise 27: DC-DC boost converter

## Exercise 24: Regenerative braking

Hybrid electric vehicles are generally provided with regenerative braking, allowing to load onboard battery when the vehicle is braking or when the vehicle acts as a driving load. In this exercise, the DC motor, having an electromotive force E and internal resistance  $R = 0.5 \Omega$  is connected (when the regenerative breaking is active) to a battery delivering a current I under the voltage V = 100 V using a chopper DC-DC converter:



- 1. Find the mean value of v(t):  $V_m$ .
- 2. Find the link between the mean input current  $I_m$  and the mean output current I.
- 3. Express the voltage V with respect to  $I_m$ , E, R and the duty cycle D.
- 4. Compute the duty cycle *D* allowing to obtain  $V_m = 60$  V.
- 5. Compute the mean braking current  $I_m$  when the motor delivers an electromotive force E = 70 V for  $V_m = 60 V$ .
- 6. Calculate the braking power *E*  $I_m$  and the braking torque  $C_m$  if the motor speed of rotation is  $\dot{\theta} = 955 RPM$ .

## Exercise 26: DC-DC buck converter

DC-DC converters are used to adapt two different voltage levels. For instance, in particular model of an electric car, the battery voltage is set to E = 302 V, whereas the auxiliaries (lights, cigar lighter, window and wiper motors, ...) are working with  $V_o = 12 V$ . A DC-DC buck converter is used to reduce the battery high voltage to the lower value (12 V) with high efficiency. The DC-DC buck converter can be modelled by the following circuit.



1. Find the waveforms of the voltage across the ideal switch ( $v_s$ ) and the voltage across the inductance ( $v_L$ ). Deduce the inductance current waveform from it.

### Exercise 26: DC-DC buck converter



Assume steady-state conditions.

- 2. Express the ratio  $\frac{V_o}{F}$  in terms of the duty cycle D.
- 3. Give the value of *D* in this situation.

The current ripple  $\Delta i$  is defined as the absolute difference between the maximum of current (during a switching period) and the average current *I* (over the same switching period).

- 4. Find the expression of the inductor current ripple  $\Delta i_L$  in terms of  $V_o$ , E, D,  $T_s$  and L.
- 5. Estimate the inductor current ripple  $\Delta i_L$  for a switching frequency  $f_s = 1 \ KHz$  and an inductance of 50 mH. Compare the value of the current ripple to the value of the output current if the auxiliaries draw 12 W.

### Exercise 27: DC-DC boost converter

DC-DC converters are used to adapt two different voltage levels. In some electronic calculator, the battery voltage is set as  $V_{in} = 3 V$ , whereas the electronic parts work under  $V_{out} = 9 V$ . A DC-DC boost converter is used to increase the battery low voltage to the higher value (9 V) with high efficiency. The DC-DC boost converter can be modelled by the following circuit.



1. Find the waveforms of the voltage across the ideal switch ( $v_s$ ) and the voltage across the inductance ( $v_L$ ). Deduce the inductance current waveform from it.

## Exercise 26: DC-DC buck converter



Assume steady-state conditions.

- 2. Express the ratio  $\frac{V_{out}}{V_{in}}$  in terms of the duty cycle *D*.
- 3. Give the value of *D* in this situation.

The current ripple  $\Delta i$  is defined as the absolute difference between the maximum of current (during a switching period) and the average current *I* (over the same switching period).

- 4. Find the expression of the inductor current ripple  $\Delta i_L$  in terms of  $V_{out}$ ,  $V_{in}$ , D,  $T_s$  and L.
- 5. Estimate the inductor current ripple  $\Delta i_L$  for a switching frequency  $f_s = 30 \ KHz$  and an inductance of 75 mH. Compare the value of the current ripple to the value of the output current if the system draws  $15 \ mW$ .