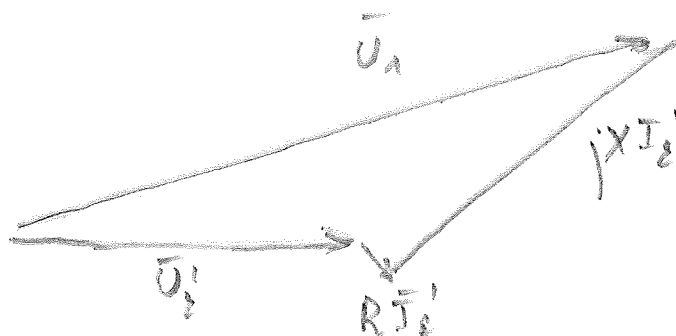


External characteristic of the transformer

- Source $\bar{U}_1$ at the primary is fixed $\bar{U}_1 = E_1 = \frac{N_1}{N_2} \bar{U}_2$
- What is the effect of connecting different kinds of loads (R, L, C)?


1°) Resistive load R_L

- Connecting a load at a circuit's terminal (here the secondary of the transformer) means giving a relationship between $\bar{U}_2'$ and $\bar{I}_2'$.
- This relationship closes the system of equations, so that one can now calculate all currents and all voltages and draw the phaser phaser diagram of the considered working point / with the considered passive load
- Resistive load $\Rightarrow \bar{U}_2' = R_L' \bar{I}_2'$



is NOT the phaser diagram of a transformer with a resistive load
WHY?

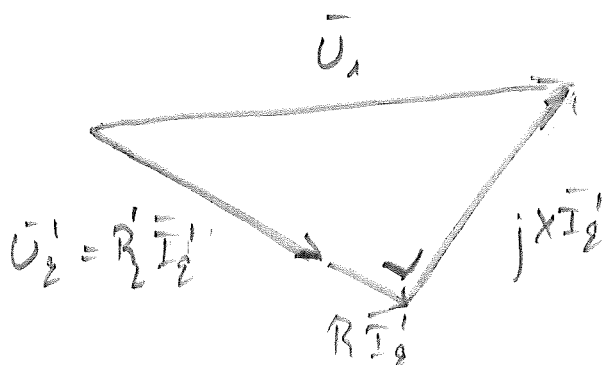This is the phasor diagram of a transformer with a resistive load



Now for the rest of the discussion in the exterior characteristic, one remembers that:

$$R \ll X \quad \text{at least a factor 10 both in } R$$

phasor diagrams contain anyway inaccuracies due to the simplifications made along the way

phasor diagrams are useful if they are simple


$\Rightarrow$ one neglects $R_1 I_1$

X (leakage) is the main characteristic that makes a transformer a real transformer (if one also neglects $X \ll X_m$ the transformer is ideal!)

So for a resistive load, one has

$$\bar{U}_1 = \bar{U}_2' + jX \bar{I}_2' \text{ with } \bar{U}_2' = R_L' \bar{I}_2'$$

phasors

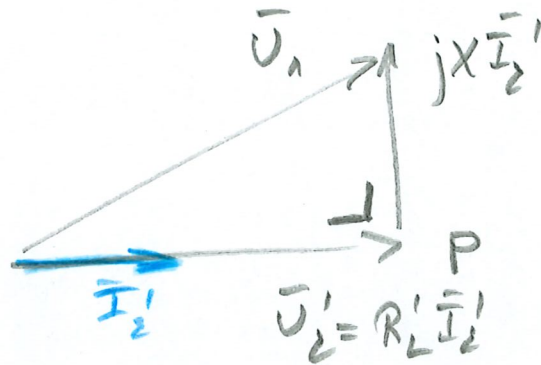


$\varphi_2 = 0$
because purely
resistive load

Pythagora: $U_1^2 = (U_2')^2 + (X I_2')^2$


with $|\bar{Z}| = Z$ as notation for the modulus
of a phasor.

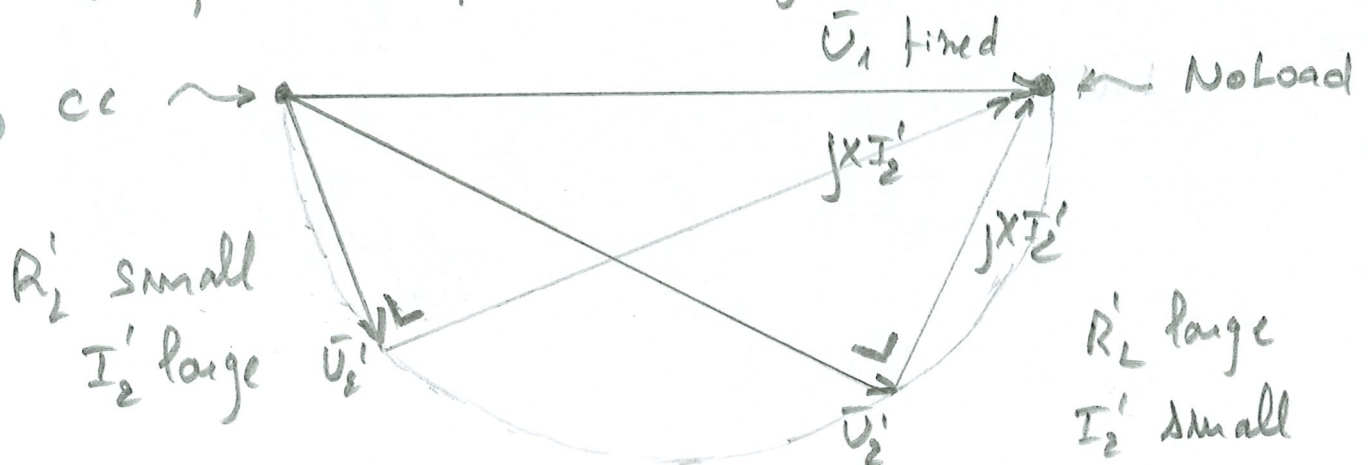Now, what if one changes the value of R_L' ?



The locus of the tip of the $\bar{U}_2'$ phasor is
a half circle.

Exterior characteristic

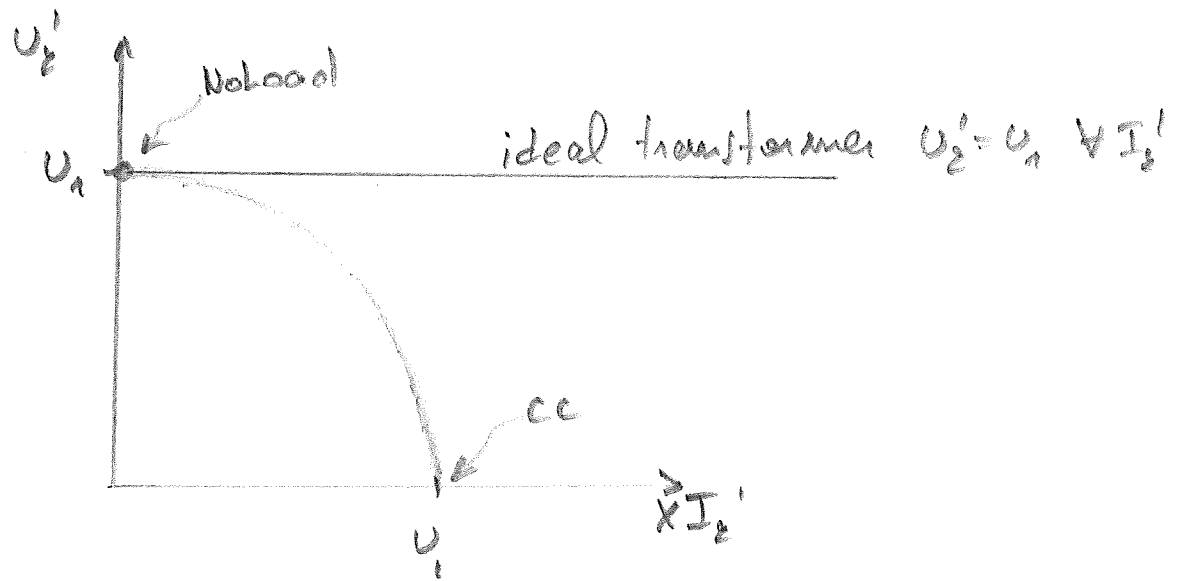

cc: $X I_2' = U_1$ and $U_2' = 0$

$$\Rightarrow (I_2')_{cc} = \frac{U_1}{X}$$

No Load: $U_1 = U_2'$ and $I_2' = 0$

Remark: Short circuit (cc) does not mean $I_2' \rightarrow \infty$ but rather

$$I_2' = \frac{U_1}{X}$$

As X is a small impedance, this current is already large, and in particular larger than the nominal current of the transformer.

A transformer is not designed to operate at the cc working point.

2°) Inductive Load X_L'

(Don't mix up X and X_L')

$$\bar{U}_2' = jX_L' \bar{I}_2' \quad \text{and} \quad \bar{U}_1 = \bar{U}_2' + jX \bar{I}_2'$$


Phasors



$\varphi_2 = +\frac{\pi}{2}$
because purely
inductive load

$$U_1^2 = (U_2' + X I_2')^2 \Rightarrow U_1 = U_2' + X I_2'$$


Exterior characteristic

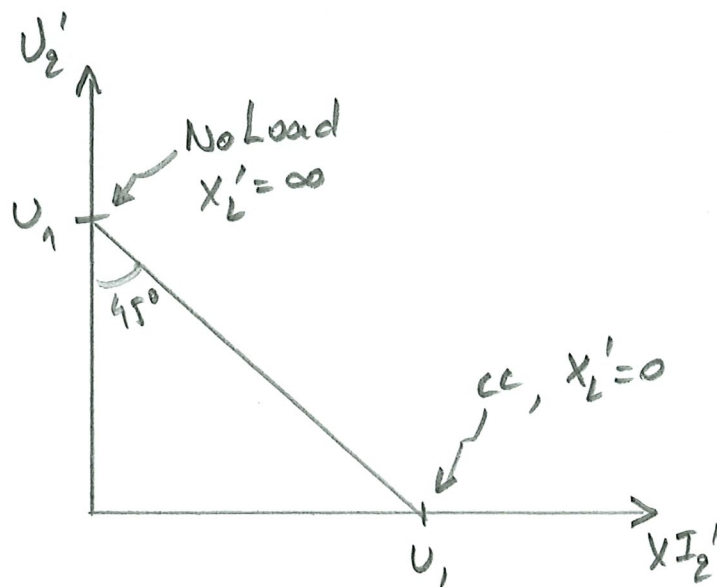

$$(I_2')_{cc} = \frac{U_1}{X}$$

$$\textcircled{*} \quad X_L' + X \leq 0 \quad \frac{\mu^2}{\omega C} \geq X$$
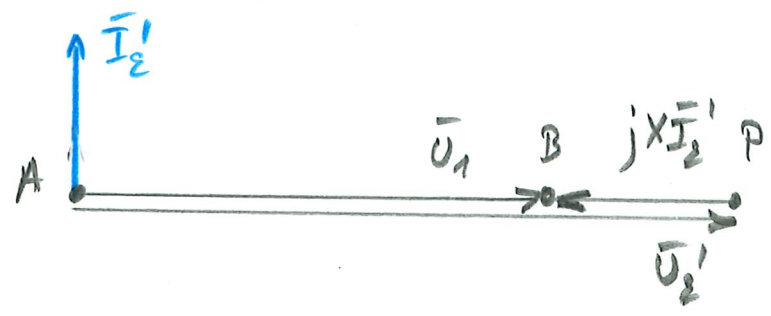
$$U_1 = -(X_L' + X) I_2' = U_2' - X I_2' \Rightarrow U_2' = U_1 + X I_2'$$



$\bar{I}_2'$ is ahead of $\bar{U}_2'$ by $\frac{\pi}{2}$
($\phi_2 = -\frac{\pi}{2}$)

No Load: $P \rightarrow B$, $X_L' \rightarrow \infty$ and $C = 0$

$$I_2' = 0, \quad U_1 = U_2'$$

Resonance: $X_L' + X = 0$

$P \rightarrow \infty$ towards right

$$I_2' = \frac{U_1}{X_L' + X} \rightarrow \infty$$

External characteristic

resonance: $\frac{\mu^2}{\omega C} = X$

