



Electromagnetic Energy Conversion

ELEC0431

AC reminder

15 March 2022

Florent Purnode (florent.purnode@uliege.be) – Nicolas Davister (ndavister@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,
University of Liège, Belgium



Basics of DC circuits: $V = RI$

In general, three fundamental values:

- The tension V [volt]
- The current I [amp]
- The impedance R [Ω]

And the relation:


$$V = RI$$

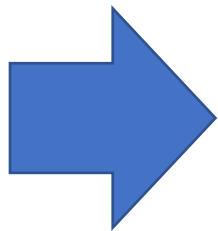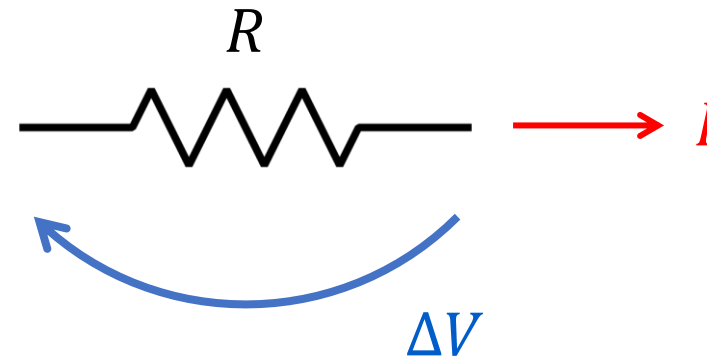

Two other important laws: Kirchhoff's laws

Basics of DC circuits: Kirchhoff's first law*

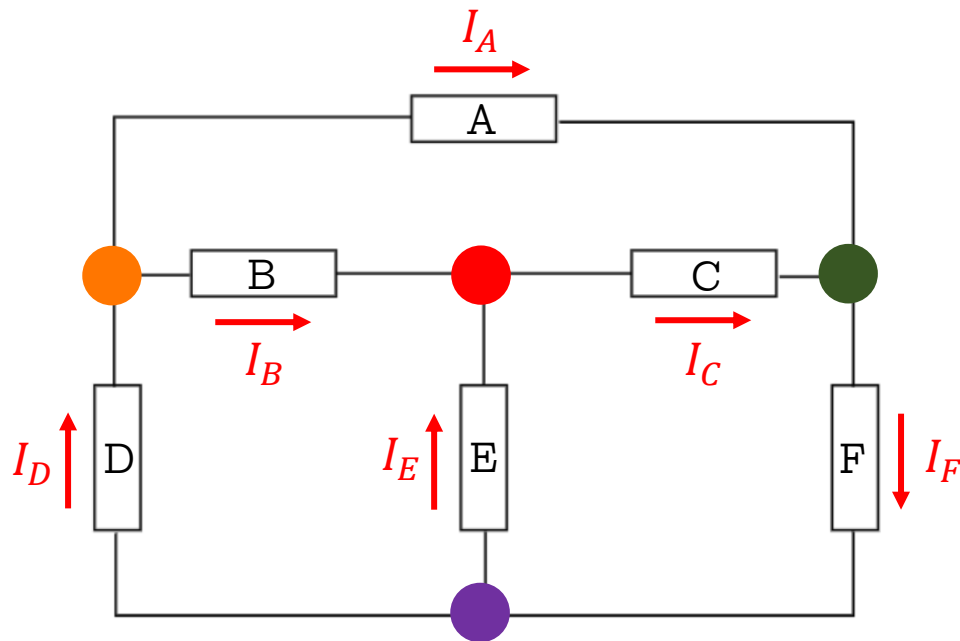At any junction in the electrical circuit, the sum of currents flowing into the junction is equal to the sum of currents flowing out of the junction



● $I_D = I_A + I_B$

● $I_B + I_E = I_C$

● $I_A = I_C + I_F$


● $I_F = I_E + I_D$

The values I can be negative. The important is to choose a convention and to stick with it !

*Assuming localised electrical circuit (which is true for all the exercises presented in this class)

Basics of DC circuits: Kirchhoff's second law*

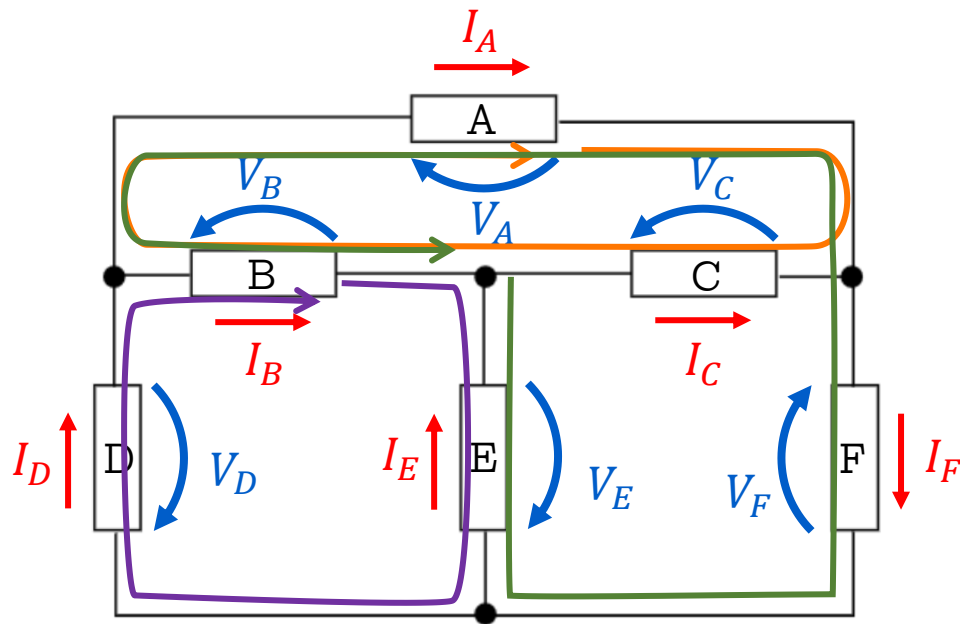Around any closed loop in a circuit, the directed sum of potential differences across components is zero



$$V_E - V_D - V_B = 0$$

$$V_C + V_B - V_A = 0$$

$$V_E + V_F + V_A - V_B = 0$$


...

The values V can be negative. The important is to choose a convention and to stick with it !

*Assuming localised electrical circuit (which is true for all the exercises presented in this class)

Basics of DC circuits: Applying Kirchhoff's laws
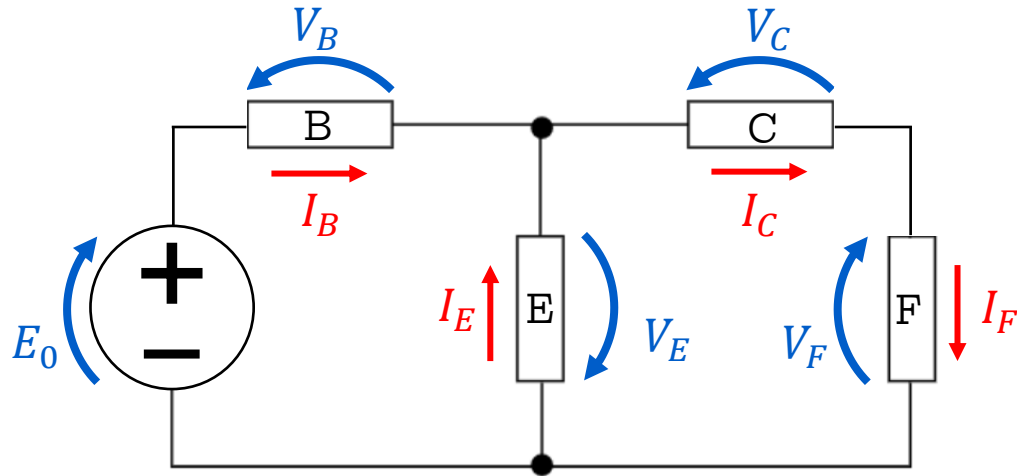
$$E_0 = 6V, R_B = 25\Omega, R_C = 8\Omega, R_E = 10\Omega, R_F = 2\Omega$$



Kirchhoff's first law:

- $I_B + I_E = I_C$
- $I_C = I_F$


Kirchhoff's second law:

- $E_0 - V_B + V_E = 0$
 $\Rightarrow E_0 - I_B R_B + I_E R_E$
- $-V_E - V_C - V_F = 0$
 $\Rightarrow I_E R_E + I_C R_C + I_F R_F = 0$

Answer:


$$I_B = 0.2A, I_C = 0.1A, I_E = -0.1A, I_F = 0.1A$$

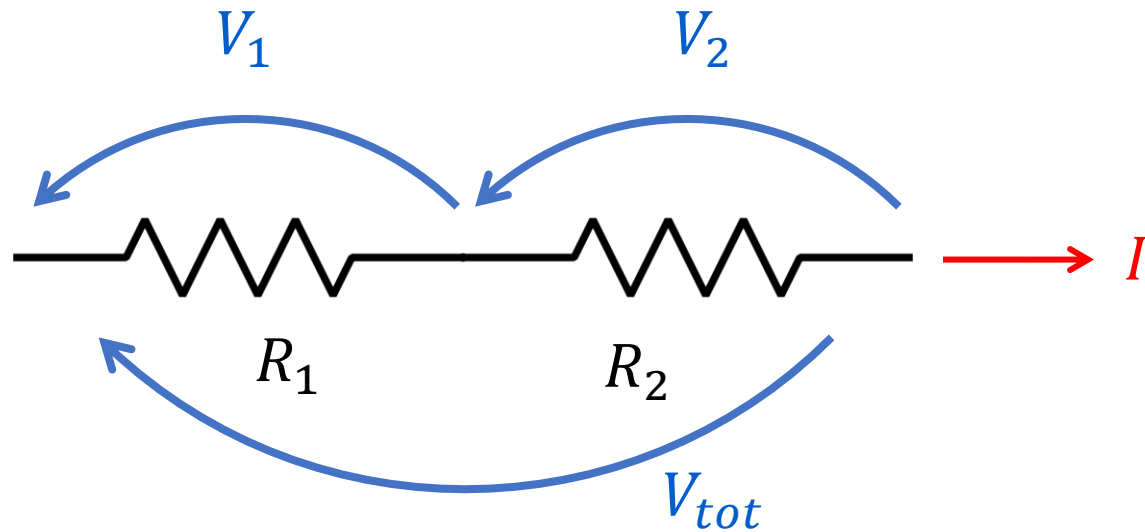Basics of DC circuits: resistors in series




$$\begin{aligned} V_{tot} &= V_1 + V_2 \\ &= I R_1 + I R_2 \\ &= I (R_1 + R_2) \end{aligned}$$

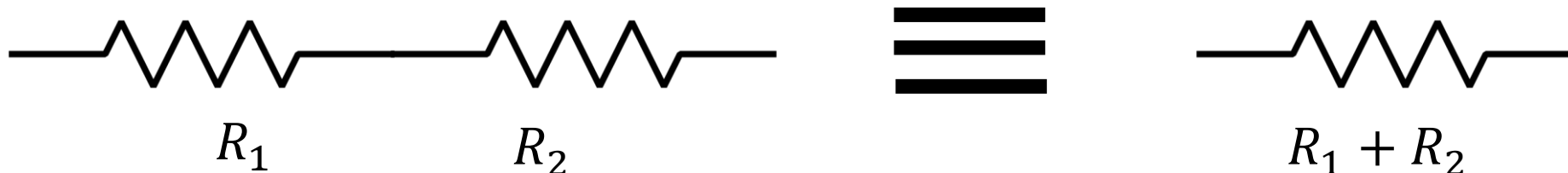Two resistors R_1 and R_2 in series act like one resistor $R_{tot} = (R_1 + R_2)$




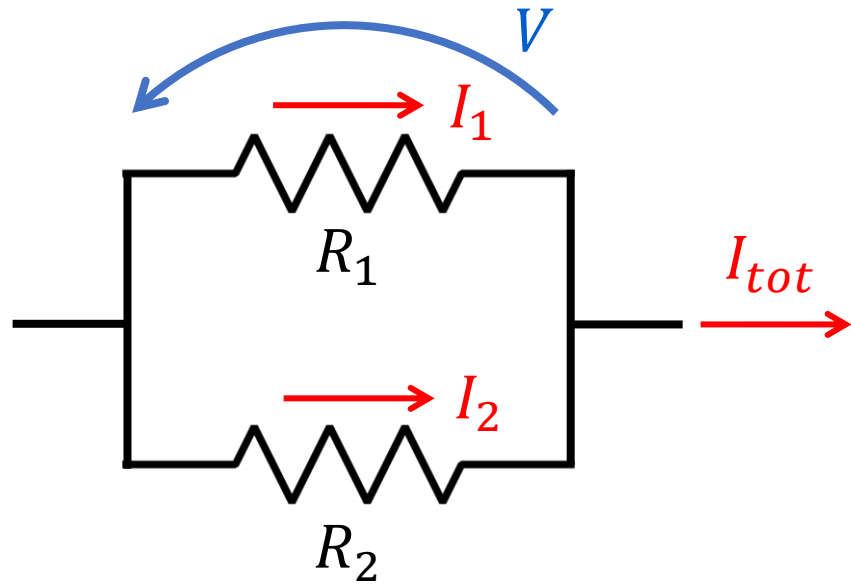Basics of DC circuits: resistors in parallel




$$\begin{aligned} I_{tot} &= I_1 + I_2 \\ &= \frac{V}{R_1} + \frac{V}{R_2} \\ \Rightarrow V &= \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} I \end{aligned}$$

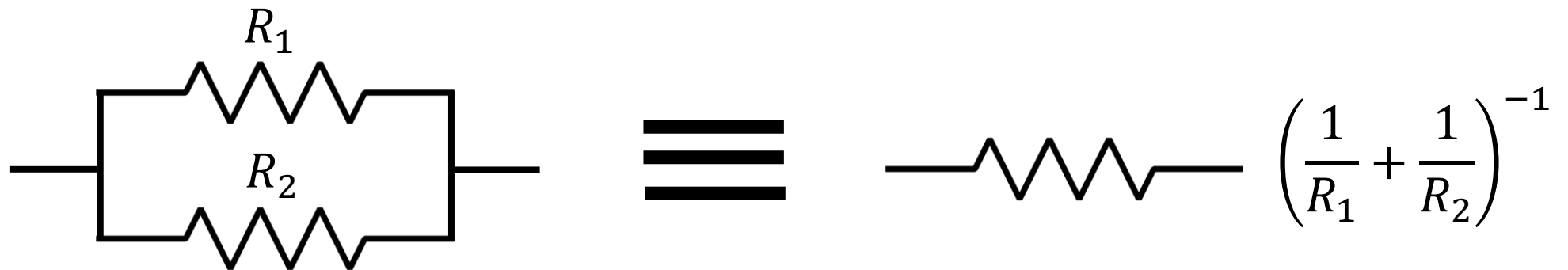Two resistors R_1 and R_2 in parallel act like one resistor $R_{tot} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$




Basics of DC circuits: Applying Kirchhoff's laws
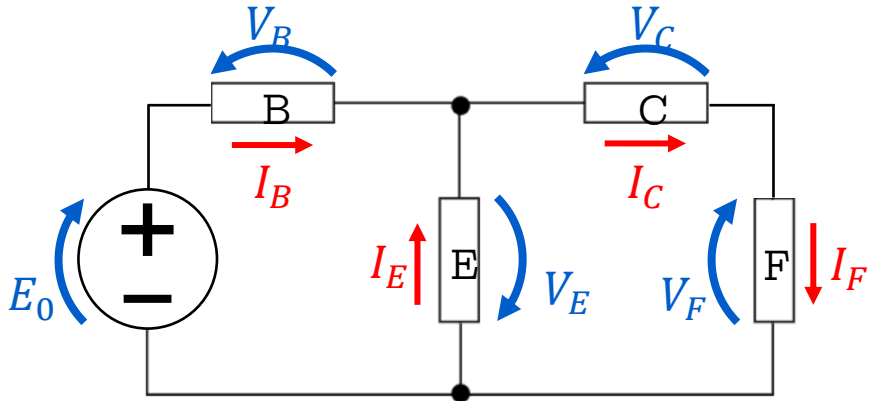
$$E_0 = 6V, R_B = 25\Omega, R_C = 8\Omega, R_E = 10\Omega, R_F = 2\Omega$$




R_C and R_F
in series

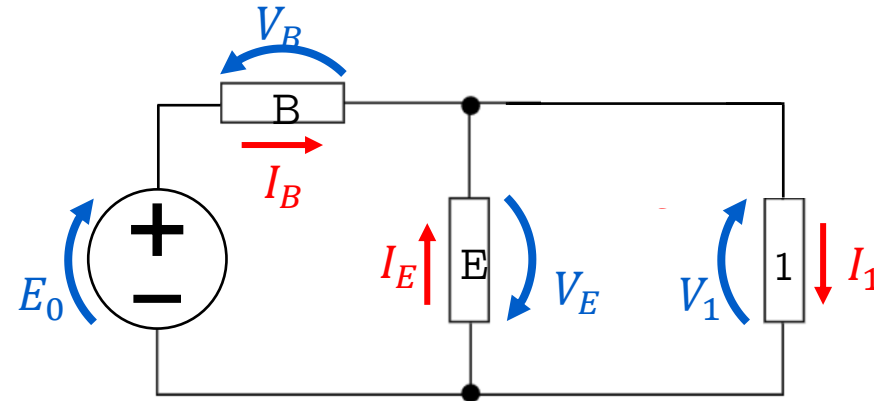


$$\begin{aligned} R_1 &= R_C + R_F \\ &= 8 + 2 \\ &= 10 \Omega \end{aligned}$$

R_E and R_1
in parallel

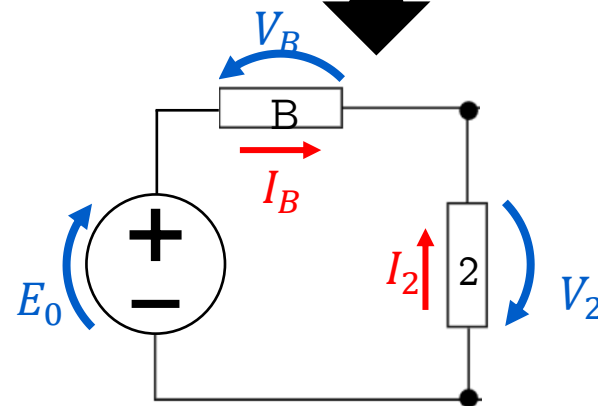

$$\begin{aligned} R_2 &= \left(\frac{1}{R_1} + \frac{1}{R_E} \right)^{-1} \\ &= \left(\frac{1}{10} + \frac{1}{10} \right)^{-1} = 5\Omega \end{aligned}$$


R_B and R_2
in series

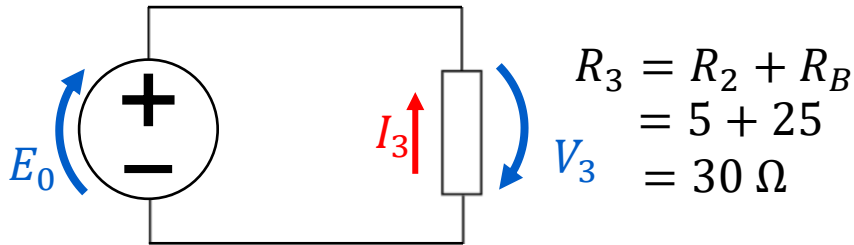

$$\begin{aligned} R_3 &= R_2 + R_B \\ &= 5 + 25 \\ &= 30 \Omega \end{aligned}$$

$$\Rightarrow I_B = \frac{E_0}{R_3} = \frac{6}{30} = 0,2 A$$

AC circuits: the capacitor

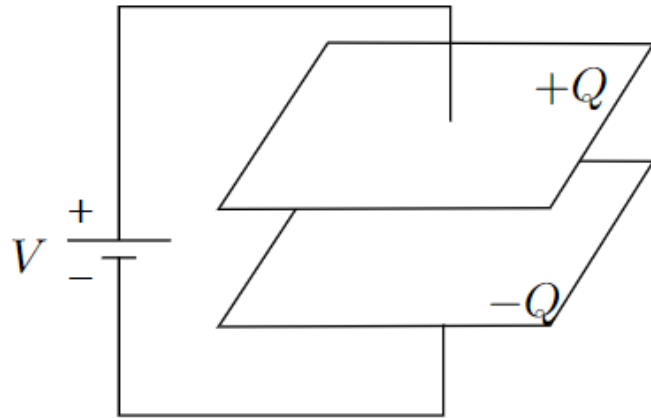

Two parallel conductive plates of surface S , placed a distance d apart and carrying charges equal and opposite $\pm Q$.

The charges give rise to a potential difference V between the plates.


The capacity of the capacitor is defined as:

$$C = \frac{Q}{V}$$

AC circuits: the capacitor

$C = \frac{Q}{V}$ If V increases \rightarrow Q increases \rightarrow a movement of charges is a current

$$q(t) = \int_{-\infty}^t i(x) dx$$

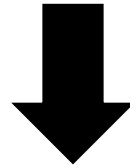

$$u(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau \quad \& \quad i(t) = C \frac{du(t)}{dt}$$

AC circuits: the inductor




$$i(t) = \frac{1}{L} \int_{-\infty}^t u(\tau) d\tau$$

$$u(t) = L \frac{di(t)}{dt}$$

AC circuits: the inductor

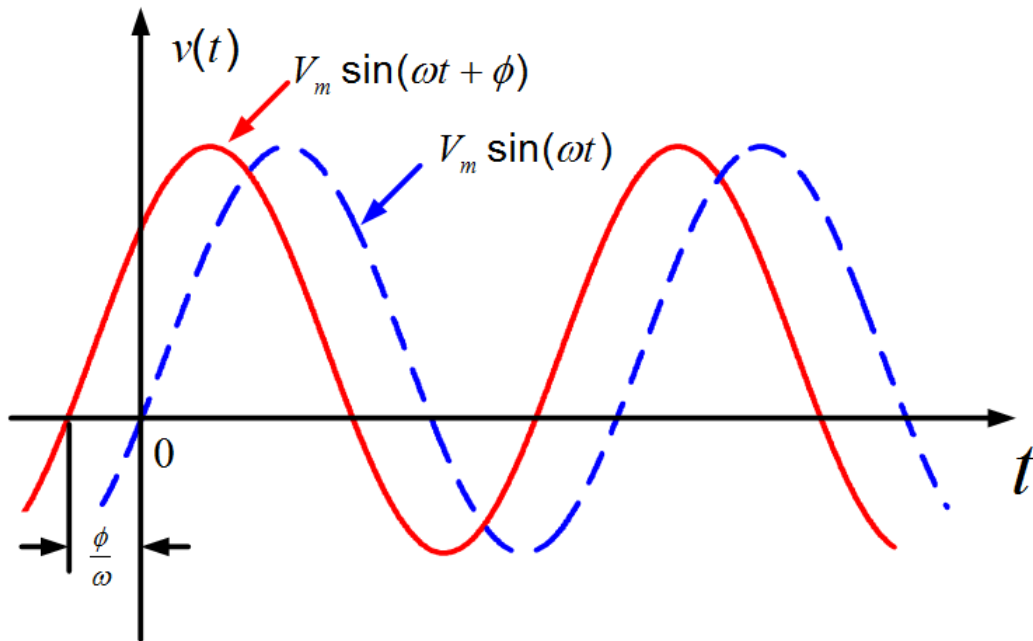In “Electromagnetic energy conversion”, we deal only with sinusoidal excitations:



What does it gives for:


- A resistor ?
- A capacitor ?
- An inductor ?

AC circuits: sinusoidal excitations and resistor


We consider a cosine wave $I(t) = I_m \cos(2\pi ft)$.

For a resistor, the constitutive law is $V = RI$

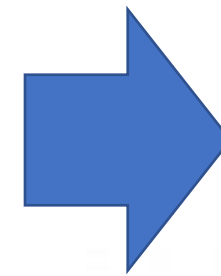
$$\rightarrow V(t) = R I(t) = R I_m \cos(2\pi ft)$$




V and I are in phase

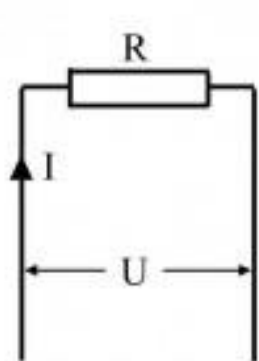

(a)

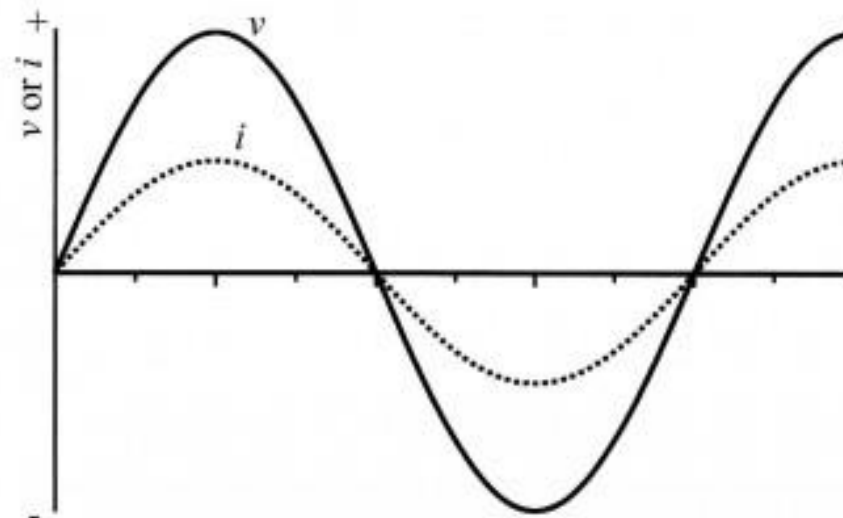

(b)

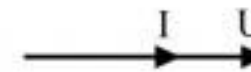

(c)

AC circuits: sinusoidal excitations and capacitor


We consider a cosine wave $V(t) = V_m \cos(2\pi ft)$.

For a capacitor, the constitutive law is $I(t) = C \frac{dV(t)}{dt}$


$$\rightarrow I(t) = C \frac{dV(t)}{dt} = C \frac{d}{dt} (V_m \cos(2\pi ft)) = -C 2\pi f V_m \sin(2\pi ft) = 2\pi f C V_m \cos\left(2\pi ft + \frac{\pi}{2}\right)$$

$$\rightarrow I_m \cos\left(2\pi ft - \frac{\pi}{2}\right) = 2\pi f C V_m \cos(2\pi ft)$$
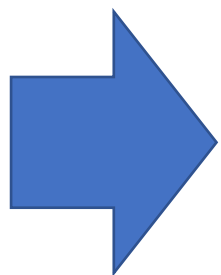
$$\rightarrow V(t) = \frac{1}{2\pi f C} I_m \cos\left(2\pi ft - \frac{\pi}{2}\right)$$



V lags I by 90°

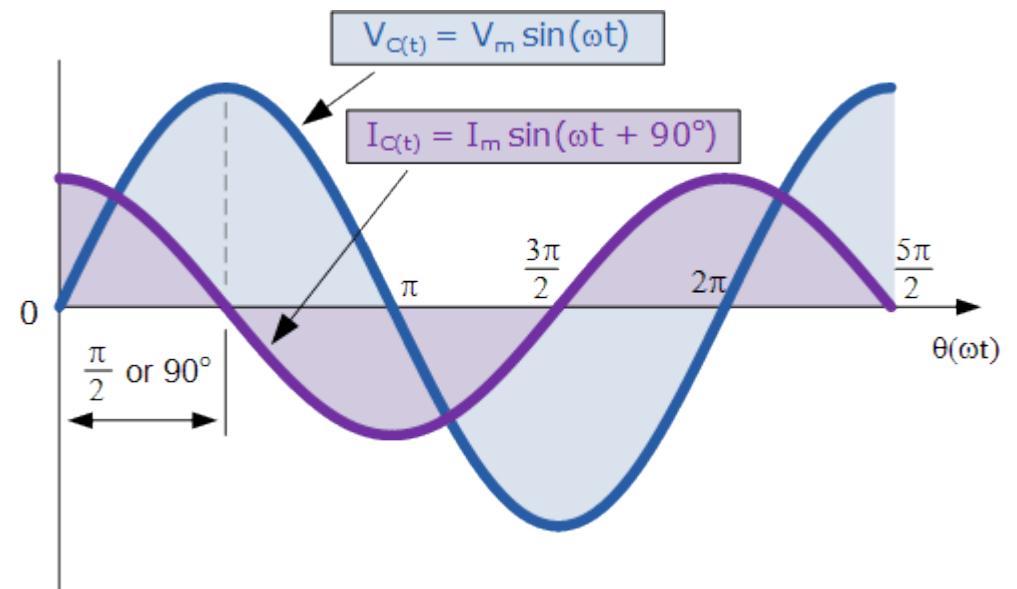


AC circuits: sinusoidal excitations and capacitor


We consider a cosine wave $I(t) = I_m \cos(2\pi ft)$.

For an inductor, the constitutive law is $V(t) = L \frac{dI(t)}{dt}$
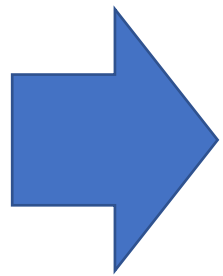
$$\rightarrow V(t) = L \frac{dI(t)}{dt} = L \frac{d}{dt} (I_m \cos(2\pi ft)) = -L 2\pi f I_m \sin(2\pi ft) = 2\pi f L I_m \cos\left(2\pi ft + \frac{\pi}{2}\right)$$



I lags V by 90°

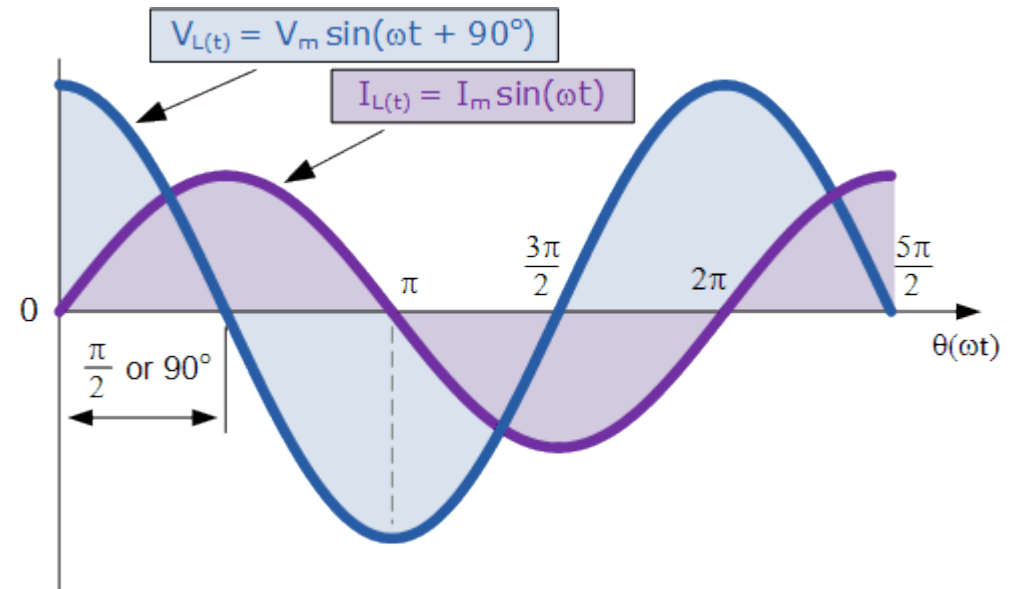

AC circuits: introduction to phasors

We found three relations:

- $V_R(t) = R I_m \cos(\omega t)$
 - $V_C(t) = \frac{1}{\omega C} I_m \cos(\omega t - \frac{\pi}{2})$
 - $V_L(t) = \omega L I_m \cos(\omega t + \frac{\pi}{2})$
- where $\omega = 2\pi f$


Let's now introduce phasors ☺

$$\begin{aligned} I(t) &= I_m \cos(\omega t + \varphi) = \sqrt{2} I \cos(\omega t + \varphi) \\ &= \mathbb{R}(\sqrt{2} I e^{j(\omega t + \varphi)}) = \mathbb{R}(\sqrt{2} I e^{j\varphi} e^{j\omega t}) \end{aligned} \quad \left. \vphantom{\begin{aligned} I(t) &= I_m \cos(\omega t + \varphi) \\ &= \mathbb{R}(\sqrt{2} I e^{j(\omega t + \varphi)}) \end{aligned}} \right\} e^{\pm j\theta} = \cos(\theta) \pm j \sin(\theta)$$



For a given frequency f (and thus given pulsation ω), **the phasor of $I(t)$ is a complex number with an amplitude I and phase angle φ .**

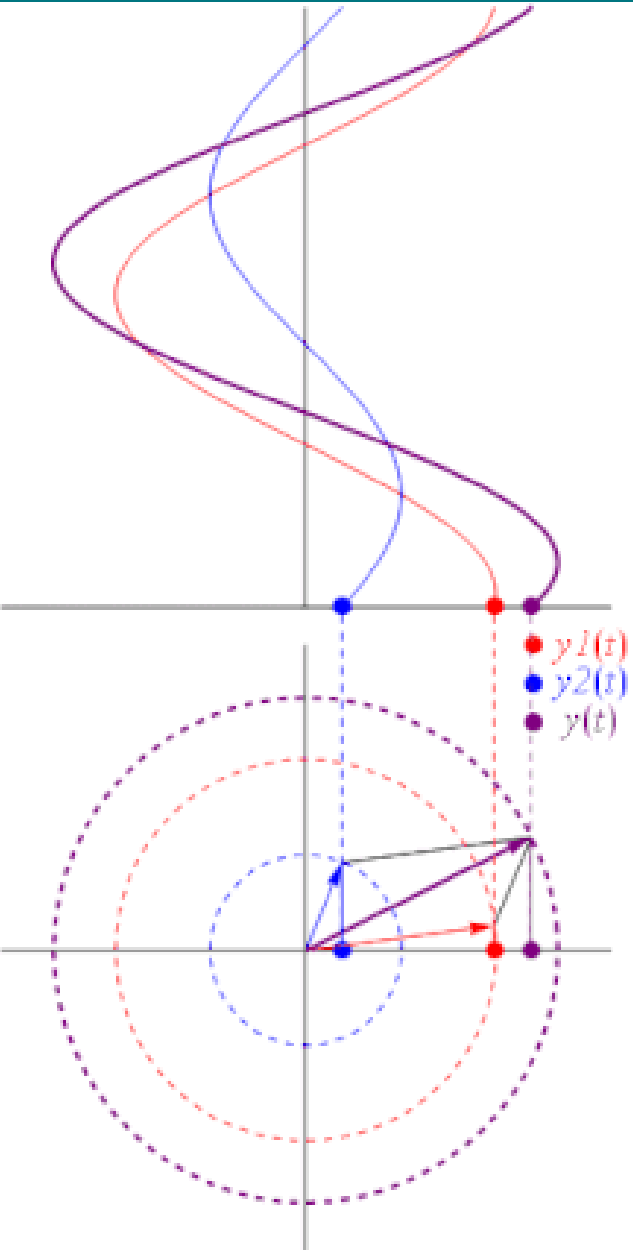AC circuits: “phasor is good, phasor is life”




For signals evolving at a same frequency, phasors are like a snapshot representation containing all the necessary information (phase angle and amplitude) and allowing easy computations.

AC circuits: phasor for a resistor

What do we get when we apply phasors to our relations ?

- $V_R(t) = R I_m \cos(\omega t)$
- $V_C(t) = \frac{1}{\omega C} I_m \cos(\omega t - \frac{\pi}{2})$
- $V_L(t) = \omega L I_m \cos(\omega t + \frac{\pi}{2})$
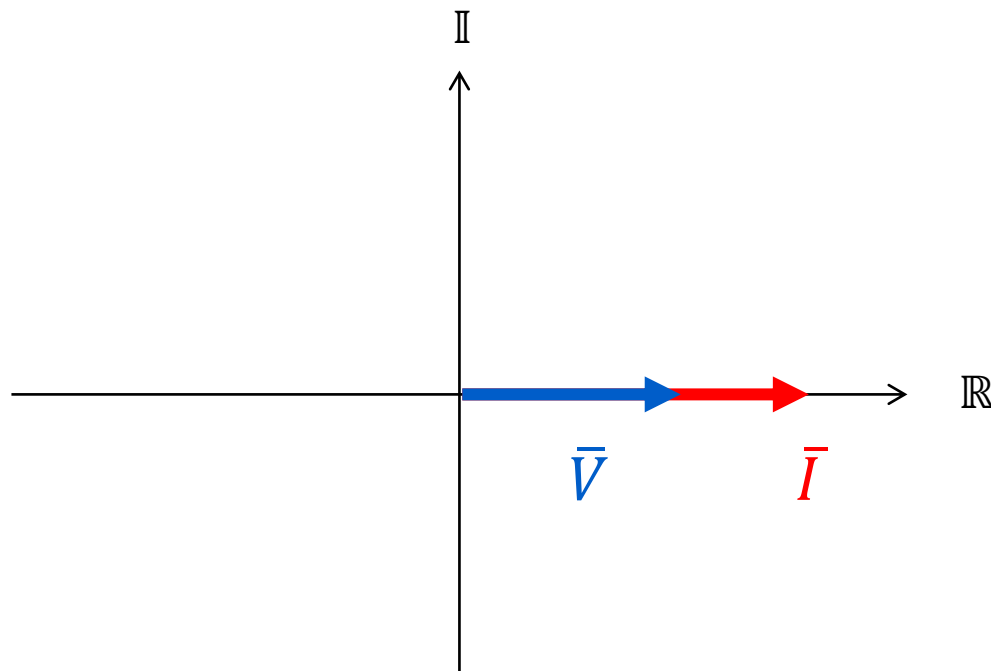
$$I(t) = I_m \cos(\omega t + \varphi) \Rightarrow \bar{I} = I e^{j\varphi}$$




Through the resistor, we have a current $I(t) = I_m \cos(\omega t)$ which generates a voltage $V(t) = R I_m \cos(\omega t)$

AC circuits: phasor for a capacitor

What do we get when we apply phasors to our relations ?

- $V_R(t) = R I_m \cos(\omega t)$
- $V_C(t) = \frac{1}{\omega C} I_m \cos(\omega t - \frac{\pi}{2})$
- $V_L(t) = \omega L I_m \cos(\omega t + \frac{\pi}{2})$
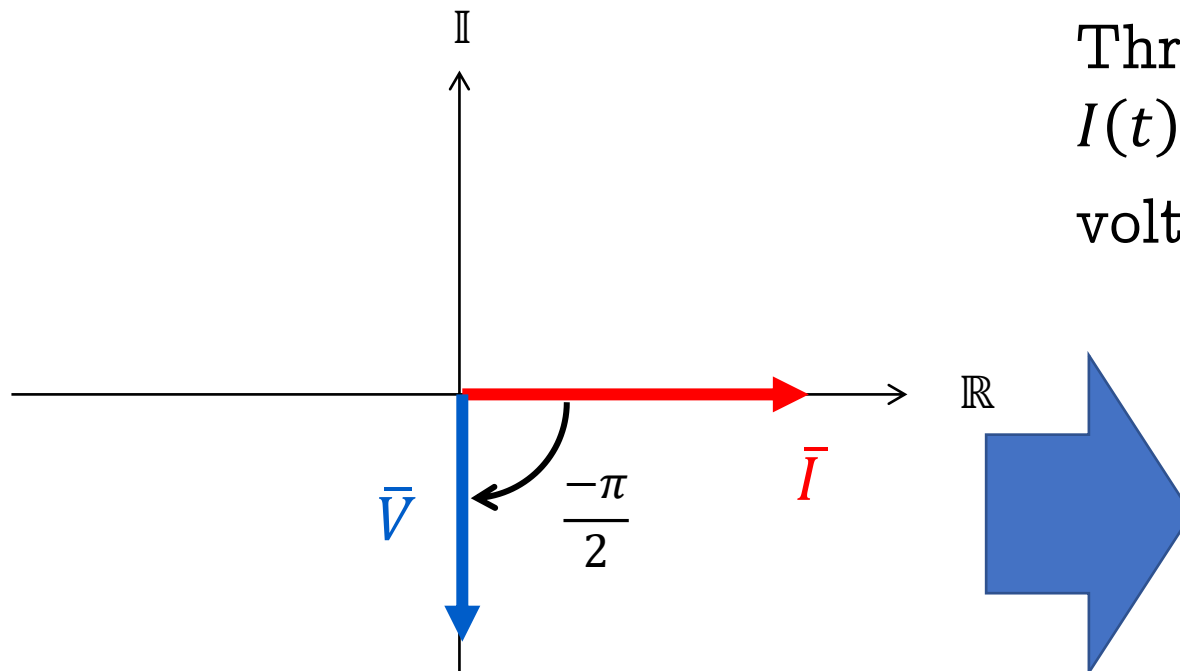
$$I(t) = I_m \cos(\omega t + \varphi) \Rightarrow \bar{I} = I e^{j\varphi}$$



Through the capacitor, we have a current $I(t) = I_m \cos(\omega t)$ which generates a voltage $V(t) = \frac{1}{\omega C} I_m \cos(\omega t - \frac{\pi}{2})$

In an complex graph, this is equivalent to multiply \bar{I} by


$$\frac{-j}{\omega C} = \frac{1}{j\omega C}$$

AC circuits: phasor for an inductor

What do we get when we apply phasors to our relations ?

- $V_R(t) = R I_m \cos(\omega t)$
- $V_C(t) = \frac{1}{\omega C} I_m \cos(\omega t - \frac{\pi}{2})$
- $V_L(t) = \omega L I_m \cos(\omega t + \frac{\pi}{2})$
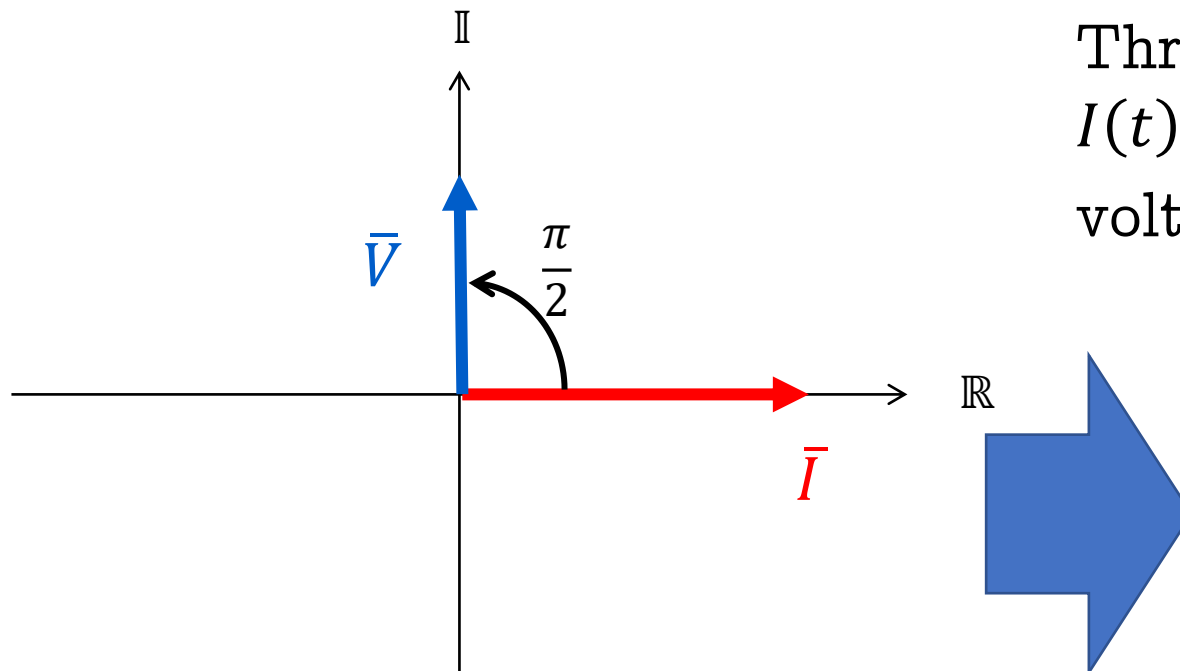
$$I(t) = I_m \cos(\omega t + \varphi) \Rightarrow \bar{I} = I e^{j\varphi}$$



Through the inductor, we have a current $I(t) = I_m \cos(\omega t)$ which generates a voltage $V(t) = \omega L I_m \cos(\omega t + \frac{\pi}{2})$

In an complex graph, this is equivalent to multiply \bar{I} by $j\omega L$

AC circuits: Impedance

For DC circuits, we have the relation $V = RI$. This relation is adapted for AC and phasors with:

$$\bar{V} = Z \bar{I}$$

where:

- $Z = R$ for a resistor
- $Z = \frac{1}{j\omega C}$ for a capacitor
- $Z = j\omega L$ for an inductor

If you know DC and phasors (complex numbers) you know AC.

Exercise 1: voltage distribution

The circuit of Figure 1 presents a resistive-inductive load powered with an AC generator of sinusoidal voltage (230 V, 50 Hz). Find the voltages across R and L (magnitude and phase angle) and represent all the voltages on a phasor diagram.

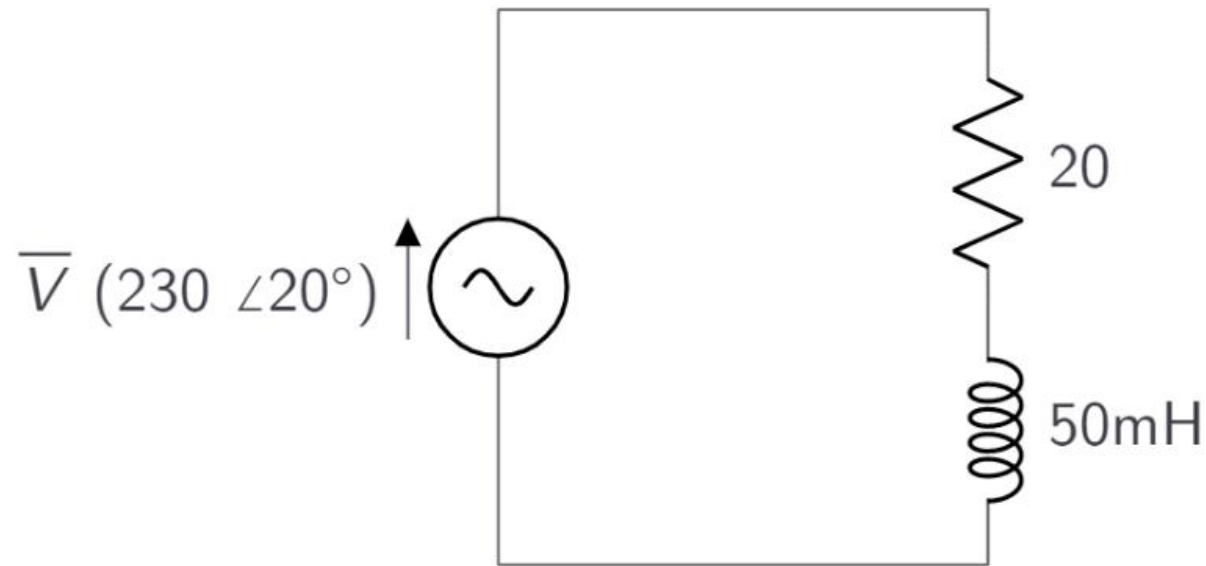


Figure: Resistive-inductive circuit.