

Tutorial 11

A performance oriented β -machine


December 13, 2016

ULg0X is slow !

- Instruction are implemented using microcode in ULg0X machines
- Microcode is a step-by-step implementation of the instruction
- Each used phase of the microcode consumes one clock cycle
- At worst:
 - 16 clock cycles on ULg01 and ULg02 per instruction
 - 32 clock cycles on ULg03 per instruction (when there are only cache hits)
 - Even worse on cache misses as we have to execute a whole procedure !
- Can we do better ?

We can do better !

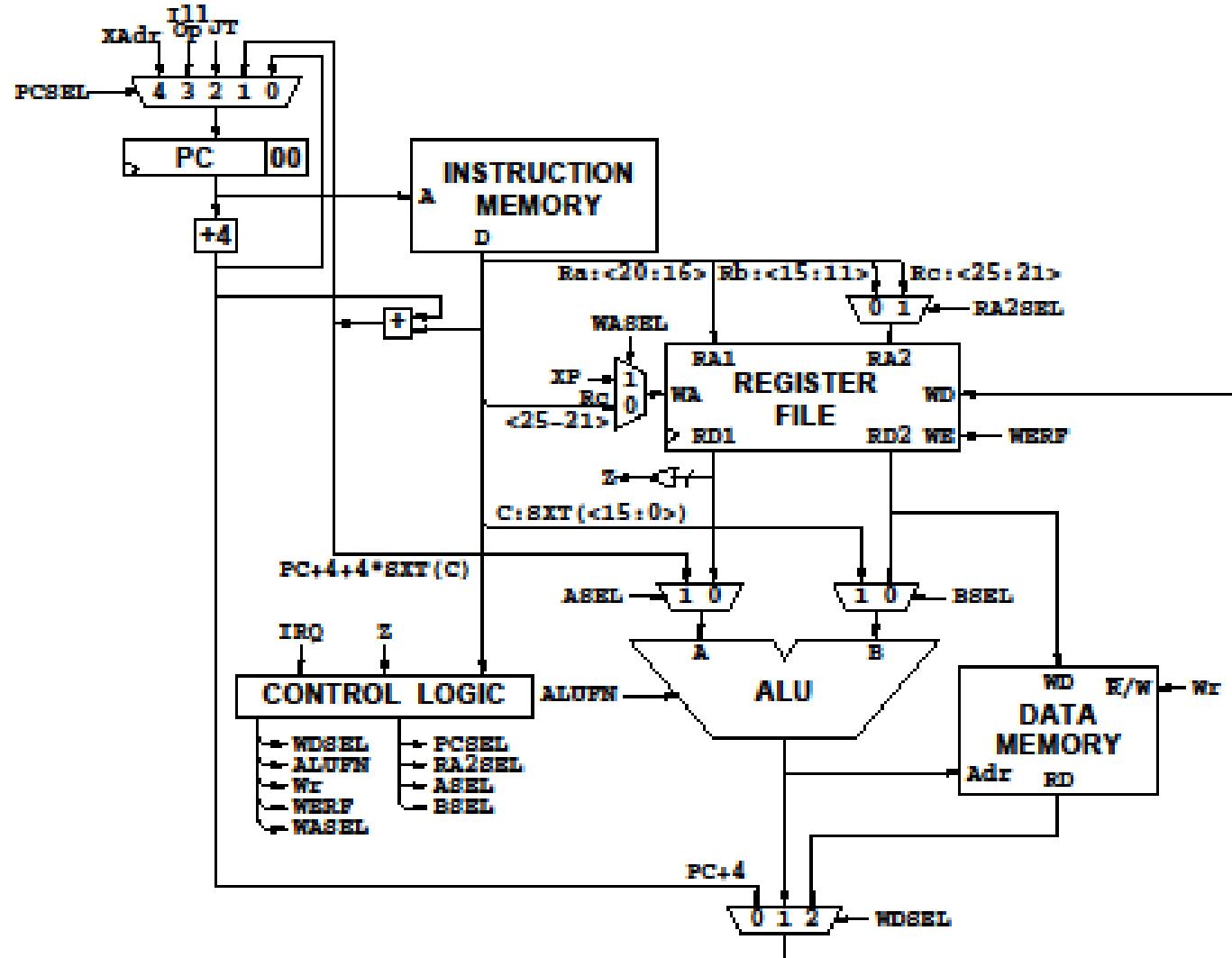- Solution: the **performance oriented β -machine** !
- Everything is executed in one clock cycle
- No more microcode




Performance oriented β -machine

- Several data transfer path
- Components' inputs are connected to multiplexers (can use signals from several sources)
- **Register file**: two reads and one write at the same time on the registers!
- Managed by a control logic component (implemented by a ROM or a PLA)
- The control logic controls the inputs and outputs of the components
- Data memory and instruction memory viewed as separate (implemented by caches)

Limitations

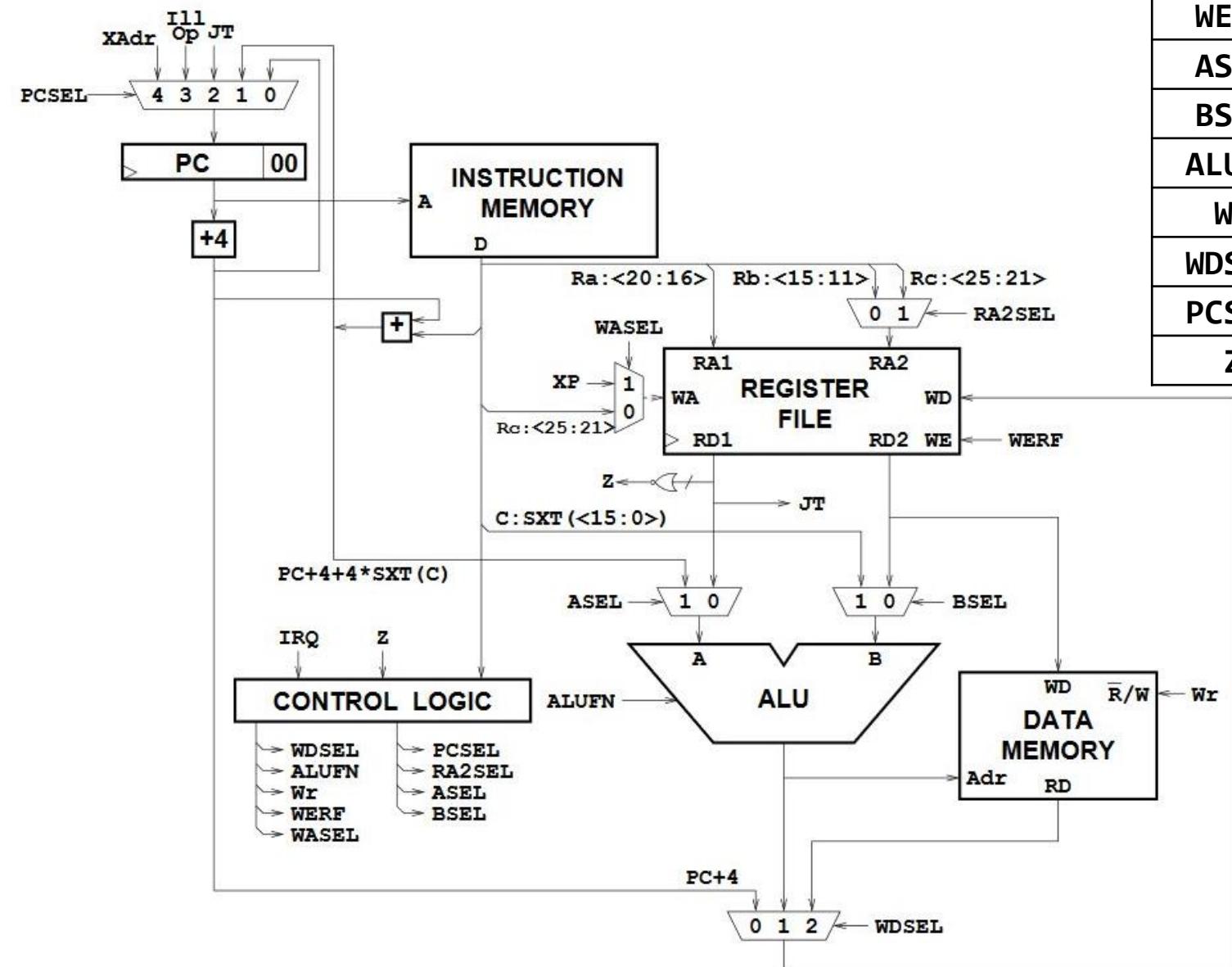- No supervisor mode
- Virtual memory not taken into account
- The circuit has a **long stabilization time**. The machine must operate at a smaller frequency than $ULg0X$.
- A solution to this last limitation is a pipeling (more about this next week)



Signals	Meaning
RA2SEL	Second register read address selection
WASEL	Register write address selection
WERF	Register write enabled
ASEL	ALU A input selection
BSEL	ALU B input selection
ALUFN	ALU function selection
Wr	Memory write enabled
WDSEL	Register write input selection
PCSEL	PC update input selection
Z	1 if RD1 is zero, 0 otherwise