



# Electromagnetic Energy Conversion

## ELEC0431

### Exercise session 6: Synchronous machines

14 March 2025

Florent Purnode (florent.purnode@uliege.be)

Montefiore Institute, Department of Electrical Engineering and Computer Science,  
University of Liège, Belgium

# Laboratory schedule

The table below presents the laboratory schedule (also available on the class webpage). There are four laboratories:

1. Transformer

2. Synchronous machines

3. Asynchronous machines

4. DC machines

**All laboratory sessions start at 8:30** and last at most 4 hours (up to 12:30). They take place in the “pyramid” ([building in front of the cafeteria of Montéfiore](#)). During these laboratories, you will have to follow the steps presented in the laboratory manual (soon available on the course website), student monitors will be present to guide you and answer your questions. You are asked to prepare each lab session by reading carefully beforehand the corresponding lab manual. Note that you will have to answer individually a quick evaluation (focusing only on concepts seen during the laboratory) at the end of each laboratory. Each evaluation represents 3.75 % of your final grade. That is 15 % of the grade for the four laboratories.

Group n°	Member 1	Member 2	Member 3	Member 4	Mon. 31 Mar.	Mon. 7 Apr.	Mon. 14 Apr.	Wed. 16 Apr.	Fri. 18 Apr.	Wed. 23 Apr.	Fri. 25 Apr.	Mon. 5 May	Wed. 7 May	Fri. 9 May	Wed. 14 May	Fri. 16 May
1	s224403	s222464	s222404	s221732	1	2						4				3
2	s221964	s224003	s224339	s224390				2		1	4		3			
3	s224695	s224930	s222056	s222878			1	3					2			4
4	s211223	s214765	s212198	s212585		3			1	2					4	
5	s221348	s221999	s221067	s224324		1	3						4			2
6	s223458	s222338	S221838	s221223				4			1	2			3	
7	s2409461	s214400	s2306485	s204049			4				2	3		1		
8	s213656	s220802	s220979	s211815					4		3			2		1
9	s215116	s224317	s210844	s216862		4				3			1		2	
10	s224802	s221224	s216230	s224693	2			1	3					4		
11	s2306965	s2409345	s203101	s222320	4				2			1		3		
12	s205570	s225656	s222644	s222641	3		2			4					1	

An active participation to the laboratories is the best way to experiment and to understand the important concepts of the course. Do not miss this opportunity, you are encouraged to ask questions whenever you encounter difficulties.

Please also note that **Laboratories are mandatory** (in the event of an unexcused absence, an absence grade will be given for the entire course).

# In this class...

➤ Exercise 10

# Exercise 10: Constant air gap alternator


Several alternators are used on airplanes which, coupled to the reactors, feed all the necessary onboard electrical grids. Those alternators are characterized by a higher generated voltage-and-current frequency compared to alternators coupled to 50 Hz or 60 Hz electrical grids. Moreover, due the variable speed of the airplane reactors, the delivered frequency is not constant.

In nominal regime, the main-alternator shaft rotates at a speed  $\dot{\theta}_n = 11\,100$  RPM, the frequency of the delivered voltages and currents is  $f = 370$  Hz, the nominal apparent power is  $|S_n| = 150$  kVA and the RMS phase voltage is  $V_n = 115$  V.

The rotation speed of the reactor  $\dot{\theta}_e$  varies from 4160 RPM to 9000 RPM. The alternator is coupled to the reactor through a gear box of ratio


$$k_m = \frac{\dot{\theta}}{\dot{\theta}_e} = 2.67.$$

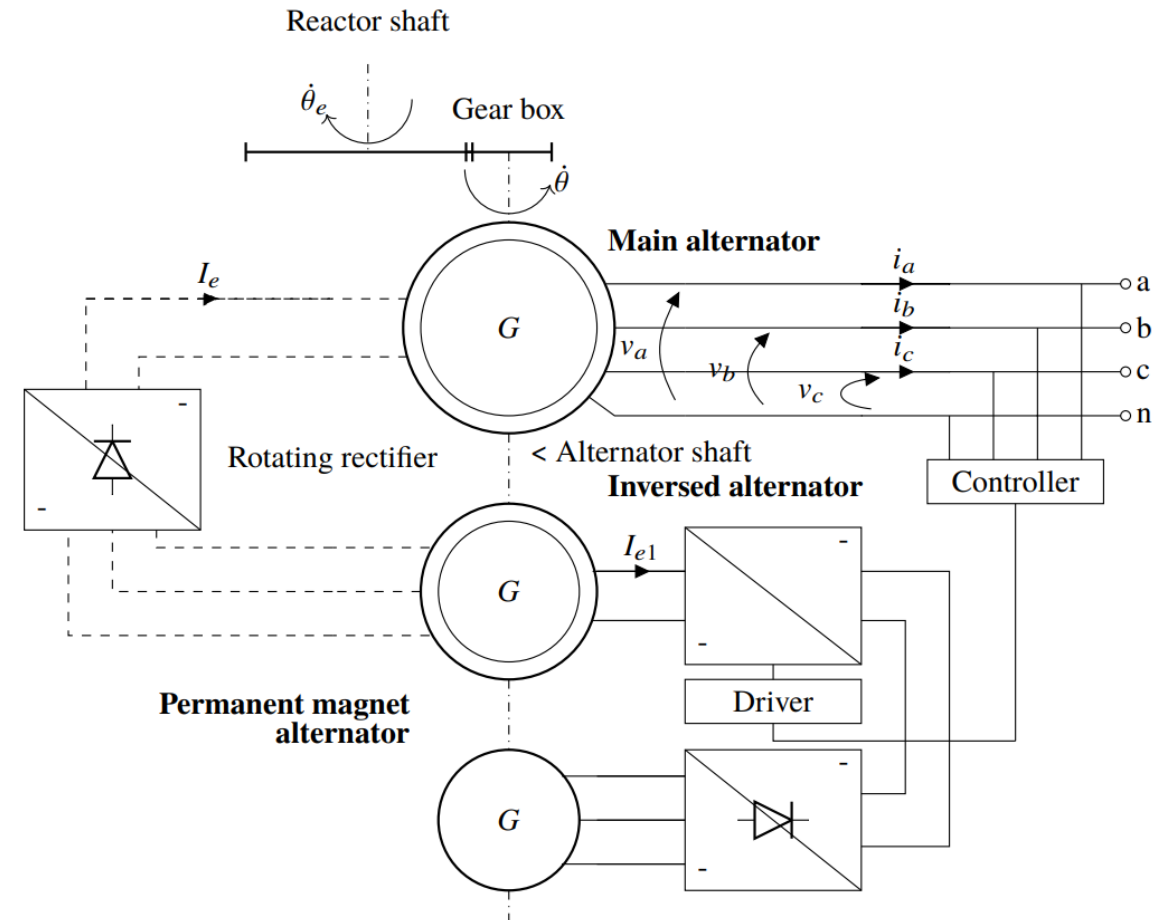The excitation of the alternator is controlled such that the output phase voltage of the alternator is 115 V (200 V line voltage). This excitation consists of an inversed alternator coupled with a permanent magnet alternator.



# Exercise 10: Constant air gap alternator

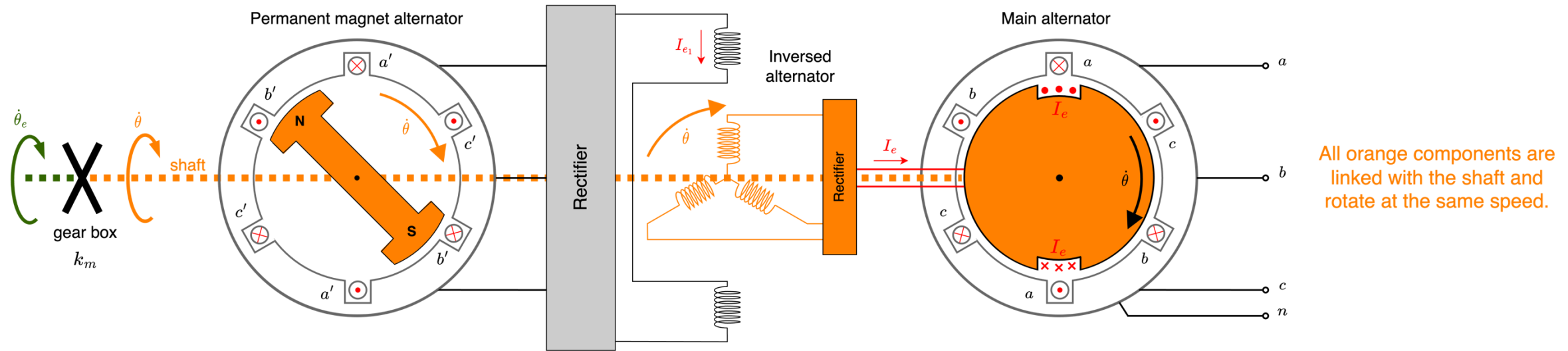1. Explain how the excitation system works. What are the main advantages of such a system?



- 1) At startup, the airplane reactor starts rotating at a speed  $\dot{\theta}_e$ , making the shaft of the alternator rotate at a speed  $\dot{\theta} = k_m \dot{\theta}_e$  using a gear box.
- 2) The shaft activates a permanent-magnet alternator, generating three-phase currents.
- 3) The three-phase currents are rectified and used for the excitation of the inversed alternator ( $I_{e1}$ ).
- 4) The shaft activates the rotor of the inversed alternator, generating three-phase currents.
- 5) The three-phase currents are rectified and used for the excitation of the main alternator ( $I_e$ ).



The first permanent magnet alternator ensures an autonomous start.

There is no use of any brush. It makes the system more reliable and safer (no sparks).

# Exercise 10: Constant air gap alternator

- Express the frequency  $f$  of the generated voltages and currents with respect to the rotation speed of the reactor  $\dot{\theta}_e$ , the gear box ratio  $k_m$  and the number of pairs of poles of the alternator  $p$ .
- Deduce the number of pair of poles, and the minimal and maximal values  $f_{min}$ ,  $f_{max}$  of the generated voltages and currents.
- For an airplane, justify the relevance of a system working at a higher frequency.
- Compute the nominal RMS line current  $I_n$  (the main alternator is connected in star configuration).
- The flux generated by one pole is:


$$\phi(t) = \phi_m \cos(p(\dot{\theta}t - \theta_0))$$

where  $\phi_m$  is the maximum flux amplitude,  $p$  the number of pairs of poles,  $\dot{\theta}$  the speed of rotation,  $t$  the time variable and  $\theta_0$  the initial angular position of the rotor. Express the electromotive force  $e_s(t)$  induced in a single turn of the rotor with respect to  $\phi_m$ ,  $f$ ,  $t$ ,  $p$  and  $\theta_0$ . Deduce the RMS value  $E_s$  of  $e_s(t)$  with respect to  $\phi_m$  and  $f$ .


- The RMS value  $E$  of the induced electromotive force in a phase is  $E = k_b N_s E_s$  where  $k_b = 0.85$  is the coil factor and  $N_s = 16$  is the number of turns per phase. The magnetic circuit is built using laminations allowing to reach a maximal magnetic field corresponding to a flux amplitude  $\phi_{m0} = 6.84 \text{ mWb}$  and a current  $I_{e0} = 2.95 \text{ A}$ .

Assuming the ferromagnetic materials remain unsaturated and neglecting hysteresis and Eddy currents, express the RMS value  $E$  of the electromotive force induced in each phase with respect to  $k_b$ ,  $N_s$ ,  $\phi_{m0}$ ,  $I_{e0}$ ,  $I_e$  and  $f$ .
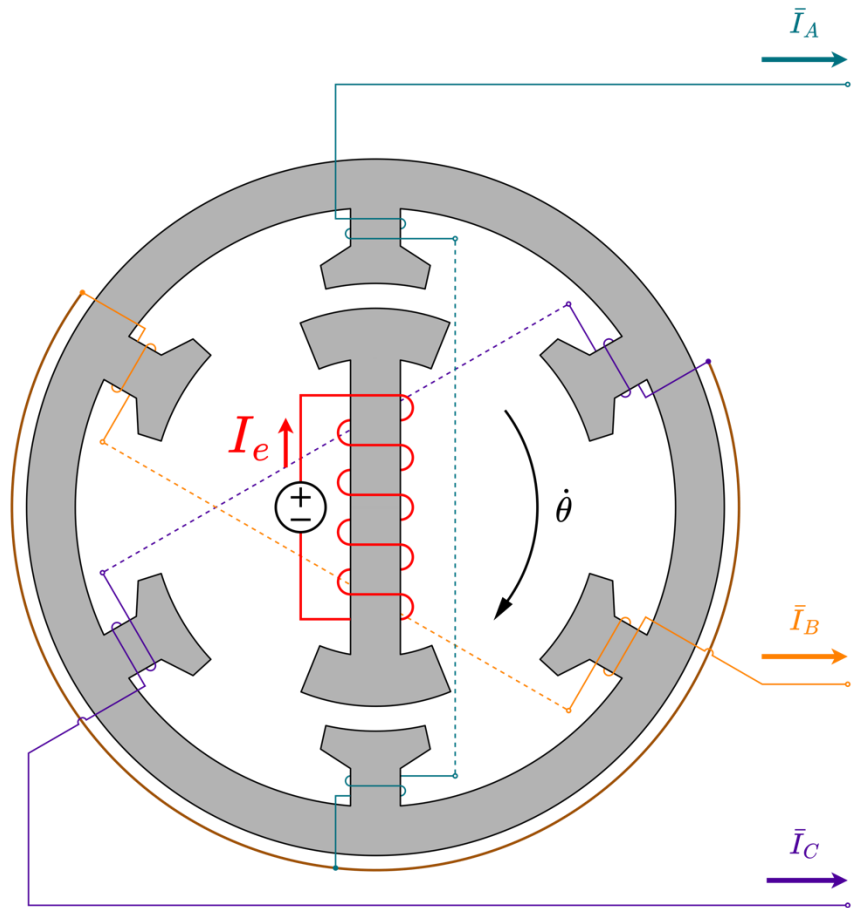
# Reminder ex session 5: Number of pairs of poles



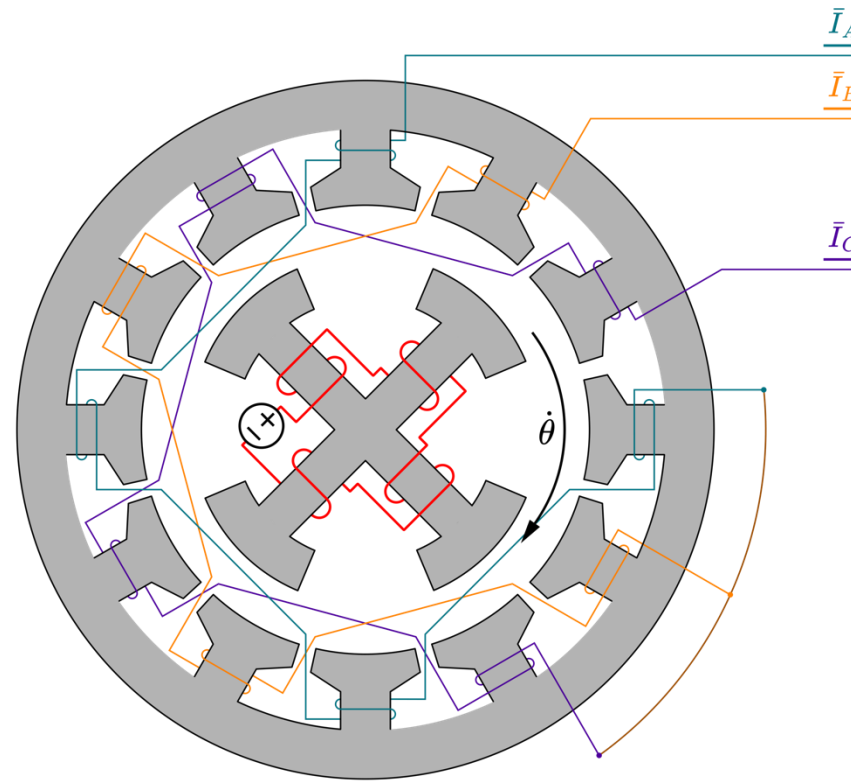Each phase has two poles  
→ One pair of poles ( $p = 1$ )



Each phase has four poles  
→ Two pairs of poles ( $p = 2$ )

The number of pairs of poles  $p$  links the speed of rotation  $\dot{\theta}$  to the pulsation  $\omega$  of the currents and voltages:


$$\dot{\theta} = \frac{\omega}{p}$$

# Exercise 10: Constant air gap alternator

The stator of the alternator is composed of three-phase windings whose phases are noted  $a$ ,  $b$  and  $c$ , while the rotor is composed of an inductor winding noted  $f$ . Each phase has an impedance composed of a resistance  $R_s$ , a self inductance  $\lambda$  (also noted  $L_s$ ) and a mutual inductance  $\lambda_m$  (also noted  $M_s$ ) with respect to each other phase.

The mutual inductances between each phase and the inductor phase have a sinusoidal pulsation with respect to the rotation angle  $\theta$ :
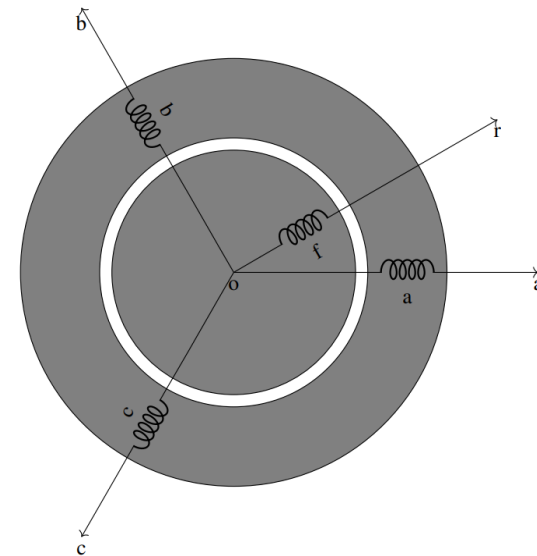
$$\begin{aligned}\lambda_{m,af} &= \lambda_{m,sf} \cos(p\theta) \\ \lambda_{m,bf} &= \lambda_{m,sf} \cos\left(p\left(\theta - \frac{2\pi}{3}\right)\right) \\ \lambda_{m,cf} &= \lambda_{m,sf} \cos\left(p\left(\theta + \frac{2\pi}{3}\right)\right)\end{aligned}$$



- Express the total fluxes  $\Psi_a$ ,  $\Psi_b$  and  $\Psi_c$  crossing the phase windings  $a$ ,  $b$  and  $c$  with respect to the flowing current intensities  $i_a$ ,  $i_b$  and  $i_c$ , the excitation current intensity  $I_e$ , the self inductance  $\lambda$ , the stator mutual inductance  $\lambda_m$ , the mutual inductance between the stator and the rotor  $\lambda_{m,sf}$  and the angle  $p\theta$ .



# Exercise 10: Constant air gap alternator

9. Express the voltages  $v_a$ ,  $v_b$  and  $v_c$  across the phase windings  $a$ ,  $b$  and  $c$  with respect to  $i_a$ ,  $i_b$ ,  $i_c$ , the total flux derivatives of  $\Psi_a$ ,  $\Psi_b$  and  $\Psi_c$  and  $R_s$ .
10. Show that the direct voltages of the stator can be written:

$$v_a = e_a - R_s i_a - \lambda_f \frac{di_a(t)}{dt}$$

$$v_b = e_b - R_s i_b - \lambda_f \frac{di_b(t)}{dt}$$

$$v_c = e_c - R_s i_c - \lambda_f \frac{di_c(t)}{dt}$$

Express the electromotive forces  $e_a$ ,  $e_b$  and  $e_c$  with respect to  $\lambda_{m,sf}$ ,  $I_e$ ,  $\dot{\theta}$ ,  $t$  and  $p$ .

# Exercise 10: Constant air gap alternator

The single-phase equivalent model of Behn-Eschenburg is now considered with  $R = 0.4 \text{ m}\Omega$ . To characterize the alternator two tests have been performed:

- Using open stator windings, at the speed of rotation  $\dot{\theta} = 11\,100 \text{ RPM}$ , the RMS phase voltage has been measured with respect to the RMS current intensity  $I_e$  flowing through the inductor.
- Using short-circuited stator windings, at the speed of rotation  $\dot{\theta} = 11\,100 \text{ RPM}$ , the RMS current intensity  $I_s$  has been measured with respect to the RMS current intensity  $I_e$  flowing through the inductor.

$I_e$ [A]	$E_v$ [V]	$I_s$ [A]
0.4	21.2	94.8
0.8	42.2	190
1.2	63.6	284
1.6	84.8	379
2	106	474
2.4	122	569
3	137	670
3.6	143	770
4.2	145	860
4.8	147	948
5.4	148	1040

- Plot the open stator windings curve,  $E_v$  with respect to  $I_e$ , for  $f_{min} = 370 \text{ Hz}$  and  $f_{max} = 770 \text{ Hz}$ .
- At nominal speed of rotation, compute the synchronous reactance  $X_s$  for the linear part of the curve. Deduce the inductance  $L_s$ .
- Plot the short-circuited stator windings curve,  $I_s$  with respect to  $I_e$ , for  $f_{min} = 370 \text{ Hz}$  and  $f_{max} = 770 \text{ Hz}$ .
- The alternator is connected to a star-shaped load composed of 3 resistors of value  $R_L = 0.5 \Omega$  working at a frequency  $f = 500 \text{ Hz}$  for an excitation current  $I_e = 2 \text{ A}$ .
  - Calculate the stator RMS current and voltage values  $I$  and  $V$ .
  - Sketch the Behn-Eschenburg diagram and explain how  $I$  and  $V$  vary when the frequency increases.

# Homework 18

A three-phase alternator coupled in star configuration provides a line current  $I_n = 200$  A under a line voltage  $U_n = 400$  V at 50 Hz. The power factor is  $\cos \varphi_n = 0.866$  with a resistive-inductive load. In between one phase of the stator and the neutral point, the resistance is  $30$  m $\Omega$  and the synchronous reactance is  $750$  m $\Omega$ . Iron losses amounts to 6 kW. Losses in the excitation system are negligible, as well as mechanical losses.

1. Compute the nominal output power of the alternator.
2. Compute the Joule losses in the stator.
3. Compute the efficiency of the alternator in this configuration.
4. Compute the RMS value of the internal *emf* under Behn-Eschenburg assumption.
5. Provide the internal load angle  $\delta_{int}$ .
6. With a purely resistive load and assuming the iron losses,  $I_n$  and  $U_n$  are kept constant, compute the efficiency of the alternator.

Answers:

1.  $P_n = 120$  kW
2.  $p_{js} = 3.6$  kW
3.  $\eta = 92.6$  %
4.  $E_v = 336$  V
5.  $\delta_{int} = 22.2^\circ$
6.  $\eta' = 93.5$  %

# Homework 19

A synchronous condenser is a DC excited synchronous motor, whose rotating shaft is not connected to any mechanical load. By controlling its excitation current, using a voltage regulator, the condenser is able to generate or absorb reactive power as needed to adjust the voltage on the power grids, or to improve the power factor.

- Synchronous speed: 428 RPM for 14 poles,
  - Star-shape coupling with a phase voltage  $V_n = 8.95$  kV,
  - Nominal intensity  $I_n = 6.33$  kA,
  - Apparent nominal power  $S_n = 170$  MVA,
  - Nominal synchronous reactance  $X_s = 1.2 \Omega$  at the nominal frequency  $f_n = 50$  Hz.
1. The machine is first used as an alternator, providing a total three-phase active power  $P_{3\phi} = 100$  MW and a total three-phase reactive power  $Q_{3-\phi} = 50$  Mvar. Calculate the phase shift  $\varphi$  and the line current intensity  $I$ .
  2. The machine is now turned into a freely spinning motor, keeping the excitation current constant and assuming  $P \approx 0$  W, calculate the reactive power  $Q$  provided to the motor.

Answers:

1.  $\varphi = 26.565^\circ, I = 4.16$  kA
2.  $Q = -69.14$  Mvar